Build Your Own Electronic Calculator

Radio-Electronics

JUNE 1958

TELEVISION • SERVICING • HIGH FIDELITY

HUGO GERNSBACK, Editor

Watch Your Audio Levels

■

Common Servicing Fallacies In Color TV

■

Electronic Boat Horn

■

Pocket Police Transistor Radio

■

Build This Electronic Compass For Land or Water

(See page 28)

35c
U.S. and Canada

F K TUSTISON 8-59
14828 OSAGE
LAWNDALE CALIF

Burton Browne Advertising

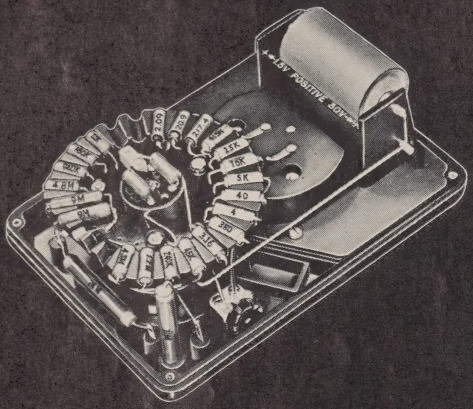

NEW TRIPLETT MODEL 630-PL | $44.50 net

new... most easy to read

- Clear, unbreakable, shadowless front for instant wide vision.
- 5 to 500,000 cps on A.C.
- Continuous resistance reading from 0.1 ohms to 100 megohms.
- Polarity reversing switch.
- *Only one* (king-sized) switch selects both circuit and range —minimizes wrong settings, burnouts.

Only Triplett affords you such a wide choice of VOMs. Whatever your application—broad or limited—there is a Triplett VOM particularly suited for it.

the mighty nine + two

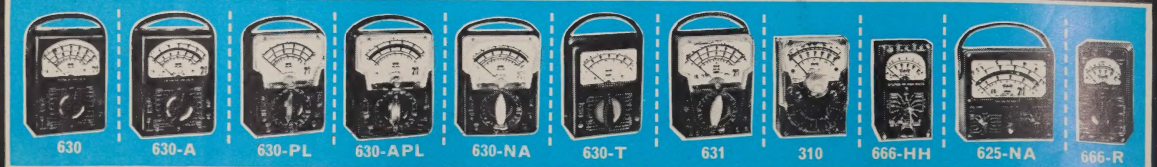

TRIPLETT ELECTRICAL INSTRUMENT COMPANY • BLUFFTON, OHIO

Learn Radio-Television

Servicing or Communications

by Practicing at Home in Spare Time

N.R.I. SENDS kits with which you practice building circuits common to Radio and TV sets. You LEARN-BY-DOING to locate Radio-TV troubles. As part of N.R.I. Servicing Course, you build Vacuum Tube Voltmeter and AC-DC receiver. Use VTVM to conduct experiments, earn extra money fixing sets in spare time.

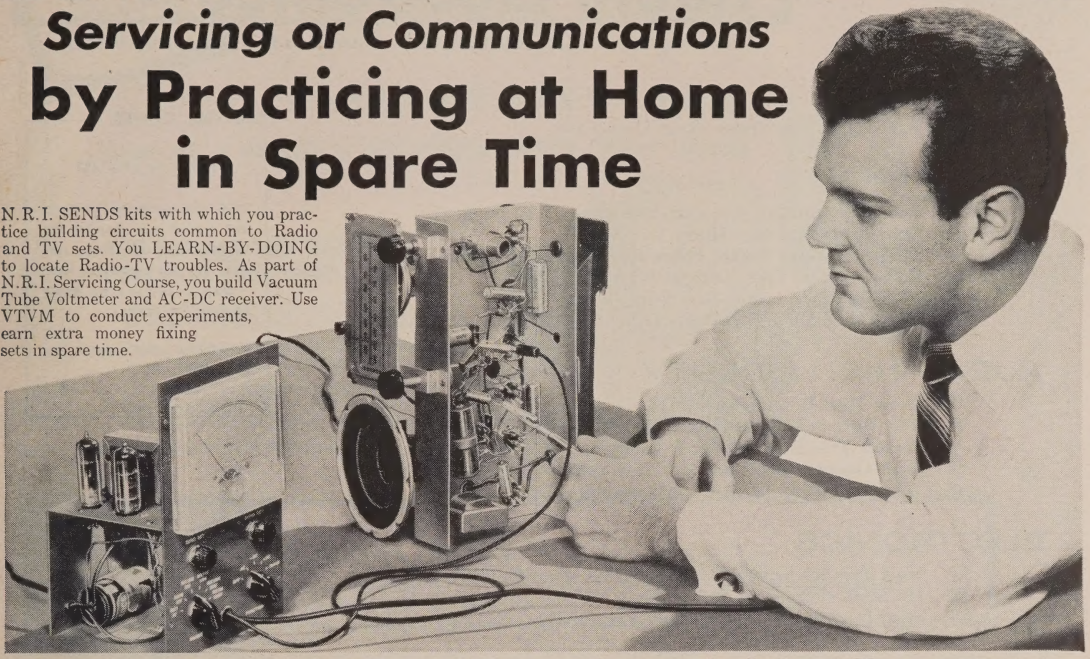

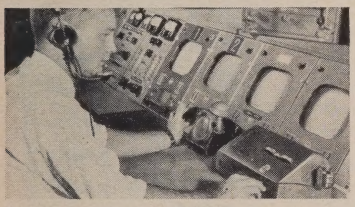

RADIO-TV BROADCASTING (see above) offers important positions as Operators and Technicians. RADIO-TV SERVICING Technicians (see below) needed in every community. Their services are respected, their skill appreciated.

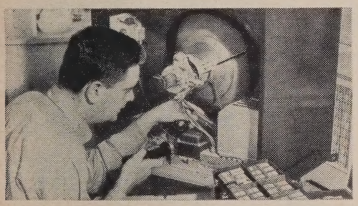

Fast Growing Field Offers You Good Pay, Success, Bright Future

J. E. SMITH
Founder

Bigger than ever and still growing fast. That's why Radio-TV has special appeal to ambitious men not satisfied with their job and earnings. More than 4,000 Radio and TV stations. More than 150 million home and auto Radios, 40 million TV sets. Color TV promises added opportunities. For the trained man, there are good jobs, bright futures in Radio-TV Servicing or Broadcasting.

Training PLUS opportunity is the *ideal combination* for success. So plan *now* to get into Radio-TV. The technical man is looked up to. He does important work, gets good pay for it. Radio-Television offers that kind of work. NRI can supply training quickly, without expense of going away to school. Keep your job while training. You learn at home in your spare time. NRI is the OLDEST and LARGEST home study Radio-TV school. Its methods have proved successful for more than 40 years.

Added Income Soon - $10, $15 a Week in Spare Time

Soon after enrolling, many NRI students start to earn $10, $15 a week in spare time fixing sets. Some pay for their training and enjoy extra luxuries this way. Some make enough to start their own Radio-TV shops. NRI training is *practical*—gets quick results. Easy to understand, well illustrated lessons teach you basic principles. And you LEARN-BY-DOING by practicing with kits of equipment which "bring to life" things you study.

Find Out What NRI Offers

NRI has trained thousands for successful careers in Radio-TV. Study fast or slow—as you like. Diploma when you graduate. Mail coupon now. Paste it on a postcard or mail in envelope. ACTUAL LESSON FREE. Also 64 page catalog that shows opportunities, shows equipment you get. Cost of NRI courses low. Easy terms. **NATIONAL RADIO INSTITUTE, Dept. 8FF, Washington 16, D. C.**

N.R.I. TRAINED THESE MEN FOR SUCCESS

"I was repairing Radios by 10th lesson. Now have good TV job." M. R. LINDEMUTH, Fort Wayne, Ind.

"Doing spare time repairs on Radio and TV. Soon servicing full time." CLYDE HIGGINS, Waltham, Mass.

"I had a successful Radio repair shop. Now I'm Engineer for WHPE." V.W.WORKMAN, High Point, N.C.

"There are a number of NRI graduates here. I can thank NRI for this job." JACK WAGNER, Lexington, N. C.

VETERANS Approved Under G.I. Bills

SEND FOR BOTH FREE

National Radio Institute
Dept. 8FF, Washington 16, D. C.

Mail me Sample Lesson and 64-Page Catalog FREE. (No salesman will call. Please write plainly.)

Name_____Age___

Address_____

City_____Zone___State_____

ACCREDITED MEMBER, NATIONAL HOME STUDY COUNCIL

JUNE, 1958

Radio-Electronics

Formerly RADIO-CRAFT ■ Incorporating SHORT WAVE CRAFT ■ TELEVISION NEWS ■ RADIO & TELEVISION

EDITORIAL

27 Radio Signals to Venus—Hugo Gernsback

RADIO

28 Electronic Compass to Guide You Home—J. E. Pugh, Jr.
31 Communications in a Hurry
32 Three-Transistor Pocket Police Receiver—Edwin Bohr
34 Radio Runs on Low Voltage—Warren J. Smith
35 Identify That Chassis—Jack Darr
38 Slug-Tuned VFO Has Stable Output—Jack Gallagher, W5HZB

AUDIO—HIGH FIDELITY

39 Know Your Levels—Norman H. Crowhurst
43 New Discs and Stereo Tapes—Chester Santon
44 Remote Transistor Ear—F. J. Bauer, Jr., W6FPO
46 A PA Dummy Load—Richard H. Houston
48 Take Your Pick: Changer or Turntable—Herman Burstein

ELECTRONICS

50 More Jobs for Semiconductors, Part II—Paul Penfield, Jr.
52 Mr. Math—Forrest H. Frantz, Sr.
56 News from the IRE 1958 Meet—Eric Leslie

WHAT'S NEW

58 Pictorial Reports of New Developments

TELEVISION

59 Transistors in the TV Set, Part II—Louis E. Garner, Jr.
84 New Look in Indoor Antennas—Larry Steckler
86 Facts and Fallacies in Color TV Service—Robert G. Middleton
88 TV Dx—Robert B. Cooper, Jr.
90 TV Service Clinic—Conducted by Robert G. Middleton

TEST INSTRUMENTS

92 Square-Wave Generator—T. W. Dresser
96 Spot-O-Matic—I. Queen
99 An Inexpensive Scope Calibrator—Joseph Chernof

124 Books
119 Business and People
121 Corrections
14 Correspondence
104 New Devices
101 New Tubes and Semiconductors
6 News Briefs
112 Patents
113 Radio-Electronic Circuits
122 Technical Literature
110 Technicians' News
117 Technotes
115 Try This One
94 50 Years Ago

ON THE COVER

(Story on page 28)

With this electronic compass and a local map showing the location of nearby radio stations you just can't stay lost.

Map copyright by Rand McNally (RL58Y8).

Color original supplied by J. E. Pugh, Jr.

Hugo Gernsback ..... Editor and Publisher
M. Harvey Gernsback ..... Editorial Director
Fred Shunaman ..... Managing Editor
Robert F. Scott ..... W2PWG, Technical Editor
Larry Steckler ..... Assistant Editor
I. Queen ..... Editorial Associate
Robert G. Middleton ..... Television Consultant
Elizabeth Stalcup ..... Production Manager
Cathy Coccozza ..... Advertising Production
Wm. Lyon McLaughlin ..... Tech. Illustration Director
Sol Ehrlich ..... Art Director
Fred Neinast ..... Staff Artist
Lee Robinson ..... General Manager
John J. Lamson ..... Sales Manager
G. Aliquo ..... Circulation Manager
Adam J. Smith ..... Director, Newsstand Sales
Robert Fallath ..... Promotion Manager

Average Paid Circulation
Over 195,000

RADIO-ELECTRONICS is indexed in *Applied Science & Technology Index* (Formerly *Industrial Arts Index*)

RADIO-ELECTRONICS, June, 1958, Vol. XXIX, No. 6. Published monthly at Mt. Morris, Ill., by Gernsback Publications, Inc. Second-class mail privileges authorized at Mt. Morris, Ill. Copyright 1958 by Gernsback Publications, Inc. All rights reserved under Universal, International and Pan-American Copyright Conventions.
SUBSCRIPTION RATES: U. S., U. S. possessions and Canada, $4.00 for one year; $7.00 for two years; $9.00 for three years; single copies 35c, Pan-American countries $4.50 for one year; $8.00 for two years; $10.50 for three years. All other countries $5.00 a year; $9.00 for two years; $12.00 for three years.
SUBSCRIPTIONS: Address correspondence to Radio-Electronics, Subscription Dept., 404 N. Wesley Ave., Mt. Morris, Ill., or 154 West 14th St., New York 11, N. Y. When requesting a change of address, please furnish an address label from a recent issue. Allow one month for change of address.
GERNSBACK PUBLICATIONS, INC. Executive, Editorial and Advertising Offices, 154 West 14th St., New York 11, N. Y. Telephone Algonquin 5-7755. Hugo Gernsback, Chairman of the Board; M. Harvey Gernsback, President; G. Aliquo, Secretary.
BRANCH ADVERTISING OFFICES and FOREIGN AGENTS listed on page 127.
POSTMASTER: If undeliverable, send Form 3579 to: RADIO-ELECTRONICS, 154 West 14th St., New York 11, N. Y.

*Trademark registered U. S. Pat. Office.

GREATEST ADVANCE IN SHOP-METHOD HOME TRAINING

EARN MORE MONEY... GET INTO TELEVISION ELECTRONICS – RADIO

Learn ALL 8 PHASES in ONE MODERN HOME-STUDY COURSE
At Home — In Spare Time

YOU GET ALL THIS NEWEST PRACTICAL EQUIPMENT

- Parts to build a modern TV set, including all tubes plus a large screen Picture Tube
- Parts to build a powerful Superhet Receiver, standard broadcast and short wave
- Parts to conduct many experiments and build Continuity Checker, RF Ocillator, TV Circuits, Audio Oscillator, TRF Receiver, Signal Generator
- A Valuable Professional Multitester

YOUR NATIONAL SCHOOLS TELERAMA COURSE COVERS ALL 8 PHASES

1. TELEVISION, INCLUDING COLOR TV
2. RADIO, FM AND AM
3. INDUSTRIAL ELECTRONICS
4. SOUND RECORDING AND HI FIDELITY
5. PREPARATION FOR FCC LICENSE
6. AUTOMATION
7. RADAR AND MICRO WAVES
8. COMMUNICATIONS

YOU ARE NEEDED IN THE TELEVISION-ELECTRONICS-RADIO INDUSTRY! You can build a secure future for yourself if you get into Electronics NOW! Today's shortage of trained technicians creates tremendous opportunities. National Schools Shop-Method trained technicians are in constant and growing demand for high-pay jobs in Broadcasting and Communications, Electronic Research, Servicing and Repair, and many other branches.

Let National Schools, a Resident Technical School for over 50 years train you for today's unlimited opportunities in electronics! Our Shop Method trains you to be a MASTER-TECHNICIAN. Completely up to date, developed by experienced instructors and engineers, your Telerama Course will teach you all phases of the industry quickly, clearly and correctly. You can master the most modern projects, such as Color TV, printed circuits — even prepare for FCC License without taking a special course. You can handle sales, servicing, manufacturing, or make good money in your own business. SEND FOR FACTS TODAY!

EARN AS YOU LEARN. Many of our students earn their entire tuition and more in Spare Time jobs we show them how to do while learning.

YOU GET EVERYTHING YOU NEED — Clear, profusely illustrated lessons, shop-tested manuals, modern circuit diagrams, practical job projects — all the valuable equipment shown above — many other materials and services — consultation privilege with our qualified staff, and Graduate Employment Service. EVERYTHING YOU NEED for outstanding success in Electronics

RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles, the world's TV capital, start NOW in our big, modern Shops, Labs and Radio-TV Studios. Here you work with latest Electronic equipment—professionally installed—finest, most complete facilities offered by any school. Expert, friendly instructors. Personal attention. Graduate Employment Service. Help in finding home near school—and part time job while you learn. Check box in coupon for full information.

MEMBER
NATIONAL HOME STUDY COUNCIL
NATIONAL COUNCIL OF TECHNICAL SCHOOLS 1945

FREE! Fully illustrated "Career" Book in TV-Radio-Electronics. PLUS actual sample lesson—yours at no cost, no obligation. CLIP COUPON NOW . . . MAIL IT TODAY!

APPROVED FOR G.I. TRAINING

NATIONAL SCHOOLS

4000 S. FIGUEROA ST., LOS ANGELES 37, CALIF.

NATIONAL SCHOOLS

TECHNICAL TRADE TRAINING SINCE 1905
LOS ANGELES 37, CALIFORNIA

GET FAST SERVICE – MAIL NOW TO
NATIONAL SCHOOLS, DEPT. RG-68
4000 S. FIGUEROA ST
LOS ANGELES 37, CALIF.

Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.

NAME _____ AGE _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____
☐ Check if interested ONLY in Resident School training at Los Angeles.
VETERANS: Give date of Discharge _____

Carefully Balanced Packaged Circuit Inventory with the NEW Centralab® PCK-40 Kit

With almost eighty million Centralab packaged circuits (identified by PEC*) already incorporated in TV chassis, packaged circuit replacement is getting to be bigger business for you all the time. Make it extra profitable by avoiding special trips and phone calls to your distributor.

The carefully balanced inventory of the new Centralab PCK-40 Kit covers 80% of your PEC* needs. You'll have the circuit you need, on hand, *when you need it.* The Kit contains 40 PEC*, divided among 14 of the most frequently used types, each in its individual rigid plastic package. They are conveniently arranged, for instant identification, in a rugged metal cabinet.

Ask your distributor to show you the new Centralab PCK-40 Kit now, with the FREE cabinet and handy guide. Price $26.93 dealer net.

Centralab products are listed in PHOTOFACTS, COUNTER-FACTS, and THE RADIO-ELECTRONIC MASTER. PEC* Guide No. 4 available on request from your local distributor or direct from Centralab.

Centralab *Trademark CRL ® Y-5832

A DIVISION OF GLOBE-UNION, INC.
922F E. KEEFE AVE. • MILWAUKEE 1, WIS.
In Canada: Mt. Pleasant Rd. • Toronto, Ontario

SWITCHES • PACKAGED ELECTRONIC CIRCUITS • CERAMIC CAPACITORS
CONTROLS • ENGINEERED CERAMICS • SEMI-CONDUCTOR PRODUCTS

News Briefs

SEMICONDUCTORS MOVE into the regulation field with the announcement of a field-effect varistor developed by R. M. Warner, Jr., H. A. Stone and E. I. Douchette of Bell Telephone Laboratories. The unit has a constant-current feature which makes it ideal as a current regulator. It can also be used as a current limiter or pulse shaper and its high ac impedance makes it useful as a coupling choke or ac switch.

The device has a single diffused junction (see Fig. 1). Current passes parallel to this junction through a constricted area called the "channel."

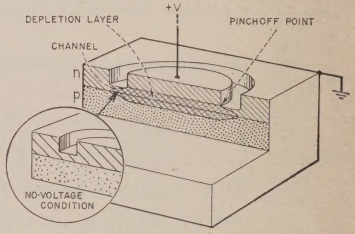

FIG. 1

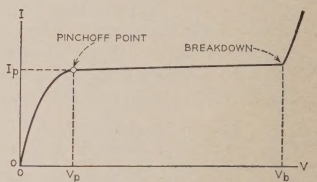

FIG. 2

As the voltage across the device is increased, current increases and a depletion area builds up which eventually reaches through the entire thickness of the channel. At this point, called the "pinchoff" point, a further increase in voltage does not increase current. As voltage is raised still higher, a breakdown point is reached, and current increases again. But between the pinchoff and breakdown points the current is essentially constant and this is the area used (see current curve in Fig. 2).

MASER AMPLIFIER BRINGS VENUS and other astronomical targets 10 times closer than previously possible, when coupled to a radio telescope. Now in use, the unit has been installed as part of the 50-foot radio telescope at the Naval Research Laboratory in Washington. The MASER (*M*icrowave *A*mplification by *S*timulated *E*mission of *R*adiation, see RADIO-ELECTRONICS, June, 1955) device operates on a 3-cm wavelength and was developed as a

LET DeVRY TECH PREPARE YOU IN SPARE TIME AT HOME AS AN

ELECTRONICS TECHNICIAN

NO PREVIOUS TECHNICAL EXPERIENCE OR ADVANCED EDUCATION NEEDED!

Laborers and bookkeepers, store clerks, shop men, farmers, salesmen — men of nearly every calling — have taken the DeVry Tech program and today have good jobs or service shops of their own in Electronics. You don't have to quit your present job. If you are 17 to 55, see how you may get yourself ready for a future in the fast-growing Electronics field.

Whether you prepare at home or in our well-equipped Chicago or Toronto Laboratories, you get sound, basic training in both principles and practice. At home, you use educational movies. You build actual circuits and test equipment. You read simple directions, follow clear illustrations. When you finish, you are prepared to step into a good job in an excitingly different field. You may even start a service shop of your own. Mail coupon for free facts today.

Live-Wire Employment Service

Puts you in touch with job opportunities—or helps you toward a better position in the plant where you are now employed.

Draft Age?

We have valuable information for every man of draft age; so if you are subject to military service, be sure to check the coupon.

SAMPLE BOOKLET FREE!

We'll give you a free copy of an interesting booklet, "Electronics and YOU." See for yourself how you may take advantage of the opportunities in this fast-growing field.

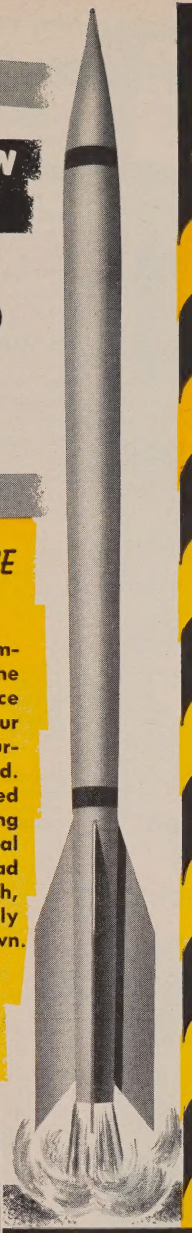

AN INDEX to a BETTER JOB, A BRIGHTER FUTURE

- Electronics
- Radar
- Guided Missiles
- Television
- Micro-Waves
- Communications
- Radio
- Industrial Electronics
- Computers
- Automation Electronics
- Remote Control Systems
- Broadcasting
- Your Own Service Shop

"One of North America's Foremost Electronics Training Centers"

Accredited Member of National Home Study Council

DeVRY TECHNICAL INSTITUTE
CHICAGO 41, ILLINOIS
FORMERLY
DeFOREST'S TRAINING, INC.

27 YEARS DeVry Technical Institute CHICAGO ILLINOIS

MAIL TODAY FOR FREE FACTS

DeVry Technical Institute
4141 Belmont Ave., Chicago 41, Ill., Dept. RE-6-O

Please give me your FREE booklet, "Electronics and YOU," and tell me how I may prepare to enter one or more branches of Electronics as listed above.

NAME _____ AGE _____
Please Print
STREET _____ APT. _____
CITY _____ ZONE _____ STATE _____

☐ Check here if subject to military training.

1090 DeVry Tech's Canadian Training Center is located at 626 Roselawn Avenue, Toronto 12, Ontario

joint project of Columbia University and the Naval Research Lab.

It is a solid-state device that uses a synthetic ruby as the Maser amplifier. Freedom from electrical noise inherent in other types of amplifiers enables Maser devices to amplify signals much too weak to be handled by conventional amplifiers.

A similar device is slated for operation with Harvard University's radio telescope. Here, a potassium cobalticyanide crystal will be used with a 21-cm wavelength.

AN ELECTRONIC COMPUTER using punched cards and magnetic tape was used to index the Dead Sea scrolls, ancient Hebrew writings discovered in 1947 in a cave in Jordan, near the west coast of the Dead Sea. This system has saved many hours of tedious labor formerly done by hand. Each word was placed on a punch card. The information cards were then converted to tape by the machine. The 29,250 words took about 2 hours and 2 reels of tape. The final step turned out a printed alphabetical summary list in Hebrew at 150 lines a minute. The computer that did the job is the IBM 705 data-processing machine.

Calendar of Events

Armed Forces Communications and Electronics Association's Show, June 4–6, Sheraton Park Hotel, Washington, D. C.

National Symposium on Production Techniques, June 5–6, Hotel New Yorker, New York, N. Y.

Southwest High Fidelity Show, June 6–8, Shamrock Hilton Hotel, Houston, Tex.

National Convention on Military Electronics, June 16–18, Sheraton Park Hotel, Washington, D. C.

French Electronic Components Show, June 20–26, 23 Rue de Lubeck, Paris.

3,000 MILE RADIO NETWORK, using tropospheric forward scatter propagation (see RADIO-ELECTRONICS, October 1957, page 6; September 1956, page 37 and August 1955, page 39), has gone into operation in Alaska. The network, project White Alice, links the radar warning outposts of the Alaskan Air Command with the Alaskan portion of the DEW (*D*istant *E*arly *W*arning) line spread across Alaska and Canada.

The system has been under construction since 1955. It was built by Western Electric and is operated by civilian employees of the Federal Electric Co.

INTEGRATED RADIO SYSTEM for San Francisco police, fire, civil defense and other local agencies brings the city's radio communications up to date. Under the new system, the Police Department will operate on four frequencies in the 40–50-mc band. A fifth frequency, in the 150-mc band, has been set aside for the use of affiliated law enforcement agencies.

Thoroughly covering the city, 17 base stations, including 10 located at police precincts, serve 185 cars and 164 motorcycles equipped with dual-channel equipment.

The earlier net, which operated on 2466 kc, will be assigned to the telephone company for ship-to-shore use.

CITATION OF RECOGNITION for his contribution to the educational program of the College of Engineering has been awarded Hugo Gernsback by New York University. Among his efforts is Mr. Gernsback's annual award, through NYU's Electrical Engineering Department, of a $1,000 scholarship to an outstanding student.

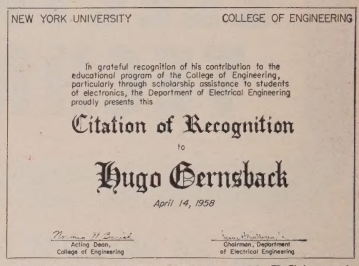
NEW YORK UNIVERSITY COLLEGE OF ENGINEERING

In grateful recognition of his contribution to the educational program of the College of Engineering, particularly through scholarship assistance to students of electronics, the Department of Electrical Engineering proudly presents this

Citation of Recognition

to

Hugo Gernsback

April 14, 1958

Acting Dean, College of Engineering

Chairman, Department of Electrical Engineering

HAVE YOU SEEN COLOR TV? RCA estimates that 75% of all Americans haven't. Of those who have color TV receivers, 91% are said to report complete satisfaction. And 80% of owners recommend buying a color receiver to their friends and two out of every three customers say they are buying a color receiver because of their friends' recommendations.

MEDICAL ELECTRONICS CONFERENCE, sponsored by the Council of International Organizations of the Medical Sciences (CIOMS), has been formed with the backing of UNESCO and the World Health Organization. The Medical Electronics Center of the Rockefeller Institute under the direction of Dr. V. K. Zworykin has undertaken the task of organizing the conference on an international scale.

The full-scale conference is tentatively scheduled for the spring of 1959. A preliminary meeting, to appoint the Conference Committee, will be held June 26, 27, 28, 1958, at the Grand Amphithéâtre, Commun de la Nouvelle Faculté de Médicine, Paris, France.

STEREO MUSIC from another station, WNBF in Binghamton, N. Y., is now on the air. The station transmits stereo tapes, using its AM and FM outlets. Listeners obtain the stereo effect by proper placement of their radio receivers. At present a 1-hour program is aired each week.

MAGNETIC FIELDS to keep missiles and spaceships cool when they hit the atmosphere has been proposed by Dr. Joseph L. Neuringer of Republic Aviation. It is a system of magnetohydrodynamic (or hydromagnetic) insulation.

When an object penetrates the earth's atmosphere at 13,000 mph, a shock wave forms ahead of it. Between this wave and the object is a stream of moving air, heated to about 12,000° F.

Leading Set Makers Specify Tung-Sol

High

IN PERFORMANCE

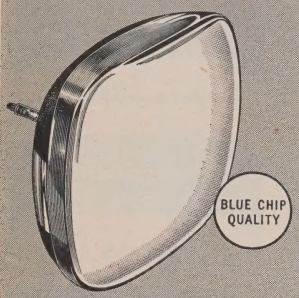

Leading Independent Service Dealers Choose Tung-Sol

LOW

IN CALLBACKS

TUNG-SOL®

Magic Mirror Aluminized

PICTURE TUBES

RECEIVING TUBES

ELECTRON TUBE DIVISION

TUNG-SOL ELECTRIC INC., NEWARK 4, N. J.

FREE from HOWARD W. SAMS!...valuable all-steel file cabinets with your purchase of PHOTOFACT—

the world's finest TV-Radio Service Data

FREE! FOR REGULAR PHOTOFACT SUBSCRIBERS

You get your File Cabinets FREE if you are a regular subscriber to PHOTOFACT Folders and buy all new Sets as issued each month. Your Folders come to you in special envelopes, each including a "Bonus Certificate." Sixty (60) of these entitle you to a single-drawer File Cabinet ABSOLUTELY FREE...

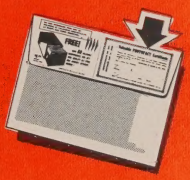

FREE! FOR PHOTOFACT LIBRARY PURCHASERS

Get FREE File Cabinets as you complete your profit-building PHOTOFACT Library... here's how:

FREE! Single-Drawer File Cabinet with your purchase of 60 Sets of PHOTOFACT Folders. Cabinet Worth... $8.95

FREE! Two single-drawer File Cabinets with your purchase of 120 Sets of PHOTOFACT Folders. Cabinets Worth. $17.90

FREE! Three single-drawer File Cabinets with your purchase of 180 Sets of PHOTOFACT Folders. Cabinets Worth. $26.85

FREE! Four single-drawer File Cabinets with your purchase of 240 Sets of PHOTOFACT Folders. Cabinets Worth. $35.80

NEW EASY-BUY PLAN

It's easy to complete your present PHOTOFACT Library or start a PHOTOFACT Library. Use the EASY-BUY PURCHASE PLAN:

- NO INTEREST
- NO CARRYING CHARGE
- AS LITTLE AS $10 DOWN
- UP TO 24 MONTHS TO PAY

Get the world's finest TV-Radio Service Data... get FREE File Cabinets with your PHOTOFACT purchases...take advantage of the Easy-Buy Plan. See your Sams Distributor today, or write to Howard W. Sams for full details.

get the full details of the HOWARD W. SAMS money-saving way to build your complete profit-making PHOTOFACT Library!

HOWARD W. SAMS & CO., INC.
2205 E. 46th St., Indianapolis 5, Indiana

☐ Send details on your FREE File Cabinet offer and EASY-BUY Plan.

☐ I'm a Service Technician: ☐ full time; ☐ part time

My Distributor is:_____

Shop Name:_____

Attn.:_____

Address:_____

City_____ Zone____ State_____

new profits available
in hi-fi servicing
and

Walsco

is Hi-Fi Service
Headquarters

Hi-Fi servicing is a booming new profit source for you, and WALSCO —always your completely dependable supplier for radio-tv service products—is ready with all the things you need to tap this growing field.

MOLDED-ON CABLES AND CONNECTORS

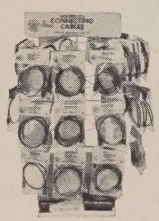

Look for this WALSCO display at your distributor. A complete assortment for your every need. Dozens of tenite shielded cables with phono pin plugs, jacks, phone plugs and alligator clips in a wide variety of combinations—in lengths up to 72".

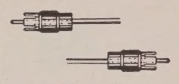

#2400 (36")
$1.05 List

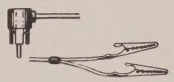

#2418 (10")
$3.25 List

PHONO-RECORDER BELTS AND DRIVES

Webcor Drive Wheel
#1463—$2.50 List

A complete replacement source for Ampro, Collaro, Crescent, Garrard, Pentron, Revere, RCA, VM, Webcor and every other standard changer and recorder.

RCA Idler Wheel
#1432—$1.00 List

HI-FI CHEMICALS

"No-Slip" for cords and pulley belts
#260-01—60c List

A full line of special chemicals for Hi-Fi servicing—to make your job easier and faster.

RH Recording Head Cleaner
#93-01—95c List

free! The latest WALSCO catalog . . . from your distributor, or write for it today.

WALSCO ELECTRONICS MFG. CO.
A division of Textron, Inc.
110 west green street
rockford, illinois

About 2% of the air's atoms are ionized at this temperature. This mixture, called a plasma, is a conductor of electricity.

When an electrical conductor is pushed across a magnetic field, current flows through it and it is slowed down.

The idea behind the new system is to form a strong magnetic field on the front surface of the spaceship or missile. With ionized air flowing across it, the breaking action of the field will cause the air to pile up in a deeper, slower-moving layer and it will not transfer as much heat to the object's surface.

According to Neuringer, a magnetic field of about 3,000 gauss should reduce heat transfer 28%. A further reduction might be obtained by coating the nose of the object with a material that ionizes easily. Its ions mixed with those of the air would make a stronger conducting plasma that would be more effectively slowed by magnetism.

TWO NEW TV STATIONS started programming since we last reported:

KVIQ, Eureka, Calif..... 6
KGHL-TV, Billings, Mont..... 8

The following new call letters were chosen:

KMSP, Minneapolis–St. Paul, Minn. 9
(formerly KMGM-TV)
KMOX-TV, St. Louis, Mo..... 4
(formerly KWK-TV)
WNTA-TV, Newark, N. J.....13
(formerly WATV)

US operating stations now total 541 (446 vhf and 95 uhf), 31 of which are noncommercial.

Havana, Cuba, has opened its sixth outlet on a 14-hour (6:00 A.M. to 2:00 A.M.) daily all-color schedule from the Havana-Hilton Hotel. Its name is simply Canal 12.

CUTS IN TAXES AND IMPORTS are the aims the Electronics Industries Association (EIA) came up with at their recent Spring Industry Conference. Specific points the EIA wants are: lower excise taxes on radio and TV receivers and phonographs—5% instead of the current 10%; curbs on rising imports of Japanese-made components and radios, and steps toward going into the testing business by taking over the operation of a tube-testing laboratory formerly run by RCA.

A TRANSISTOR BURGLAR ALARM which uses an infra-red beam modulated at 55 cycles as its light source and a synchronous phase-sensitive demodulator pickup is now available. The all-transistor device, developed at Walter Kidde & Co., uses a different frequency than the standard 60-cycle line source to prevent intruders from using another light to keep the alarm from going off. Interruption of the 55-cycle beam or a change in its frequency keys the alarm.

The unit uses a transistor amplifier and oscillator, and a phototransistor to detect the light. A reference signal is compared with the 55-cycle light. Any variation sets off the alarm. END

HOW TO PASS Your FCC Commercial LICENSE EXAMS*

GET YOUR FCC LICENSE IN A HURRY!

Get your FCC Commercial License —or your money back

See Free Catalog for complete details

Cleveland Institute training results in success with commercial FCC examinations
. . . easily . . . and quickly

"Investment in training really pays off"

"Thought you would like to know that in almost two years since I completed your course and obtained my first phone license, my pay has increased $5 per week every six months. I don't believe any other investment could pay off as well as this one did."

Harold E. Phipps
North Augusta, S. C.

Cleveland Institute training results in job offers like these!

Electronic Technicians

RCA has positions for technicians, field engineers & instructor technicians to install, maintain, and teach military radar, communications, and fire control equipment. Usual locations at military bases throughout U.S., some overseas. Experience on recent military electronics equipment preferred. Company benefits.

Radio Operator

Capital Airlines (Ohio) is looking for a radio operator. A touch typing speed of 40 wpm is necessary. Must have at least a restricted operator's permit, but a radio-telephone 2nd or 1st class license is desirable.

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
Desk RE-18 4900 Euclid Ave. Cleveland 3, Ohio

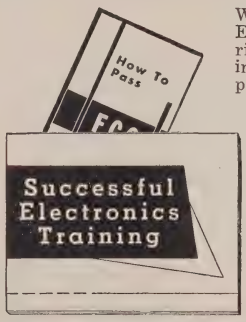

We can train you to pass your License Exams if you've had any practical experience—amateur, military, radio servicing, or other. Our proven plan can help put you on the road to success.

- Your FCC ticket will be recognized by employers as proof of your technical ability.

good training doesn't cost . . . it pays!

Mail Coupon Now and get both FREE

Accredited by the National Home Study Council

Cleveland Institute of Radio Electronics
Desk RE-18, 4900 Euclid Ave., Cleveland 3, Ohio

Please send Free Booklets prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below.

- ☐ Military
- ☐ Radio-TV Servicing
- ☐ Manufacturing
- ☐ Amateur Radio
- ☐ Broadcasting
- ☐ Home Experimenting
- ☐ Telephone Company
- ☐ Other

In what kind of work are you now engaged?

In what branch of Electronics are you interested?

Name_____ Age_____

Address_____

City_____ Zone_____ State_____

RE-18

How to make more money as an independent

RAYTHEON BONDED ELECTRONIC TECHNICIAN

Prominently display your Raytheon Bonded Certificate. It impresses your customers just like a doctor's diploma or lawyer's certificate.

Feature the Raytheon Creed Display and the Bonded Dealer Decal in your windows. The Creed Display shows potential customers your Code of Business Ethics. The Decal identifies you as a nationally advertised Bonded Dealer.

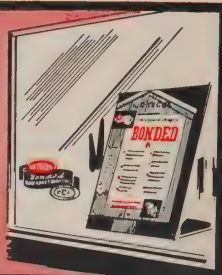

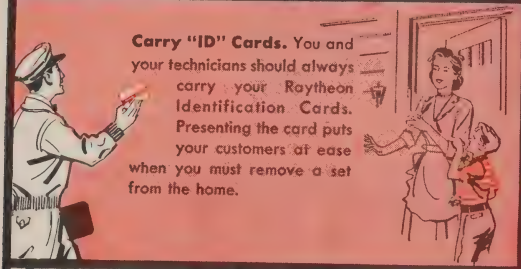

Carry "ID" Cards. You and your technicians should always carry your Raytheon Identification Cards. Presenting the card puts your customers at ease when you must remove a set from the home.

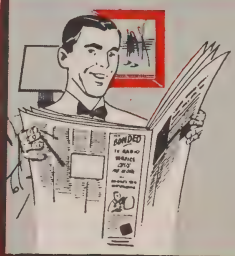

Advertise your Bonded Dealer standing. Use the newspaper mats Raytheon makes available to you for local newspaper advertising. Rates are low, results high. Scripts for radio and TV spots are also available to you at no cost.

Use the Yellow Pages. List your shop as a Bonded Dealer shop in the Classified Telephone Directory — many customers select service dealers from this source.

Make Mailings to Potential Customers. Raytheon has available to you many attractive Post Card mailers and a special Bonded Dealer self-mailer. Regular mailings stimulate service business.

Identify your shop. This traffic stopping metal sign will tell all passersby that you are the Bonded Dealer in your community — the Bonded Dealer that Raytheon is presenting to America as the top TV-Radio technician in the country.

Finally, make the most of the hundreds of helpful sales and shop aids Raytheon has available to you. They're all shown in this Raytheon Business Builders booklet. Get a copy from your Raytheon Tube Distributor, today.

P.S. If you're not a Raytheon Bonded Dealer call the Raytheon Tube Distributor who sponsors the Bonded Program in your neighborhood. He'll tell you if you can qualify.

RAYTHEON MANUFACTURING COMPANY

Receiving Tube and Semiconductor Operations

NEWTON 58, MASS. 55 Chapel Street | CHICAGO, ILL. 9501 Grand Ave. (Franklin Park) | ATLANTA 6, GA. 1150 Zonolite Rd. N.E. | LOS ANGELES 7, CALIF. 2419 So. Grand Ave.

Raytheon makes all these { Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes, Semiconductor Diodes and Transistors, Nucleonic Tubes, Microwave Tubes.

RAYTHEON®

Excellence in Electronics

Dreams for some...

but not for you when you get advanced CREI training in Electronic Engineering Technology

The Electronic dreams of just 10 years ago—*are realities today!* New Electronic applications call for new abilities. Enroll at CREI and you are assured of up-to-date training, revised to include the newest electronic advancements.

CREI has turned dreams of success, careers, good pay—into reality for thousands of ambitious men like you. CREI graduates are in the fore-front of the most advanced electronic applications, including Servomechanisms, Computers, Radar, Automation, Aeronautical Electronics, Broadcasting, Communications and Manufacturing, and the Electronic Principles associated with Guided Missiles, Telemetering, Astronautics, and Instrumentation.

These men received advanced practical technical training at home . . . and forged ahead. A typical graduate says:

"In this time of less than two years, I have almost doubled my salary, and have gone from wireman to engineering assistant, and now to junior engineer. I have CREI to thank."
—Frank A. Eckert, 22 Clover Lane, Levittown, Pa.

At CREI you are not held back by a class; not pushed to keep up with others with more experience or education. CREI instructors grade your written work personally. You master the fundamentals, then you elect specialized advanced training in the area that appeals to you most. Does it pay? One $10-a-week raise repays your tuition investment leaving you a substantial profit the very first year. Pay raises thereafter are pure profit.

What's the next step? The coupon below, completely filled out, will bring you a fact-packed booklet, "Your Future in the New World of Electronics." It describes opportunities, courses, and full school and tuition details. Mail coupon today, or write: Capitol Radio Engineering Institute, Dept. 146-E, 3224—16th St., N.W., Wash. 10, D.C.

CREI also offers *Residence* training in Washington, D.C. at the same high technical level. Day and evening classes start at regular intervals. Qualified residence school graduates earn degree of "Associate in Applied Science." Check coupon for catalog.

CAPITOL RADIO ENGINEERING INSTITUTE
ECPD Accredited Technical Institute Curricula
Founded 1927
3224 - 16th St., N.W.
Washington 10, D.C.

MAIL THIS COUPON FOR FREE BOOKLET!

CAPITOL RADIO ENGINEERING INSTITUTE
ECPD Accredited Technical Institute Curricula • Founded 1927

Dept. 146-E 3224 16th St., N. W., Washington 10, D. C.

Please send me your course outline and FREE illustrated Booklet "Your Future in the New World of Electronics" . . . describing opportunities and CREI home study courses in Electronics Engineering Technology.

CHECK FIELD OF GREATEST INTEREST
- ☐ Radar, Servo and Computer Engineering Technology
- ☐ Electronic Engineering Technology
- ☐ Broadcast (AM, FM, TV) Engineering Technology
- ☐ Television Engineering Technology
- ☐ Aeronautical Electronic Engineering Technology

N

Name.....Age.....
Street.....
City.....Zone.....State.....
Check: ☐ Home Study ☐ Residence School ☐ Korean Veteran

NOT FOR BEGINNERS. If you have had a high school education, and experience in electronics — and realize the need of a high-level technical knowledge to make good in the better electronic jobs—you can qualify for CREI home study training. (Electronics experience is not required for admission to CREI Residence School.) **Please fill in the following information:**

EMPLOYED BY .....
TYPE OF PRESENT WORK.....
.....
EDUCATION: YEARS HIGH SCHOOL.....
YEARS COLLEGE.....
ELECTRONICS EXPERIENCE .....
.....

The Tube-Tester that's always up-to-date!

- fast...
- fully automatic...
- pays for itself

RCA WT-110A
Automatic Electron Tube Tester
$199.50* includes 239 punched cards locked in sequence—covers 95% of active TV types...
USER PRICE (Optional) *Prices higher in Hawaii and Alaska
Plus—at no extra cost...
These bonus accessories...24 additional punched cards, 24 unpunched cards, and sturdy new card punch!

With RCA's exclusive *accessory punch and card kit,* your WT-110A tester is always up-to-date as fast as new tube type punching information is announced. When you use the RCA WT-110A—the ultra-modern way to test tubes—you gain speed and accuracy for *extra* service income, and improved efficiency which pays for the tester in a very short time!

Remember, when you choose RCA's WT-110A *Automatic* Electron-Tube Tester, you also choose a brighter profit picture —now and in the future.

- *Fully automatic!* Sets up *all* socket connections and *all* operating voltages for heater, control grid, plate, screen grid, and bias.
- Checks for shorts and leakage between each element and all others consecutively—plate, screen, control grid, cathode. Multiunit tube sections checked individually.
- Checks amplifier tubes for transconductance—green scale indicates normal range of tube's transconductance.
- File capacity for 700 cards.
- High- and low-sensitivity ranges for gas and leakage tests.
- Automatically selects correct test conditions from 220 different heater voltages (from 0.1 volt to 120 volts) at currents up to 4 amps., 10 bias voltage, and 11 values of cathode resistance.
- Rectifier-type tubes tested for emission under heavy load currents (up to 140 ma per plate).
- 12-volt plate-and-screen supply for testing new auto-radio tubes.

See Your Authorized RCA Test Equipment Distributor!

RCA® **RADIO CORPORATION OF AMERICA**
Electron Tube Division *Harrison, N. J.*

Correspondence

STANDS BEHIND THE OTL

Dear Editor:

As a proponent of the OTL (output *transformerless*) power amplifier I must take exception to some of the statements made by Herbert Ravenswood in his article "Is the Output Transformer Out" which appeared in the January, 1958, issue. It is evident that he is biased (way down to class C) against the OTL amplifier. The single-ended push-pull output stage has made the OTL power amplifier practical. To say that this configuration produces more distortion than the usual form of push-pull stage is not true. Provided the output tubes are matched and driven symmetrically, then they are both equally capable of low-distortion operation. This is so with triodes or pentodes, under class-A, -AB and -B, conditions.

Mr. Ravenswood also states that the single-ended push-pull output stage requires very unequal drive for its operation and this also is not true. As shown in Fig. 1 of the Peterson-Sinclair article, cited by Mr. Ravenswood, a push-pull driver transformer providing equal signal voltages, 180° out of phase, is used to drive each output tube; exactly as in the customary push-pull output stage. However, modern feedback amplifier design cannot tolerate a driver transformer and in the usual push-pull circuit it has been eliminated by various types of phase-inverter and phase-splitter circuits. These are well known in the art.

The single-ended push-pull output stage, however, when used with these circuits does not operate in true push-pull; hence the increased distortion cited by Mr. Ravenswood. Two circuit configurations have been developed that do operate the single-ended push-pull output stage in true push-pull under any and all conditions. These are the Peterson-Sinclair and the Futterman circuits.

Mr. Ravenswood is not impressed with the idea of eliminating the output transformer. Let me list briefly some of the advantages gained:

1. Elimination of notch distortion: This form of distortion shows up as a ragged treble response, usually blamed on the tweeter, and will occur, even with triodes when operated under class-AB or -B conditions.

2. More negative feedback can be used: With 40 db and more of negative feedback, entirely practical with the OTL power amplifier, distortion in the

FREE! ALLIED'S 1958 CATALOG

404 value-packed **PAGES**

the only COMPLETE catalog for everything in electronics

Get ALLIED's 1958 Catalog—it's *complete*, up-to-date—404 pages packed with the world's largest selection of quality electronic equipment at lowest, money-saving prices. Get *every* buying advantage at ALLIED: fastest shipment, expert personal help, lowest prices, guaranteed satisfaction...

EASY-PAY TERMS:

Only 10% down. Available on orders over $45. Fast handling—no red tape.

WORLD'S LARGEST STOCKS

- Latest Hi-Fi Systems and Components
- Money-Saving, Build-Your-Own KNIGHT-KITS
- Recorders and Supplies
- Public Address Systems and Accessories
- TV Tubes, Antennas and Accessories
- Amateur Receivers, Transmitters, Station Gear
- Test & Lab Instruments
- Specialized Industrial Electronic Equipment
- Huge Listings of Parts, Tubes, Transistors, Tools, Books

featuring:

ALLIED'S money-saving knight-kits:

Finest electronic equipment in money-saving kit form. Over 50 quality kits available—Hi-Fi amplifier, tuner and speaker kits, Hobby kits, Test Instruments, and Ham kits. ALLIED KNIGHT-KITS are easiest to build and they SAVE YOU MORE.

EVERYTHING IN HI-FI

World's largest selection of quality Hi-Fi components and complete music systems—available for immediate shipment from stock. Save on exclusive ALLIED-Recommended complete systems. Own the best in Hi-Fi for less!

Our 37th Year

ALLIED RADIO

World's Largest Electronic Supply House

send for the leading electronic supply guide FREE!

ALLIED RADIO CORP., Dept. 2-F8
100 N. Western Ave., Chicago 80, Ill.

☐ Send FREE 404-Page 1958 ALLIED Catalog

*Name*_____

*Address*_____

*City*_____ *Zone*____ *State*_____

When a serviceman needs a Mylar capacitor, he turns to Pyramid for the capacitor with high reliability, high resistance to moisture penetration and high insulation resistance.

Pyramid's Mylar capacitor guarantees the serviceman a highly dependable capacitor, designed for today's modern circuit requirements, at a price competitive with standard paper capacitors.

Available in standard capacitances and voltage ratings – Pyramid Mylar capacitors are ideal for use as by-pass and coupling capacitors.

Write today for complete information about Mylar capacitors or see your Pyramid distributor. Remember when a serviceman uses Pyramid, he uses the finest and eliminates costly call-backs.

CAPACITORS—RECTIFIERS
FOR ORIGINAL EQUIPMENT
AND REPLACEMENT

®DuPont Reg. trademark

PYRAMID
ELECTRIC COMPANY
North Bergen, New Jersey
Export: 458 Broadway, New York 13
Canada: Wm. Cohen, Ltd., 7000 Park Ave., Montreal

amplifier does not have to be considered in the reproducing chain.

3. Better transient response: Large amounts of negative feedback, besides reducing all forms of distortion to negligible values, also greatly improves the transient response of the amplifier. This can be heard.

In conclusion I might add that I have designed and constructed OTL power amplifiers and they have been reproduced without difficulty or trouble by scores of amateurs. What is really needed in OTL amplifier design is an output tube made specifically for this.
New York, N. Y. JULIUS FUTTERMAN

MR. RAVENSWOOD REPLIES

Dear Editor:

Mr. Futterman's letter, together with two received from different departments of the Philips' organization, reminds me of a reported conversation about the relative qualities of various social groups. Commented one, "There are good and bad among all of them." "He's prejudiced," said another, who was strongly imbued with the supposed superiority of his own group.

That I am not prejudiced against OTL amplifiers on principle, note my comments in the last paragraph of the article ("Is the Output Transformer Out," RADIO-ELECTRONICS, January, 1958): transistors do promise to make the OTL amplifier really practical. Mr. Futterman himself states that an output tube specially designed for it is really needed. So why do we not have such a tube type? Surely because the natural impedance ranges of tubes and dynamic loudspeakers differ so widely as to make it impractical.

The most logical impedance-matching device is the transformer. It does this job with less inherent distortion than a tube, and can be designed to avoid the deficiencies of its early prototypes. The cost aspect is answered by the recent twin-coupled design ("High Fidelity at Low Cost With Twin-Coupled Amplifier," RADIO-ELECTRONICS, November, 1957), to which I called attention in my penultimate paragraph. This design also solves the "impossible" situation relative to including the output transformer in the feedback loop.

To answer Mr. Futterman's points:

1. *Notch distortion: (a)* I acknowledge that notch distortion can occur with triodes—what I pointed out is that it is less likely; *(b)* it can also be eliminated using both pentodes and output transformers; vide McIntosh and twin-coupled.

2. *Feedback:* Mr. Futterman and the Philip's people apparently subscribe to the "more feedback the better" school. Demonstrations have repeatedly shown by subjective listening tests, that well-designed nonfeedback amplifiers, or ones with little feedback, are credited with giving "cleaner" reproduction than types using fabulously large amounts to achieve such wonderful specifications —(0.1% or better).

(*Continued on Page* 20)

F.C.C. COMMERCIAL OPERATOR LICENSE

Training... for Jobs in Electronics

F.C.C. LICENSE—THE KEY TO BETTER JOBS

An F.C.C. *commercial* (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire *licensed* technicians.

WHICH LICENSE FOR WHICH JOB?

The THIRD CLASS radiotelephone license is of value primarily in that it qualifies you to take the second class examination. The scope of authority covered by a third class license is extremely limited.

The SECOND CLASS radiotelephone license qualifies you to install, maintain and operate most all radiotelephone equipment except commercial broadcast station equipment.

The FIRST CLASS radio telephone license qualifies you to install, maintain and operate every type of radiotelephone equipment (except amateur) including all radio and television stations in the United States, its territories and possessions. This is the highest class of radiotelephone license available.

GRANTHAM TRAINING PREPARES YOU

The Grantham Communications Electronics Course prepares you for a *FIRST CLASS* F.C.C. license, and it does this by TEACHING you electronics. Each point is covered simply and in detail, with emphasis on making the subject easy to understand.

LEARN BY CORRESPONDENCE OR IN RESIDENT CLASSES

Grantham School of Electronics *specializes* in preparing students to pass F. C. C. examinations. Correspondence training is conducted from Washington and Hollywood; resident DAY and EVENING classes are held in both cities. Either way, we train you quickly and well—NO previous training required. A beginner may qualify for his First Class commercial F.C.C. license in as little as 12 weeks!

OUR GUARANTEE

If you should fail the F. C. C. exam after finishing our course, we guarantee to give additional training at NO ADDITIONAL COST. Read details in our free booklet.

HERE'S PROOF...

that Grantham students prepare for F.C.C. examinations in a minimum of time. Here is a list of a few of our recent graduates, the class of license they got, and how long it took them:

	License	Wks.
Edward Dahl, 7800 Old Chester Rd., Bethesda, Md.	1st	11
Griffin Kane, 3125 Wabash Ave., Los Angeles, Calif.	2nd	9
Beamon Meares, 1536 17th St., NW, Washington, D.C.	1st	11
Larry Pacifico, 65 Main St., Roseto, Pa.	1st	12
Tooru Iwahashi, Honohina, Hakalua, Hawaii	2nd	8
Basil D'Imperio, 2223 H St., NW, Washington, D.C.	1st	12
John Ward, 407 E. Cowden Ave., Midland, Texas	1st	10
Herbert Halbig, 315 Park St., Tupper Lake, N.Y.	1st	11
Vregh Godoshian, 312 E. Wilson St., Pontiac, Mich.	1st	11
Antone Mello, 68 Union St., Nantucket, Mass.	1st	10

Grantham School OF ELECTRONICS

Hollywood Division
1505 N. Western Ave.
Hollywood 27, Calif.
Phone: HO 2-1411

for **FREE** Booklet CLIP COUPON and mail in envelope or paste on postal card.

Washington D.C. Division
821 - 19th Street, N.W.
Washington 6, D.C.
Phone: ST 3-3614

MAIL COUPON TO SCHOOL NEAREST YOU

Grantham Schools, Desk 84-G

821 - 19th Street N.W.
Washington 6, D.C.

OR

1505 N. Western Ave.
Hollywood 27, Calif.

Please send me your free booklet telling how I can get my commercial F. C. C. license quickly. I understand there is no obligation and no salesman will call.

Name_____ Age_____

Address_____

City_____ State_____

I am interested in: ☐ Home Study, ☐ Resident Classes

YES! WE HAVE

STILL NO PRINTED CIRCUITRY IN CHASSIS

Even though Dr. Alexander Ellett, head of Zenith's research department, is recognized as the daddy of printed circuitry through his work on radio proximity fuses, still Zenith uses no printed circuitry in its TV chassis because it means more service headaches and often causes service delays.

LESS SERVICE HEADACHES FOR SERVICEMEN

Easier to service...more accessible

ZENITH'S HANDCRAFTED SERVICE-SAVER HORIZONTAL CHASSIS WITH NO PRINTED CIRCUITS IN THE CHASSIS

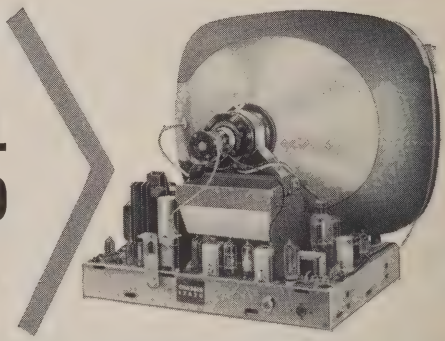

We think it's worth the extra cost of HANDcrafted standard circuitry to get the best performance and fewer service headaches and so do thousands of dealers who would sooner sell customer satisfaction than a price tag.

ZENITH

ZENITH RADIO CORPORATION, Chicago 39, Illinois
The quality goes in before the Zenith name goes on.
Backed by 39 years of leadership in radionics exclusively.
Also makers of Radio, High-Fidelity Instruments and fine Hearing Aids.

NO PRINTED CIRCUITS IN ZENITH TV CHASSIS

ZENITH HANDCRAFTED STANDARD CIRCUITRY COSTS MORE BUT IT MEANS MORE SATISFIED CUSTOMERS FOR ZENITH DEALERS AND SERVICEMEN

QUALITY BY

ZENITH®

THE ROYALTY OF TELEVISION

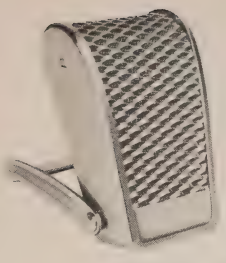

NEW SUPER-CARDIOID
...and super value!

Difficult acoustic conditions are child's play for this sensational new super-cardioid microphone. Background noise, undesirable echo, and other unwanted sounds disappear when the ESL-SC403 is used for high fidelity broadcasting or recording of music and speech.

Excellent performance, inconspicuous size, and inexpensive price make this advanced moving coil microphone additionally suitable for lecture halls, churches, and conventions. A high impedance model is designated the ESL-SC403H. Write for details on other new ESL microphones.

	ESL-SC403	ESL-SC403H
FREQUENCY RESPONSE:	*50 to 12,000 cps ±3 db*	
DIRECTIONAL CHARACTERISTIC:	*super cardioid*	
INTERNAL IMPEDANCE:	*200 ohms*	*45,000 ohms*
OUTPUT LEVEL:	*—50 db*	*2.2 mv/μbar*
REFERENCE LEVEL:	*1 mw/10 dynes/cm²*	
DIMENSIONS:	*2" x 1½" x 3¾"*	
NET PRICE:	*$25.50*	*$28*

FOR LISTENING AT ITS BEST

ESL *Electro-Sonic Laboratories, Inc.*

Dept. E • 35-54 Thirty-sixth Street • Long Island City 6, N.Y.

BENCO

UNMISTAKABLY - THE FINEST NAME IN COMMUNITY TV

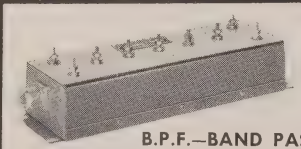

B.P.F.—BAND PASS FILTER

A multi-stage HI-Q filter incorporating two HI-Q bridged T traps. Total attenuation in excess of 80 db on the trap frequencies. Will remove adjacent channel interference where other devices have failed. $89.50

H. C. A. HIGH OUTPUT SINGLE CHANNEL AMPLIFER

5 VOLTS R. F.

Maximum output

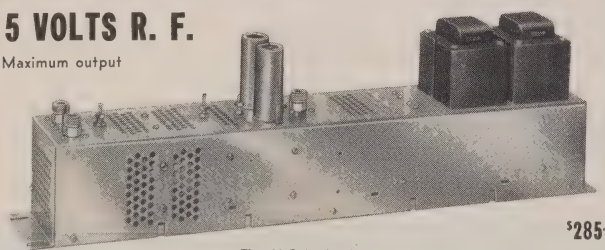

$285.00

- ★ 20 db gain minimum
- ★ 6 mc/s bandwidth
- ★ Silicon Rectifier
- ★ Drives a low band signal thru 2½ mi. of K-14 type cable

The H.C.A. is designed for use as a final TV channel amplifier and provides the highest output of any known model on the market today. A commercial transmitting tube (6252) is used to deliver the full-rated output without distortion.

PRICES ARE SUGGESTED USER NET — SLIGHTLY HIGHER IN SOME U.S. AREAS

BENCO
TELEVISION ASSOCIATES LTD.
27 Taber Rd., Rexdale, Ontario, Canada

Sirs: Please send me full details on the ☐ BPF ☐ HCA

Name .....

Address .....

City State or Prov.

3. *Transient performance:* Mr. Futterman's statement here requires qualification. Large amounts of feedback do serve to reduce transient distortion, but only one form of it. Often other forms are introduced by it. Although the latter forms may not be shown by standard measurement techniques, they can be very audible.

I would like to pass on a correction to Fig. 5 of my article, as noticed by Philips. The plate-coupling resistor for the ECC83 comes from the screen of the upper UL84, not the B-plus line, as shown. While this arrangement does give theoretical true phase inversion, similar to the Peterson-Sinclair circuit of Fig. 6, my basic point stands:

The audio voltage to *ground*, which is responsible for any stray electrical coupling that may occur, is still much greater from the plate than the cathode of the ECC83, and the circuit is of quite high impedance to make it susceptible to such transfer. This comes back to Mr. Futterman's point about tubes. Transistors provide us with much lower impedance circuits and make OTL design much more practical.

HERBERT RAVENSWOOD

New York, N. Y.

WHAT'S IT ALL ABOUT?

Dear Editor:

With reference to the discussion on Doppler effects by Messrs. Klipsch, Janszen, et al, it is puzzling to me, having listened with innocent pleasure to reproduced organ music on my Ultra-Linear and other devices for, lo, these many, to learn that the literature rates this effect at the same time as being both imperceptible and intolerable.

With a sincere desire to confuse the issue further, I (no electronics pundit) wonder if anybody has considered the relation between FM effects in reproduced music and possibly similar effects occurring in sound; for example, from an actual organ. In such a case, doesn't the varying velocity of the air in wave movements at, say, 60 cycles, carry with it, as wavelets on a tide, a complex, shifting pattern of frequencies as it strikes the ear? If so, who has complained? And if these FM effects are perceptible, or intolerable, is it not possible to determine the ratio of the effects in the reproduced music to those in the original? Or the ratio between mikeside and the middle of the hall?

How does all the above appear compared to an analysis of the wild and wonderful sound of a pipe organ in a cathedral with uncontrolled acoustics? The instruments of music are allowed to retain their ancient peculiarities; the air will not be denied its eccentricities as a conveyor of sound; the human ear is variable between individuals, times and places. Must the mind, itself fallible in its judgments, now be driven mad by an endless consideration of whether a thing is perceptible or not?

ARTHUR QUALEY

La Puente, Calif.

END

1948—*Early "point contact" transistor.*

The remarkable transistor observes its 10th birthday

In 1948, Bell Telephone Laboratories announced the invention of the transistor. In 1958, the transistor provided the radio voice for the first United States satellite.

To advance the transistor to its high level of usefulness, Bell Labs had solved problems which, in themselves, approached the invention of the transistor itself in scientific achievement.

First, there had to be germanium of flawless structure and unprecedented purity. This was obtained by growing large single crystals—and creating the "zone refining" technique to purify them to one harmful part in *ten billion.*

The "junction" transistor, another radical advance, spurred transistor use. Easier to design, lower in noise, higher in gain and efficiency, it became the heart of the new electronics.

An ingenious technique for diffusing a microscopically thin layer on semiconductors was created. The resulting "diffused base" transistor, a versatile broadband amplifier, made possible the wide use of transistorized circuits in telephony, FM, TV, computers and missiles.

In telephony the transistor began its career in the Direct Distance Dialing system which sends called telephone numbers from one exchange to another.

For Bell System communications, the transistor has made possible advances which would have been impossible or impractical a brief decade ago.

1958—*Satellite transistor, incorporating 10 years of Bell Labs research and development.*

BELL TELEPHONE LABORATORIES

WORLD CENTER OF COMMUNICATIONS RESEARCH AND DEVELOPMENT

POWER TUBES
E-290T
triodes, tetrodes, pentodes and beam tubes — 8 pages.

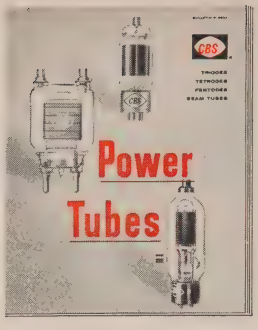

MILITARY AND SPECIAL-PURPOSE TUBES
E-290S
military, computer, uhf, hi-fi and pass tubes — 12 pages.

GAS TUBES AND POWER RECTIFIERS
E-290C
gas diodes, gas triodes and tetrodes (cold cathode and thyratron) and power rectifiers — 16 pages.

PHOTOTUBES AND PHOTOCELLS
E-290P
vacuum and gas phototubes and photocells — 12 pages.

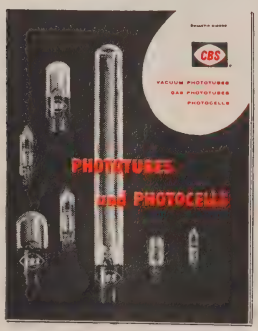

Now...the most comprehensive industrial tube line ...over 400 CBS types!

In keeping with the growing importance of industrial tubes, CBS-Hytron has more than doubled its industrial tube line. Over 400 types make it the most extensive line. For example, CBS-Hytron now offers the widest selection of gas tubes, phototubes and photocells.

The four industrial tube catalogs illustrated include: reference charts with ratings and typical operating conditions, basing and circuit diagrams, and application notes. Ask your CBS-Hytron distributor or write us for the ones you need.

CBS tubes®

CBS-HYTRON, Danvers, Mass.
A Division of
Columbia Broadcasting System, Inc.

For the best in entertainment tune to CBS

WE'RE MAKING IT EASIER THAN EVER TO BECOME A WELL PAID

RADIO-TELEVISION SERVICE TECHNICIAN

NOW – Just $6 Starts You Training in RADIO-TELEVISION

the SPRAYBERRY "Learn-by-Doing" Way . . .

25 BIG, COMPLETE KITS of PARTS & EQUIPMENT

To help you learn *fast* the practical side of Radio-Television, we send you expertly engineered training kits to test and assemble for interesting, valuable shop-bench practice!

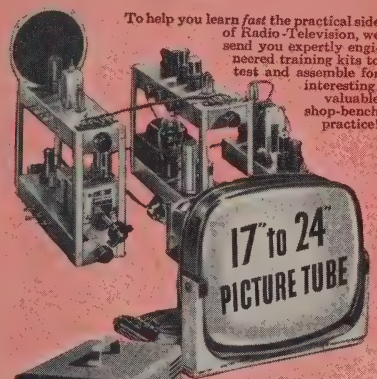

- The new Sprayberry Training Television Receiver, built and tested in 5 sections.
- Now offered . . . this fine modern oscilloscope.
- You build this powerful two-band superheterodyne radio receiver.

Big New CATALOG AND Sample Lesson FREE!

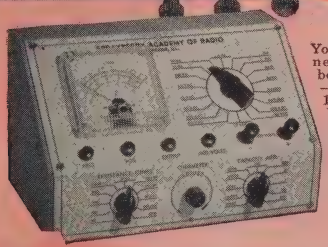

You build the new Sprayberry tester—a complete 18-range Volt-Ohm-Milliammeter test meter.

★ ★ ★ ★ **This great industry is begging for trained men . . . to step into good paying jobs or a profitable business of their own! Our new plan opens the doors of Radio-Television wide to every ambitious man who is ready to act at once!**

Men by the thousands... trained Radio-Television Service Technicians...are needed at once! Perhaps you've thought about entering this interesting, top paying field, but lack of ready money held you back. Now—*just $6 enrolls you* for America's finest, most up to date home study training in Radio-Television! Unbelievable? No, the explanation is simple! We believe Radio-Television *must* have the additional men it needs as quickly as possible. We are willing to do our part by making Sprayberry Training available for less money down and on easier terms than ever before. This is your big opportunity to get the training you need...to step into a fine job or your own Radio-Television Service Business.

Complete Facts Free—Act Now; Offer Limited

Only a limited number of students may be accepted on this liberal and unusual basis. We urge you to act at once...mail the coupon below and get complete details plus our big new catalog and an actual sample lesson—*all free.* No obligation...no salesman will bother you.

HOME STUDY TRAINING IN SPARE TIME

Under world-famous 27-year old Sprayberry Plan, you learn entirely at home in spare time. You keep on with your present job and income. You train as fast or as slowly as you wish. You get valuable kits of parts and equipment for priceless shop-bench practice. And everything you receive, lessons and equipment alike, is all yours to keep.

LET US PROVE HOW EASILY YOU CAN LEARN!

Radio-Television needs YOU! And Sprayberry is ready to train you on better, easier terms, that any ambitious man can afford. *Just $6 starts you!* Mail coupon today... let the facts speak for themselves. You have everything to gain. Let us prove the kind of opportunity that's in store for you!

SPRAYBERRY Academy of Radio-Television
1512 Jarvis Avenue, Dept. 20-H, Chicago 26, Illinois

Mail This Coupon Now—No Salesman Will Call

Sprayberry Academy of Radio-Television
Dept. 20-H, 1512 W. Jarvis Ave., Chicago 26, Ill.

Please rush all information on your ALL-NEW Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me. Include New Catalog and Sample Lesson FREE.

NAME..... Age.....

ADDRESS.....

CITY..... ZONE ..... STATE.....

Up goes another Winegard!

More Winegard Colorceptors are being sold today than any other all-channel yagi.

Discover for yourself the profit and personal satisfaction that come from selling the very finest antenna that can be installed on your customer's home.

See your distributor for free Winegard sales aids and displays. Write for Technical bulletin WCL4.

Winegard Co.

3013-6 Scotten Blvd., Burlington, Iowa

Shown is Model CL-4

Photo by R. K. Sunderbruch

the experts say... in High Fidelity the best buys are EICO®

EICO KITS and WIRED

HFS2 Speaker System

BETTER ENGINEERING Since 1945 EICO has pioneered the concept of test instruments in easy-to-build kit form — has become world-famous for laboratory-precision instruments at low cost. Now EICO is applying its vast experience to the creative engineering of *high fidelity*. Result: high praise from such authorities as Canby of AUDIO, Marshall of AUDIOCRAFT, Holt of HIGH FIDELITY, Fantel of POPULAR ELECTRONICS, Stocklin of RADIO TV NEWS, etc. — as well as from the critical professional engineers in the field.†

SAVE 50% Mass purchasing, and a price policy deliberately aimed to encourage mass sales, make this possible.

EASY INSTRUCTIONS You need no previous technical or assembly experience to build any EICO kit — the instructions are simple, step-by-step, "beginner-tested."

DOUBLE 5-WAY GUARANTEE Both EICO, and your neighborhood distributor, guarantee the parts, instructions, performance . . . as well as *lifetime* service and calibration at nominal cost . . . for any EICO kit or wired unit.

BEFORE YOU BUY, COMPARE At any of 1200 neighborhood EICO distributors coast to coast, you may examine and listen to any EICO component. Compare *critically* with equipment several times the EICO cost — then *you* judge. You'll see why the experts recommend EICO, kit or wired, as best buy.

†Thousands of unsolicited testimonials on file.

HFT90 FM Tuner with "eye-tronic" tuning

HF61 Preamplifier

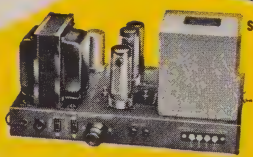

HF60, HF50 Power Amplifiers

HFS2 Speaker System: Uniform loading & **natural** bass 30-200 cps achieved via **slot-loaded** split conical bass horn of 12-ft path. Middles & lower highs from front side of 8½" cone, edge-damped & stiffened for smooth uncolored response. Suspensionless, distortionless spike-shaped super-tweeter radiates **omni-directionally.** Flat 45-20,000 cps, useful to 30 cps. 16 ohms. HWD: 36", 15¼", 11½". " . . . rates as excellent . . . unusually musical . . . **really** non-directional" — Canby, AUDIO. "Very impressive" — Marshall (AUDIOCRAFT). **Walnut or Mahogany, $139.95. Blonde, $144.95.**

HFT90 FM Tuner equals or surpasses wired tuners up to 3X its cost. New, pre-wired, pre-aligned, temperature-compensated "front end" — drift-free. Sensitivity, 1.5 uv for 20 db quieting, is 6X that of other kit tuners. DM-70 traveling tuning eye. Response 20-20,000 cps±1 db. Cathode follower & multiplex outputs. **Kit $39.95*. Wired $65.95*. Cover $3.95. *Less cover, excise tax incl.**

HF61A Preamplifier, providing the most complete control & switching facilities, and the finest design, offered in a kit preamplifier, " . . . rivals the most expensive preamps . . . is an example of high engineering skill which achieves fine performance with simple means and low cost." — Joseph Marshall, AUDIOCRAFT. **HF61A Kit $24.95, Wired $37.95, HF61 (with Power Supply) Kit $29.95. Wired $44.95.**

HF60 60-Watt Ultra Linear Power Amplifier, with Acro TO-330 Output Transformer, provides wide bandwidth, virtually absolute stability and flawless transient response. " . . . is one of the best-performing amplifiers extant; it is obviously an excellent buy." —AUDIOCRAFT Kit Report. **Kit $72.95. Wired $99.95. Matching Cover E-2 $4.50.**

HF50 50-Watt Ultra-Linear Power Amplifier with extremely high quality Chicago Standard Output Transformer. Identical in every other respect to HF60 and same specifications up to 50 watts. **Kit $57.95. Wired $87.95. Matching Cover E-2 $4.50.**

HF30 30-Watt Power Amplifier employs 4-EL84 high power sensitivity output tubes in push-pull parallel, permits Williamson circuit with large feedback & high stability. 2-EZ81 full-wave rectifiers for highly reliable power supply. Unmatched value in medium-power professional amplifiers. **Kit $39.95. Wired $62.95. Matching Cover E-4 $3.95.**

HF-32 30-Watt Integrated Amplifier Kit $57.95. Wired $89.95.

HF52 50-Watt Integrated Amplifier with complete "front end" facilities and Chicago Standard Output Transformer. Ultra-Linear power amplifier essentially identical to HF50. The least expensive means to the highest audio quality resulting from distortion-free high power, virtually absolute stability, flawless transient response and "front end" versatility. **Kit $69.95. Wired $109.95. Matching Cover E-1 $4.50.**

HF20 20-Watt Integrated Amplifier, complete with finest preamp-control facilities, excellent output transformer that handles 34 watts peak power, plus a full Ultra-Linear Williamson power amplifier circuit. Highly praised by purchasers, it is established as the outstanding value in amplifiers of this class. **Kit $49.95. Wired $79.95. Matching Cover E-1 $4.50.**

Prices 5% higher in the West

HF12 12-Watt Integrated Amplifier, absolutely free of "gimmicks", provides complete "front end" facilities & true fidelity performance of such excellence that we can recommend it for **any** medium-power high fidelity application. Two HF12's are excellent for stereo, each connecting directly to a tape head with no other electronic equipment required. **Kit $34.95. Wired $57.95.**

HFS1 Two-Way Speaker System, complete with factory-built cabinet. Jensen 8" woofer, matching Jensen compression-driver exponential horn tweeter. Smooth clean bass; crisp extended highs. 70-12,000 cps ± 6 db. Capacity 25 w. Impedance 8 ohms. HWD: 11" x 23" x 9". Wiring time 15 min. **Price $39.95.**

THE HI-FI EXPERTS SAY:

"For those who have been looking for a well-engineered yet inexpensive power amplifier, the newly-released EICO Model HF20 unit might offer a simple solution to their problem. Not only does this unit provide 20 watts of power but the circuit incorporates a preamplifier and a variety of controls on a single chassis."
William A. Stocklin, Editor, RADIO TV NEWS

"The new EICO 'standard' speaker system . . . produces sound that to my musical ears rates as excellent, from high top to clean low bottom."
Edward Tatnall Canby, AUDIO Magazine

Fill out coupon on other side for FREE CATALOG

HF52, HF20 Integrated Amplifiers

HF12 Integrated Amplifier

HF30 Power Amplifier

HFS1 Speaker System

EICO®

33-00 Northern Boulevard, L. I. C. 1, N. Y.

Over 1 Million EICO instruments in use the world over.

©1958

the specs prove it . . your BEST BUY is EICO

for COLOR & Monochrome TV servicing

FREE CATALOG

shows you HOW TO SAVE 50% on 50 models of top quality professional test equipment.

MAIL COUPON NOW!

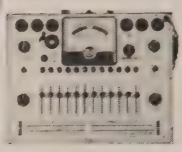

NEW! DYNAMIC CONDUCTANCE TUBE & TRANSISTOR TESTER #666

KIT $69.95 WIRED $109.95

COMPLETE with steel cover and handle.

SPEED, ease, unexcelled accuracy & thoroughness. **Tests all receiving tubes** (and picture tubes with adapter). **Composite indication of** Gm, Gp & peak emission. **Simultaneous sel** of any 1 of 4 combinations of 3 plate voltages, 3 screen voltages, 3 ranges of continuously variable grid voltage (with 5% accurate pot). **New series-string voltages:** for 600, 450, 300 ma types. **Sensitive** 200 ua meter. **5 ranges meter sensitivity** (1% shunts & 5% pot). **10 SIX-position lever switches:** freepoint connection of each tube pin. **10 pushbuttons: rapid** insert of any tube element in leakage test circuit & speedy sel. of individual sections of multi-section tubes in merit tests. **Direct-reading** of inter-element leakage **in ohms. New gear-driven rollchart. Checks n-p-n & p-n-p transistors:** separate meter readings of **collector leakage current & Beta** using internal dc power supply. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet. **CRA Adapter $4.50**

5" PUSH-PULL OSCILLOSCOPE #425

KIT $44.95 Wired $79.95

7" PUSH-PULL OSCILLOSCOPE #470

KIT $79.95 Wired $129.50

TUBE TESTER #625

KIT $34.95 Wired $49.95

- tests 600 mil series string type tubes
- illuminated roll-chart

Pix Tube Test Adapter $4.50

6V & 12V Battery Eliminator & Charger #1050:

KIT $29.95 Wired $38.95

Extra filtered for transistorized eqpt, #1060: KIT $38.95, Wired $47.95

NEW! TV-FM SWEEP GENERATOR & MARKER #368

KIT $69.95 WIRED $119.95

Entirely electronic sweep circuit (no mechanical devices) with accurately-biased **incereductor** for excellent linearity. **Extremely flat** RF output: **new AGC circuit** automatically adjusts osc. for max. output on each band with min. ampl. variations. **Exceptional tuning accuracy:** edge-lit hairlines eliminate parallax. **Swept Osc. Range** 3-216 mc in **5 fund. bands. Variable Marker Range** 2-75 mc in **3 fund. bands:** 60-225 mc on harmonic band. **4.5 mc Xtal Marker Osc., xtal supplied.** Ext. Marker provision. Sweep Width 0-3 mc lowest max. deviation to 0-30 mc highest max. dev. 2-way blanking. Narrow range phasing. Attenuators: Marker Size, RF Fine, RF Coarse (4-step decade). Cables: output, 'scope horiz., 'scope vertical. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet.

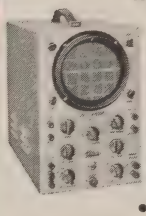

NEW! COLOR and Monochrome DC to 5 MC LAB & TV 5" OSCILLOSCOPE #460

KIT $79.95 WIRED $129.50

- **Features DC Amplifiers!**

Flat from DC-4.5 mc, usable to 10 mc. **VERT. AMPL.:** sens. 25 rms mv/in; input Z 3 megs; direct-coupled & push-pull **thruout;** K-follower coupling bet. stages; 4-step freq-compensated attenuator up to 1000:1. **SWEEP:** perfectly linear 10 cps-100 kc (ext. cap. for range to 1 cps); **preset TV V & H positions;** auto. sync. ampl. & lim. **PLUS:** direct or cap. coupling; bal. or unbal. inputs; edge-lit engraved lucite graph screen; dimmer; filter; bezel fits std photo equipt. High intensity trace CRT. 0.06 usec rise time. Push-pull hor. ampl., flat to 400 kc, sens. 0.6 rms mv/in. Built-in volt. calib. Z-axis mod. Sawtooth & 60 cps outputs. Astig. control. Retrace blanking. Phasing control.

Sep. hi-gain RF & lo-gain audio inputs. Special noise locator. Calibrated wattmeter.

KIT $24.95 Wired $39.95

DELUXE MULTI-SIGNAL TRACER #147

20,000 Ohms/Volt MULTIMETER #565

KIT 24.95 Wired $29.95

1000 Ohms/Volt MULTIMETER #536

KIT $12.90 Wired $14.90

NEW! RF SIGNAL GENERATOR #324

KIT $26.95 WIRED $39.95

150 kc to 435 mc with ONE generator! Better value than generators selling at 2 or 3 times its cost! Ideal for IF-RF alignment, signal tracing & trouble-shooting of TV, FM, AM sets; marker gen.; 400 cps audio testing; lab. work. **6 fund. ranges: 150-400 kc, 400-1200 kc, 1.2-3.5 mc, 3.5-11 mc, 11-37 mc, 37-145 mc; 1 harmonic band 111-435 mc. Freq. accurate to ±1.5%;** 6:1 vernier tuning & excellent spread at most important alignment freqs. **Etched tuning dial,** plexiglass windows, **edge-lit hairlines.** Colpitts RF osc. **directly plate-modulated by K-follower for** improved mod. **Variable depth of int. mod. 0-50%** by 400 cps Colpitts osc. **Variable gain ext. amplifier:** only 3.0 v needed for 30% mod. **Turret-mounted coils slug-tuned** for max. accuracy. Fine & Coarse (3-step) RF attenuators. RF output 100,000 uv; AF sine wave output to 10 v. 50-ohm output Z. 5-way jack-top binding posts for AF in/out; coaxial connector & shielded cable for RF out. 12AU7, 12AV7, selenium rectifier; xmfr-operated. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet.

NEW! PEAK-to-PEAK VTVM #232 & UNI-PROBE (pat. pend.)

KIT $29.95 WIRED $49.95

Half-turn of probe tip selects DC or AC-Ohms.

Uni-Probe — exclusive with EICO — only 1 probe performs all functions!

Latest circuitry, high sensitivity & precision, wide ranges & versatility. **Calibration without removing from cabinet.** New balanced bridge circuit. High Z input for negligible loading. 4½" meter, can't burn-out circuit. **7 non-skip ranges on every function.** 4 functions: ±DC Volts, —DC Volts, AC Volts, Ohms. Uniform 3 to 1 scale ratio for extreme wide-range accuracy. **Zero center.** One zero-adj. for all functions & ranges. **1% precision** ceramic multiplier resistors. Measure **directly** peak-to-peak voltage of complex & sine waves: 0-4, 14, 42, 140, 420, 1400, 4200. DC/RMS sine volts: 0-1.5, 5, 15, 50, 150, 500, 1500 (up to 30,000 v. with HVP probe & 250 mc with PRF probe). Ohms: 0.2 ohms to 1000 megs. 12AU7, 6AL5, selenium rectifier; xfmr-operated. Deep-etched satin aluminum panel, rugged grey wrinkle steel cabinet.

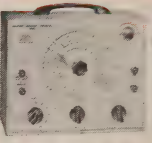

Reads 0.5 ohms —500 megs, 10 mmfd—5000 mfd, power factor.

KIT $19.95 Wired $29.95

R-C BRIDGE & R-C-L COMPARATOR #950S

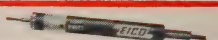

VTVM PROBES	KIT	Wired
Peak-to-Peak	$4.95	$6.95
RF	$3.75	$4.95
High Voltage Probe-1		$6.95
High Voltage Probe-2		$4.95
SCOPE PROBES		
Demodulator	$3.75	$5.75
Direct	$2.75	$3.95
Low Capacity	$3.75	$5.75

EICO, 33-00 Northern Blvd. Long Island City 1, N. Y. C-6

Show me HOW TO SAVE 50% on Test Equipment and Hi-Fi. Send me FREE Catalog and name of neighborhood distributor.

Name .....

Address .....

City ..... Zone ..... State .....

TURN PAGE FOR MORE EICO VALUES

Prices 5% higher on West Coast.

EICO®

Send for FREE CATALOG now

33-00 Northern Blvd., Long Island City 1, N.Y.

RADIO SIGNALS TO VENUS

. . . Radio to the Planets Is Now Assured . . .

THE idea of bouncing radio signals from heavenly bodies is not new. It originated with the writer in an article entitled "Can We Radio the Planets?" in the February, 1927, issue of *Radio News*. It was then proposed to send a radio signal from the earth to the moon and back via short waves. The calculated elapsed time of the signal transit was 2.5 seconds to cover the two-way distance—twice 238,854 miles, or 477,708 miles, to and from the moon. Nineteen years later, on Jan. 10, 1946, Lt. Col. John H. DeWitt and associated scientists of the US Signal Corps first established actual radio contact with the moon. The elapsed time was 2.4 seconds. Our original predicted time was 2.5 seconds, an error of 0.1 second. In the article mentioned, we also spoke of signaling Mars and Venus, but refrained from giving elapsed signal time, because of the extreme complexity of the problem. In 1927, we had little practical knowledge of the penetration of short waves beyond the earth's atmosphere and into space, as well as eventual reflection of the returning high-frequency waves on the Heaviside layer.

It is gratifying to note that in the fall of 1959 man will at last attempt to signal the planets—Venus and Mars, not as a stunt but for serious astronomic and scientific purposes. British radio astronomers, using the world's largest radio telescope at the Jodrell Bank radio observatory, intend to radio-contact Venus first. The scientists state that they will have a power output 3,000 times greater than the average military or airfield radar installation! Many new and important facts will be learned from such a series of experiments in bouncing signals off Venus. One will be the rotation of Venus on its axis, not known now. Our closest sister planet is constantly shrouded in dense clouds. Hence man has so far not seen the surface of Venus. Its rotation period is thought to be 20 to 30 days—a guess at best. Radio astronomy via reflected signals may give us a clue to Venus' exact time of rotation.

Let us now consider how the scientists will "shoot" Venus at its inferior conjunction in the fall of 1959, when Venus will approach within 30,000,000 miles of the earth. (The closest approach was 26 million miles on Jan. 28, 1958.) At the speed of 186,000 miles a second, the radio signal will take 5.36 *minutes* to cover the distance out and back between the two planets (2.68 minutes to go to Venus, 2.68 minutes to return).

The inherent difficulty with the present-day state of the art of radio is our inability to concentrate a beam of radio-frequency signals—the diffusion is too great. The same is true of light. With the tremendous distances with which we have to work, the beam spreads. It is as if we aimed a high-pressure stream of water at a distant large football. Most of the water will not hit the object. A large part of that which hits will splash and reflect at different angles and only a comparatively minute amount will come back in the direction of the nozzle.

It is for this reason that the British scientists must use a large power output if they hope to get back an intelligible radio echo signal from Venus.

The Jodrell Observatory radio telescope, the largest known in the world today, has a great advantage in making these experiments. On account of its large size, it can concentrate the transmitter power output into a narrower beam and, again due to its large size, it concentrates the weak echo of the returned signal more effectively.

If in the future it should become possible to concentrate and narrow the radio beam further, much less power would be required to contact the various planets. Obviously, the greater the distance between earth and the outlying planets, the more difficult the problem of bouncing back signals.

It can be seen from the above that as earth and Venus pull apart, the distance between them increases rapidly, until at maximum separation—at superior conjunction—the distance is 161 million miles. Here it would take the round-trip signal 28.8 minutes to bridge the space. But now the sun would become an obstacle, partly blocking the path of the signal.

Would the signal be absorbed by the sun? Yes. Another interesting and perhaps far-reaching test would be the effect of the sun's gravitational attraction on the returning radio echo. This is known as the Einstein shift. If, before or after superior conjunction of Venus, we send a signal to Venus in such a manner that the return signal comes close to the sun, the signal should be bent toward the sun. The Einstein shift has been confirmed with light rays, but not with radio waves up to now. This, however, at the present time can only remain a theoretical consideration. The experiment could not possibly be conducted with present radio frequencies unless we had a radio-astronomical bowl transmitting and receiving antenna *at least 60 miles in diameter!*

In the future when we can produce super high frequencies of the electronoptical variety, which approach the frequency of light, it will be possible to record the Einstein shift electronically.

There will not be very much practical difference when we try to signal Mars, because the distances between our two planets are not too great at nearest approach—about 35 million miles for Mars, 26 million for Venus. We can therefore look forward to an early radio contact with Mars, too.

What about the further outlying planets? Possible, but increasingly difficult the further out we go. To bounce a radio signal off Jupiter will take 1 hour and 10 minutes for the two-way transit; 2 hours, 22 seconds for Saturn; 12 hours, 50 minutes for Pluto! To hit *squarely* such a distant planet, say Neptune, 2,677 million miles away at its closest, is in itself a difficult feat; for the signal to return to earth *without missing it altogether* would be an achievement of a high order—at least at the present state of the art.

—*H.G.*

Combining a 2-band transistor superhet radio and a marching compass gives you a compact, accurate, portable direction finder

ELECTRONIC COMPASS

TO GUIDE YOU HOME

By J. E. PUGH, JR.

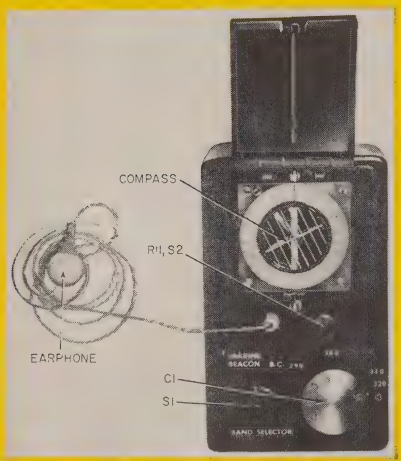

Completed unit is small enough to slip into coat pocket.

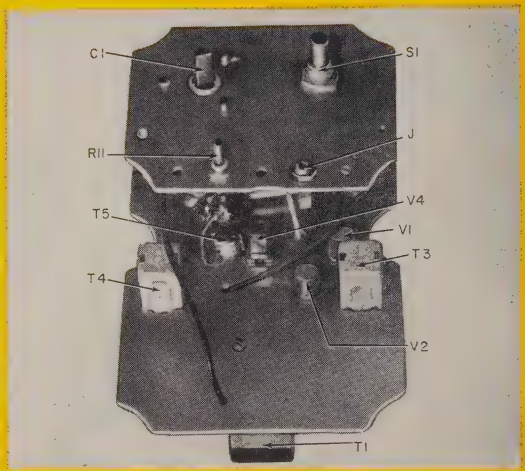

Top view of the inside chassis assembly.

AN electronic compass is a worthwhile investment for people interested in outdoor activities such as motorboating, sailing, hunting, trapping, berry picking, camping, hiking or other activity where there is a possibility of getting lost.

The instrument described here was designed especially for uses where portability and ruggedness are important. It is housed in a strong Bakelite case that is easily waterproofed. It is small, lightweight, sensitive; has a sharp null point and incorporates a built-in magnetic compass. This combination of directional receiver and built-in compass is a true electronic compass and not just a radio homing device. It makes a rapid and accurate determination of actual position possible.

The superhet receiver

The receiver is a direction-sensitive superheterodyne using a class-B detector and a single audio stage. Two tuning ranges are used: the broadcast band (550 to 1,600 kc) and the marine radio-beacon band (285 to 325 kc). The broadcast band is used so bearings can be taken from nearly any location and to provide entertainment while outdoors.

The radio-beacon band provides an extra degree of usefulness to boat owners. It is a desirable feature because many rivers, canals and harbors have radio beacons located near their entrances. Broadcast stations ordinarily will not permit such close work since they are seldom found in such a desirable location. If the electronic compass is used only for nonboating activities, the marine radio-beacon band can be eliminated.

A compact, flat ferrite loop antenna provides the directional properties needed for taking bearings on radio stations. It is mounted parallel to the length of the case to obtain the null point when the long axis of the receiver is in line with the station. The antenna has a high Q (about 450 to 790 kc) for maximum selectivity and sensitivity. A matching two-gang tuning capacitor tunes the antenna and local oscillator coil over the band.

The broadcast band is tuned with the BAND SELECTOR (S1) in position BC. When the switch is thrown to MARINE BEACON, capacitor C4 is shunted across C1-a, C2 and T1 to drop the resonance range of this circuit to the radio-beacon band and at the same time restrict the tuning range so it fits this narrower band. Similarly C6 is shunted across C1-b, C3 and T2. And C5 is switched into the circuit to permit more accurate tracking of the oscillator circuit.

Although its value is not critical, C7 may have to be changed to a slightly different value in some instances. It must be large enough so the local oscillator functions properly at the lowest frequency in the marine band, but at the same time it must not be so large that feedback is excessive at the highest broadcast frequency. Too much feedback causes the oscillator to generate harmonics and reception of signals above the desired range will result.

Agc circuitry

The first three stages use 2N247 drift transistors. These transistors have high gain through the highest frequency used and, because of their very low base-to-collector capacitance, do not need neutralization. The converter and if stages are entirely con-

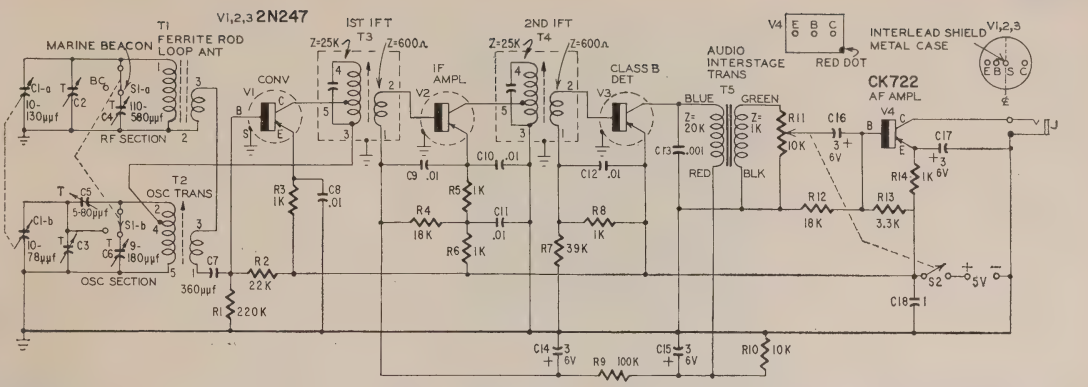

R1—220,000 ohms
R2—22,000 ohms
R3, 5, 6, 8, 14—1,000 ohms
R4, 12—18,000 ohms
R7—39,000 ohms
R9—100,000 ohms
R10—10,000 ohms
R11—pot, 10,000 ohms, miniature, with spst switch S2 (Lafayette VC-28 or equivalent)
R13—3,300 ohms
All resistors ½-watt 10%
C1—tuning capacitor; antenna section, 10–130 $\mu\mu$f; oscillator section, 10–78 $\mu\mu$f
C2, 3—trimmers on C1
C4—110–580 $\mu\mu$f, trimmer (El Menco 467 or equivalent)
C5—5–80 $\mu\mu$f, trimmer (El Menco 462 or equivalent)
C6—9–180 $\mu\mu$f, trimmer (El Menco 463 or equivalent)
C7—360 $\mu\mu$f, silver mica
C8, 9, 10, 11, 12—.01 μf
C13—.001 μf, ceramic
C14, 15, 16, 17—3 μf, 6 volts, miniature electrolytic
C18—1 μf, paper, miniature
J—miniature phone jack (LaFayette MS-281 or equivalent and matching plug)
S1—dpdt rotary (Centralab 1462 or equivalent)
S2 —spst on R11
T1—ferrite-strip transistor antenna for 130-$\mu\mu$f tuning capacitor (Miller 2005 or equivalent)
T2—transistor oscillator coil for 78–100-$\mu\mu$f tuning capacitor (Miller 2022 or equivalent)
T3, 4—transistor if transformer, 455 kc: primary, 25,000 ohms; secondary, 600 ohms (Miller 2041 or equivalent)
T5—transistor audio interstage transformer: primary 20,000 ohms; secondary, 1,000 ohms (Merit A-2741 or equivalent)
V1, 2, 3—2N247 (RCA)
V4—CK722 (Raytheon)
Battery, 5-volt mercury type (Mallory TR-134R or equivalent)
Battery holder (Acme type 69 or equivalent)
High-impedance magnetic earphone
Tuning dial (Lafayette KN-26 or equivalent)
Knob for ⅛-inch shaft
Knob for ¼-inch shaft
Bakelite instrument case, 2 x 3¾ x 6¼ inches (Lafayette MS-216 with matching cover)
Marching compass (Lafayette F-15 or equivalent)
Transistor sockets, 5-pin (4)
Miscellaneous hardware

Circuit of the four-transistor unit.

ventional, while the detector is a class-B type instead of the usual diode. This detector provides a worth-while gain and a dc collector voltage that can be used for avc, since its level is determined by the rf signal level.

Resistors R9 and R10 are part of the V2 base-biasing network and R10 is also in V3's collector circuit. The avc voltage developed across R10 is applied to V2's base to regulate its gain with variations in carrier level.

The audio transformer (T5) is a subminiature type well suited for this application. It as well as all other components must contain a minimum of iron to minimize errors in the magnetic compass. *A larger transistor audio transformer will not be satisfactory unless it is mounted far from the compass.*

The earphone is a high-impedance magnetic type and is satisfactory where the signal level is high and the noise level low. Sometimes, these conditions may be reversed, making a conventional pair of headphones more desirable.

A 5.0-volt mercury battery powers the unit. It has a 1,000-milliampere-hour rating and should provide about 500 hours of service since receiver drain is only about 2 ma. When near the compass, this battery has a slightly greater influence on needle deflection than conventional flashlight cells but, when mounted as shown in the photos, its effect is not measurable. The battery is easily replaced when the bottom of the case is removed.

All stages use base-bias stabilization to minimize variations in performance caused by temperature changes since the electronic compass will normally be used outdoors and frequently in the hot sun.

The magnetic compass is a small marching type. It has a rotatable scale for ease and accuracy of bearing determination. A notch and foresight on the compass let you select landmarks (when visible) in line with the desired course.

Let's put it together

All parts of the receiver are mounted on a long flat aluminum lower plate and a short flat aluminum upper plate as in the photos. The unit is fastened into the plastic instrument case with a second hex nut and lockwasher on the threaded switch bushing and with screws that run through the case into two threaded holes along the outer edge of the upper chassis plate.

The compass is mounted near the front end of the case with the needle pivot along the center line of the long dimension. Take your time while aligning the compass to insure the best possible accuracy. The rear mounting screw is a 6-32 flat head in a countersunk hole to permit the compass cover to be closed. The front mounting screw can be a round head but both *must be brass with brass nuts.* (Try them with a magnet.)

The aluminum chassis plates are shaped to fit the inside of the case with about 1/16-inch clearance on all sides. Make sure of this clearance after bolting to the tuning capacitor and switch but before the complete assembly of small parts is made. Otherwise, when the receiver is fastened in the case, pressure on one of these plates could upset the alignment by twisting the tuning capacitor.

One of the easiest ways to register the receiver parts with the case is to drill all necessary holes in the upper chassis plate. Then use this plate as a template for drilling the case *from the inside.* Be careful while drilling and avoid chipping. This problem can be minimized by backing each hole with a wood block while drilling and by making each hole somewhat undersize and bringing it to size with a tapered reamer.

The tuning capacitor is mounted with its trimmers facing the outer edge of the chassis for easy adjustment. The adjustment screws should be about ⅛ inch from the outer edge of the chassis to provide adequate spacing between their heads and the plastic case.

One of the mounting holes on the rear of the tuning capacitor matches the corresponding front hole and the top chassis plate can be used as a template to locate this one. The other two must be located by measurement. If the same tuning dial is used as shown, the capacitor shaft will need to be flattened slightly on one side but its length will be satisfactory.

Final assembly

The oscillator coil can be fastened to the bottom chassis plate if desired but a better arrangement of terminals is possible if it is mounted on the top plate. To do this, remove the metal mounting clip and cement a threaded plastic plug in this end. A setscrew in a threaded hole in the top chassis plate is then used to hold the coil. A small hole is drilled in the lower plate directly below the coil for adjustment.

Mount the antenna by first cutting

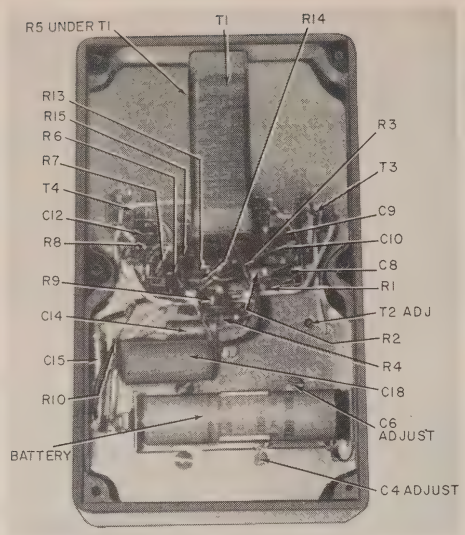

Although there is plenty of room, placement of the antenna and battery is important.

Side view shows parts layout between the two chassis plates. In this model a small mica capacitor in parallel with C4 was needed.

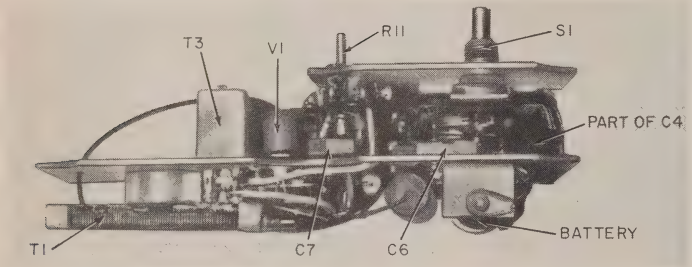

its fiber mounting strip about ⅜ inch shorter than the antenna. Then retape the antenna to this strip with their front ends flush and apply a small amount of coil dope along the joining edges. The undercut end allows room for some parts underneath. A ⅜-inch piece of ¾-inch-diameter polystyrene rod is threaded for two 6/32 x ¼-inch screws, and matching holes are drilled in the lower chassis plate. Mount this piece of rod on the plate and fasten the antenna to it with polystyrene coil dope, making sure that the antenna is parallel to the long side of the chassis.

Capacitors C4 and C6 are positioned so that their adjustment screws just clear the battery holder (see photos). These capacitors are mounted directly under the range switch with their outer plates making contact with the chassis. Their end terminals are soldered to the switch and their grounded terminals are bent over and soldered together for rigidity. Examine the ungrounded plates and rivets to be sure the "hot" ones are not grounded.

Both these capacitors should be set to within one-half to one turn from maximum capacitance before soldering. Capacitor C5 is mounted in the same way as C4 and C6, except that it is insulated from the chassis with a small piece of 1/16- or ⅛-inch insulation.

The if transformers are mounted along the sides of the chassis to reduce their effect on the magnetic compass, and the audio transformer is mounted directly in front of the volume control with a couple of dabs of cement.

A two-terminal tie point is used for B-plus and for the R9, C14, T3 junction. A ground lug is located under the mounting screw and a No. 20 bare wire connected to it is used as a ground bus. This bus is connected to the shield terminals of the three 2N247's and various small parts are grounded to it along its length. Rubber feet are mounted on each corner of the case to prevent slippage if the weather gets rough.

Steps in weatherproofing

If the electronic compass is to be used in salt-water areas, some weatherproofing will be necessary. Even in fresh-water areas the possibility of wetting by rain, spray and high humidity and falling overboard will make such a step profitable. First obtain some sheet rubber, about 1/32 inch thick, and cut a gasket about ⅛ inch wider on all sides than the bottom cover. Now, with a file, trim the base plate to give a clearance of slightly less than 1/32 inch between all of its edges and the case, and chamfer its inner edge slightly. Glue the rubber gasket to the inner surface of the base plate and allow it to dry thoroughly.

Gaskets made of the same material can be placed under the compass securing nuts, under the switch shaft nut and under the upper chassis securing screws. The tuning control shaft, the switch shaft, the volume control shaft and the phone jack can be gasketed by splitting soft rubber grommets edgewise. Use grommets with a ½-inch outside diameter and ¼-inch hole for the three controls and ⅜-inch outside diameter with a 3/16-inch hole for the phone jack. In addition, it is advisable to spray the aluminum chassis and if transformer cans with clear plastic to provide an extra degree of protection.

Aligning the receiver

The first step is to align the if transformers for maximum output at 455 kc. An output meter or oscilloscope can be connected across the headphones, or a high-impedance dc voltmeter to V3's collector or the R10, C15, T5-red junction for an output indicator.

After the if transformers have been peaked, turn the bandswitch to the broadcast-band position (BC) and adjust T2's core and C3 until the tuning range covers 550–1,600 kc. This is done by alternately adjusting T2's core at 550 kc and C3 at 1,600 kc until both ends of the range fit the dial. Next adjust C2 for maximum output at approximately 600 kc and check for satisfactory tracking at 1,400 kc. If C2 has to be decreased for maximum output at 1,400 kc, bend the slotted plates of C1-a outward and then readjust C2 for maximum output at 1,400 kc. Now adjust for maximum output at approximately 600 kc by simultaneously varying the tuning capacitor in very small steps and adjusting T2's core until the maximum is found. Alternately repeat the C2 adjustment at 1,400 kc and the T2 core adjustment at 600 kc until maximum output is obtained at both points.

The next step is to align the radio-beacon band. Throw switch S1 to RADIO BEACON and alternately adjust C6 at 285 kc and C5 at 325 kc until this range fits the dial. Next, adjust C4 for maximum output at approximately 290 kc and check for satisfactory tracking at 320 kc. *When aligning this band, do not touch the core of T2, C2, C3 or the slotted C1-a plates, as these parts are adjusted only for the broadcast band.* When alignment is completed, you can calibrate the dial.

How to use it

When the electronic compass is completed, check its accuracy by obtaining the null point on a visible station and at the same time checking to see that the station is directly in line by using the sights on the compass. If possible, check stations at various frequencies

in both bands. These checks should be made some distance from the station antenna and well away from any shore line, electric or telephone lines, metal buildings, or automobiles for maximum accuracy. In addition, hold the compass with the hands away from the antenna end of the case.

The overall accuracy of the electronic compass depends on antenna pattern, compass accuracy, compass alignment with respect to antenna, size and proximity of metal objects, and the nearness of a shore line and the station antenna. The compass error including alignment error should be very small. If any sizable error should be present, it can be compensated for by adding or subtracting a correction factor.

To use the electronic compass with the least amount of error and confusion, obtain a map of the area in which you will be operating. First mark a North–South line through the section of the map to be used and locate all the radio broadcast and beacon stations in your area on the map. Now set the North mark on the compass card under the red hairline, align one edge of the electronic compass case with the North–South line on the map, and rotate the map until the compass card North is aligned with the North end of the needle.

This orients the map so its North is pointed North. Now rotate the electronic compass (but not the map) to obtain a null on a station of known location, place one edge of the electronic compass to intersect with this station as located on the map while maintaining the null and draw a line through the station along the edge of the case. Do the same with a second station. The point where the two lines intersect is *your* location. Now that you know your location, it is a simple matter to get home either by following a plotted course to the desired point or by riding the null straight in if one of the stations is near your destination.

Satisfactory results can be obtained without the map. Simply use the compass to orient yourself with respect to North and then take compass readings on the null points of two stations of known location. The compass card is calibrated in degrees (0 to 360) and also has the usual *N, E, S, W* markings. Therefore, the readings on the two null points will immediately show you where you are with respect to the two stations. For greatest accuracy, keep your hands away from the antenna end of the case.

After making several trial runs using both methods, you will be able to decide which you prefer—with or without the map. However, try using the electronic compass each time you are engaging in your favorite outdoor activity, even in clear weather, to become completely familiar with it and to gain confidence in its usefulness.

For those who are interested, the US Coast Guard publishes lists of lights for the US coastal and Great Lakes areas. These light lists include a chart and tables of the various radio beacons including their frequency, identification code and location. Write to the Superintendent of Documents, Washington 25, D. C., for information and prices.

Final notes

Sensitivity, on the broadcast band, will be adequate for nearly any condition, but the radio-beacon range may need a slight boost if there are no nearby stations. In such cases, try a 5- or 7-inch ferrite antenna instead of the 2¾-inch one used in this model. This longer antenna will also increase the sharpness of the null point. A second if amplifier can also be added if so desired. This stage is identical with the V2 stage, except that the resistor corresponding to R6 should be about 3,300 ohms.

A speaker can be included by adding a pair of CK722's in a conventional push-pull class-B output stage after V4. Also a null-indicating meter can be added to V3's collector circuit to obtain a sharper null reading. All of these changes will require a somewhat larger case and will cause a slight loss of portability.

(When adding a speaker or null-indicating meter to the direction finder, be sure to mount them in a place where their magnets will not disturb the magnetic compass. It might be advisable to install the meter and speaker in a separate box connected to the receiver by a cable.—*Editor*)

For some uses it may be desirable to attach a leather or plastic shoulder strap to two *brass* screws mounted on the sides of the case, below the compass but above the receiver chassis.

Where you want to eliminate the radio-beacon band, delete S1, C4, C5 and C6. The tuning capacitor shaft can now be aligned with the center of the chassis, or the extra space can be used for a speaker. END

Communications In a Hurry

TENNESSEE stands ready to meet any emergency—flood, tornado, forest fire or explosion—with its unique mobile disaster communications bus.

Moments after arriving on the scene, the bus offers six radio sending and receiving sets which can operate simultaneously, first-aid equipment, a generator which can supply outside power and an emergency field kitchen.

The unit, operated by the Tennessee Highway Patrol and Civil Defense Organization, is available for use anywhere in the state and surrounding states.

The planning of Capt. P. E. Griffith, of Nashville, Tenn., made it possible to jam so many features into so little space. Captain Griffith heads the communications division of the Tennessee Highway Patrol which also handles communications for the State Highway Department and Civil Defense.

The bus is divided into three compartments, all in radio contact with each other. The front section houses the driver and six radio booths. From here, six radiomen can simultaneously direct operations of six service units.

The center compartment houses 10 transmitters which enable the center to use 40 frequencies, including those of public-service groups both in Tennessee and surrounding states. This section also contains the kitchen unit. Room was made for the field kitchen, Griffith noted, because frequently rescue workers at tornadoes and similar emergencies had gone 15 hours without food.

The rear portion holds first-aid equipment, including a respirator and generator. The generator can be rigged to supply power outside—to a hospital, for example.

The bus has two complete public-address systems and outside plugs to supply power to other electrical units.

Tele-Vue Towers, St. Petersburg, Fla.

This Tennessee Highway Patrol and Civil Defense mobile communications unit is equipped to handle any emergency.

Everything is geared to place units in operation almost instantaneously on arrival at the disaster scene. For example, the Tele-Vue aerial towers lie flat along the top of the bus while it is in motion. But as fast as cranks can be turned, they are hoisted to vertical positions and a second set of cranks swiftly telescopes them up to 45 feet in height. The bus cost $14,442.

Miniature fixed-frequency superregenerative receiver that can be held in the palm of your hand. May be set for frequencies between 30 and 45 mc

3-TRANSISTOR Pocket Police Receiver

By EDWIN BOHR

THE idea of owning a police receiver is always intriguing. Interest spans all age groups from children to grandparents. There is a thrilling vicarious experience; listening to emergency broadcasts is exciting to all but the most blase.

Added to this, we have an extra-special police receiver. It is hand- or pocket-size and completely transistorized. Its operating frequency range is about 30 to 45 mc.

The small size makes it ideal for auxiliary police, Civil Defense workers, merchant police, ambulance crews and the like. Also, it is just the thing for those who like to know what is going on.

The circuit is simple and there are few parts (see diagram). One of the transistors is a surface-barrier type. It is used just like a p-n-p fused-junction type. However, SB units can operate at very high frequencies.

The SB transistor is used as a high-frequency superregenerative detector. The other two transistors are audio amplifiers.

The receiver, as illustrated, is a fixed-frequency type. Tuning can be changed only by adjusting C1 through a hole in the case, and even the amount of *superregeneration is set at a fixed value.* These are desirable features, since they eliminate controls.

Receiver sensitivity

To appraise its performance, here is a report on the receiver in use. However, bear in mind that signal strengths vary tremendously in this type of service.

From experience, the audio output is strong and clear 5 miles from a central police transmitter. Reception is usually good, even without an antenna. Reception of patrol cars or utility-truck transmissions is another matter. Unless the vehicle is very close, audio is weak and garbled.

This circuit has been used with a third audio stage and a small speaker. Still, earphone operation seems preferable for one-man listening. If a third stage is added for speaker operation, considerable audio decoupling is necessary to eliminate motorboating.

Detector circuit

The superregenerative detector is the receiver's nerve center. Superregeneration develops tremendous amplification in a single stage.

Inherently, the superregenerative detector is not very selective. Also, it has a natural automatic volume control action.

With rare exceptions, the stations in the 30–60 mc band are narrow-band frequency-modulated. The pocket police receiver picks up these stations by slope detection.

Because the detector is broadly tuned and the frequency swing is very small, audio output from the detector is low. This makes the two medium-gain audio stages necessary.

The superregenerative detector's selectivity can be sharpened somewhat by setting the value of superregeneration carefully. In fact, it *must* be set for greatest selectivity for really good performance. This procedure requires a signal generator and is explained later.

The maximum frequency at which the detector will superregenerate depends upon the Q of the coil, transistor characteristics, the value of C2, the position of the coil tap and transistor bias.

To operate the receiver at 40 mc or higher, you may have to juggle or vary all of these values for maximum superregeneration.

High-frequency performance is particularly dependent upon coil L. For this reason, we will give it special mention. First, the coil must be kept away from the sides of the case, transformers and other metal parts. If at all possible, use a larger metal case, a plastic case or no case at all. Test the circuit before placing it in a case.

The receiver I built operated up to 45 mc before placed in its case. In the case, it works to about 39 mc. I used a selected, hot-performing 2N346/SB-103 transistor. Other units may not perform as well.

A lot of experiments were carried out with some of the completely shielded miniature iron-core coil forms now available. These would do away with effects caused by nearby components. But, because their performance was lower initially, they made no improvement.

I found the Miniductor type coil gave the best results. Coil L consists of 7

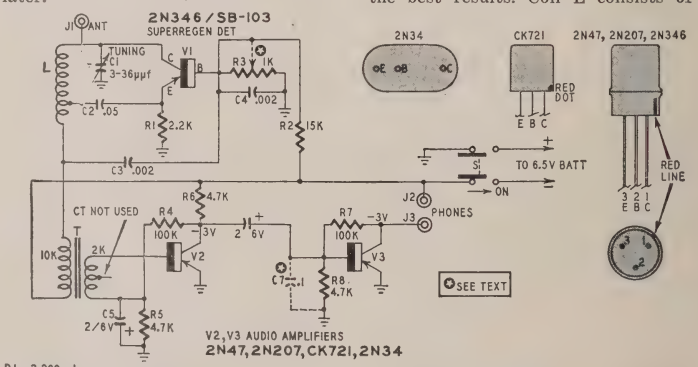

Circuit of the miniature receiver.

R1—2,200 ohms
R2—15,000 ohms (see text)
R3—1,000 ohms (see text)
R4, 7—100,000 ohms
R5, 6, 8—4,700 ohms
All resistors ½-watt 10%
C1—3–36-μμf trimmer (Bud MT-833 or equivalent)
C2—.05 μf ceramic, subminiature type
C3, 4—.002 μf, disc ceramic
C5, 6—2 μf, 6 volts, miniature electrolytic
C7—0.1 μf ceramic (see text)
J1, 2, 3—pin jacks
L—7 turns, tap at 2¼ turns (Barker & Williamson type 3003 Miniductor)
S—dpst slide
T—driver transformer; primary, 10,000 ohms; secondary, 2,000 ohms ct (Argonne AR-109 or equivalent)
V1—2N346/SB-103 (Philco)
V2, 3—2N47 (2N34, CK721, 2N207 may be substituted)
Battery, 6.5 volts (Mallory TR-165R or equivalent)
Terminal board
Case
Miscellaneous hardware

turns of a B & W No. 3003 coil, tapped at 2¼ turns. This coil is ½ inch in diameter, with a pitch of 16 turns per inch.

Resistors R2 and R3 control superregeneration. I found that, with fixed frequency operation, fixed values of resistance can be used. For each individual receiver and frequency, however, these values will have to be changed for best performance. Either decrease R3 or R2. (Decreasing R2 has an opposite effect from decreasing R3.)

To make superregeneration variable, substitute a 1,000-ohm potentiometer for R3 and connect the center terminal of the control as indicated by the dotted lines in the schematic. Also, decrease R2 to 10,000 ohms.

Capacitor C2 should be a subminiature ceramic. The rather large value for C2 is necessary for superregenerative action.

Another essential is transformer coupling. The transformer characteristics have an effect on the detector's quench action. The Argonne AR-109 or something very similar should be used.

Only surface-barrier transistors will work properly in the detector circuit. The 2N346/SB-103 made by both Philco and Sprague is satisfactory (so are the military types 2N128 and 2N129).

The prices of surface-barrier transistors have recently been reduced. Now they do not cost much more than high-frequency junction types.

Audio amplification

The two audio transistors have medium beta (current-gain) figures—about 40 to 45. Any other p-n-p transistor with about the same gain is suitable. I used 2N47's, but as this transistor has been discontinued you may not be able to get any. The 2N202, 2N34 or CK721 can be substituted without making any circuit changes.

Direct-current feedback stabilization is used. While this is not as good as having emitter stabilization, it is sufficient and saves the space occupied by two emitter bypass capacitors.

The feedback does not compensate for individual transistor variations, but it does hold temperature changes of the collector current to a reasonable amount. The circuit works like this: If collector current tends to increase because of temperature effects, collector voltage decreases because of the drop across the collector load resistor. This, in turn, tends to decrease the base bias current and reduces the total change considerably. This bias method is infinitely better than just a single resistor from the base to the supply voltage.

Collector voltage of transistors V2 and V3 should read −3 volts (±0.5 volt) using a 20,000-ohms-per-volt meter. If higher, *decrease* the value of R4 or R7, as the case may be, to *decrease* the collector voltage and vice versa.

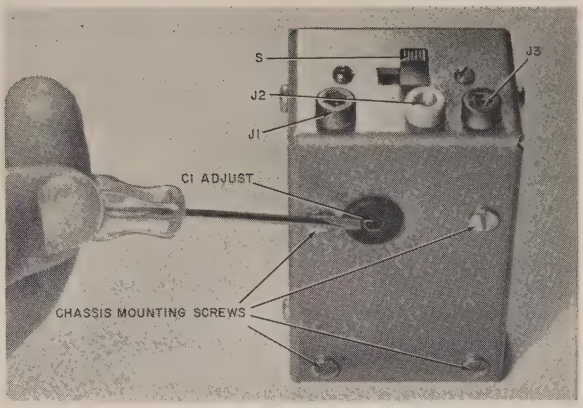

The tuning adjustment can be reached through a hole in one side of the case.

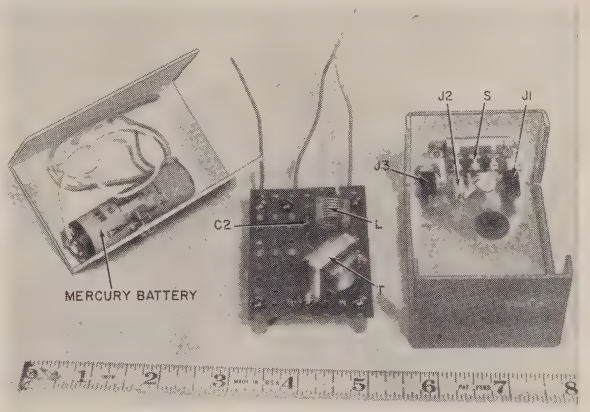

Three subassemblies make up the completed receiver.

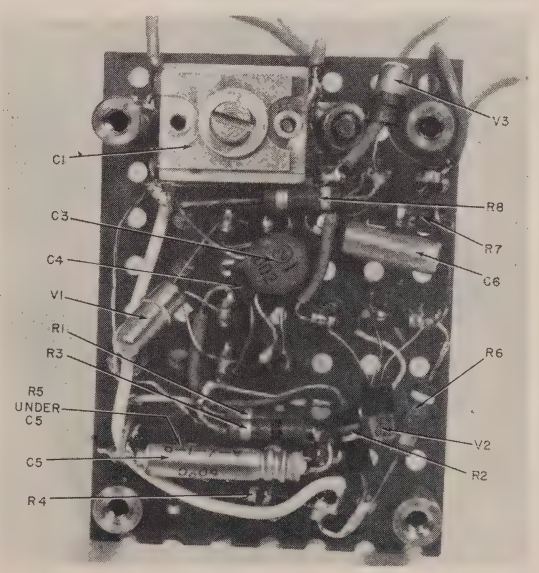

Most of circuit's components are mounted on a small phenolic terminal card.

If a 2,000-ohm earphone is used, R7 may have to be reduced to about 47,000 ohms.

You may find that listening is more comfortable when the optional capacitor C7 is added. Capacitor C7 suppresses the ultrasonic quench frequency before it reaches the earphones or overloads V3.

A small terminal card simplifies construction. The components are wired to the card. Then the card is bolted into the case with four brass standoff spacers.

The TR-165R mercury cell is clamped to the case cover with a piece of strapping material. Of course, a capacitor clip or battery holder could also be used.

My antenna is a heavy piece of Copperweld wire, about 12 inches long, that plugs into the antenna jack. Increasing the antenna length does not seem to improve reception very much. Too much antenna length will load the oscillator and reduce the maximum working frequency.

Final check

For reception of narrow-band FM, detector superregeneration must be set for maximum selectivity. To do this, a signal generator is necessary. Assuming the set is working, a hiss or frying sound is heard when the detector is superregenerating. With the antenna connected, tune the receiver to the carrier frequency. This is found by setting the generator at the carrier with tone modulation. Now, rock the tuning capacitor C1 back and forth and adjust the value of R3 until the sharpest selectivity is obtained.

Turn off the generator and listen for a police carrier. The instant the carrier is heard, turn *C1 very slightly* for best reception. This is necessary to account for inaccuracies in the signal generator's calibration and *because the detector must be tuned to one side of the carrier for slope detection.* In other words, best audio *will not* be obtained with the detector tuned exactly to the carrier.

If the detector does not superregenerate, check the connections to the surface barrier transistor. It is easy to confuse the emitter with the base lead.

Next, check the transistor voltages. There should be about 6 volts from ground to collector and, very roughly, 0.1 volt from emitter to base. The base should be negative with respect to the emitter. Also, check to see that none of the parts have been omitted.

When the receiver is first connected to the battery, set R3 at maximum resistance. This protects V1 if the battery is inadvertently connected with wrong polarity.

The pocket police receiver gives the constructor a new project, but it is not something for the beginner. I recommend the circuit only to those who have had some previous experience with transistor circuits and vacuum-tube superregenerators. END

Radio Runs on Low Voltage

By WARREN J. SMITH

With slight modifications, 3-way portable radios can be made to work on line voltage as low as 90

THREE-WAY portable radios often succumb to oscillator instability or failure when operated on the low line voltage in my locality (90 to 95 volts). These receivers almost invariably have a 1R5 or similar converter tube which is extremely sensitive to line-voltage fluctuation. The 1R5 cannot tolerate a drop in screen voltage of more than 10 to 15% without some ill effects. Filament voltage tolerance is even more critical. Although normally operated from 1.4 to the rated 1.5 volts, the tube functions erractically or not at all when filament voltage drops to 1.2 or 1.15. Many other portable radio faults not so readily apparent, such as low gain and poor sensitivity, can also often be attributed to low line-voltage operation.

To correct for inadequate supply voltage, I simply reduce the value of the power supply's dropping resistors or eliminate them. Resistance changes, as illustrated in the diagram, let this particular portable operate satisfactorily, while previous operation was extremely unstable and erratic. Normal battery operation is not disturbed by this type of modification since the altered circuitry is switched out with the ac-dc rectifier circuit.

Use a Variac or similar variable ac source to determine the dc output voltage of the selenium or vacuum-tube rectifier (points A and B in the diagram) with a normal input voltage of 117. (This information usually appears in the manufacturer's service notes, but it is best to make your own tests.) Next, measure the rectifier output voltages with an ac input voltage equal to the minimum and maximum extremes of line-voltage variation in your particular area. Then, from the following formula, determine the total value of filament-dropping resistance (R1) needed.

$$R1 = \frac{\left(\frac{E_a max + E_a min}{2}\right) - E_f}{.05}$$

where $E_a max$ and $E_a min$ are the measured maximum and minimum extremes of rectifier output voltages at point A, E_f the total voltage drop of the filament string.

Substituting actual values for line operation in our area (for the Emerson portable shown in the diagram):

$$R1 = \frac{\left(\frac{84.7 + 89.1}{2}\right) - 6.8}{.05} = 1{,}602 \text{ ohms}$$

The closest standard resistance value, 1,500 ohms, is much too small. Therefore a series, a parallel or series-parallel combination of resistors must be made up. In this particular instance I used a series combination of standard values—1,500, 100 and 2.2 ohms for a total of 1,602.2 ohms.

In the portable used as an example, the dropping resistor in the B-plus line was unnecessary because an ac input of 90 to 95 volts (our line voltage) produced a variation of 84.7 to 89.1 volts at the rectifier output for an average of 86.9 volts. This represents a drop of only 1–6% in the B-plus voltage compared to the previous example of 12–23% with the 1,500-ohm dropping resistor. (A small, low-dc-resistance choke was wired in the circuit in place of the dropping resistor for filtering purposes—its resistance is negligible but it does provide a margin of safety.) If a dropping resistor in the B-plus line should be required, use the following formula to calculate its nominal value:

$$R2 = \frac{E_{av}}{\left(\frac{E_{na} - E_{nb}}{R_n}\right)}$$

where E_{av} is the average of the low line voltage as determined from

$$\frac{E_a max + E_a min)}{2}$$

E_{na} is the normal voltage at point A and E_{nb} is the normal voltage at B with an input of 117 volts ac and R_n the original value of the B-plus dropping resistor (R2). END

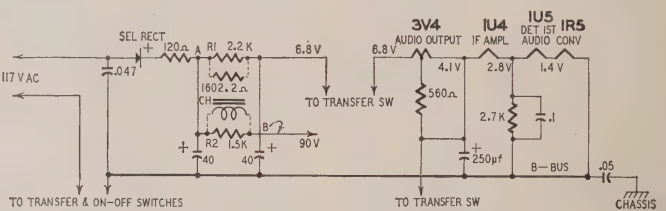

Power supply circuit of an Emerson portable. Parts shown in dashed lines replace existing components.

IDENTIFY THAT CHASSIS

A little detective work is all it takes to pin a model number on an unmarked chassis. Just follow the Old-Timer along as he shows you how

By JACK DARR

THE Old-Timer grunted loudly as he burned the tip of the finger he had unwisely poked into the small TV set he was working on. "Oww! Dad-burn it!" he grumbled. "I'll bet you I know what would be good useful equipment for a TV man—a set of asbestos fingers! Ouch!" and he sucked the damaged digit. The Young Ham, meanwhile, sat quietly at his end of the long bench, his crew-cut head bent over a car radio. Suddenly, he exploded.

"Darn it all!" he glared at the little chassis. "Why can't people put model numbers or somethin' on their radios! You'd think they were ashamed of 'em!"

"Well, some of 'em may be, and some of 'em ought to be," agreed the Old-Timer, looking up. "What's your trouble, Junior?"

"Aww, this little stinker!" growled the Young Ham. "No model number, no nothin'! This resistor's burned out, and I can't find anything on the set. How the heck do they expect us to fix 'em if you can't find out something about 'em?"

"Get out your crystal ball!" The Old-Timer grinned. "Let's see it." He got off his stool and ambled down to the end of the bench. "Ohh. That oughta be simple. I've seen several of them before."

"Well, I haven't!" burst out the Young Ham. "I can't tell beans from bones about it!"

The Old-Timer smiled at the young man's use of one of his own favorite expressions and studied the set closely. "Well, now, look here," he said, pointing into the upturned bottom of the set. "See that bypass? Says 'Bendix' on it, very plainly, don't it? Transformer does, too. Don't that tell you something?"

"OK, OK! So it's a Bendix, but what model? I've looked over the whole thing, case, lids and all, and I can't find anything on it at all!"

"Hang on, help's comin'," said the Old-Timer, reaching up to the well-filled bookshelf that ran the whole length of the shop. "You remember what kind of a car you got it out of, don't you?"

"Ford," said the Young Ham. "'53 Ford."

"Now, lessee; Chrysler, General Motors, Ford! Here we are," and he pulled a service manual down. "Now, look. Here's a Rider manual covering all the Ford radios from quite a ways back. '53 Ford, you say. Lessee. '52, '52. Here. See? Here's a picture of the front of the set. See? Looks somethin' like it, wouldn't you say?"

"Yeah! That's it!" said the Young Ham. "Now, let's see what that resistor was, before it burned up. Here it is. 1,800 ohms. Now, by golly!"

"Ah, Junior," said the Old-Timer quietly. "Ain't you a mite previous. Are you sure that's the same set?"

"Sure. Look at that front panel and the controls. Same set, see?" and the Young Ham pointed at the photograph.

"Well, that's true, but there might be one little difference. There was three people made Ford radios that year, Sylvania, Zenith and Bendix, according to the book. The one you're lookin' at happens to be a Zenith. Since when did Zenith start usin' Bendix capacitors and transformers? Huh?"

"Huh? Oh! I see what you mean," said the Young Ham sheepishly. "Got too previous, didn't I? Now, let's see in the Bendix set. Hmm. 1,000 ohms. Oopps!"

"Yeah, you did get a mite quick," agreed the Old-Timer. "Now, you see what too much speed can do. It's a good idea to check up on everything before you make any rash moves, especially in a case like this!"

"Tell me, why in the world don't people put the model numbers and the maker's names on their radios and TV sets?" asked the Young Ham, as he replaced the resistor. "You'd think they *were* ashamed of 'em!"

"Junior, that's somethin' that'll never be known, I guess," opined the Old-Timer, as he replaced the cover on his little TV set. "That problem's puzzled radiomen since 1920, and it would have before that, except they didn't begin to make sets until that year! Only way you can find out anything about 'em is by a long and painful process of deduction. Got that resistor in yet? I want a coke, while I let my fingers cool off. Danged little tubes sure do run hot!"

Let's go for a coke

He was answered by a burst of rock and roll music from the car radio, and the Young Ham snapped it off. Leaping up, he announced, "I'm ready! Let's go!"

The pair trotted down the long hall and out the back door. As they crossed the alley and took their regular short-cut through the drugstore, the Young Ham said, "Gee, I wish I could find 'em that quick! I'd have been hunting all day, and you found it in just a second!"

"Hi, Hop!" said the Old-Timer, as they passed the pharmacist at his prescription counter. "How's the poison shop today?" Ignoring the rude reply, they passed on out the front door and across the street. When they were seated at a table in the soda shop, the Old-Timer got around to replying to the young man's question. "Well, Junior, it ain't so much a matter of genius as it is a combination of experience and patience," he explained. "Time you've had that button nose into as many of the things as I have, you'll be able to recognize 'em on sight, too. Main thing is, you gotta take advantage of every little clue you can find as to who made the thing and when."

"Maybe so, but what do you do when you find a set that hasn't got any clues as to who made it?" asked the Young Ham.

"They ain't no sich," said the Old-Timer, truthfully but ungrammatically. "I don't believe it's possible to build a set without leavin' some kind of a clue. Y'see, the only ones we'll have trouble with is the sets from the mail-order houses and other outlets like that. They don't build their own sets; they buy 'em from the manufacturers who make a business out of makin' sets just for such people. In fact, there used to be set makers who sold more sets under other people's names than they did their own—Wells-Gardner, for instance. Haven't seen one with their own name on it for more than 20 years, but there was more WG's than you could shake a stick at. Sears Roebuck, Mont-

gomery Ward, Walgreen, Spiegel—everybody at one time or another sold Wells-Gardner sets, I reckon!"

"Well, what do you do then?" asked the Young Ham. "Hey, how about a coke over here?" He pounded the table, then ducked quickly as the waitress flung a water-soaked paper napkin at him.

"Well, Y'see . . . glupff!" said the Old-Timer, as the wet paper wad took him squarely in the mouth. "Hey! Phoo! How'd *I* git into this argument? I'm just an innocent bysitter!"

The waitress rushed over and mopped the Old-Timer's face with her apron, much to the delight of the Young Ham, then brought their cokes. The Old-Timer stirred his, then tasted it, gingerly. "Well, that takes the taste of that paperwad outa my mouth," he commented.

"Wow!" said the Young Ham. "They sure do make it cold!" and he ducked again. This sally was ignored by both waitress and proprietor, and the two finished their cokes in peace. Going out the door, they trotted back across the street, through the drugstore and back to the shop. Reaching up to the bookshelf, the Old-Timer took down a thick blue-backed book out of a set there. Opening it on the bench, he located a diagram.

"Here's a good example of what I mean, about some of those old-timers," he said. "See here? Here's a Sears Roebuck set listed under their trade name, Silvertone. Now, looky here," and he turned to the back of the book. "See? Under Wells-Gardner, here's the same set—Look at the tube lineup, the circuit and so forth."

"Yes, I can see that," said the Young Ham, "but how are you going to tell just who made the thing if you've never seen one like it before?"

"Well, that's the hardest part," admitted the Old-Timer, "but there's a kinda method you can use on all of 'em and find out what you've gotta know. It's a kinda combination of every little thing you can see: the cabinet, the chassis, the tube lineup, the general appearance of the set and everything else about it. If they all agree, then you're home free. Some people use a code in the model numbers, that's a big help. Montgomery Ward's Airlines, f'rinstance, since about—lemme see, 1939, I think. Yeah. See here?" and he pointed out a listing in the index.

"How can you tell anything by that?" asked the Young Ham. "Just looks like a mess of numbers to me."

"Nope; they're just full of information, if you know how to read 'em," said the Old-Timer. "Look at this model number here. '93BR508A.' Turn the first two numbers around and you've got the year it was made: 93—1939. Then the 'BR' tells you that it was made by the Belmont Radio Co. or, if it was 'WG,' by our old friend Wells-Gardner, and so forth. That'll help, if you can find the year it was made."

"Where do you go from there?" asked the Young Ham. "Even if you do know the year, how do you find it in all that stuff," indicating the 20-foot bookshelf, filled with manuals.

Lots of service data

"Well, that's not too hard, either," said the Old-Timer. "All these Rider manuals are roughly numbered according to the year they came out, beginning with Vol. 1, which came out in 1930. So, if you wanted a set made in 1940, you'd be like to find it in Vol. 10, and so forth. Feller needs a pretty complete set of all the service data he can git his hands on, to do much of anything with this kind of work."

"Well, you've got that, I'll say that for you," said the Young Ham, eying the well-filled bookshelf and the stacks of assorted service information which covered nearly every flat surface in the shop.

"Yep, I have," admitted the Old-Timer. "And I use it all at one time or another too. Tell you what though. One of these days I'm gonna git in here and straighten out all of this stuff and file it like it oughta be! Lessee now, where were we?"

"You were talking about Airlines," said the Young Ham.

"Oh, yes. Now, look here. Here's another helpful soul—the Truetone sets sold by Western Auto Stores. They give you model numbers with codes in 'em, too. See this one? Model D-1191WG: 'Factory No. 6C18-3.' This means Wells-Gardner again. If it was BRC, Belmont; DRT, Detrola, and so on, just like the others. Then, you can look this up under Wells-Gardner and probably find it listed under model 6C18."

"Tube lineups are helpful, too," he continued, "especially on the older sets and once in a while on the new ones. Take this guy here, f'rinstance. Look. He's used a 12J5 as an oscillator and a 12SA7 as only a mixer tube, instead of using the 12SA7 as both. Well, all you have to do is look through your manuals until you find somebody else using the same circuit with the same tubes, and you've got him. Lots of other little peculiarities like that, if you take the time to look 'em up. Certain designers have certain habits and the chances are they'll use 'em over and over again, for several years, anyhow. If a certain guy uses a kind of trick circuit one year, you can be fairly sure that you'll find the same circuit in several sets, especially if it works fairly well!"

"You mean they use the same circuits in all the sets?" asked the Young Ham, with a bewildered look.

"No, not at all," answered the Old-Timer. "What I meant was just certain parts of the circuit, like the if's, the oscillator stage, the front end and so on. Take Philco, for instance. One year they used an if stage with a little tertiary winding in the if amplifier screen circuit. Well, they used that same circuit for at least three years. So, if you had if troubles and couldn't find the right diagram, you could look up the same circuit in another set, even if it was a year later. See?"

"Oh, I get it, now," said the Young Ham: "You can kinda make up enough information to get what you need, even if you have to use the diagrams of several different sets!"

"Now you're getting the idea." The Old-Timer applauded. "It's not where you find it, but what you find! There's a heck of a lot more service information available now than there was when I started, too. Why, they're even pasting schematics inside the cabinet on a lot of sets now, and that's a big help. TV sets, well, that's a different story. A TV set's a heck of a lot more complicated than a radio, and there's still a heck of a lot of variation between makes as to the different circuits. Thank goodness, they're beginning to settle down some by now, though. Different manufacturers are beginning to use the same circuits in the same places, with only minor variations here and there. Like the high-voltage supply—I guess about everybody uses the same general circuit by now. You don't find any more line-voltage supplies with the tremendous transformers, or rf power supplies with the separate oscillators and stuff like that, that we had in the early-day sets, and hurray for that!"

"No, sir, TV sets are not all alike, yet," agreed the Young Ham. "Not with all the funny tubes they're coming out with now."

TV set clues

"Well, that's sometimes a hindrance and sometimes a help," said the Old-Timer. "Some manufacturers have a habit of using certain tubes. That'll help you identify their sets, no matter what name they're under. For instance, Zenith used the 6BN6 tube as the sound discriminator for several years and no matter what set you had, if it had a 6BN6, chances are it was a Zenith. Now, we've got the same situation in

TV that we had in radio. Different makers are selling sets to chain stores, mail-order houses, and so on. The only way you can tell what kind of a set it is is to give it the same treatment. Look it over carefuly, check for brand names on the tubes, transformers and so forth. Look at this one here. This is an easy one." The Old-Timer indicated a small TV console in the finished-work department. "Says 'Truetone' on the cabinet, but look at it closely. What does it look like? We've had several of them in here lately, from ol' Walker's, down the road. Recognize it?"

"Why, it looks just like those—Oh, what was the name of that set—Oh, yes! Raytheon! That's what it is, a Raytheon!" said the Young Ham, excitedly.

"Kee-rect the first time," said the Old-Timer. "You'll also find that same set under Silvertone—had one the other day, out on 15th St. And, you know Ol' Dingbat's Stewart-Warner? The Gasman's? The 9300 series? I found one of them the other day, carrying a Silvertone nameplate, but it was a Stewart-Warner 9300 'cause the first thing I spotted was that characteristic heavy metal bridge over the yoke. That's another thing you want to remember. Look for characteristic construction features—like that bridge, or something distinctive. For instance, maybe some company always mounts their tuners way out to the side, actually off the main chassis. That's a trademark. Maybe they use a certain given kind of printed-circuit assembly—like Westinghouse or Admiral or G-E. Why, I even identified an Airline TV set one time by the dern knobs! It turned out to be a Bendix and they had those peculiar cutout knobs, with the inside shaft on the outside knob, and so on. Nobody used them that year but Bendix, and I spotted it that way!"

"Gosh, it'd take you a lifetime to learn all of the darn things," sighed the Young Ham in discouragement.

"No, not necessarily," said the Old-Timer. "All it takes is a pretty good memory for those little quirks and characteristics I've been talkin' about, and the ability to put 'em all together and make 'em spell out the name of the set. That, and somethin' you could use just a wee bit more of—patience!"

"Who, me?" said the Young Ham, aggrievedly.

"You," rejoined the older man. "In common with all kids, you want to git everything done today! Don't forget, there's always tomorrow, and you've got plenty of time! Take it slow and easy, and be sure you're right before you go ahead.

"But, back to the subject of identification. It's only once in a while you really need a schematic, especially since so many people got thoughtful and started puttin' tube layouts inside the cabinets on TV sets. Why, some actually put the heater string layout in the sets with series heater circuits and don't think that ain't handy! If they ever stop doing that, we'll sure be up that well-known creek without any form of propulsion!

"Anyhow, like I said, the only time you've got to have a schematic is when something's burnt up, like a resistor or a coil and you can't get the identification from it. Although, come to think of it, coils, transformers, yokes and the like ain't too much of a chore. Look here." He dug a catalog from the file. "Here's a catalog put out by Merit that lists all kinds of TV sets and their components, especially yokes, transformers and stuff like that. Sets are listed by make and model number, and it's very little trouble to look up one and find out just what part you need. Thordarson, Sprague, Miller and several others put out similar catalogs. You can get 'em from your parts supply house or direct from the manufacturers. Sure are handy, too!

"Do you know that you can even use these books backward? Instead of looking up the parts from the make and model of the set, you can look up the set from the make and part number of the part!"

"How's that again?" queried the Young Ham. "Run that by slowly, and let me get a better shot at it."

"All right, look. You've got a TV set. You know it's a Silvertone, say, but the model number's been scratched off or something. From the tubes, you've got a reasonable suspicion as to about what year it is, and—"

"How's that, now?" interrupted the Young Ham. "How can you tell from the tubes what year a set was made?"

"Well, you can't, too definitely, but you can get a general idea," admitted the Old-Timer. "Take the 3-volt series. When'd they come out, first? Last year, was it? Anyhow, if the set has 3-volt tubes in it, you know it was made sometime within the last 2 years, on account of they didn't make the tubes until then! Older sets, if they have tubes that haven't been in common use for several years, you know they aren't *newer* than a certain year, and so forth. Oh, just f'rinstance, if you find a 6AC7 in the video output, the set's apt to be over 3 years old because they haven't, as a rule, been using 6AC7's there since about that period. It's just a general hint, that's all."

"I see—I think," admitted the Young Ham.

"Now, where was I? Oh, yes. I was lookin' up sets by part numbers. Yeah. All right. First thing, you take the part numbers off two or three big parts, like the yoke, power transformer, flyback transformer, vertical output transformer and so on. Copy 'em down on a piece of paper, and start lookin' through the catalog for a set, of the right make, which has *all* of those numbers! Chances are, when you find it, it'll be the right one. If it ain't, you can usually get so close that you can use the diagram of that set to find out what you want to know! Why? Because, if it uses all of the same parts, there's bound to be a pretty good similarity between the two sets, see?"

"I think I'm beginning to get a glimmering of the idea," said the Young Ham.

"Well, it's usually a lot of dern trouble, any way you look at it," said the Old-Timer, "but sometimes that's the only way you can get the information you have to have. Guess the only way you could sum it up would be to compare it to a detective, lookin' for clues. You've got to take every little clue you can find. The cabinet, the shape and size of the chassis, the tubes, even the kind of parts, the type of construction used and every little detail. Why, I remember, a long time back, I even identified a radio because one part had a big long part number! Happened to think that the Colonial people had a fancy for great long part numbers, looked one up and there it was! So, if you take advantage of every clue, no matter how small, and add 'em all up right, you come up with the right answer, just like Friday. All you gotta do is get the facts, ma'am."

"Dum-di-dum-dum!" agreed the Young Ham.

"Yes, sir!" said the Old-Timer, leaning back on the bench, "that's gotta be your motto. No fact too small, no clue too insignificant!"

"Well, I can tell you one small insignificant fact you're overlookin' right now," said the Young Ham.

"Huh?"

"There," pointing to the clock. "It's 5 after 6, and I've got a heavy date. We're on overtime right now!"

"Ye Gawds, we can't afford that," cried the Old-Timer, leaping off the bench. "Let's git outa here. My wife's gonna kill me. I told her I'd be home early tonight, too!"

"Down scope, crash dive, all ahead flank," yelled the Young Ham, his voice fading rapidly as he dashed down the hall. " 'Night!" The Old-Timer grinned, pulled the master switch, looked around for cigarettes left burning and ambled after him. END

An easy-to-build oscillator without a tuning capacitor

slug-tuned VFO has stable output

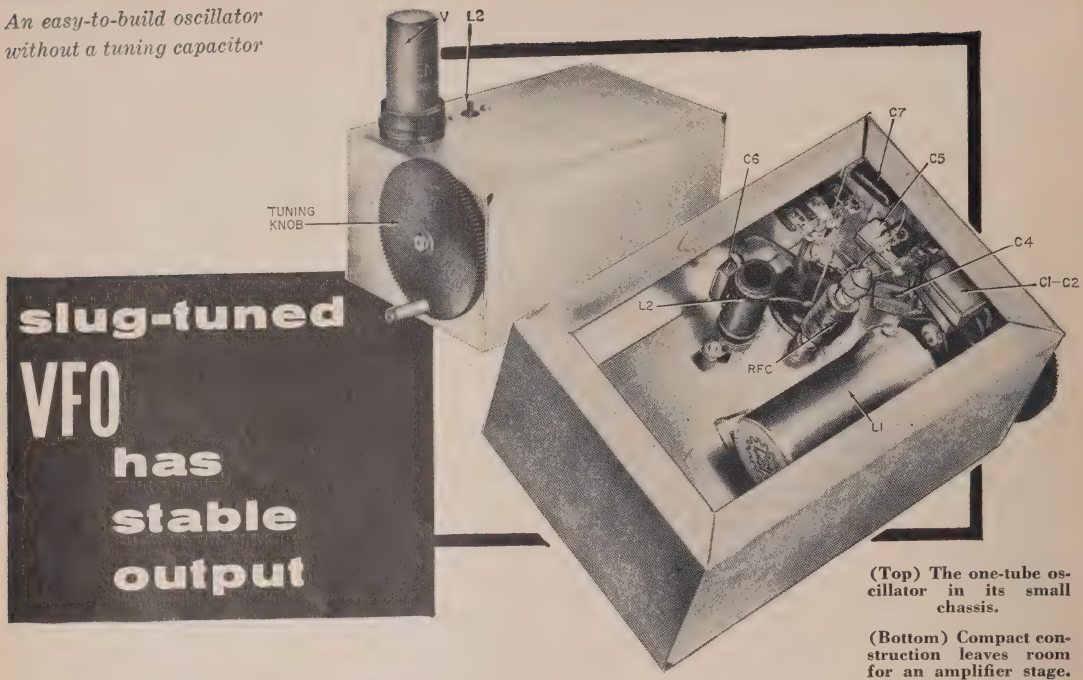

(Top) The one-tube oscillator in its small chassis.

(Bottom) Compact construction leaves room for an amplifier stage.

By JACK GALLAGHER, W5HZB

THE difficulties which arise in the construction of a vfo can be reduced by proper choice of circuits. The Clapp oscillator—a very popular circuit because of its stability—is a good choice for a vfo if space is not a major consideration. Although it has good voltage stability, the output varies over the band unless gang tuning is used.

If space is to be considered, a circuit requiring low inductance will make large coils unnecessary. A circuit of this type will require a large amount of capacitance in the form of fixed and variable capacitors and would normally offset the space gained by using a small coil.

A high-C Colpitts oscillator whose frequency is between 1.7 and 2.2 mc, and has a high degree of stability and uniform output over the band is shown in the diagram. To eliminate space-consuming variable capacitors, a slug-tuned coil (L1) is used for frequency variation. A total tank capacitance of some 2,320 $\mu\mu$f is used across the coil in the form of two .001-μf silver mica padding capacitors (C1 and C2) and the series combination of the feedback capacitors of 470 $\mu\mu$f and .001 μf.

Since the Q of a coil for use in a Colpitts circuit can be low compared to the Q required for the Clapp circuit, the Millen type 74001 slug-tuned form is a compact and easily adjusted coil to use with this oscillator.

To keep cost to a minimum, complicated and sometimes troublesome mechanical drive assemblies were rejected. The knob for the unit shown in the photographs was made from a bakelite gear removed from an old tuning capacitor. Since the travel of the slug screw is less than ½ inch, it is easy to make fine adjustments with the tuning knob.

While the 6-40 screw threads on the slug screw provide smooth adjustment and about 40 kc of variation for one revolution of the shaft, almost any variation can be obtained by winding the coil in a different manner.

The coil in this unit is wound with 18 turns of No. 20 enamel, spaced in a distance of ⅝ inch. First, the slug was placed at the bottom of the form and the winding started at the top of the slug. The first 9 turns were spaced slightly greater than the wire diameter and the last 9 turns were closewound, ending about ¾ inch below the top of the form.

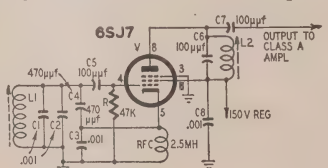

R—47,000 ohms, ½ watt
C1, 2, 3—.001 μf, silver mica
C4—470 μμf, silver mica
C5, 6, 7—100 μμf, mica
C8—.001 μf, disk
L1—18 turns of No. 20 enameled spaced in ⅝ inch (see text)
L2—60 turns of No. 30 enameled closewound on a Millen No. 74001 ½-inch-diameter slug-tuned form
RFC—2.5 mh
V—6SJ7
Chassis—4 x 5 x 6 inches
Knob
Miscellaneous hardware

Circuit of the slug-tuned vfo.

Although a similar winding method can be used to provide linear bandspread for slug tuning, it was not attempted in this case. The turns were spaced as described merely to cover the frequency range previously mentioned. After the range was checked, the coil was doped sparingly to hold the turns in place.

The construction of the oscillator is simple and straightforward with the exception of mounting the slug-tuned coil. It was mounted as shown in the photographs with a standard octal socket, which clears the aluminum box by ¼ inch, leaving ample room to remove the coil for adjustments. A ⅜-inch hole provides clearance for the slug screw.

The slug-tuned plate coil (L2) is mounted to the right of the 6SJ7 oscillator and is adjusted from the top of the chassis. The slug is set for maximum output. If the oscillator is set at 1950 kc, the output will be almost constant as the tuning is varied from 1.7 to 2.2 mc.

Since the oscillator occupies about half the 4 x 5 x 6-inch chassis, there is room to add a class-A amplifier stage. This will help increase stability when a transmitter is keyed and also provides an ideal keying position. The plate supply of 150 volts should be regulated with a VR150 or an OA2. END

KNOW YOUR LEVELS

Both low- and high-level amplification have built-in complications. Discover what they are and how to beat them

By NORMAN H. CROWHURST

SOME things about designing or using amplifiers you can find in any textbook. But for some unexplainable reason other items of information that ought to be easy to find seem to get left out. For example, operating levels at various points in an audio system.

The amplifier user needs to know this so he can put the right items of equipment together and get the best performance out of the whole system. The amplifier designer needs this knowledge to select the right components for his amplifier.

A closely related piece of information—that of impedance matching—gets discussed in every second article on amplifiers. So it is common knowledge that a 50-ohm microphone must be connected to a 50-ohm amplifier input. A number of articles have shown how to make resistance pads to match one impedance to another.

I was called in recently on a case which aptly illustrates the lack of this knowledge. My job was to make a microphone–amplifier–loudspeaker combination work. The man who called me had paid careful attention to matching. The microphone was 50 ohms and the amplifier had a 600-ohm input, so he used a line transformer from microphone to amplifier. However, he was unable to get any output from the system.

Examination showed that the amplifier was designed to operate from an input level of 0.5 to 1 volt at 600 ohms. The microphone was one of the higher-sensitivity dynamic types which gives about 3-mv output across 50 ohms for normal speech. The matching transformer from 50 to 600 ohms stepped this voltage up about 3.5 times, delivering a little more than 10 mv to the amplifier. But 10 mv is not enough for an amplifier that needs an input of 0.5 volt (500 millivolts).

"You need more amplification," I told my caller.

"That's easy," he replied, "I have another of these amplifiers here on the shelf, and you know how to make a matching pad so I can work the 16-ohm output of one into the 600-ohm input of the other."

I explained that what he needed was not another power amplifier but a preamplifier for working at low level. This he did not seem to understand. He thought amplification was amplification, and between the two amplifiers there should be enough of it. So I explained briefly why this arrangement would not work.

But how many of us have had to find this out the hard way—by trying it—simply because there was no one on hand to tell us what would happen? Fortunately this job did not prove difficult, because he did have a comparatively high-sensitivity microphone and it wasn't too hard to find a preamp that would work successfully with this power amplifier.

If he had been trying to use a mike with a much lower output level, there would have been bigger problems in finding a satisfactory preamplifier. So let's start at the input end and see what it takes to make a good amplifier that will handle signals at all levels.

Low-level components

When we set out to build an amplifier for amplification at low levels, from insensitive microphones and pickups, particularly the ribbon type, we have to be very careful when selecting components. The first tube gets a *maximum* signal of only a few millivolts at its grid. It is expected to make these signals audible at the output. This is getting down to the level of tube hiss and the hum generated in a good many tubes.

The input circuit must be carefully shielded to avoid hum pickup. This part of the story, though, has been well discussed elsewhere from time to time.

Tube hiss is due to plate current, which consists of electrons flowing from cathode to plate. Each electron transit is a separate event, so the plate current is made up of a random sequence of separate charges passing from cathode to plate. The average rate of transit determines the measured current. When amplifying low-level signals, changes in plate current due to the applied audio grid voltage are not much more than the fluctuation in rate of arrival of electrons at the plate due to the random nature of their departure from the cathode. Therefore, tube hiss is apt to be almost as loud as the audio signal we want to use.

Ways have to be found to minimize tube hiss. The noise a tube generates due to these effects is obviously proportional to the total current flowing—the proportion of fluctuation in electrons arriving at the plate is proportional to the average total number arriving. The noise voltage they develop at the plate is also proportional to the fluctuation in the velocity at which they arrive. The fluctuation in velocity is proportional to the actual velocity

Therefore, halving the *plate current* will approximately halve the noise output of a tube and halving the *plate voltage* will also approximately halve the output. But halving the plate current or plate voltage does not necessarily halve the tube's gain.

Over a wide range of variation in plate current and voltage, a tube's amplification does not vary by too much. Operating the tube with low plate voltage and current gives almost the same amplification as a higher plate voltage and current, but considerably reduces noise introduced by the tube.

From the standpoint of noise, two things are required of an input stage:

(a) it must have minimum noise itself; (b) it should have as much gain as possible, to lift the signal as far as possible above noise. Pentodes have good gain, but generate more noise than triodes. About the best compromise seems to be the use of a twin triode in the cascode circuit shown in Fig. 1.

Another factor in operating tubes at low levels is their microphonic characteristics. A tube's plate current is determined by the electric field produced by the grid and plate at the cathode. Fluctuations in this field vary the plate current and this constitutes signal. If one of the electrodes, particularly the grid, is subject to any vibration, the field controlling the plate current is altered.

As the variations we are concerned with are very small, it takes very little vibration to produce an audible output. This characteristic is known as microphonics. To prevent microphonics, special attention has to be paid to providing a rigid tube construction so the electrodes are not free to vibrate.

Another way in which a tube can inject a spurious signal is by hum, especially if ac is supplied to its heater. Tubes designed for use at low levels have the heater specially constructed to radiate a minimum ac field.

In short, a tube specially designed for operation in audio amplifiers at low levels has to have the following special characteristics:

It should be a hi-mu tube which can be used with low plate voltage and current.

Its construction should prevent microphonic vibration.

The heater must be made so it does not inject hum into these low-level circuits.

One tube to which careful attention has been paid is the double-triode 12AY7.

Usually, feedback is not applied over the first stage of an amplifier designed for low level inputs. This is because a feedback loop over a low-level input reduces the input voltage seen by the tube to a fraction of the input voltage provided by the microphone or pickup. This aggravates the noise problems we have been discussing rather than helping reduce them.

Distortion problems

However, in these days of low distortion, when some designers are working to get figures in the region of 0.1%, feedback is used to reduce the distortion factor of all the other stages to a minimum, so the input stage is sometimes the limiting factor in distortion.

When this is first discovered, it comes somewhat as a surprise. The classic treatment of distortion tells us it is due to curvature of tube characteristics and, if we use the tubes well inside of their maximum rating, the distortion will be low. Surely, by using only a few millivolts of the tube's characteristic, distortion should be negligible.

This you would expect. But it does

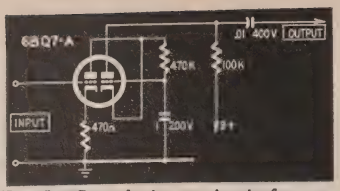

Fig. 1—Cascode input circuit for preamplifier input stages where noise must be minimized. Resistors and capacitors should be high-stability low-noise components.

not work this way in practice. You would expect a similar thing of high-quality transformers because their distortion is also due to nonlinearity. However, distortion measurements on the magnetizing current of high-quality transformer cores, suitable for input transformer use, show that reduction in level reaches an ultimate minimum in distortion—about 1% of the magnetizing current.

Of course, the distortion is likely to show up only at low frequencies because the magnetizing current itself is a small fraction of the currents that the transformer handles as signal currents at frequencies above the low-frequency cutoff. This means that such a transformer at low levels produces a distortion of maybe 0.5% in the region of 50 cycles, dropping to about 1/20th of this, or .025%, at 1,000 cycles. This residual value of distortion is due to a hysteresis effect in the magnetic core material.

It appears, although little work has been published on this, that tubes exhibit a small "hysteresis" effect, which is normally so minute as not to be worth considering. But, in comparison with the minute fluctuation of current we have to handle in low-level input stages, this hysteresis effect in the tube current characteristic is enough to represent harmonic distortion of about 0.1 or 0.2%, according to tube type.

This kind of distortion does not disappear—like the transformer magnetizing-current distortion—at higher frequencies, because the tube current fluctuations are the same whatever frequency the tube is amplifying.

So, in selecting a tube for low-level amplification, a number of factors have to be considered. Fortunately, tube manufacturers as well as amplifier designers are working on this, so we are able to call on their assistance to provide the best tubes for the purpose. What the amplifier *user* has to realize, however, is that you cannot just plug in, say, a 12AX7 as a replacement for a 12AY7 because it happens to give a similar gain in the same electrical circuit. It may even give a little more amplification, but it will probably introduce other troubles which have been taken care of in the design of the 12AY7.

Other components that need special attention in low-level input circuits are the resistors and capacitors. The capacitors must be low-leakage types. Their insulation resistance must be better than that required for normal amplifier applications, because any leakage through this insulation will cause increased noise.

Resistors should be made of a highly stable material that will not give appreciably more than the basic minimum of noise due to thermal agitation, which is a characteristic of all resistors.

The big problem in input transformers for low-level stages is shielding against hum pickup. Where the input level is very low, a triple-shielded transformer, giving a reduction in hum pickup of as much as 90 db, may be necessary.

Now we can see why a power amplifier would not do as a substitute for a preamp to provide the initial stages of amplification. A power amplifier's input transformer is intended to handle a normal signal of 0.5 to 1 volt. In trying to work at a level of 10 mv, it will probably pick up excessive hum because there is no necessity for superfine shielding in this application.

Further, the input tube of a power amplifier, while quite satisfactory for its purpose, would probably prove to be quite noisy and microphonic as well as introducing its own quota of hum when used for amplifying at low levels.

High-level components

From low-level operation we will turn to high-level operation because that is where the next group of problems arises. There seem to be no particularly tough problems in providing amplification at intermediate levels because then we are well away from the extremes which cause problems at either low- or high-level operation.

As you know, the big problem in high-level amplification is distortion. Here the curvature of the tube is the controlling factor. The problem of output stage design has been discussed many times, but there are other relatively high-level circuits where you must be careful in selecting tubes to give the best performance.

For example, pursuing the comparison made between the 12AX7 and 12AY7 for low-level work, when we compare the data, we find that the 12AY7 gives a larger harmonic distortion than the 12AX7 for the same output level if the signal voltage on the grid is more than about 0.1 volt.

Similar comparisons can be made between other tubes such as the 12AU7 and its nearest counterpart in the octal range, the 6SN7-GT. The 6SN7 will give both a little more output and a little less distortion than the 12AU7, operating as a single-ended tube. But at levels less than one-third of the maximum handling capacity, the 6SN7 gives considerable less distortion than the 12AU7. However, there is a consoling factor for the latter tube in that most of its distortion is second harmonic, and the pairs in the same envelope are usually pretty well matched.

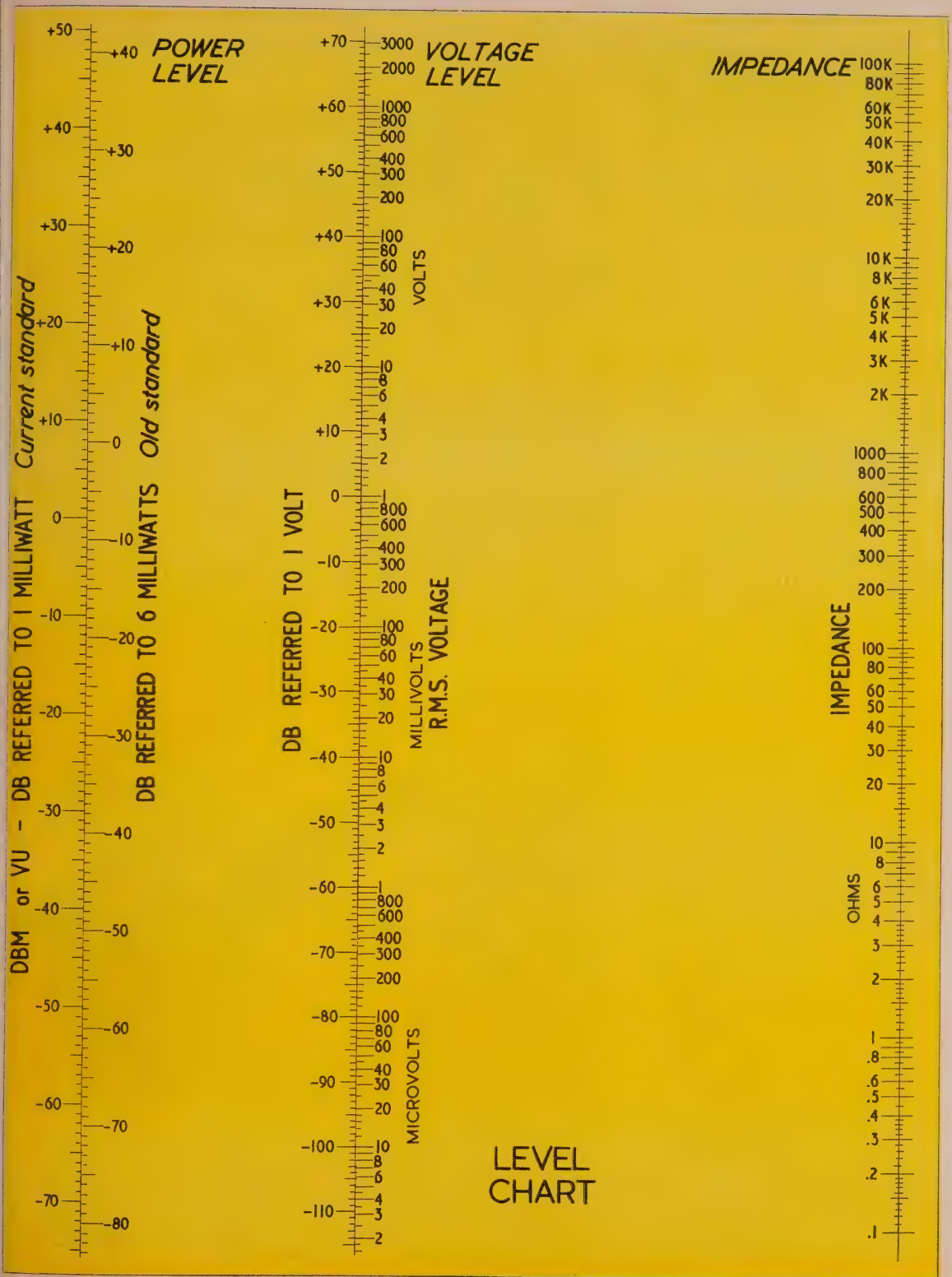
POWER LEVEL
DBM or VU – DB REFERRED TO 1 MILLIWATT Current standard
DB REFERRED TO 6 MILLIWATTS Old standard
VOLTAGE LEVEL
DB REFERRED TO 1 VOLT
VOLTS
MILLIVOLTS
MICROVOLTS
R.M.S. VOLTAGE
IMPEDANCE
IMPEDANCE
OHMS
LEVEL CHART

Fig. 2—Matching pad used between preamp and power amplifier permits best operation of overall system. The values suit the example given in the text. For other problems values should be worked out to suit the combination of equipment.

This means that a 12AU7, operated with its two triodes in push-pull, gives distortion and output comparable with a 6SN7, a considerable aid toward miniaturization.

A tube that may look tempting for some purposes is the 12AT7. It gives considerably more gain than either of the others just mentioned and its output is not too much less than theirs. While the 12AT7 has a very acceptable distortion figure at low levels—an input voltage of not more than 0.1—its distortion figures at higher levels do not compare favorably with the other tubes.

I could go on to discuss a whole range of tube types and their relative advantages and best modes of operation. The point I want to stress here is that in the design and use of amplifiers it is important to use the correct type for the purpose.

Other components in the circuit also have different requirements to meet for high-level operation than those at low-level operation. For low-level operation the important feature is reducing noise. At high-level operation the component must be able to handle maximum signal.

A point that can easily be overlooked is the dissipation of resistors. We may determine that a resistor has to drop 100 volts at 20 ma. Its value should be 5,000 ohms. A 4,700-ohm resistor looks like the nearest preferred value for this purpose. How often has the prospective amplifier builder dipped in his box of 4,700-ohm resistors (½-watt rating) and cheerfully put one into his circuit?

Had he stopped to do a little figuring he would have found that 100 volts at 20 milliamps is a dissipation of 2 watts. This would have saved him from finding his voltage-dropping resistor burned out before the amplifier had been in service very long.

So it's a safe rule to check the dissipation of all resistors in high-level circuits. Allow a safe margin, remembering that signals on top of dc potentials *always* increase the resultant dissipation.

There is one more component to consider in high-level circuits—the output transformer. However, designing or selecting an output transformer that will work successfully in a power amplifier is a story in itself. The output transformer is the heart around which a power amplifier is designed. As this is the subject of another article I will not take up space discussing it here.

When putting a system together it is important to know what levels are so you can arrange to minimize both noise and distortion. For example, working a preamplifier into a power amplifier, the power amplifier requires a certain input to give the full power output of which it is capable—usually between 0.5 and 1 volt. The preamp may be capable of giving out as much as 4 or 5 volts before it runs into serious distortion.

If a direct connection is made between these two items of equipment, the gain control of the preamplifier will have to be set between 10 and 20 db below the best operating level. As a result, the input fed to the power amplifier is likely to have more hum and noise than if the amplifier were designed to accept the full output of the preamplifier. The way to get the best performance out of this combination is to insert a resistance pad of the type shown in Fig. 2 so the preamp can deliver its full output of 4 or 5 volts while the power amplifier gets only the output of 0.5 to 1 volt that it needs.

Values can be calculated to suit the particular circuit in hand. Those shown in Fig. 2 suit a preamp with cathode-follower output, working into a power amplifier designed for a 600-ohm input. Although cathode-follower outputs are sometimes advertised as being 600-ohm or similar impedance, they work much better into an impedance higher than this, so it is well to build up the load impedance applied to the output of the preamplifier rather than using the nominal value given.

Use the chart as an aid in calculating the various levels in a system, taking into account impedance changes. To illustrate how it is used, one microphone is listed as giving an output level of −56 dbm for 10 dynes/sq cm, impedance 50 or 50,000 ohms. Another is listed as −59 db referred to 1 volt per microbar. How can we correlate this information?

A microbar is the same as a dyne/sq cm, but some people prefer to use one or the other. And 10 microbars or 10 dynes/sq cm represents normal speech level.

The first microphone is listed with a power-level rating for both available impedances. Using the chart, you will find that −56 dbm corresponds to 350-μv at 50 ohms, or −69 db referred to 1 volt. This form of reference is seldom used for low-impedance circuits. For 50,000 ohms, −56 dbm corresponds to 11 mv or −39 db referred to 1 volt.

The second microphone, being only high impedance, uses the voltage reference as being more direct. But it is quoted as −59 db for 1 microbar. Microbars being a unit of acoustic *pressure*, 10 times as many will induce 10 times the voltage. Since −59 db is 1.1 mv, 10 microbars will give 11 mv, or −39 db.

So the ratings mean both microphones have the same output, which we would never have known without this calculation! END

You appreciate him only when you need him . . .

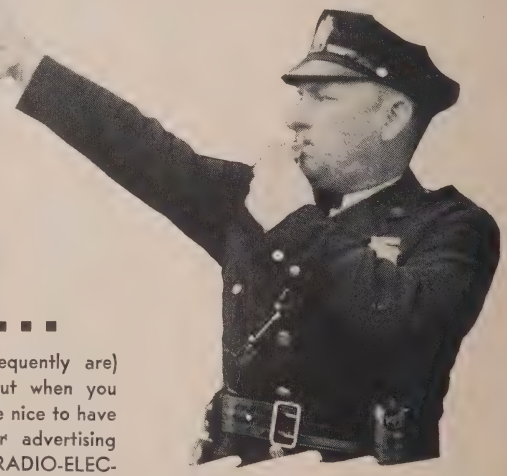

Cops can be (and frequently are) a pain in the neck. But when you really need one—they're nice to have around. That goes for advertising cops too. Maybe RADIO-ELECTRONICS mail-order tube policy is a nuisance to some people—certainly it is to the "fast buck" operators. But it's good to know it's working for you when you buy tubes by mail.

Since January, 1956, the publishers of RADIO-ELECTRONICS have insisted that mail-order tube advertisers state the condition of the tubes they sell —new or used, perfect or seconds, rejects, or surplus. It's no fun to play "cop"—but as long as it saves you from being gypped, we'll keep on doing it.

Reviewed by
CHESTER SANTON
Station WQXR, New York City

LAST month we looked into a special category of tape releases—individually made tapes designed to test the performance of tape machines. In general circulation these days are two other test tapes. These, however, are processed on duplicators: Westminster-Sonotape's 24-minute test extravaganza *Stereophonic Alignment Tape* (SWB-AL 101) at $11.95 and Stereophony's 4-minute *Test Tape for Stereo Balancing* (T-50) at $1.98. Containing more than test tones, both tapes have wide appeal. Playback in each case is 7.5 ips. At that speed, tape response today is reasonably flat to 10,000 cycles. Above that figure, frequency response falls off. For that reason, the Ampex and Livingston test tapes reviewed last month confine themselves to top test tones of 10 kc in the former and 12 kc in the latter.

Sonotape, by "strong-arm" tactics in gain boosting, manages a high-frequency tone labeled "15,000 cps for head alignment." The tone has audible intensity at normal listening level. The test frequencies are followed by an elaborate series of tests for balancing volume and equalization in the two channels. Perhaps the most useful of these is an excerpt from *Peter and the Wolf*. The music is switched several times from one channel to the other. With equalization controls of each channel in a flat position, this test is a good reference if further adjustments are necessary in the bass and treble setting on either channel. All told, the Westminster tape is quite a production. As a grand finale, the sounds of a subway train are merged with Tchaikovsky's *Fourth Symphony*.

The Stereophony tape performs its function without fuss or frill. Test tones of 3,000 cycles are alternately heard on each channel. The process is then repeated with tones of 100 cycles. In the final episode, the narrator moves from one microphone to the other. If the channels are in balance, he comes to a halt at a point midway between the two speakers.

If your system has separate volume controls, even the simplest tape for alternate-channel balancing can be useful in locating the "center of gravity" of the sound suspended between the speakers. Once located, its value is obvious, especially in the opening measures of classical music where one side of the orchestra provides most of the sound.

Stereophonic Recordings

Now that the stereo record is on the market, experiment in this medium has reached the consumer level. Audio Fidelity made this possible with its release in March of four Stereodiscs: *Dukes of Dixieland* (1851), *Railroad Sounds* (1843), *Music of the Bullring* (1835) and *Johnny Puleo and His Harmonica Gang* (1830)—all priced at $6.95. Played with the Electro-Voice ceramic stereo cartridge, these records exhibit reasonable stereo effect when the recommended distance of 6 to 8 feet separates the loudspeakers. The audio quality is passable. In my opinion, cleaner sound was present on the first truly compatible stereo disc demonstrated by Columbia Records during the recent IRE convention. As in stereo records, the commercial releases will tell a more complete story.

Walter Schumann presents the Voices
RCA-Victor Stereo Tape APS-103
(7-inch; playing time, 15 min. $6.95)

This tape offers very realistic projection of solo voices from within a highly trained mixed chorus. The acoustics of the recording studio are exceptionally "live." This liveness aids greatly in shifting the apparent sound source from the speakers to the area between them. This phenomenon remains the first sign of true stereo. Of the five tunes on the tape, *Blue Tango* and *Would You Like to Take A Walk* get outstanding treatment.

VIENNA
Fritz Reiner conducting Chicago Symphony Orchestra
RCA-Victor Stereo Tape ACS-63
(7-inch; playing time, 15 min. $6.95)

In stereo, RCA bows to no one in the concert waltz. Between them, the Chicago under Reiner and Fiedler's Boston Pops have taken over the field. Johann Strauss' *Morning Papers* and *Village Swallows* by Joseph Strauss are heard in excellent dynamic range that lends weight to the percussion without introducing distortion. With a proper stereo setup, the swallows are truly airborne.

TCHAIKOVSKY: *Symphony No. 5*
Herbert Albert conducting Mannheim National Symphony
Livingston Stereo Tape 4001 K
(7-inch; playing time, 48 min. $17.95)

The first Tchaikovsky *Fifth* to appear on stereo tape. Exceptional sonority and warmth in the woodwinds highlight a relaxed performance. The intimate miking in stereo explores, in a new way, the moody content of this music. It also reduces the already low tape hiss.

A Miracle in Sound
Mercury Stereo Demonstration Tape DEMS-2
(7-inch; playing time, 15 min. $5.95)

A recent cross-section of the Mercury catalog. The 10 stereo excerpts range from calypso to classics. The equalization is not the same on all samples. On expensive systems, the *Gaîté Parisienne* excerpt reveals exaggeration in the highs.

Dance Atop Nob Hill
Ernie Heckscher and His Orchestra
Verve Stereo Tape VST-10009
(7-inch; playing time, 31 min. $12.95)

Verve presents 25 ultra-danceable favorites in clean, bright sound—effervescence without the hiss. The recording technique matches the brisk style of Ernie Heckscher's orchestra—a fixture at San Francisco's Fairmont Hotel for the past 10 years. Well-centered stereo will add a new dimension to your next party.

The Big Reunion
Fletcher Henderson All Stars in Hi-Fi
Concert Hall Stereo Tape DX-71
(7-inch; playing time, 12 min. $6.95)

Memories of one of the first large jazz bands revived in today's sound. The Great South Bay Jazz Festival of 1957 brought together a number of the alumni of the Fletcher Henderson band. This inspired recording, made a few weeks later, puts stereo to good use. Wonderful definition in the ensemble work in the classic *King Porter Stomp* with the brasses appearing several feet above and beyond the sax section. The disc version (Jazztone J-1285) offers far more music in equally straight-forward sound.

Modern Orchestral Textures
Willis Page conducting New Orchestral Society of Boston
Cook Stereo Tape 1068
(7-inch; playing time, 19 min. $12.95)

Audiophiles familiar with the *Pacific 231* performance on 10-inch LP will welcome the same Cook version on stereo tape. Honegger's orchestral portrayal of a locomotive demands a spatial medium for full impact. The miking, unusually distant, dictates a moderate volume setting to stay below the noise level of that day. The tape includes Debussy's short, atmospheric *Danse* and a performance of Barber's *Adagio for Strings*, which I prefer to most other recorded versions.

Monaural Recordings

Note: Records below are 12-inch LP and play back with RIAA curve unless otherwise indicated.

BEETHOVEN: *Piano Concerto No. 5 in E Flat (Emperor)*
Rudolf Firkusny, Pianist
William Steinberg conducting Pittsburgh Symphony Orchestra
Capitol PAO 8419

Capitol's time-tested miking formula for the Pittsburgh hall contains a recent refinement. According to Frank Abbey, chief recording engineer at their sessions, the single Telefunken located in the first row of the concert hall's second balcony remains the basic microphone for overall pickup. All of the Pittsburgh recordings have utilized it. On stage, however, three Telefunkens have now replaced the ribbon mikes formerly used for solo passages in the orchestra. An extra Telefunken picked up the piano. The result—a true concert hall balance. The performance of Beethoven's greatest piano concerto is an excellent one.

London Microgroove Frequency Test Record
London FFRR 5343

London's new test recording is based on the RIAA curve. Its 25 tones range from 30 to 18,000 cycles. The separate frequency bands are arranged in groups of five. Frequencies above 10 kc are recorded 6 db below standard curve. Side 2 contains gliding frequencies with the same range and levels.

Espana, Vol. 9
Ataulfo Argenta conducting Orquesta de Camera de Madrid
London FFRR LL-1740

Orchestral interludes from the Spanish lyric theatre directed with smooth authority by the late Ataulfo Argenta. London's latest recording in *The Music of Spain* series enhances the reputation for sound established in previous volumes. This disc holds its richness of sound at all levels. A deluxe item.

Bagpipes and Drums
9th Regiment, New York State Guard Pipe Band
Audio Fidelity AFLP 1857
Giant Wurlitzer Pipe Organ
Leon Berry, Organist
Audio Fidelity AFLP 1844

On a good system, the low bass on these two records will jar loose the fillings in your teeth, so close is the pickup. Audio Fidelity has added to its microphone roster the Electro-Voice 667 with transistorized features. Their closest miking to date does away with virtually all room acoustics. To reinstate some of them, try listening to these in an adjoining room. Traditional bagpipe music on the first record. The second offers rumpus-room fare on the Wurlitzer that Leon Berry has installed in the basement of his home. END

Name and address of any manufacturer of records mentioned in this column may be obtained by writing Records, RADIO-ELECTRONICS, *154 West 14 St., New York 11, N.Y.*

Remote Transistor Ear

This 3-transistor intercom has a ½-watt output

By F. J. BAUER, JR., W6FPO

NOW that low-priced power transistors are generally available, you can build transistor equipment with power output equal to that obtainable with vacuum tubes. The intercom described in this article is an all-transistor device which plugs into the 117-volt ac power line. It has an audio output of approximately 1 watt which is instantly available as no warmup time is required.

There are three transistor audio stages, and a selenium bridge rectifier for the power supply. The circuit is simple and conventional except for the input stage, which is connected as a common-base amplifier. This configuration does not require an input transformer since its input impedance is low enough to work directly as speaker voice-coil impedances. Eliminating the input transformer also reduces the possibility of hum pickup by the input stage and results in a quiet, high-gain amplifier. The .015-μf ceramic disc capacitor connected across the amplifier's input eliminates broadcast-station interference when the intercom is used with a long remote-speaker line. The rest of the amplifier circuit is straightforward, employing transformer-coupled common-emitter stages.

All parts are standard and readily available, with the possible exception of output transformer T3. I used an Acme Electric Corp. T-24041. If you cannot obtain this unit, you can use a Thordarson TR-61. The primary's ct is not used and only the 3.2-ohm tap on the secondary is shown in the diagram. The power transformer is a 6.3-volt heater transformer with a 1-ampere rating.

No attempt was made to miniaturize the unit. Plenty of room was available for standard components on the 6½ x 4-inch chassis. Standard components also reduce the cost of parts.

The 2N255 power transistor is plugged into a nine-pin miniature tube socket with no heat sink for the collector. Its case must be insulated from the chassis. A heat sink is not required because the power input to the 2N255 is limited to 1.25 watts, or half the transistor's maximum dissipation rating.

Hints for better construction

The parts layout is not particularly critical. In general, the amplifier follows a logical layout from left to right when viewed from the rear, with low-level components such as the small transistors and interstage transformers mounted at the left end. The output transformer, power transistor and selenium rectifier are mounted at the right end of the chassis, as shown in the photographs. When laying out the amplifier, pay particular attention to the following items to avoid possible feedback troubles:

A ½-inch separation between the speaker frame and output transformer core is minimal, as shown in the photographs. If the transformer is too close to the speaker, you'll get audio feedback when the intercom speaker is used as a microphone.

The output transformer's secondary leads must be routed well away from the speaker, preferably below the chassis to prevent feedback. Shield this lead and ground it to the chassis.

Do not mount the power transformer on the chassis. The field from the transformer will induce a 60-cycle hum in the speaker when it is used as a microphone, no matter where the transformer is placed on the chassis.

This problem is solved by completely isolating the transformer from the intercom. The transformer is mounted in a small metal box which plugs directly into the ac outlet. The ac line running

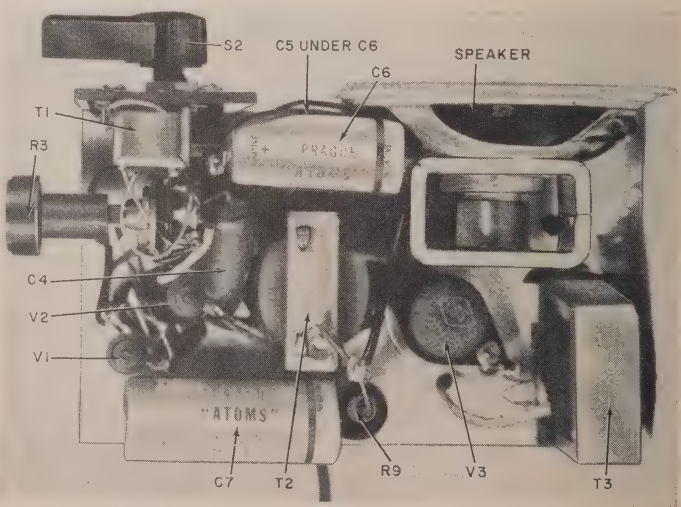

Top view of the completed intercom. The remote speaker connects to terminals on the rear of the unit.

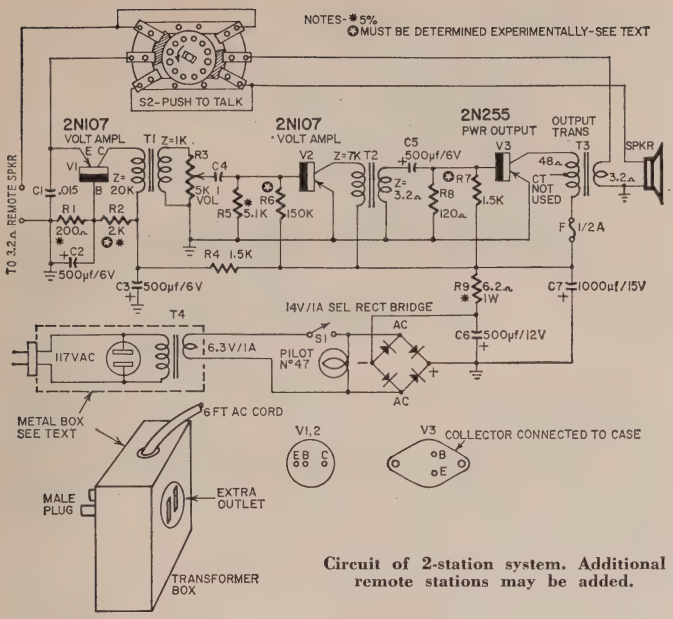

Circuit of 2-station system. Additional remote stations may be added.

R1—200 ohms, 5%
*R2—2,000 ohms 5%
R3—pot, 5,000 ohms, audio taper
R4—1,500 ohms
R5—5,100 ohms, 5%
*R6—150,000 ohms
*R7—1,500 ohms
R8—120 ohms
R9—6.2 ohms, 1 watt
All resistors ½-watt 10% unless noted
**Values shown for these resistors are the ones used by the author. However, the proper values for your unit must be determined experimentally. See text for details*
C1—.015 μf, disc ceramic
C2, 3, 5—500 μf, 6 volts, electrolytics
C4—1 μf, metallized paper
C6—500 μf, 12 volts, electrolytic
C7—1,000 μf, 15 volts, electrolytic
F—0.5-amp fuse
RECT—selenium-bridge rectifier, 14 volts dc, 1 amp (Barry Electronics Corp., 512 Broadway, New York 12, N.Y.)
S1—spst
S2—dpdt, spring-return wafer type (Centralab 1464 or equivalent)
T1—interstage transformer: primary, 20,000 ohms; secondary, 1,000 ohms (Argonne AR-104 or equivalent)
T2—output transformer for 50L6 or 50C5. Primary impedance 7,000 ohms; secondary impedance 3.2 ohms
T3—output transmormer: primary impedance 48 ohms, ct not used; secondary impedance 3.2/8/16 ohms (Thordarson TR-61 or equivalent)
T4—heater transformer: primary, 117 volts; secondary, 6.3 volts, 1 amp (Thordarson 21F08 or equivalent)
Speakers, 3.2-ohm; 3-, 4- or 5-inch
Fuse holder
Pilot-lamp assembly and No. 47 bulb
Chassis, 6½ x 4 inches
Cabinet, 6½ x 5½ x 4 inches
Transformer box, 4 x 2⅛ x 1⅝ inches
Male plug
Miscellaneous hardware

from the transformer box to the intercom unit carries 6 volts. During operation, the remote power transformer is left on continuously and the intercom switch is used to turn the unit on and off. The switch merely opens a lead to the bridge rectifier. This arrangement is practical since the transformer draws negligible power from the line, especially with the intercom switch in the off position.

I mounted some of the electrolytic capacitors above the chassis since they are bulky and chassis space is available. The capacitor leads are covered with insulating tubing and routed through holes in the chassis as required.

Selecting the bias resistors

The unit should be completely wired except for the base bias resistors (R2, 6 and 7) and the push-to-talk switch (S2). Connect the intercom speaker to the output transformer temporarily and connect a remote speaker to the amplifier input. Be sure the remote speaker is placed so it does not cause acoustic feedback. Connect a 500-ma meter across the fuse holder with no fuse installed. The amplifier is now ready for bias adjustments of the various stages.

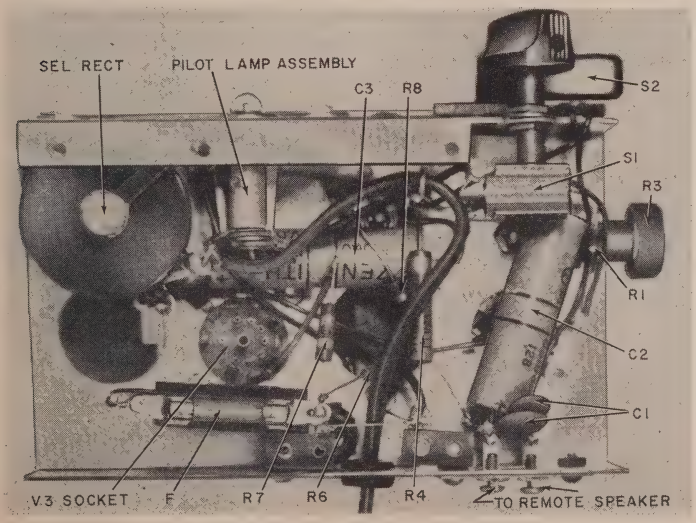

Parts layout under the chassis.

Connect a 5,000-ohm potentiometer in the circuit for R7 and make certain that the full potentiometer resistance is in the circuit before the power is turned on. Adjust the potentiometer for a collector current of 250 ma. Allow the 2N255 power transistor to reach full operating temperature by letting it run for about 20 minutes, meanwhile readjusting the potentiometer to keep the collector current at 250 ma. When the output stage has stabilized, as evidenced by no further change in collector current, check the potentiometer's resistance on an ohmmeter and install the nearest standard-value resistor permanently. Now check the collector current with the resistor installed and, if all is well, you can disconnect the milliammeter and put the 0.5-amp fuse in its holder.

Follow the same procedure to determine the proper bias resistor for the driver stage, starting with approximately 300,000 ohms for R6. Adjust the 2N107's collector current to 1 ma and again allow sufficient time for the stage to stabilize with respect to collector current.

If collector current cannot be limited to 1 ma, the 2N107 transistor should be replaced with another. Some experimental transistors, such as the 2N107, have a tendency to draw excessive current even with zero bias when operated near maximum ratings of 5 volts or so, due to the lack of uniformity in these low-priced units. Such transistors will still perform satisfactorily in low-level low-voltage applications.

When adjusting the bias of the common-base amplifier stage, use a 5,000-ohm potentiometer to determine the value of R2. You will find that the base voltage adjustment for a given tran-

sistor is fairly critical. Low emitter-base voltage will result in low collector current and noise with low amplification.

As the emitter-base voltage is increased, the thermal noise heard in the speaker is gradually reduced and amplification increases noticeably. If the bias adjustment is carried too far, the useful amplification will drop and the amplifier will cease to function. The proper adjustment for maximum gain is just below that point. I find that the easiest way to make this bias adjustment is to place the remote test speaker in a quiet location and use the ticking of an alarm clock as the signal source.

After adjusting the bias on the various stages and checking the amplifier for stability, wire in the PUSH-TO-TALK switch. If the amplifier tends to oscillate on talk-back, reroute the output transformer lead to minimize feedback. Careful routing of the output transformer's output lead is very important.

The routing of this lead is particularly critical where it connects to the push-to-talk switch, since it is close to the amplifier input at this point. The best procedure is to shield the lead and move it around until there is no feedback on talk-back with gain nearly wide open. During this test be sure that the remote speaker is far enough from the master unit so you will not be fooled by a case of acoustic feedback.

Most of the time electrical feedback cannot be completely eliminated with the gain wide open on talk-back.

Final steps

It will probably be necessary to treat the cone of the intercom speaker. If the speaker size is less than 5 inches, it tends to produce distortion, when used as a microphone because of the thinner cone material used in such a small unit. If distortion is experienced on talk-back, give the speaker cone two coats of shellac to increase the diaphragm stiffness. Shellac the flat conical section only and leave the ribbed outer section near the frame untouched. This will give you a relatively stiff diaphragm with a flexible suspension. This way, performance as a microphone is greatly improved without impairing its performance as a loudspeaker.

No station-selector switching system was built into the unit because this feature was not desired. However, a regular station-switching system may be added if you want more than one remote station.

If excessive thermal hiss develops after the intercom has been in service for a while, it is an indication that the first stage has changed characteristics due to transistor aging. This may be corrected by determining a new value for bias resistor R2. Low-noise transistors are now available, so if you feel that the residual amplifier noise is objectionable, after bias adjustment, try a 2N106 or 2N189 in place of the 2N107. END

a PA DUMMY LOAD

Lets you test your amplifier without raising the roof

By RICHARD H. HOUSTON

IN PA work, particularly on jobs other than the run-of-the-mill type, a dummy load is helpful. The amplifier builder finds a dummy load handy for testing purposes. An actual setup we used recently is an example. The job called for recorded music and live program material to be "broadcast" from the park in which the community Christmas tree had been set up. Since the programs were to continue during the entire Christmas season, I decided to establish a temporary studio in my home. The park was several hundred feet from the studio, making a volume indicator and aural monitor necessary. The wide variety of live program material presented the problem of auditioning each "act" in advance to determine correct microphone placement, gain settings, etc. A dummy load resistor to replace the speaker line solved the problem since the volume indicator, monitor, PA amplifier and other equipment operated just as though the speakers were connected.

When a dummy load is needed, the PA operator can connect an appropriate resistor across the amplifier's output, but this necessitates a certain amount of haywire and does not lend itself to rapid switching from load to speakers as is sometimes necessary. A far smoother program and a better impression on the customer will result if a neat, easily installed, quickly operated dummy load box is used.

Such a load box, capable of absorbing 40 watts of audio power, is shown in the photos and Fig. 1. Switch S2 connects either the speakers or the dummy load to the amplifier output. Switch S1 selects the load impedance to match the amplifier and speakers. Connections to the amplifier and speakers are made through sockets on the rear of the cabinet or a terminal strip mounted above the sockets.

Building the load box

Construction of the load box is simple. The entire unit is contained in a 6 x 6 x 6-inch steel box with removable panels at the top and bottom. Input J1 has a separate terminal for each common PA output impedance. Each of these terminals is connected to a corresponding terminal on S1-a. When S2 is in the SPKR position, the rotor of S1-a is connected to the rotor of S1-c. When S2 is thrown to the LOAD position, the rotor of S1-a connects to the rotor of S1-b, which selects a dummy load resistor to match the amplifier impedance.

The impedances available are 2, 4, 8, 15, 200 and 500 ohms. Other values may be used if these do not match the speakers or amplifiers you use. The load resistances are made up of combinations of individual resistors in series and parallel. If single resistors of the desired resistance and power rating could be obtained the construction would be simplified, but some values are very difficult to find. However, it is not difficult to make up any required value from standard units. A more refined unit built with noninductive resistors would enable the experimenter to make precise measurements of output, distortion and other factors. For most PA purposes, ordinary wirewound resistors are adequate.

I made up the load resistances from my junkbox (Fig. 2). Four 500-ohm 10-watt resistors in series-parallel form the 500-ohm load. Two 400-ohm 20-watt units in parallel make up the 200-ohm load. The 15-ohm load is made from four 15-ohm 10-watt resistors in series-parallel.

The 8-ohm load is a combination of five 10-watt resistors in parallel (obviously a junkbox combination). I used 33-, 39-, 40-, 44- and 50-ohm resistors. Their actual resistance is 8.1 ohms, but this difference is negligible. The 4-ohm load is four 1-ohm 20-watt resistors in series with a tap to form the 2-ohm load. Each combination of resistors is secured to the rear wall of the cabinet by a threaded rod passed through the hollow core of two of the resistors.

It is a fairly simple matter to make up the required combinations of resistors from a well-stocked junkbox or from manufacturer's stock. The resist-

(Right) The PA load box has only two controls.

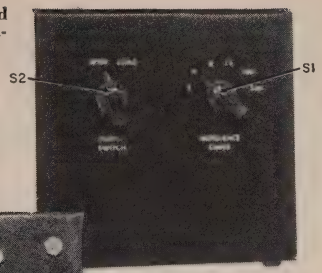

(Below) Input and output connections are on rear of cabinet.

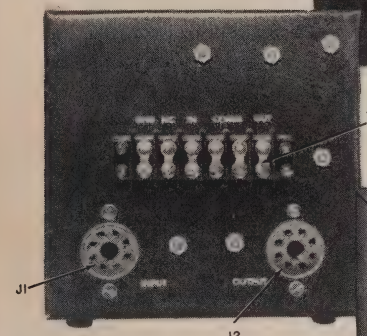

(Below) Load resistors are fastened to rear of case.

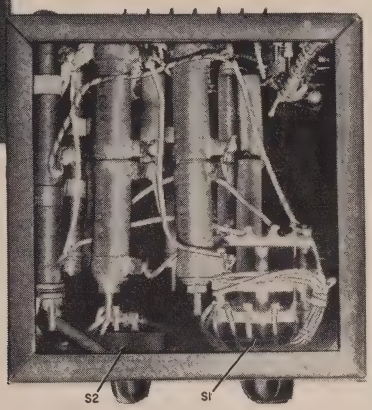

R1—500 ohms
R2—200 ohms
R3—15 ohms
R4—8 ohms
R5, 6—2 ohms
All resistors 40 watts or more, wirewound. See text
J1, 2—octal sockets
S1—3-pole 6-position rotary
S2—spdt rotary
Terminal strip, 5 or more contacts (1)
Cabinet, 6 x 6 x 6 inches
Knobs
Miscellaneous hardware

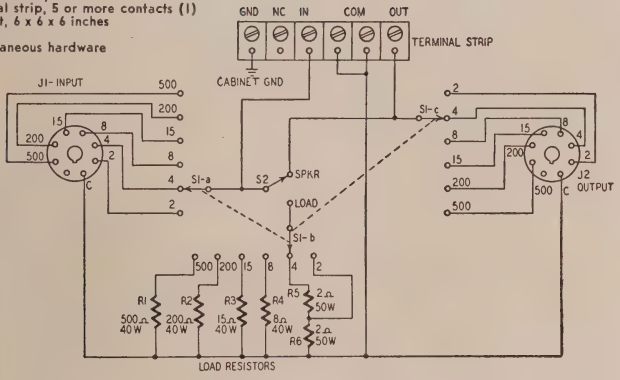

Fig. 1—Circuit of the PA dummy load.

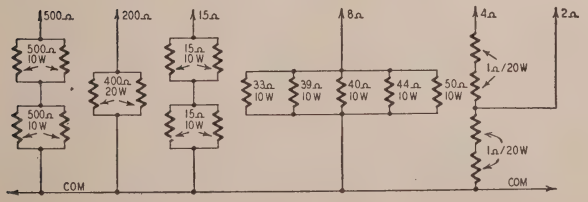

Fig. 2—Author used this method to obtain proper load impedances.

ance of a combination is calculated with the usual parallel- and series-resistor formulas. Keep a sharp eye on the wattage ratings to see that the total rating of the combination will equal or exceed the desired rating, which was 40 watts for this equipment. If identical resistors are used in series, in parallel or in a *symmetrical* series-parallel arrangement (as in the 500- and 15-ohm loads), the total wattage is the sum of the individual wattages. If dissimilar resistances are connected in any way or identical resistors are connected in a nonsymmetrical circuit (one resistor in series with a parallel combination of two others), the total wattage is a bit more difficult to calculate.

Wattage calculations

The easiest way to calculate the wattage of a circuit is to figure on the basis of the voltage across a parallel circuit or the current through a series circuit. For example, the 10-watt resistors used for the 8-ohm load are all in parallel, and the total power is easily calculated on a voltage basis. Since power is equal to E^2/R and the same voltage must of course appear across all resistors in a parallel combination, the lowest resistance unit will dissipate more power than any of the rest. In our case, the voltage is limited to that which will cause the 33-ohm resistor to dissipate its full 10 watts. This 10 watts equals $E^2/33$, so E, the maximum permissible voltage, is 18.2. This voltage across the entire combination, whose combined resistance is 8.1 ohms, corresponds to a total power rating of $(18.2)^2/8.1$, or 40.7 watts.

(Compare catalogs of various resistor manufacturers. Available resistances and wattages vary in different lines. It is possible to obtain all resistors except R4 in single units of either 40 or 50 watts, depending on the brand. R4 can be a series combination of 3 and 5 ohms or 4 and 4 ohms, each at 25 watts, or a parallel network of two 15-ohm 20-watt units. The selection depends on the brand or brands handled by your dealer.—*Editor*)

The input and output jacks are ordinary octal sockets since these connectors are standard in my equipment. Other types of connectors can be substituted to match any system. In any unusual or experimental situation where standard plug connections are inadequate, lines connected to the terminal board may be switched in exactly the same way as cables connected through the plugs. The SPKR–LOAD switch is a rotary switch, since switching may be necessary when silence must be maintained.

Probably few PA men have provided dummy loads for their work, but for the unusual job the convenience is well worth the effort of construction. Within a short time a flexible, easily used dummy load box will become an indispensable part of PA gear. END

AUDIO—HIGH FIDELITY

TAKE YOUR PICK: CHANGER or TURNTABLE

Some like changers, others prefer turntables—an outstanding one in each category is described here: the Glaser-Steers GS-77 changer and the Weathers ML-1 turntable

By HERMAN BURSTEIN

WHILE a transcription turntable is preferred for the utmost in high fidelity, the better record changers manage to keep only a step behind in performance. This step is so short that for many audiophiles the difference between a turntable and record changer is insignificant. Considering the numerous operating conveniences that changers offer and their generally lower price compared with a transcription turntable plus tone arm, it is easy to understand why changers are popular in high-fidelity systems.

Glaser-Steers GS-77

The Glaser-Steers GS-77 record changer is a newcomer that incorporates several novel and important features together with those that have become standard for changers in general. Despite its many features, the mechanism is relatively simple, as changers go, which is important from the viewpoints of reliability and ease of servicing.

The most striking innovation is the automatic speed change made possible when the speed-selector knob is in the Speed Minder position. Then 10- and 12-inch 33⅓-rpm records can be intermixed with 45-rpm records, and the machine will change automatically from one speed to the other as necessary. The index finger (see photos) contacts each record to gauge its size and adjust the starting point of the pickup arm accordingly. The finger cannot contact a 7-inch 45-rpm disc. This actuates the speed-change mechanism. The automatic speed-change and intermix feature does not extend to the 16-rpm speed. The speed knob must be turned to the 16-rpm position.

Although 33⅓- and 78-rpm records cannot be intermixed with an automatic speed change, the GS-77 in Speed Minder position shifts automatically to 78 rpm when a modified G-E VR-II cartridge, optionally available with the changer, has its 78-rpm stylus brought into position. A small arm on the cartridge strikes a lever on the rest post and causes the shift to 78 rpm. Piezoelectric cartridges frequently use a flipover arm for changing from microgroove to standard stylus, and in some cases this arm can serve the same purpose as the special arm on the G-E. Glaser-Steers reports that a number of manufacturers of cartridges with dual styli are modifying them to incorporate such an arm. For cartridges without a flipover arm or with a specially attached one, the GS-77 comes with a clip which is mounted on the pickup arm to actuate the 78-rpm lever on the rest post.

The automatic change to 78 rpm, accomplished by changing from microgroove to standard stylus on a turnover cartridge, is not merely a convenience but also a matter of record safety. Many users of turnover cartridges have had the sad experience of accidentally playing a microgroove record with a 3-mil stylus and damaging the grooves. The automatic change to 78 rpm when the 3-mil stylus is brought into position provides an immediate alarm—Donald Duck sound—if a 33⅓-rpm disc is played.

The change cycle is very brief, about 5 seconds, and remains the same at all four speeds as the change mechanism is independently driven by the motor rather than the turntable. During the cycle the turntable is stopped—by a brake against the inner rim—to prevent possible record abrasion as one disc drops onto another and so that the stylus will not cut across a moving groove as the arm comes down. Turntable motion resumes only after the stylus is in the lead-in groove, and full speed is reached in a fraction of a revolution.

For correct operation, three adjustments are readily accessible to the user at the pickup arm. One, to vary stylus tracking force; another to index the pickup arm so it will start at the proper point on the record, and the third to adjust the height at which the stylus stops above the turntable.

The tracking force remains within 1 gram from bottom to top of a stack of records. This is done by mounting the counter-tension spring of the arm as nearly horizontal as possible, so its length changes very little as the pickup arm moves up and down.

Resonance of the tone arm, always a problem and more so in changers, is kept below 20 cycles by using an aluminum casting with reinforced ribbing, having no parallel surfaces and isolated from the deck by a rubber bushing.

The GS-77 can be operated manually if desired, and by placing the balance arm over the spindle the changer will shut off automatically when the record is over. The tripping mechanism that actuates the change cycle does not operate until the pickup arm reaches the last few grooves, so premature tripping due to cuing or groove irregularities is much less likely to occur. If the pickup arm is moved during a change cycle, the mechanism will not be damaged—frequently a bugaboo in record changers. The idler wheel, which drives the turntable rim, is automatically disengaged from both the motor pulley and turntable rim when the changer shuts off, preventing wow due to deformation of the rubber on the idler. Sound output is muted during the change cycle and when the tone arm is on the rest post. An R-C filter across the motor switch prevents a disturbing pop in the speaker when the changer shuts off.

In addition to quality of design, parts and assembly, performance of a product depends vitally upon adequate testing. After alignment and inspection for correct operation, *every* changer is checked for conformance with the following requirements: flutter (above 20 cycles) no more than 0.1% rms; wow (below 20 cycles) no more than 0.25% rms; rumble equivalent to at least 40 db below a 500-cycle signal recorded at 7 cm/sec peak (NARTB specifies rumble to be 35 db down); speed accurate within 2%. The inspected units are placed in racks of eight, and three of these eight are checked over again. If one of these three fails to meet standards, all eight undergo a complete check.

Weathers ML-1 turntable

The Weathers ML-1 turntable follows a design philosophy quite contrary to other professional units, yet comes up with truly professional specifications—wow 0.1%, flutter .01%, rumble 70 db below a recorded level of 7 cm/

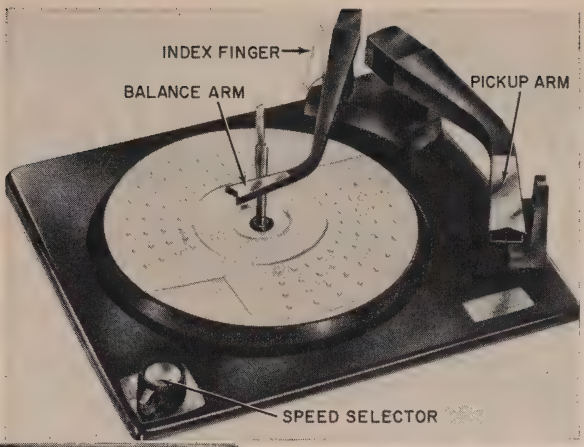

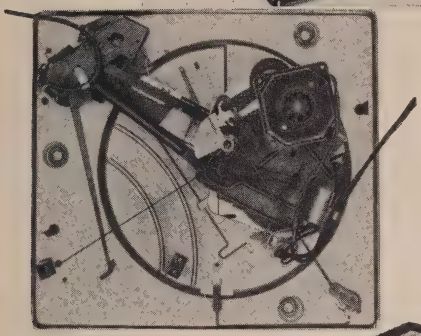

The Glaser - Steers GS-77 ready to use.

A bottom view shows the comparative mechanical simplicity of the GS-77 changer.

The Weathers ML - 1 turntable. The firm's FM capacitance pickup is shown.

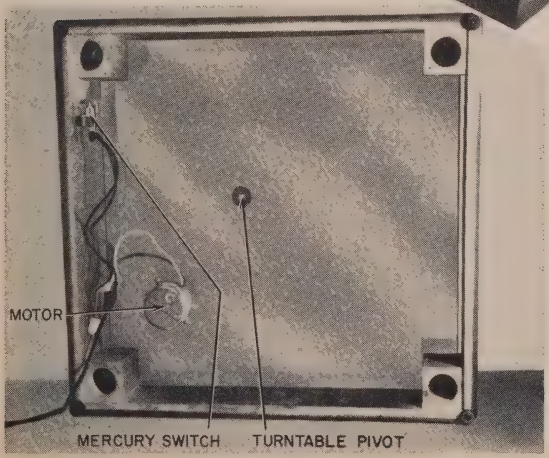

The diminutive motor mounted under the motorboard presents an unusual appearance to the audiophile and represents a new approach to professional type turntables.

sec, and speed accurate within 0.25%.

The basic problems of a turntable are rumble, flutter and wow, which originate in motor vibration. Mr. Charles J. Gillies, a Weathers engineer, points out in a letter he wrote me that the vibration causes the rumble, while flutter and wow are due to shock-mounting of the motor and to the speed-reducing idler wheel used in many turntables.

In his words, the Weathers design philosophy is: "Why not use a very small precise motor which is practically free of vibration? This is exactly what we have done. The motor is a 12-pole synchronous type which rotates at only 600 rpm. It is so free of vibration that we can mount it solidly on the motor board. . . . The turntable can be driven directly from the shaft of the motor by a small rubber wheel of special shape which is made of very live pure gum rubber.* The bearing system is extremely free, and the platter itself is very light. Since the motor is very free of vibration, it is not necessary to use excessive weight to damp out the rumble."

Synchronous motors are known to have a tendency to hunt about their nominal speed and, partly for this reason, heavy turntables are used to provide a steadying flywheel action. How does the Weathers unit get around the hunting problem despite use of a table weighing less than a pound?

Mr. Gillies replies: "Many manufacturers defeat some of the truly fine features of a synchronous motor by making it much too big. When the armature is heavy, it takes considerable power to turn it at this speed and there always is a tendency to hunt around the correct speed, due to the moving part of the motor. Our tiny motor has so little mass that this effect is mitigated. Also . . . you still get flywheel action from our turntable since its mass in relationship to motor mass is large. . . . The Weathers turntable will come from a dead stop to synchronous speed in three-quarters of a revolution and will not go beyond this synchronous speed. Thus, the hunting of the entire turntable as well as the hunting of the motor have been eliminated."

It is interesting to note that the ML-1 comes complete with base, and that resonance of the suspension system between turntable and base is kept low enough to minimize the effects of floor vibration, often a serious problem when the cartridge is operated with very low tracking force. The turntable pad is designed to suspend the record only at the outer rim, and a plastic disc around the center post supports the center, thereby preventing contact with the playing surface and resulting abrasion, pickup of dirt, etc. Although the ML-1 operates only at 33⅓ rpm, an electronic control is optionally available to drive it at the other speeds in common use. END

* To isolate such little vibration as does exist.

more jobs for SEMICONDUCTORS

Part II—They measure heat and light . . . make heat and light batteries . . . air-condition and refrigerate without moving parts

By PAUL PENFIELD, JR.

LAST month we saw how semiconductors could be used as voltage-variable capacitors and electronic switches or to measure magnetic fields. Now we will go on to photoresistors, photodiodes, photocells, thermistors and thermocouples.

Photosensitive devices

Many kinds of photosensitive semiconductor devices are possible. There are photoresistors, photodiodes, photovoltaic cells, phototransistors, PME photocells and lateral photocells.

The effect of light on a semiconductor is easy to understand. As you may know, light comes in small packets or photons. Each photon that hits a semiconductor makes an electron jump across the forbidden band—that is, it simultaneously creates an electron and a hole. Practical photocells use these electrons and holes.

Photoresistors are merely pieces of semiconductor, with two leads attached as in Fig. 5. A voltage is applied across the sample but only a small amount of current flows, since the number of holes and electrons available for conduction is small in a semiconductor. As soon as the photoresistor is exposed to light more electrons and holes are available and much more current flows.

Practical photoresistors can be extremely small. The recent cadmium sulfide and lead sulfide photocells are actually photoresistors. Germanium and silicon can also be used.

Another device is the photodiode. This is nothing more or less than an ordinary diode—either point-contact or junction. In operation it is reverse-biased, so very little current flows. But when the junction is illuminated, hole-electron pairs are formed. These pairs flow, forming current. Very high efficiencies are possible, and the photodiode is a widely used device.

You can get the same effect using ordinary diodes, but with less efficiency. Try it yourself on one of the diodes that come in a glass case. The circuit of Fig. 6 demonstrates this principle. Be careful about battery and diode

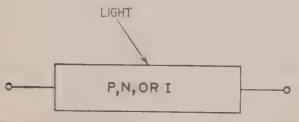

Fig. 5—Photoresistor made of p, n or intrinsic material.

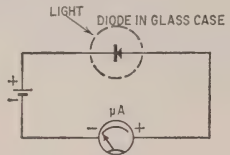

Fig. 6—Circuit for checking effect of light on diode. Use either point-contact or junction diode.

polarity, so that the diode is really reverse-biased. With a 100-watt bulb as a light source and using a 1N34-A you should get 20–30 μa, easily read with a vom.

A phototransistor is similar to a photodiode, except that it is physically identical to a transistor instead of a diode. Either p-n-p or n-p-n phototransistors are possible. In operation the base lead is not used, but the normal collector-to-emitter bias is applied. The current will be the normal cutoff current until light is applied to the collector junction. Then current rises sharply to a value about β times the equivalent photodiode current. Transistor action accounts for this amplification of the hole–electron pairs formed. The phototransistor can be considered a photodiode with a built-in amplifier.

Photovoltaic cells

A photocell that does *not* require a bias is the photovoltaic cell. Its physical structure is the same as the photodiode, and it can be used either way—as a photodiode or as a photovoltaic cell.

Strange as it may seem, if you shine light on an ordinary diode, you will develop a voltage across it. If the circuit is closed, current caused by the light will flow. For absolute proof of this effect you can try it yourself. Use any diode—point-contact or junction—that has a glass case. On bright illumination the output will be readable on a vom. The same setup as Fig. 6 can be used, without the battery.

The so-called barrier-layer photocell is nothing but a photovoltaic cell. Again, the practical devices were in use long before the theory was well developed but, along with the theory, came improved techniques for making the devices, improved efficiencies, better materials, etc. The physical shape of present-day photovoltaic cells and the materials used differ from the early models, but the fundamental process is the same.

Photovoltaic cells are used in photographic exposure meters and in many control applications. Practically any semiconductor can be used—typical cells use copper oxide, selenium, germanium, silicon, etc.

Because they require no bias, photovoltaic cells are useful for converting energy—they can be used as a battery. Shine light on the device, and the energy of the light is converted into electricity. The solar battery developed at Bell Telephone Laboratories is a photovoltaic cell designed specifically for energy conversion. Another similar device is one of the recently announced nuclear batteries. Instead of trying to convert nuclear energy directly into electrical energy, the inventors let the nuclear radiation hit a fluorescent material so it would glow, like a "radium" wristwatch dial. This light was used to power a photovoltaic cell.

Another type of photocell which is useful for converting energy, since it requires no bias, is the PME photocell, or the *PhotoMagnetoElectric* cell. This was developed simultaneously by two groups, one in England and the other in France, a few years ago. The principle is very simple.

Fig. 7 shows the device. It is similar to the Hall-effect devices (described last month) except that, instead of the current from left to right, the electrons and holes are supplied by light. Electrons and holes are formed right at the surface and they tend, because of their large numbers, to move away from the surface. As they diffuse back into the material, they get caught by the magnetic field and the holes are pushed up and the electrons down. Then a voltage appears across the two terminals—the PME voltage. Thus, the PME cell takes advantage of the Hall effect operating

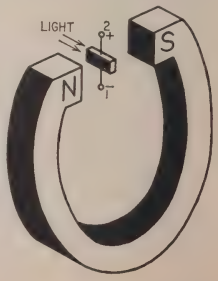

Fig. 7—PME photocell uses Hall effect acting on light-induced electrons and holes.

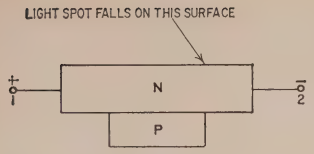

Fig. 8—The Wallmark lateral-effect photocell.

on the electrons and holes formed by the light.

The PME effect is used to measure certain properties of the semiconductor and is in less use as a practical photocell. It has certain advantages, however, and in the future will be used more, both as an indicating device and as a battery.

Just one more type of photocell, now —the Wallmark lateral-effect photocell. The theory here is a bit more complicated, but the device has some unique properties. As Fig. 8 shows, it consists of a p-n junction with two contacts to the n-material. If one of these contacts and a contact to the p-region were used, we would have an ordinary photodiode or photovoltaic cell. However, we prefer to use the two contacts to the n-region. The p-n junction then becomes a floating junction since no net current passes through it.

If the device is lighted with a small spot right at the center, nothing will happen except that a photovoltaic voltage will be generated. The two terminals (1 and 2) will be at the same voltage. However, if the spot is moved to one side or the other, the action of the floating junction is to cause a voltage between terminals 1 and 2. This lateral-effect photocell, developed by RCA, tells us the position of the spot of light—something none of the other photocells would do. Useful in many control applications, this photocell, not yet commercially available, will find many specialized applications.

Heat-operated devices

There are many ways to use the unique temperature properties of semiconductors. Thermistors or diodes can be used for reading temperature. For heating or cooling objects, we can use a Peltier refrigerator. We can use a thermocouple as a battery. All this is possible with semiconductors because the effects are more noticeable than with metals.

A thermistor is merely a piece of semiconductor with two leads on it. It is useful because its resistance depends on the temperature—the higher the temperature, the lower the resistance, *contrary to the way metals act.*

A thermistor can be used to "read" temperature, the same way a photoresistor is used to "read" light intensity. The action of these two devices is quite similar.

Thermistors are made in many sizes and shapes for all types of control purposes. They are useful, for example, in controlling the bias of a power transistor stage, to prevent the transistor's burning up at higher temperatures.

A diode also can be used as a thermometer. Diode reverse current is a very sensitive indication of the temperature. In this respect it is similar to a photodiode whose reverse current is a very sensitive indication of the light level.

Thermocouples have been known for some time. The basic circuit is in Fig. 9, showing two kinds of conductors (here copper and iron) connected together to form two junctions—one at the end on the left, and the other at the voltmeter. If the junctions are not at the same temperature, there will be a voltage generated by the thermoelectric or Seebeck effect. This effect has been used for many years to measure temperatures, since the voltage output depends only on the temperatures of the two junctions and on the type of material used.

For measuring purposes, the materials are usually metals and the output voltages run a few millivolts. The possible power output is so small that it would not be practical to use such a system as a battery. However, using semiconductors, the output voltages are hundreds of times larger, and it is quite practical to build semiconductor heat batteries which are really nothing more or less than simple thermocouples. Many such thermocouples can be connected in series or parallel to provide whatever current or voltage is needed.

More work is required to make such thermocouple batteries cheap enough to be practical. However, for the power-starved areas of the world, even expensive batteries are better than none, especially since these thermocouples require no maintenance and no charging. This type of battery, using semiconductors, has been developed in Russia and China to run small transistor radios. The higher temperatures are produced by a kerosene lamp. The thermocouples are mounted on the lamp's chimney to use the heat that would otherwise escape. It is only a matter of time before this type of battery can be made cheap enough to be useful throughout the world.

One more important device using semiconductors and heat is the Peltier refrigerator. The Peltier effect is the direct opposite of the Seebeck effect—instead of getting a voltage generated by a difference in temperature, now we get a difference in temperature caused by a current passing through a junction. The same device that works as a thermoelectric battery will also work as a refrigerator, although not too efficiently.

It is somewhat baffling to understand how passing a current through a junction will cool it, especially when all our experience tells us material heats when current is passed. The two processes, however, are different. With metals, ordinary I^2R heating is much more important. Even with semiconductors, special pains have to be taken to detect the slight cooling that is possible. However, under the right conditions, with enough junctions and the right material, with the current set at just the right level, appreciable cooling is possible. Within a few years you can expect to see electric Peltier refrigerators, home freezers and air conditioners. The advantage is that there is no electric motor, no fluid or piping, nothing to wear out, and no maintenance required.

Other semiconductor devices

One other application for semiconductors should be mentioned because it is surprising that semiconductors should be used at all. We normally think of the transistor and the vacuum tube as competitors in some sense. Yet vacuum tubes use semiconductors in their construction.

Most modern vacuum tubes use an oxide-coated cathode, so the heater can be run at a lower temperature. The oxide used is a semiconductor—and the lower temperature comes from the unusual properties of semiconductors. Here, they allow the electrons to escape more easily.

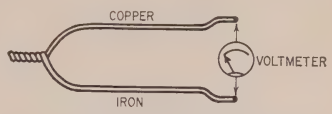

Fig. 9—A basic thermocouple. Its output can be used to indicate temperature or run transistor equipment.

Among the devices used to detect *nuclear radiation* is the crystal counter whose resistance changes sharply when it is hit by a particle from a radioactive material. The action of this type of counter is similar to the action of a photoresistor when a light photon hits it—electron–hole pairs are formed. The material used is a semiconductor, and the electrons and holes formed after each hit are removed quickly. The pulses of current can then be counted, giving us a practical radiation detector.

If this last device is similar to a photoresistor, picture a device that is similar to a photovoltaic cell but uses nuclear radiation to form the electron–hole pairs, instead of light. This device can be used as a battery if a piece of radioactive material is placed near it. This then is a *direct* way to convert nuclear energy into electrical energy. In the future, special semiconductor materials will be used to give us nuclear batteries with very desirable properties.

Of all the devices described here, no one can predict which will become the most important. There is no doubt that the transistor has arrived. But remember it was only 10 years ago that the first crude transistor was made. Enough is now known about semiconductors to make many other devices possible, as outlined in this article. I wonder how many of these will become as commonplace in the *next* 10 years as the transistor is now. END

Simple electronic computer adds, subtracts, divides and multiplies

Mr. Math

Analog Computer

By FORREST H. FRANTZ, SR.

INDUSTRY spends millions of dollars each year for computing instruments to free engineers, technicians and office workers from the labor of doing long computations by hand. Time that was spent doing this work is now used in more creative and productive pursuits.

Can this work for you as a service technician, ham, hi-fi enthusiast or experimenter? Yes, it can! With a modest calculator you can enjoy these benefits on a smaller scale. Mr. Math is just such an instrument. It will help you make accurate calculations for most electronic and electrical problems. Mr. Math opens the door to analog computing for you. You'll find math less laborious and more interesting. Your understanding and ability to use it advantageously will increase as you use Mr. Math.

What Mr. Math can do

What can you expect from Mr. Math in problem ability and accuracy?

Ability: Mr. Math can be used to work problems involving these commonly encountered formulas:

$E = IR$, $I = E/R$, $R = E/I$,
$P = E^2/R$, $P = I^2R$, $e = E_m \sin\theta$,
$e = E_m \cos\theta$, $X_L = 2\pi fL$,
$X_C = 1/(2\pi fC)$, $Z = \sqrt{R^2 + X^2}$,
$\tan\theta = X/R$, $\cos\theta = R/Z$,
$\sin\theta = X/Z$, $X = R \tan\theta$,
$X = Z \sin\theta$, $R = Z \cos\theta$,
$\text{Gain} = E_{out}/E_{in}$,
$\text{Gain} = \mu Z_L/(r_p + Z_L)$, $\mu = g_m r_p$,
$f_o = 1/(2\pi\sqrt{LC})$, and others.

Accuracy: 1% is usually considered adequate for engineering purposes. Mr. Math is accurate within 1% when carefully constructed, calibrated and used for most problems. With average construction, calibration and use, Mr. Math's error will be less than 3%.

Here's how Mr. Math is used:

Problem: You're fixing an old ac–dc radio that has a burned-out series-heater resistor. The total drop across the tubes must be 68 volts at 0.3 ampere. The line voltage is usually 120 in your locality. What should the resistance of the replacement be and how much power will it have to dissipate?

All you do to solve the problem is set four dials to obtain the resistance in ohms and readjust two of them to obtain the power in watts that the resistor will dissipate. Simple, isn't it?

Mr. Math's circuit is simple, but, before you become too involved with it, glance at Fig. 1-a. A battery of voltage E is connected to series resistors R1 and R2. In a series circuit, the current through each resistance is the same and the sum of the voltage drops across the resistances is equal to the battery voltage. Therefore, V2 = I R2. And, if R1 plus R2 equals 1,000 ohms and R2 equals 200 ohms when E is 10 volts, V2 will be 2 volts. Thus, V2/E equals 0.2.

If resistances R1 and R2 of Fig. 1-a are replaced by a potentiometer as shown in Fig. 1-b, voltage V2 may be varied by rotating the pot's shaft. R1 plus R2 is constant and is equal to the potentiometer's total resistance. R2 is equal to the percentage of shaft rotation times total resistance. Total mechanical rotation possible with the potentiometers used in Mr. Math is 300°. But, the metal connector tabs on the ends of the resistance element take up 10° each. Therefore, the electrical rotation is only 280°. So a 28° rotation of the shaft corresponds to a 10% rotation, and V2 will increase by 10% of E. If the potentiometer has a scale with ten 28° divisions, each marked from 0 to 10, and E is 10 volts, a

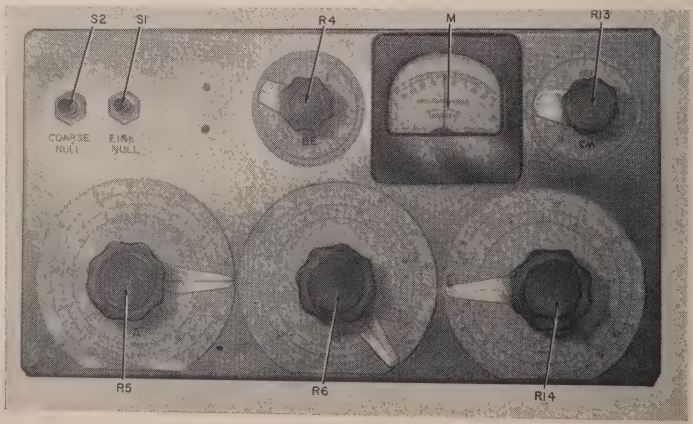

Mr. Math ready for use.

pointer knob on the potentiometer will indicate the magnitude of V2 directly in volts. Thus we've generated the numbers between 0 and 10.

How can we multiply?

With a little thought, you will see that we already know one way to multiply. In Fig. 1-b we multiplied E by numbers between 0 and 1 and, when E equaled 10, generated the numbers between 0 and 10. This was done when the potentiometer input voltage was constant. If we add a second potentiometer with its outer terminals across V2 as shown in Fig. 1-c, we can multiply V2 by another number between 0 and 1. We can calibrate R_{TB} from 0 to 10 if we wish and increase E to 100 volts. Thus, with R_{TB} and R_{TA} set to 10, we have $10 \times 10 = 100$. However, there's no need to let the number 1 equal 1 volt. If we let it equal .01 volt, we can let E equal 1 volt and still graduate the potentiometers from 0 to 10. Thus, for 2×4, V3 equals .08 volt, or 8 units. A voltmeter with the proper

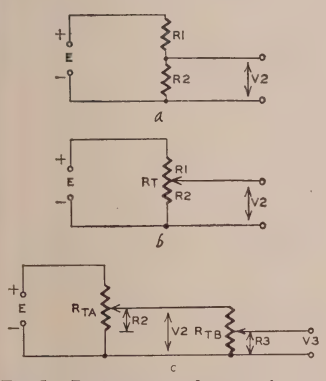

Fig. 1—Basic system of generating numbers and multiplying with cascaded potentiometers.

range could be calibrated to read directly in units from 0 to 10, and the meter range switch could be calibrated in multiples of 10.

To make the multiplication method of Fig. 1-c work properly, R_{TB}'s resistance should be at least 10 times R_{TA} if you want to use linear scales. Even then, there'll be some error (approaching 2% maximum) if you try to use linear scales. Furthermore, to multiply more than two-digit numbers with a string of cascaded pots, you run into the problems of using a large input voltage, a very low resistance for the first potentiometer to get a reasonably low resistance for the last pot and a very-high-sensitivity meter for answer read-out. Another disadvantage is that you cannot divide unless you provide a reciprocal scale (difficult to make and use) and multiply to divide. Thus, 3 divided by 7 would be 3 times 1/7.

But, there's another way to multiply and divide that is also handy for squaring and taking cube roots.

You can multiply by adding, and can

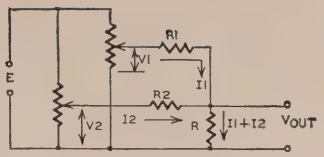

Fig. 2—Electronic adding with a mixing circuit.

divide by subtracting, logarithms. Recalling your high school math, let the letters A and B represent numbers. Then, the *log* of A times B is equal to the *log of A plus the log of B*. And the *log* of A divided by B equals *log A minus log B*. To use these principles in our analog calculator, we need only find a method for adding either voltages or currents.

Let's use a signal mixer

The circuit in Fig. 2 is familiar to most people in electronics. It's a simple signal mixer usually used to mix phono and mike inputs for a single-channel amplifier. The output voltage (V_{out}) is proportional to V1 + V2.

Now, to get back to multiplication and division. Granting that logarithms are to be used for multiplication and division, Mr. Math would have a limited value if we had to resort to log tables. To get around this, we provide the potentiometers with log scales for these tasks. With *log scales and linear scales* we can multiply, divide, add or subtract.

To simplify Mr. Math's design further, a simple bridge circuit is used. In this way, the need for a more expensive output meter is eliminated, and problem answers may be read from a 280° potentiometer scale instead of a 90° meter scale. Furthermore, division and subtraction may be done without reversing the voltages applied to the potentiometers. The multiplication scheme for Fig. 1-c is important though, and it is used in Mr. Math to square and to take square roots. The math principle involved is that *the log of* A squared is equal to *two times the log of A*. Similarly, *the log of the* square root of A is *one half the log of A*.

Mr. Math's circuit

Now let's take a closer look at the circuit (Fig. 3) of this calculator we're going to build. The letters which identify the potentiometers correspond to the front-panel markings on the controls and dials. Pot A (R5) furnishes a voltage output proportional to a dial-number setting as explained in conjunction with Fig. 1-b. Pot B (R6) furnishes a voltage output proportional to a dial-number setting multiplied by the control pot BE (R4) setting of ½, 1 or 2. This circuit is similar to that of Fig. 1-c. The outputs of pots A and B add in the summing network consisting of R7, R8 and R9. This is an application of the circuit of Fig. 2. The voltage representing this sum is introduced to one side of the meter. The sum of the output of pots C (R14) and CM (R13) connects to the other side of the null meter. This summation takes place in the summing network consisting of R10, R11 and R12. The output of pot C is proportional to the number set on the dial. The output of pot CM is proportional to 0, 1 or 2.

The numbers stated are for the linear scales on the dials (see Fig. 4). The calculator equation for meter null with these scales is:

(A) + (BM) (B) = (CM) + (C)

where BM = 0, ½ or 2; CM = 0, 1 or 2 and A, B and C are continuously variable from 0 to 1.00 with dial scale divisions of .02.

This equation provides for adding and subtracting. But Mr. Math computes to only two significant figures. Since addition and subtraction can be performed rapidly with paper and pencil, principal calculator applications are in multiplication and division.

By assuming that the linear scales of pots A, B and C are the logarithms of numbers, new scales can be provided

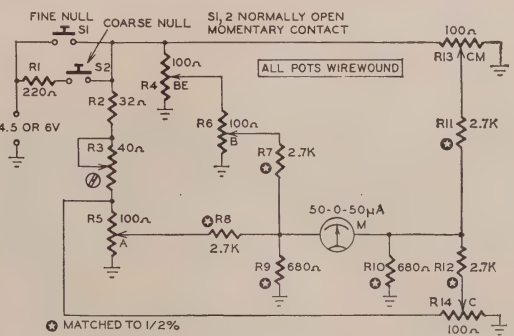

R1—220 ohms
R2—32 ohms
R3—pot, 40 ohms, wirewound, screwdriver adjust (Mallory C40P or equivalent)
R4, 5, 6, 13, 14—pots, 100 ohms, wirewound (Clarostat 58C1-100 or equivalent)
*R7, 8, 11, 12—2,700 ohms, matched to ½%
*R9, 10—680 ohms, matched to ½%
All resistors ½-watt 10% unless noted

**Use 1% resistors if you do not have access to a Wheatstone bridge*
M—50-0-50 μa (Triplett 327-T or equivalent)
S1, 2—spst, normally open, momentary contact type (Cutler-Hammer 8411-K4 or equivalent)
Chassis, 2 x 13 x 7 inches
Knobs
Miscellaneous hardware

Fig. 3—Mr. Math's easy-to-build circuit.

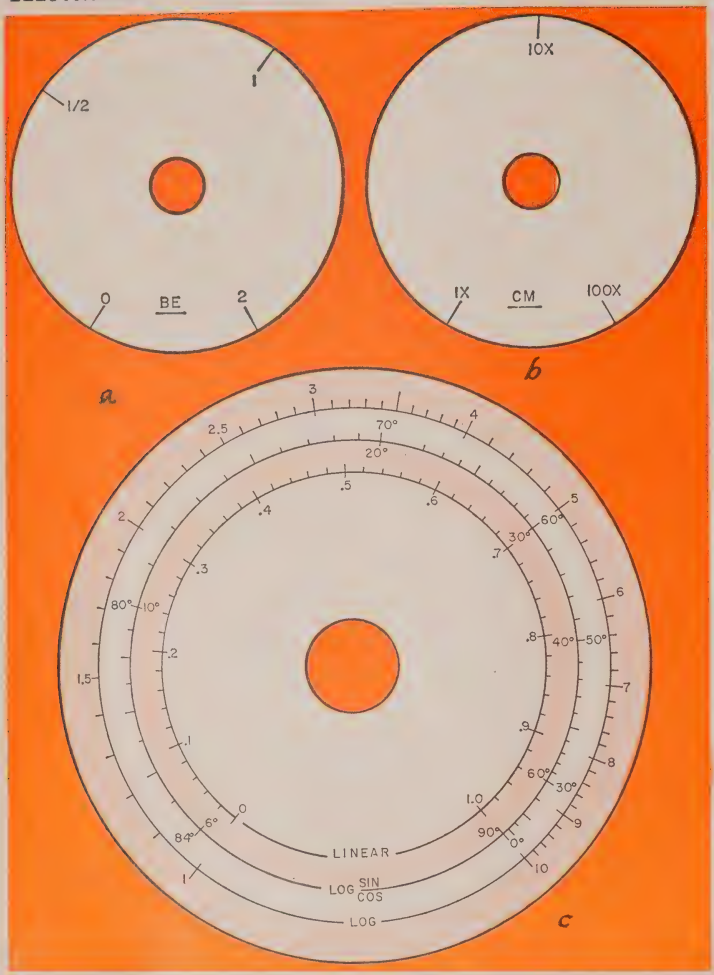

Fig. 4—Calibrated dials for Mr. Math: a and b—The end marks (0, 2, 1X and 100X) are placed at the extremes of the mechanical rotation (300°). In use, these dial settings are not critical. The ½, 1 (on BE) and the 10X (on CM) settings must be accurate. Do not ink in the ½ mark on BE until calibration is completed. c—Linear and log scales are marked off on all three main dials.

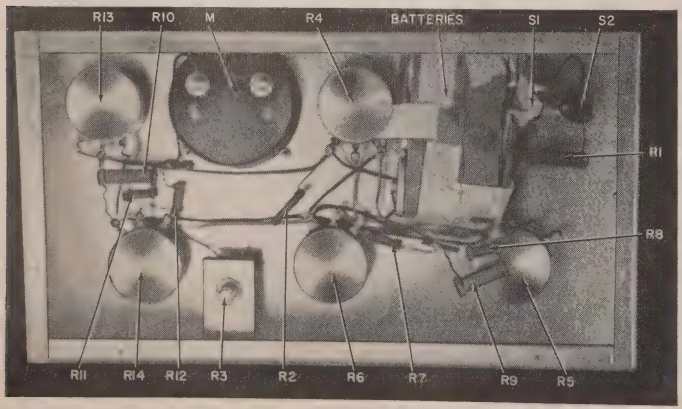

Inside view shows location of parts. I taped the batteries to the case, but a battery holder could be used for a more secure mounting.

which are logarithmically related to the linear scale. Thus, with Mr. Math you can multiply, divide, square and take square roots. These are the most commonly required calculations in electronic work and they're the most time-consuming.

The calculator equation for Mr. Math using the log scales (outer scale in Fig. 4) is:

$$A \times B^{BE} = C \times CM$$

where BE = ½ (for taking the square root of B),
= 1 (if B is not to be squared or its square root taken)
or = 2 (if B is to be squared)
CM = 1, 10 or 100 (to set the decimal point for the number on pot C)

A, B and C are continuously variable from 1 to 10. Trig scales and scales of numbers multiplied by commonly used constants (eg, 2π) may be laid out against the log scales to increase Mr. Math's memory.

The three large dial scales have a 4-inch diameter. These are prepared by first laying out a linear scale with a radius of 1¼ inches. The calibrated portion of the scale covers 280° and principal divisions are spaced 28° apart. The full-scale value is 10 and the 10 principal divisions are numbered from 0.1 to 1.0. After these are laid out, a 1¾-inch radius circle is drawn for the logarithmic scale. The principal points for this scale were laid out using a log table or a slide rule. Remember that the inner linear scale corresponds to logarithms. There is enough space for an additional scale with a radius of 1½ inches on each dial. My calculator has a log 2π scale in this space on the A pot dial, a log tangent–cotangent scale in this space on the B pot dial and a log sine–cosine scale in this space on the C pot. The explanation of these middle scales and their layout is difficult. Unless you've had a good bit of trigonometry, I suggest you wait to lay these out until you've become accustomed to Mr. Math's operation with the inner and outer scales. Mr. Math's scales are somewhat consistent with slide-rule scales. This allows you to use either without confusion if you know how to use a slide rule or learn how to use one in the future.

The calculator draws current from the battery only when the COARSE NULL or the FINE NULL button is depressed. The COARSE NULL switch is depressed first and an approximate null is established. Then the FINE NULL switch is depressed and fine null is established.

Calibrating Mr. Math

A series of adjustments of the pointer knobs and one semifixed pot is used to calibrate your calculator. The technique used is to set in several sample

problems and adjust for the correct answer. You might call it an approximation method. Here's what to do:

1. Index knobs. Proper indexing is set when the hairline overrides the extreme clockwise and counterclockwise index marks by equal amounts.

2. Set controls so that (numbers given for A, B, and C are on linear scales)

A = 0, B = 0.5, C = 1.0,
BE = 2, CM = 1X

Adjust the 40-ohm screw-adjust pot under the panel (R3) for null with the fine-null switch depressed.

3. Set controls so that

A = 0, B = 0.5, C = 0,
BE = 2, CM = 10X

Check the null. If it is poor, adjust CM for null with the fine-null switch depressed. Loosen the knob setscrew on CM and move the knob until the hairline coincides with 10X again. Tighten the knob setscrew. Check to be sure that the null was not disturbed.

4. Set controls so that

A = 0, B = 1.0, BE = 1,
C = 1.0, CM = 1X

Depress the FINE NULL switch. If the null is not exact, turn BE for exact null, loosen the setscrew on BE and adjust the knob till the hairline coincides with 1. Tighten the knob setscrew. Check to be sure that the null was not disturbed.

5. Set controls so that

A = 0, B = 1.0, BE = ½,
C = 0.5, CM = 1X

Depress the FINE NULL switch. If null is not exact, adjust BE for exact null and place a new graduation line for ½ on BE.

The dial indexing and calibration should be rechecked if error greater than 3% is noted on any calculation.

To use Mr. Math

The calculator is used as follows:

1. To add two numbers (3.5 + 4.5, for example) use linear scales.
   - **a.** set A at 0.35.
   - **b.** set B at 0.45.
   - **c.** set BE at 1.
   - **d.** set CM at 1X.
   - **e.** adjust C for meter null, read answer on C. C nulls at 0.80. (The answer is 0.80 × 10. The multiple is used since the numbers were divided for entry.)

   NOTE: If the sum of the numbers is greater than 10, set CM to 10X. The answer is 10 plus the number at which C nulls. Thus to add 7.2 and 8.7:
   - **a.** set A at 0.72.
   - **b.** set B at 0.87.
   - **c.** set BE at 1.
   - **d.** set CM at 10X.
   - **e.** set C for meter null, read answer on C. C nulls at 0.59. [The answer is 10 × (1 + 0.59) or 15.9.]
2. To subtract two numbers (8.3 — 4.1, for example) use linear scales.
   - **a.** set B to 0.41 (number to be subtracted).
   - **b.** set C to 0.83 (number to be decreased).
   - **c.** set BE to 1.
   - **d.** set CM to 1X.
   - **e.** adjust A for null. A nulls at 0.42 (The answer is 10 × 0.42, or 4.2.)
3. To multiply two numbers (3.9 × 7.1) use log scales.
   - **a.** set A at 3.9.
   - **b.** set B at 7.1.
   - **c.** set BE at 1.
   - **d.** set CM at 1X.
   - **e.** attempt to adjust C for null. If null is not possible, set CM to 10X and adjust C for null. C nulls at 2.77. (The answer is 10 × 2.77, or 27.7.)
4. To divide one number into another (26/3.1, for example) use log scales.
   - **a.** set C to 2.6.
   - **b.** set CM to 10X.
   - **c.** set BE at 1.
   - **d.** adjust A for null, and read answer on A. A nulls at 8.4. (This is the answer.)
5. To square a number (7.9^2, for example) use log scales.
   - **a.** set B at 7.9.
   - **b.** set BE at 2.
   - **c.** set A at 1 on log scale.
   - **d.** set CM at 1X and adjust C for null.
   - **e.** If no null can be obtained, set CM to X10 and adjust C for null.
   - **f.** C nulls at 6.22 with CM at 10X. (the answer is 6.22 × 10, or 62.)
6. To take the square root of a number (8) use log scales.
   - **a.** set B at 8.
   - **b.** If number has odd number of places, set A at 1. If number has an even number of decimal places, set A at 3.16. Set A at 1.
   - **c.** set BE at ½.
   - **d.** set CM at 1X.
   - **e.** adjust C for null. C nulls at 2.8. (This is the answer.)

Since the computer may have an error of 1 or 2%, answers should be read out to only two significant figures. Thus, 27.7 should be read as 28, 272 as 270.

Since the A, B and C log scales are scaled from 1 to 10, multipliers of 10, 100, etc. are used to represent numbers greater than 10. Thus to multiply 71 × 832, the dial settings of A and B are the same as for 7.1 × 8.32, and the result from CM and C is multiplied by 10, 100 or 1,000 to get the final answer.

The trigonometric scales (which I suggested you add later) are actually 10 times the respective functions which they represent. This requires the use of a scaling factor in the answer. Thus 5 tan 45° gives the result 50 on C and CM. This result must be divided by 10 to obtain the correct answer.

To get most accurate results from your construction work:

a. Match R7, R8, R11, and R12 within ±½% with a Wheatstone bridge.

b. Match R9 and R10 within ±½%.

c. Use the potentiometers specified; others may not possess the linearity required.

d. Prepare dial scales accurately. Be sure knob pointers fit close to scale to prevent parallax errors.

e. Calibrate carefully according to the procedure outlined.

f. Set numbers into the calculator accurately when working problems.

Happy calculating! END

NEXT MONTH

Horizontal Ringing Troubles

What to do when those vertical bars show up on the screen

Electronic Boat Horn

This useful device works as a low-power loud-hailer as well as a horn

Improving the Small Receiver

There are still more radios that TV's. Here are a few useful service hints

The JULY issue of Radio-Electronics

on sale June 24 Reserve your copy now

NEWS from the IRE 1958 meet

55,000 electronic engineers gather to discuss another year of progress

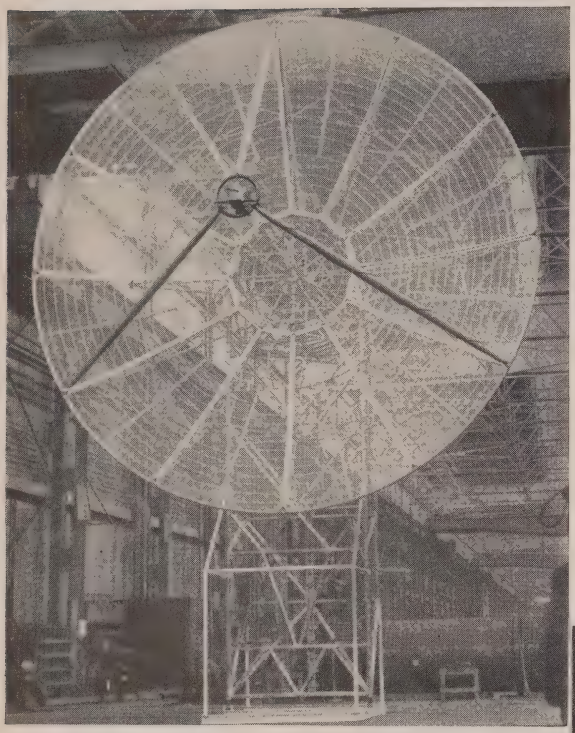

This mobile antenna stands almost three stories high—its radiation center is 24 feet above the ground.

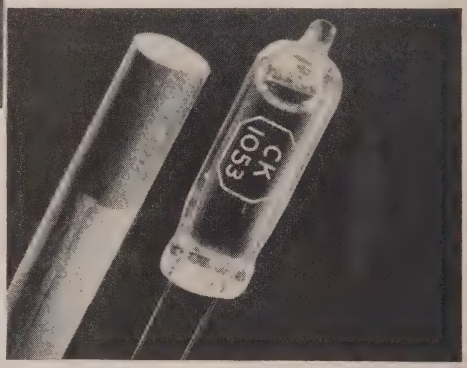

The Raytheon operating-time indicator tube.

By ERIC LESLIE

THE year's most striking example of how fast yesterday's wonders become commonplace was probably the 1958 convention of the Institute of Radio Engineers, held in New York City the third week of March. The engineers not many years ago had thrilled to the news that a radar message had been returned from the moon—now they talked calmly about shooting a manned rocket around it. Medical electronics was married to computer technology, and the old concept of gas tubes was expanded out of recognition. (Engineers talked of a plasma of electrons and ions at a temperature of 100 million degrees, carrying currents several times as great as could an equivalent bulk of copper, and held in an envelope consisting of a magnetic field that would constrict the plasma on itself.)

A complete session was in fact devoted to thermonuclear power. Another, a panel, was entitled Electronics in Space. A more mundane subject that would have been equally surprising to the old engineer was engineering education. Two sessions were devoted to that subject, and another to a related one, engineering writing and speech. Devices that would read books and papers, then prepare engineering abstracts from them, were described, as well as an electronic Russian translater.

Another complete session was devoted to masers (microwave gas or semiconductor amplifiers) and atomic

clocks. One of these—a gas-cell clock described by Federal Telephone engineers—was visualized as "necessary equipment on any rocket ship."

Luminescent panels for flat-tube television were discussed by Sylvania engineers, who pointed out avenues of research in that direction and reported on progress in producing moving pictures on such panels, but concluded that "major breakthroughs" would be needed before luminescent panels could be used as TV screens.

The field of sound

Audio was possibly the livest subject at the convention. One complete session was devoted to stereophonic disc recordings, and another to audio, amplifier and receiver developments. It was at that session that Dr. Peter Goldmark presented his surprise paper on the CBS compatible stereo-disc system.

It resembles the Westrex 45/45 system in general (Dr. Goldmark suggested that the 45/45 might be considered a special case of the CBS technique), but avoids some of the disadvantages of that system by putting most of the program into the lateral signal fed to the cutter. Only a few percent of the total signal remains for the vertical component. The record can be played back perfectly (as a monaural recording) with an ordinary long-play cartridge. As a stereo disc it can be played with any 45/45 setup, or even with a vertical–lateral cartridge. This last feature caused Goldmark to describe it as "compatible even with the incompatible!" Wear—either with a stereo or long-play pickup—was stated to be the same as with a regular long-play record.

[Stereo developments at the convention were sufficiently important to justify a complete article. This is being prepared by Mr. Norman H. Crowhurst, and will probably appear in an early issue.]

Computers and therapeutics

Biology was one of the important subjects. One session was devoted to medical electronics and one to biological transducers.

Top item on the medical–biological program was an infra-red spectrometer–computer for analyzing complex biochemical mixtures such as hormones. The instrument, developed by International Telephone & Telegraph Corp., is expected to be of great value in cancer research. In analyzing by chemical methods, one constituent is identified and removed from the compound, then the process is repeated for another—a time-consuming and laborious process. The new method, explained president Henri Busignies of Federal Telecommunications Labs (research division of IT&T), is to treat the absorption spectrum of the compound as a signal and to use the communications man's long experience with mixing and unmixing signals to discover not only the components of the compound but also their relative quantities.

A pressure transducer, working on the strain-gauge principle, that can take measurements of blood pressure inside the human heart, at the same time bringing back blood samples from the heart's interior, was discussed by electronics researchers of the Ford Motor Co. laboratory.

Another paper described the use of a Nipkow disc in making biological microphotographic measurements, and still another covered the electronic evaluation of the condition of the unborn fetus.

An electronic postoffice

Experiments in electronic mail sorting had been started before last year's convention. This year a whole session was devoted to the method being tried at Ottawa, Canada. Each letter is readdressed by an operator, the new address being put on the back of the envelope in fluorescent ink. A simple code, easily learned by unskilled labor, is used. From this point, the various sortings for province, city and street address or carrier's route are entirely electronic.

An almost opposite system, which handles preliminary sorts only, is undergoing experiment at Washington, D. C. Letters fed to the electronic machine are sorted by states—and a few cities. The apparatus reads typewritten addresses in various sizes of type, but cannot as yet read handwritten addresses nor those written in all capitals.

Broadcast techniques

A new concept in the broadcasting field was presented by Leonard Kahn, developer of a compatible single-sideband AM transmission system. Described a year ago in the *Proceedings of the IRE*, the system has been tried out by several stations, including New York's WMGM and WABC. One sideband is greatly reduced in power without making special receiving techniques necessary, as in conventional types of single-sideband transmission. The reception in fringe areas is improved, since more power is concentrated in the single sideband, and fading—often due to interactions between the two sidebands—is not so marked. Interference can be reduced because of the smaller bandwidth of the single-channel signal.

Multiplex transmission received a couple of papers. Color TV was represented by a few scattered papers at different sessions.

The IRE show

The exhibition which is so impressive a part of the annual meetings was on a highly practical level, following last year's pattern of accenting improvements on existing practice rather than strange new equipment. One old-timer was heard to murmur that he could remember when the bulk of the exhibits had to do with entertainment electronics—broadcasting and receiving equipment—but that now it had become practically a pure military–industrial setup. A number of striking things did however appear among the 17,000-odd pieces of equipment exhibited.

One of these was an elapsed-time tube exhibited by Raytheon. It looked like a miniature tube envelope with two terminals, filled with a bluish liquid. This liquid, a copper sulphate solution, gradually clears up as current passes through it, till—at the end of 20,000 microampere hours—it is entirely clear. If one wishes to find out how long a piece of equipment has been in operation while the tube still shows considerable color, a colorimeter indicates the number of microampere hours rather accurately. The device—if it reaches the popular market—should have a number of interesting applications. The high-fidelity enthusiast would be particularly interested. He could hook up one of these tubes in a circuit drawing 20 μa dc, and at the end of 1,000 hours the clear liquid in the tube would tell him it was time to replace the diamond stylus.

A battery-operated TV set was another interesting exhibit. The battery consisted of 10 Yardney Silvercells and a solid-state converter manufactured by Interelectronics Corp. Viewers were informed that it would operate the set up to 6 hours and could be recharged overnight (at a low charging rate).

Inertial guidance systems were displayed by a number of exhibitors. Inertial guidance is a method of locating one's position on the globe by starting from a fixed known point with equipment that tells how far and in what direction one moves. It consists of a "stable table" that maintains its position with relation to the earth and to any change in the position of the vehicle carrying it. Three gyroscopes, one in each direction of motion, give it that stability. Accelerometers take note of any acceleration in any of these directions, and electronic devices record their output in terms of direction and distance. It is a system which might be called super dead reckoning, and can be used—for example—by a submarine traveling under Arctic ice, to indicate its position accurately.

A number of other displays were impressive in themselves, but revealed no startling advances in electronics. One, a portable antenna, brought back to the minds of old-timers the early days of portable radios, some of which were said to be best transportable by Mack truck. The antenna, exhibited by Kennedy Corp., was a parabola 28 feet across. It looked substantial enough for any permanent job, but two rubber-tired wheels were visible part way up the tower, and the whole job could be demounted and towed by a pickup truck. Probably it is the biggest piece of portable electronic equipment that is in existence. END

what's new?

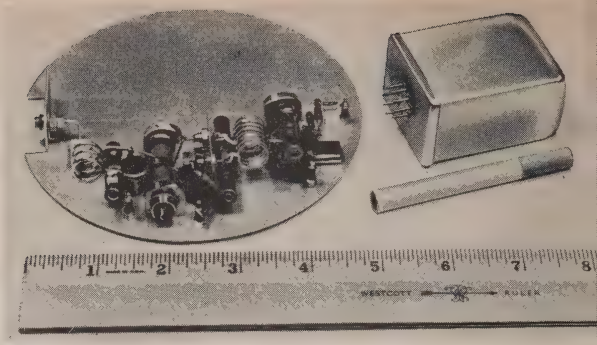

SATELLITE TRANSMITTER with 500-mw output is smaller than a pack of cigarettes. It weighs less than 3 ounces and takes up less than 6 cubic inches of space. Operating at 108 mc, the crystal-controlled transmitter uses three transistors. The unit, which operates 1¼ to 4 times as long as existing transmitters, was constructed by engineers of the DuKane Corp., St. Charles, Ill., under contract to the Naval Research Laboratories.

ULTRASONICS CLEANS DISHES in this dishwasher. The noiseless machine thoroughly cleans dishes, pots and pans in seconds with sound waves pitched too high for the human ear to detect. The prototype model shown in the photo was manufactured by Acoustica Associates, Inc., Culver City, Calif., and may be commercially available before the end of the year.

GERMANIUM RESISTANCE THERMOMETER for measuring temperatures near absolute zero is dwarfed by a common pin. The heart of the unit is a tiny bridge of arsenic-doped germanium. The doped germanium presents a variable resistance to currents flowing through it. Temperature is measured by determining the potential drop when a small known current (approximately 10 μa) is passed through the bridge. Developed at Bell Telephone Labs, the unit may be useful for accurately measuring temperatures in outer space, when mounted in a suitable carrier.

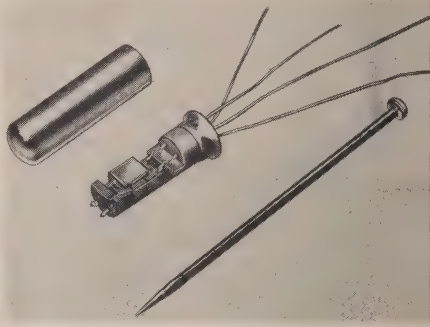

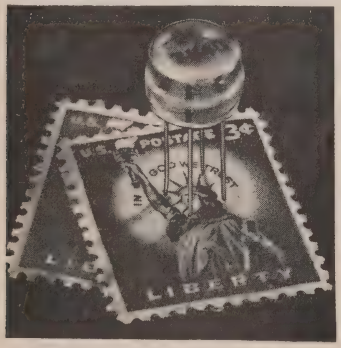

GLASS TRANSISTOR HOUSING developed by G-E is the first in glass to meet the JETEC-recommended standard for low-power transistors. Eventually, mass-produced glass transistors may be much cheaper than those with metal cases.

FIVE-STAGE MODULAR RADIO RECEIVER little bigger than an ordinary paper clip illustrates a new miniaturization technique. Using micro-modules (see photo insert), employing transistors and greatly reduced wiring, a typical missile guidance unit's size and weight could be reduced 90% or more. Developed by RCA, now under 2-year contract to the Army Signal Corps, the final aim of the project is to bring micro-module construction to the point where the weight of a 30-pound airborne radio system could be reduced to about 4 pounds.

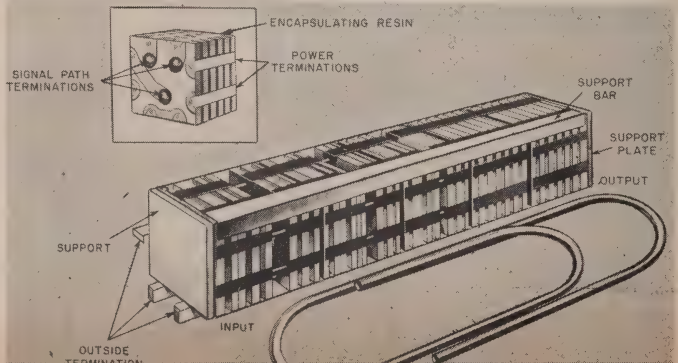

TRANSISTORS In The TV SET

Part II—*We complete our survey of the transistor TV receiver with a trip through the audio if, audio amplifier, audio output, sync separator, high voltage, and horizontal and vertical sweep circuits*

By LOUIS E. GARNER, JR.

LAST month we examined the early stages of the transistor TV receiver. We discussed the front end, video if strip, video detector and video amplifiers. Now we will continue our first detailed look at an all-transistor TV set.

Audio if amplifier

A transistor TV receiver's audio if strip will probably consist of one or two stages, with the final stage driving a standard FM detector circuit modified to use semiconductor diodes in place of vacuum tubes. A deluxe receiver might use a three- or four-stage audio if amplifier, with the last stage or two serving as limiters, followed by a conventional discriminator type FM detector.

A two-stage 4.5-mc audio if amplifier and ratio detector circuit is shown in Fig. 5. Transistors V10 and V11 serve as common-emitter amplifiers. Rf transistors would be used in these stages, with suitable units including surface-barrier rf triodes, tetrodes and drift types. We have assumed the use of p-n-p rf transistors here.

The 4.5-mc signal obtained from the video amplifier is link-coupled to if transformer T10. A tap is provided on this unit's secondary winding to insure a good impedance match to V10's input circuit. Base bias current for the first stage is supplied by voltage divider R39–R40, bypassed by C31. Emitter resistor R41, bypassed by C32, establishes a small reverse bias for stage stabilization. R42 and C33 form a decoupling filter in V10's collector circuit.

Transformer T11 has a tuned primary winding and an untuned stepdown secondary. The primary–secondary turns ratio is chosen to provide a good impedance match to V11's base input circuit. A tap is provided on the transformer's primary to provide an optimum compromise between circuit Q and stage gain.

V11's base bias is furnished by voltage divider R43–R44, bypassed by C34. Unbypassed emitter resistor R45 introduces a small amount of degeneration to improve circuit stabilization. R46 and C35 form a decoupling filter.

The amplified audio if signal developed across transformer T12's primary is coupled to its center-tapped secondary and to coil L13. From here, the signal is applied to an FM detector which abstracts the audio modulation from the FM if carrier. The FM detector used in Fig. 5 is a modified ratio detector, with the customary vacuum-tube diodes replaced by semiconductor diodes D1 and D2, shunted by resistors R47 and R48. C36 serves as the if bypass and C37 as the dc stabilizing capacitor. The audio output signal is obtained through filter R49–C39.

Audio amplifier

The audio signal obtained from the ratio detector is next fed to audio amplifier and output stages very similar to those used in present-day transistor radios. Standard audio transistors would be used in these circuits. However, chances are that the output stage will supply more power than a portable radio. To conserve operating power, the output stage may be operated as a class-AB or class-B push-pull amplifier, with medium-power transistors in portable sets and large multi-watt transistors in receivers intended

(*Continued on page* 76)

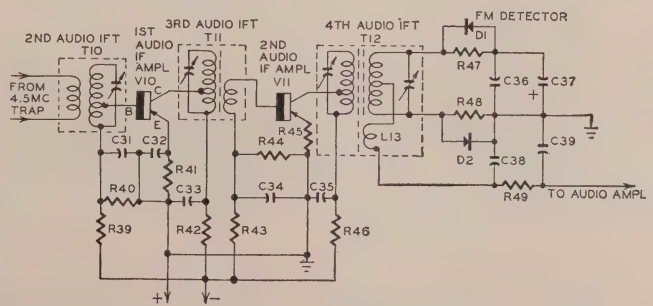

Fig. 5—The audio if strip. Two if amplifiers, and two diodes for FM detection are used.

"HEATHKITS®

gave me my start and I'm still sold!"

"... they are my lowest cost way to real quality and dependability in electronic equipment of any kind ...

... The clean, modern styling of HEATHKITS make me proud to own them. They make a handsome and useful addition to my workshop.

... Rigid quality standards of components used in HEATHKITS assure me of performance equal to or surpassing instruments costing many times more.

... after assembling a HEATHKIT myself, I know what "makes it tick"... I know that the thoughtful circuitry design and name-brand components used throughout guarantee me years of trouble-free service.

... HEATHKITS cost me half as much as ordinary equipment ... and I get so much more. In assembling my own instruments I am sure of the quality that goes into them. Plus the complete assembly and operating instructions as well as detailed schematics that are at my fingertips for future reference."

NEW: Stereophonic Sound for your home with the new HEATHKIT STEREO CENTER. This, and other exciting new high fidelity developments are now available from the world's largest maker of "do-it-yourself" electronic kits.

NEW: For the Ham Radio fans—an all new Ham Transmitter and companion Receiver—featuring all the latest developments in Ham communication—including single-sideband operation.

NEW: A competely up-to-date Oscilloscope answering the long felt needs of electronic engineers and servicemen everywhere.

NEW: A host of newly developed marine instruments for the safety and convenience of the boat owner.

HEATHKIT

HEATH COMPANY Benton Harbor 20, Michigan

a subsidiary of Daystrom, Inc.

The HEATH TIME PAYMENT PLAN allows you to outfit your whole workshop at one time with needed test instruments while you pay in easy monthly installments.

HEATHKIT

PROFESSIONAL OSCILLOSCOPE KIT

An exciting development in the Heathkit test instrument line is the introduction of the Heathkit model OP-1 Professional Oscilloscope. Emphasizing complete flexibility in any application, the OP-1 features DC coupled amplifiers and also DC coupled CRT tube un-blanking. The triggered sweep circuit will operate on either internal or external signals and may be either AC or DC coupled. The polarity of the triggering signal may also be selected, and any point on the wave form may be selected for the start of the sweep by using the "triggering level" control. An automatic position is also provided, in which the sweep recurs at a 50 cycle rate, but can be driven over a wide range of frequencies with no additional adjustments. The sweep frequencies are provided by switch-selected base rates of 2 and .2 milliseconds/CM, and 20, 2, and 1 microseconds/CM, in conjunction with a continuously variable 10 to 1 multiplier. Sweep frequencies are calibrated to within 10% at all control settings, and the sweep frequency may be reduced by adding capacity to the "ext. cap" binding post on the front panel. A 5ADP2 flat face CR tube is used for accurate readings on an edge lighted grid screen. A high quality conetic-fernetic CR tube shield prevents stray AC fields from distorting trace. A 12-position vertical attenuator is calibrated in volts-per-CM and the horizontal sweep is calibrated in time-per-CM. Prewired terminal boards are used for rapid, easy assembly of all critical circuits. Simply install and connect the color coded leads. Power supply is transformer operated utilizing silicon diode rectifiers and is fused for protection. Under development for over a year the OP-1 promises outstanding results in any application requiring the use of an oscilloscope.

HEATHKIT OP-1 **$179.95**

Here's the scope you've been waiting for!

AVAILABLE AFTER JUNE 15

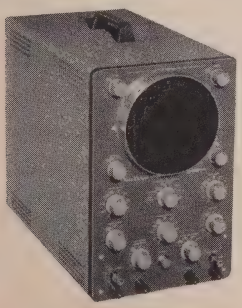

Laboratory Performance At Less Than Utility Scope Price

HEATHKIT O-12 **$64.95**

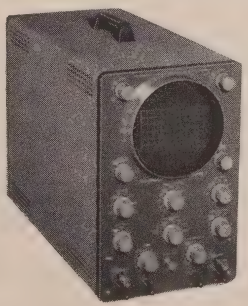

A Scope You Will Be Proud To Own

HEATHKIT OM-3 **$39.95**

"EXTRA DUTY" 5" OSCILLOSCOPE KIT

Top quality features at half the cost of ordinary equipment sum up the advantages of this popular kit. Critical observations in your laboratory or shop are handled easily, with clear, sharp pattern displays in every application. Vertical frequency response extends from 3 CPS to 5 mc +1.5 db —5 db without extra switching. Response is down only 2.2 db at 3.58 mc. The Heath patented sweep circuit functions effectively from 10 CPS to better than 500 kc in five steps, giving you 5 times the usual sweep obtained in other scopes. An automatic sync circuit with self-limiting cathode follower provides excellent linearity and lock-in characteristics. Extremely short retrace time and efficient blanking action. Both vertical and horizontal output amplifiers are push-pull and the scope incorporates a 1 V peak-to-peak calibrating source, step attenuated and frequency compensated vertical input, plastic molded capacitors and top quality parts throughout. The 11-tube circuit features a 5UP1 cathode ray tube, and provision is made for Z-axis input for intensity modulation of the beam. Frequency response of the horizontal amplifier is within ±1 db from 1 CPS to 200 kc. Horizontal sensitivity is 0.3 volts RMS per inch. Construction is simplified through the use of two metal circuit boards and precut, cable wiring harness. Shpg. Wt. 22 lbs.

GENERAL PURPOSE 5" OSCILLOSCOPE KIT

For servicing and routine laboratory work this fine kit is a favorite with technicians throughout the country. It incorporates many extras not expected at this low price. Features wide vertical amplifier frequency response, extended sweep generator operation, and improved stability. Frequency response of the vertical amplifier is within ± 3 db from 4 CPS to 1.2 mc. Vertical sensitivity is .09 volts RMS per inch at 1 kc. Sweep generator functions reliably from 20 CPS to over 150 kc. A modern etched circuit board is featured for high stability and reduces assembly time considerably. Standard components are mounted on this board with each position clearly marked preventing wiring errors. Both vertical and horizontal amplifiers are push-pull types. Uses a 5BP1 CRT. Provision for external or internal sweep or sync, built in 1 V peak-to-peak reference voltage and calibrated grid screen. An adjustable "spot shape" control is provided to insure a sharp trace. Input to the vertical amplifiers is through a step attenuated, frequency compensated circuit. The OM-3 is an extremely versatile instrument and has a multitude of practical uses in electronic testing fields. Particularly useful in alignment of television receivers, for testing audio amplifiers and circuits, and checking the quality of modulated RF signals in Ham Radio transmitters. Shpg. Wt. 22 lbs.

Equip Your Service Bench...

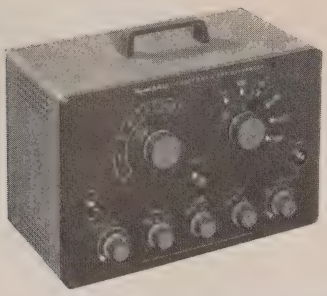

HEATHKIT CD-1 **$59.95**

Cash In Now On Color TV

★ 10 VERTICAL COLOR BARS
★ CRYSTAL CONTROLLED ACCURACY
★ CHOICE OF 6 DIFFERENT PATTERNS

COLOR BAR AND DOT GENERATOR KIT

Colored television is now a reality and as the number of these sets increase the need for a reliable service instrument is apparent. Nothing on the market . . . in this type of generator has as many features as the CD-1 at such a tremendous price saving. This unit combines two basic color service instruments, a color bar generator, and white dot generator in one versatile portable unit which has crystal controlled accuracy and stability for steady locked-in patterns (requires no external sync leads). Color receivers converged with the CD-1 will still be converged properly on a television program from the station. The 13-tube circuit has been carefully laid out for ease of assembly and provides choice of six different patterns. Produces white-dots, cross hatch, horizontal and vertical bars, ten vertical color bars, and a new shading bar pattern for screen and background adjustments. Variable RF output on any channel from 2 to 6. Positive or negative video output, variable from 0 to 10 volts peak-to-peak. Crystal controlled sound carrier with off-on switch. Voltage regulated power supply uses long-life silicon rectifiers. Kit includes three crystals and test lead, plus an information packed instruction manual covering convergence, and screen and background adjustments of a color TV set. Compare with other generators on the market and you will see that this instrument is loaded with extras and top quality all the way through. Shpg. Wt. 13 lbs.

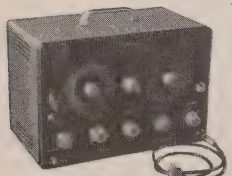

HEATHKIT TS-4A **$49.50**

For fast, easy alignment of TV sets

HEATHKIT AG-10 **$49.95**

Sine and square waves for countless uses

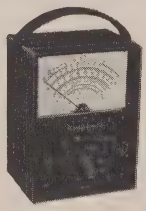

HEATHKIT MM-1 **$29.95**

High accuracy in a portable meter

HEATHKIT M-1 **$17.95**

An all-round meter of many uses

TV ALIGNMENT GENERATOR KIT

This generator has many special design features for flexible, easy operation and reliability. The all-electronic sweep circuit insures stability and covers 3.6 mc to 220 mc in four bands. Sweep deviation is controllable from 0 to 42 mc. Crystal and variable marker oscillators are built in. Crystal (included with kit) provides output at 4.5 mc and multiples thereof. Variable marker provides output from 19 to 60 mc on fundamentals and from 57 to 180 mc on harmonics. Effective two-way blanking and phasing control also provided. A truly outstanding number of features at a tremendous price saving. Shpg. Wt. 16 lbs.

SINE-SQUARE GENERATOR KIT

High quality sine and square waves are produced by this generator over a wide range. Frequency response is ±1.5 db from 20 CPS to 1 mc on both sine and square waves, with less than .25% sine wave distortion, 20 to 20,000 CPS. Output impedance is 600 ohms on sine wave and 50 ohms on square wave (except on 10 volt range). Square wave rise time less than .15 microseconds. Five-position bandswitch—continuously variable tuning—shielded oscillator circuit—separate step and variable output attenuators in ranges of 10, 1 and .1 volts with extra range of .01 volt on sine wave. Shpg. Wt. 12 lbs.

20,000 OHMS/VOLT VOM KIT

This meter is ideal for use in field applications where accuracy is important. Employs a 50 ua 4½" meter, and features 1% precision multiplier resistors for high accuracy. Requires no external power for operation (batteries supplied). Sensitivity is 20,000 ohms-per-volt DC and 5,000 ohms-per-volt AC. Measuring ranges are 0-1.5, 5, 50, 150, 500, 1500 and 5,000 volts AC and DC. Measures direct current in ranges of 0-150 ua, 15 ma, 150 ma, 500 ma and 15 a. Resistance multipliers are x 1, x 100 and x 10,000 Covers -10 db to +65 db. Batteries and test leads are also included with this kit. Shpg. Wt. 6 lbs.

HANDITESTER KIT

Small enough to carry with you wherever you go, this fine handitester is ideal for use in portable applications when making tests away from the work bench or as an "extra" meter in the service shop, when the main instruments are occupied. The combination function-range switch simplifies operation. Measures AC or DC voltage from 0-10, 30, 300, 1000 and 5000 volts. Direct current ranges are 0-10 ma and 0-100 ma. Ohmmeter ranges are 0-3000 and 0-300,000. Top quality precision components employed throughout. Very popular with home experimenters and electricians. Shpg. Wt. 3 lbs.

with Low-Cost Dependable Heathkits

HEATHKIT

ETCHED CIRCUIT VTVM KIT

The fact that this instrument is outselling all other VTVM's says a great deal about its accuracy, reliability, and overall quality. The precision and quality of the components used in this VTVM cannot be duplicated at this price through any other source. Its attractive appearance as well as its performance will make you proud to own it. A large 4½" panel meter is used for indication, with clear, sharp calibrations for all ranges. Front panel controls consist of a rotary function switch and a rotary range selector switch, zero-adjust and ohms-adjust controls. Precision 1% resistors are used in the voltage divider circuit. An etched circuit board is employed for most of the circuitry, cutting assembly time and eliminating the possibility of wiring errors. It also assures duplication of laboratory instrument performance. This multi-function VTVM will measure AC voltage (RMS), AC voltage (peak-to-peak), DC voltage and resistance. There are 7 AC (RMS) and DC voltage ranges of 1.5, 5, 15, 50, 150, 500 and 1500. In addition there are 7 peak-to-peak AC ranges of 0-4, 14, 40, 140, 400, 1400 and 4,000. Seven ohmmeter ranges providing multiplying factors of x 1, x 10, x 100, x 1000, x 10 k, x 100 k and x 1 megohm. Center scale resistance readings are 10, 100, 1000, 10 k, 100 k ohms, 1 megohm and 10 megohms. A zero-center scale db range is also provided. Battery and test leads included with kit. Shpg. Wt. 7 lbs.

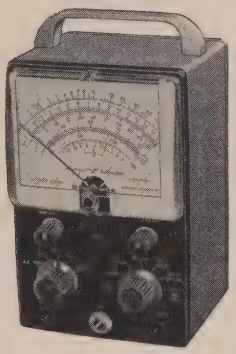

HEATHKIT V-7A **$24.50**

World's largest selling VTVM kit

★ LARGE EASY-TO-READ 4½" 200 UA METER
★ 1% PRECISION RESISTORS EMPLOYED FOR HIGH ACCURACY

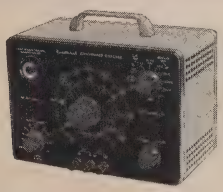

HEATHKIT C-3 **$19.50**

Checks all types of condensers accurately

HEATHKIT T-4 **$19.95**

Locate faults quickly by tracing signals

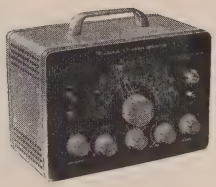

HEATHKIT SG-8 **$19.50**

Easy-to-build—prewound and calibrated coils

CONDENSER CHECKER KIT

Check unknown condenser and resistor values quickly and accurately. Capacity measurements are made in four ranges of .00001 mfd-.005 mfd; .001 mfd-.5 mfd; .1 mfd-50 mfd; 20 mfd-1,000 mfd. Checks paper, mica, ceramic, and electrolytic condensers. Leakage test provides switch selection of five polarizing voltages, 25 volts to 450 volts DC to indicate condenser operating quality under actual load conditions. Electron beam "eye" tube indicates balance and leakage. A spring return test switch automatically discharges condenser under test and eliminates shock hazard to the operator. Measures resistance from 100 ohms to 5 megohms in two ranges. Shpg. Wt. 7 lbs.

VISUAL-AURAL SIGNAL TRACER KIT

Here is a brand new signal tracer completely redesigned with compact dimensions and new circuit layout. Features built-in speaker and electron beam "eye" tube for signal indication and a unique noise locator circuit. Ideal for use in AM, FM and TV circuit investigation. RF and audio inputs are provided in one convenient probe with switch on probe to select either input. Useful for checking microphones, phono cartridges, record changers, tuners, etc. Makes a handy substitution speaker for servicing TV sets at the shop. Transformer operated for safety and high efficiency. Complete with test leads and informative construction manual. Shpg. Wt. 6 lbs.

RF SIGNAL GENERATOR KIT

Save valuable time in aligning RF tuned circuits of all kinds with this easy-to-use kit. Also a quick way to trace signals in faulty RF, IF and audio circuits. Designed for general service applications-the SG-8 covers 160 kc to 110 mc on fundamentals in five bands, and from 110 mc to 220 mc on calibrated harmonics. The entire oscillator circuit is built on a special sub-chassis, using prewound and calibrated coils. No further calibration is required so it is ready to use as soon as construction is completed. RF output is in excess of 100,000 microvolts, controlled by both step and continuously variable controls. Complete with output cable and instructions. Shpg. Wt. 8 lbs.

HEATH COMPANY • a subsidiary of Daystrom, Inc. • **Benton Harbor 20, Mich.**

Enjoy Rich 3 Dimension Sound...

Beautifully Styled with Plenty of Room for the Most Complete Stereo System

AVAILABLE IN THE FOLLOWING MODELS:
Model SE-1B—Stereo Equipment Cabinet (birch)
Model SE-1M—Stereo Equipment Cabinet (mahogany)
Model SC-1BR—Stereo Wing Speaker Enclosure (birch—right end)
Model SC-1BL—Stereo Wing Speaker Enclosure (birch—left end)
Model SC-1MR—Stereo Wing Speaker Enclosure (mahogany—right end)
Model SC-1ML—Stereo Wing Speaker Enclosure (mahogany—left end)

HEATHKIT
SE-1
PRICE TO BE ANNOUNCED

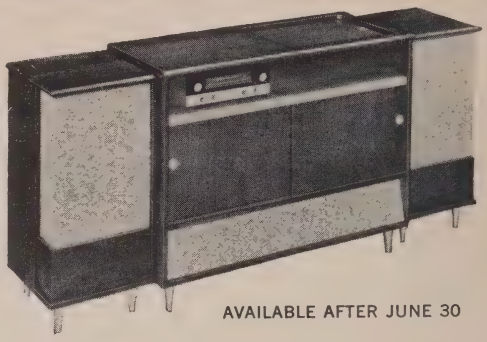

AVAILABLE AFTER JUNE 30

STEREO EQUIPMENT CABINET KIT

Imagine! . . . Stereophonic sound in your own home. This superbly designed cabinet holds all of your hi-fi stereo equipment and lends striking elegance to your living room. The attractive gold and black panels, trim and hardware brilliantly highlight the overall effect. Rich toned grille cloth, flecked in gold and black, complement the cabinet. The unit has ample room provided for an AM-FM tuner, tape deck, stereo preamplifier, amplifiers, record changer, record storage and speakers. Beautifully grained ¾" solid core Philippine mahogany or select birch plywood is used for construction. The top features a shaped edge and sliding top panel for easy access to the stereo tape deck and stereo preamplifier. Sliding doors are employed for convenient front access to the changer and record storage compartment. All parts of the cabinet are precut and predrilled for simple assembly. The speaker wings and center cabinet may be purchased separately if desired. Note: the kit is delivered equipped with panels precut to accommodate Heathkit components and also blank panels to cut out for your own equipment. Measurements of the individual component areas follow: tape deck and preamplifier area 20¾" L. x 17¾" W. x 10" D., record changer area 21" W. x 16" D. x 9⅝" H., record storage area 22⅜" W. x 14½" H. x 12½" D., speaker wing area (inside) 14" W. x 29½" H. x 15¾" D., AM-FM Tuner area 20½" W. x 5¼" H. x 14" D., amplifier (2 areas) 15¼" W. x 10¾" H. x 13¼" D.

Model HH-1B Birch
Model HH-1M Mahogany
Now only **$299.95** each

The Same Superior Performance At a New Low Price

HEATHKIT SS-2 **$39.95**

OPTIONAL LEGS EXTRA

Economical Hi-Fi For Your Home

"LEGATO" HI-FI SPEAKER SYSTEM KIT

The increasing sales of the Legato has made more economical quantity production possible so we are passing the savings on to you by offering you this magnificent speaker system at a reduced price. Truly a "queen" among hi-fi speaker systems, the Legato was specially designed to meet and surpass the most stringent requirements of high fidelity sound reproduction. Two 15" Altec Lansing low frequency drivers cover frequencies of 25 to 500 CPS while a specially designed exponential horn with high frequency driver covers 500 to 20,000 CPS. A unique crossover network is built in making electronic crossovers unnecessary. Internal reflections are absorbed by splayed back panel and a 3" fiber glass lining. The Legato emphasizes simplicity of line and form to blend with modern or traditional furnishings. Cabinet construction is ¾" veneer surface plywood in either African mahogany or white birch and measures 41" L. x 22¼" D. x 34" H. All parts are precut and predrilled for easy assembly. Shpg. Wt. 195 lbs.

"BASIC RANGE" HI-FI SPEAKER SYSTEM KIT

True high fidelity performance at modest cost make this basic speaker system a spectacular buy for any hi-fi enthusiast. The amazing performance of this popular kit is made possible by the use of high quality speakers in an enclosure specially designed to receive them. The cabinet is a ducted port bass reflex type enclosure 11½" H. x 23" W. x 11¾" D. It features an 8" mid range woofer to cover 50 to 1600 CPS and a compression-type tweeter with flared horn covering 1600 to 12,000 CPS. Both speakers are by Jensen. The adjustable flared tweeter horn allows speaker to be used in either upright or horizontal position. The cabinet is constructed of ½" veneer surfaced plywood suitable for light or dark finish of your choice. All wood parts are precut and predrilled for easy assembly. Shpg. Wt. 25 lbs.

Attractive brass tip accessory legs convert SS-2 into attractive consolette. Legs screw into brackets provided. All hardware included. Shpg. Wt. 3 lbs. No. 91-26 $4.95

with a Heathkit Stereo System

HEATHKIT

HIGH FIDELITY STEREO TAPE DECK KIT

For your unparalleled enjoyment in the world of stereophonic sound Heathkit brings you an all new stereo tape deck. This tape deck is a precision engineered instrument providing monaural record/playback, and stereo playback of prerecorded tapes. Incorporates three separate heads, erase-record-stereo playback (stacked). The mechanical tape deck assembly is supplied complete. You build only the record and playback circuit employing two etched circuit boards for ease of wiring. Low noise EF-86 tubes in input stages and efficient push-pull bias-erase oscillator insures complete freedom from hum and noise in recording and playback. Provision made for 3¾ and 7½ IPS tape speed selected by a push button. Deck handles up to 7″ reels of tape. Other features are: provision for monitoring tape while recording, built in VU meter for proper recording level, pause control for editing tape, "fast forward" and "rewind" control. Frequency response at 7½ IPS tape speed is ±2 db from 40 to 12,000 CPS, at 3¾ IPS speed 40 to 6,000 CPS. Signal-to-noise ratio is 55 decibels with less than 1% total harmonic distortion. NARTB tape playback equalization. A safety interlock button prevents accidentally switching to record position causing erasure of recorded tapes. Shpg. Wt. 33 lbs.

Model TR-1C monaural tape deck incorporates all of the features described for the model TR-1D with the exception of stereo playback. $131.95.

No. C-TR-1C conversion kit converts model TR-1C to include stereo function of model TR-1D. $15.95.

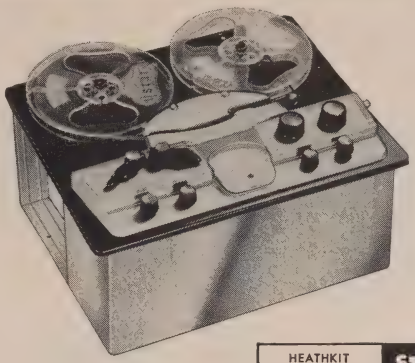

HEATHKIT TR-1D **$143.95**

Preassembled Tape Mechanism . . . You Build Only Electronic Circuit

AVAILABLE AFTER JUNE 30

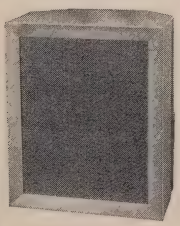

HEATHKIT SS-1B **$99.95**

Fill out the Hi-Fi Range of Your SS-2 Speaker

AVAILABLE AFTER JUNE 30

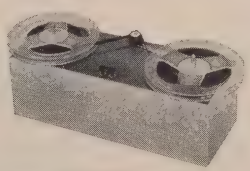

HEATHKIT SW-1 PRICE TO BE ANNOUNCED

Save Time Rewinding Tape

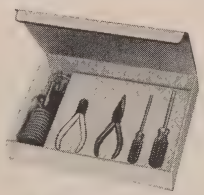

HEATHKIT TK-1 **$9.95**

All The Tools You Need For Building Heathkits

"RANGE EXTENDING" HI-FI SPEAKER SYSTEM KIT

This is not a complete speaker system in itself, but is designed to extend the range of the SS-2. The SS-1B uses a 15″ woofer and a small super tweeter to supply the very high and very low frequencies to fill out the response of the basic SS-2. The SS-2 and SS-1B when used together, form an integrated four speaker system. The SS-2 and SS-1B combination provide an overall response of ±5 db from 35 to 16,000 CPS. The kit includes circuit for crossover at 600, 1600 and 4,000 CPS. Impedance is 16 ohms and power rating is 35 watts. A control is also provided to limit output of super tweeter. The handsome cabinet measures 29″ H. x 23″ W. x 17½″ D. Constructed of beautiful ¾″ veneer surface plywood. Complete step-by-step instructions make this kit easy to build. No woodworking experience required. Shpg. Wt. 80 lbs.

"SPEEDWINDER" KIT

This handy device leaves your tape recorder free for operation while it rewinds tape at the rate of 1200′ in 40 seconds. Prevents unnecessary wear to the tape and recorder by eliminating wear against guides and heads. It will handle up to 10½″ tape reels as well as 800′ reels of 8 and 16 millimeter film. A very useful aid to operators of movie projection equipment. The Heathkit Speedwinder features an automatic shutoff which prevents whipping of tape when it has rewound. A manual shutoff is also provided. An automatic braking device is built in for protection against power failure. Driven by a heavy duty four pole motor. Handsome cabinet is constructed of furniture grade plywood. Step-by-step instructions are provided to make this kit easy to assemble even by one with no experience.

COMPLETE TOOL SET

A clear illustration of just how easy Heathkit building is. The pliers, diagonal sidecutters, two screw drivers and soldering iron are all the basic tools you need for building practically any Heathkit. Pliers and sidecutters are equipped with insulated rubber handles. The American Beauty soldering iron has a replaceable tip to facilitate cleaning. All the tools are of top quality case hardened steel for rugged duty and long life. With these simple, inexpensive tools in your hand you need not be afraid to tackle the most elaborate kit. The manual included with this handy kit provides you with many useful tips on the use and care of your tools. It shows the all important step of making proper solder connections. A truly worthwhile investment for the beginner in electronic kit building. Shpg. Wt. 3 lbs.

HEATH COMPANY • a subsidiary of Daystrom, Inc. • **Benton Harbor 20, Mich.**

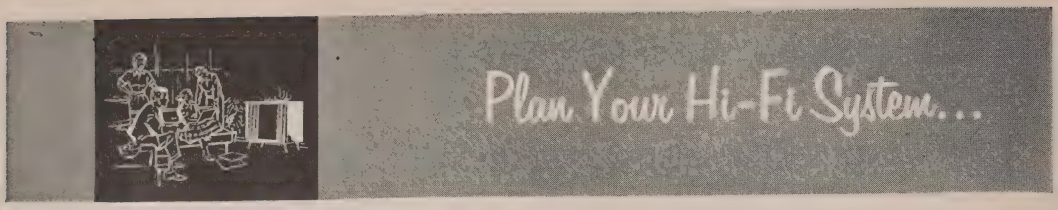

AVAILABLE AFTER JUNE 30

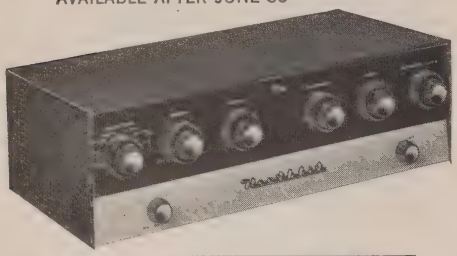

HEATHKIT SP-2 — PRICE TO BE ANNOUNCED

Model SP-1 (monaural)
Model SP-2 (monaural-stereo)
Model C-SP-1 (converts SP-1 to SP-2)

Control both stereo channels simply and conveniently

MONAURAL-STEREO PREAMPLIFIER KIT

This expertly designed preamplifier provides all the controls required for either standard monaural (single channel) or stereo (dual channel) sound reproduction. Features building block design . . . you can start with a basic preamplifier and add a second channel for stereo later on, without rewiring. Second channel plugs in for fast conversion. The complete model SP-2 (stereo) features twelve separate inputs, six on each channel with input level controls. Six dual-concentric controls consist of: two 8-position selector switches, two bass, two treble, two volume level and two loudness controls, a scratch filter switch and a 4-position function switch (separate on-off switch). The function switch provides settings for stereo, two-channel mix, channel A or B for monaural use. Inputs consist of tape, mike, mag phono and three high-level inputs. Tape input has NARTB equalization and input selector provides for RIAA, LP, 78 record compensation. EF86 tubes are used in the input stages along with hum balance controls to assure low hum and noise. Two cathode follower outputs with level controls provided in addition to two separate tape outputs for stereo recording. A remote balance control with twenty feet of cable allows balancing the stereo system from listening position. Construction is greatly simplified through the use of two printed circuit boards (one in each channel) and encapsulated printed circuits. The beautiful vinyl clad steel cover has leather texture in black with inlaid gold design. Built-in power supply.

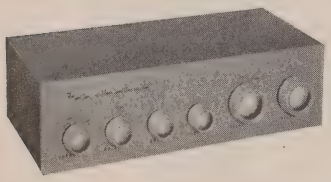

HEATHKIT WA-P2 — $19.75

Finger-tip controls for your operating convenience

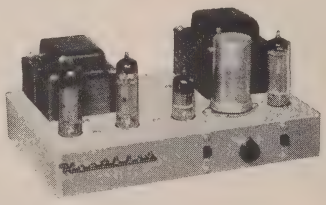

HEATHKIT UA-1 — $21.95

A low cost versatile performer

"MASTER CONTROL" PREAMPLIFIER KIT

Designed as a control center for basic amplifiers the WA-P2 provides you with true high fidelity performance for the finest audio systems. Five switch-selected inputs accommodate a record changer, tape recorder, AM-FM tuner, TV receiver, microphone, etc., each with level control. Provision is also made for a tape recorder output. Ideal for "remote" installations, the WA-P2 features a low impedance cathode-follower output circuit allowing greater length of output lead. Full frequency response is obtained within ±1½ db from 15 to 35,000 CPS and will do full justice to the finest available program sources. Equalization is provided for records through separate turnover and rolloff switches for LP, RIAA, AES, and early 78's. A special hum balance control allows setting for minimum hum level. Power for operation is required from basic amplifier or external source. Shpg. Wt. 7 lbs.

"UNIVERSAL" 12-WATT AMPLIFIER KIT

A true high fidelity performer in every sense of the word, the UA-1 makes an ideal basic amplifier for any hi-fi system and is a perfect addition to gear your present hi-fi system for stereo sound. Uses 6BQ5/EL84 push-pull output tubes for less than 2% harmonic distortion throughout the entire audio range (20 to 20,000 CPS) at full 12 watt output. The on-off switch is located right on the chassis and an octal socket is provided for connecting a preamplifier for remote control operation. The specially designed output transformer provides excellent stability and frequency response. Taps for 4, 8 and 16 ohm speakers, with switched damping for "unity" or "maximum" on the 16-ohm tap. An input level control is provided for use in wired music systems where a preamplifier is not required. This versatile unit is the latest addition to the fine line of Heathkit basic amplifiers. Shpg. Wt. 13 lbs.

With Flexible Heathkit Components

HEATHKIT

DELUXE AM-FM TUNER KIT

Outstanding features in both styling and circuitry are combined in this 16-tube deluxe AM-FM combination tuner to bring you the very finest in program sources, for your listening enjoyment. Features include three circuit boards for easy construction and high stability—prewired, prealigned FM front end—built-in AM rod antenna—tuning meter—AFC (automatic frequency control) with on-off switch and flywheel tuning. AM and FM circuits are separate and individually tuned making it ideal for stereo applications. Cathode follower outputs with individual controls are provided for both AM and FM. Other features include variable AM bandwidth, 10 kc whistle filter, tuned-cascode FM front end, FM AGC and amplified AVC for AM. The unique IF limiter design automatically provides the number of limiting and IF stages required for smooth non-flutter reception. The silicon diode power supply is extremely conservatively rated and is fuse protected assuring long service life. A tuning meter shows when the station is tuned-in for clearest reception on AM or FM. Use of three circuit boards greatly simplifies construction of circuit, you do only a minimum of wiring. All IF transformers and coils are prealigned so it will be ready to operate as soon as construction is completed. Appearance of this top-quality unit is further enhanced by the vinyl-clad steel cover in black with inlaid gold design. A multiplex jack is provided for addition of converter unit to receive multiplex stereo broadcasts on FM. A top dollar value.

AVAILABLE AFTER JUNE 30

HEATHKIT PT-1 **$89.95**

A deluxe AM-FM tuner combination loaded with extras!

HEATHKIT BC-1A **$25.95**

Wide range broadcast reception

HEATHKIT FM-3A **$25.95**

Enjoy static-free FM entertainment

HIGH FIDELITY AM TUNER KIT

This AM tuner was designed especially for high fidelity applications. It incorporates a special detector using crystal diodes, and the IF circuit features broad bandwidth to assure low signal distortion. Audio response is ±1 db from 20 CPS to 9 kc, with 5 db of pre-emphasis at 10 kc to compensate for station rolloff. Sensitivity and selectivity are excellent and the tuner covers the entire broadcast band from 550 to 1600 kc. Quiet performance is assured by a 6 db signal-to-noise ratio at 2.5 uv. Prealigned RF and IF coils eliminate the need for special alignment equipment. Incorporates AVC, two outputs, two antenna inputs, and built-in power supply. Edge-lighted glass slide rule dial for easy tuning. Your "best buy" in an AM tuner. Shpg. Wt. 9 lbs.

HIGH FIDELITY FM TUNER KIT

FM programming, your least expensive source of high fidelity will provide you with years of real enjoyment. This beautifully styled FM tuner features broad-banded circuits for full fidelity and better than 10 uv sensitivity for 20 db of quieting to pull in stations with clarity and full volume. Covers the complete FM band from 88 to 108 mc. Stabilized, temperature-compensated oscillator assures negligible drift after initial warmup. A ratio detector provides high-efficiency demodulation without sacrificing hi-fi performance. IF and ratio transformers are prealigned, as is the front end tuning unit, making special alignment equipment unnecessary. Edge-lighted glass slide rule dial for easy tuning. You need not wait to have FM in your home at this low price. Shpg. Wt. 8 lbs.

HEATH COMPANY • a subsidiary of Daystrom, Inc. • **Benton Harbor 20, Mich.**

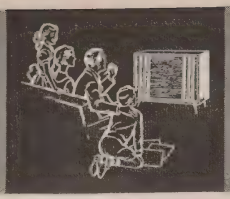

You can be sure you're buying High Fidelity

HEATHKIT W-7M **$54.95**

"EXTRA PERFORMANCE" 55 WATT HI-FI AMPLIFIER KIT

Another Heathkit first! An honestly rated high power amplifier with many top quality features at less than a dollar per watt. Full audio output is conservatively rated at 55 watts from 20 CPS to 20 kc with less than 2% total harmonic distortion throughout the entire range. Unique paired output connections permit instant switch selection of "unity" or "maximum" damping factors for all 4, 8 or 16 ohm speakers. Each output has an optimized current feedback circuit for unity damping so that there will be no compromise in performance when any of the impedances is used. This current feedback circuitry is entirely shorted out when not in use to obtain the highest possible damping factor. Features include level control and "on-off" switch right on the chassis plus provision for remote control from preamp, etc. Famous "bas-bal" circuit conveniently balances EL-34 output tubes. These heavy duty push-pull tubes operate into a high quality tapped-screen transformer designed especially for this unit. A 70-volt output on the transformer provides for P.A. or large music systems. The silicon diode power supply features a protection device that controls current until tubes have warmed up, greatly increasing service life of all components. The stylish black and gold case measures 6" H. x 8½" D. x 15" W. Convenient pilot light on the chassis. Thoughtful circuit layout makes this kit easy to build. Dollar for watt you can't beat this buy. Shipped express only. Shpg. Wt. 28 lbs.

55 watts of hi-fi power at only $1 per watt

★ BEAUTIFULLY STYLED IN BLACK AND GOLD

★ UNITY OR MAXIMUM DAMPING

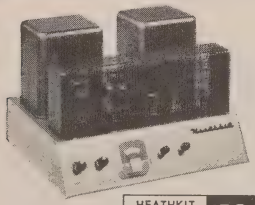

HEATHKIT W-6M **$109.95**

Plenty of Reserve Power Without Distortion

"HEAVY DUTY" 70-WATT HI-FI AMPLIFIER KIT

Here is an amplifier that will provide the extra "push" needed to drive any of the fine speaker systems available today, for truly fine performance at any power level. Silicon-diode rectifiers are used to assure long life and a heavy duty transformer gives you extremely good power supply regulation. Variable damping control provides optimum performance with any speaker system. Quick change plug selects 4, 8 and 16 ohms or 70 volt output and the correct feedback resistance. Frequency response at 1 watt is from 5 CPS to 80 kc with controlled HF rolloff above 100 kc. At 70 watts output harmonic distortion is below 2%, 20 to 20,000 CPS and IM distortion is below 1%, 60 and 6,000 CPS. Hum and noise 88 db below full output. Metered balance circuit. Designed especially for easy assembly and years of dependable service. Shipped express only. Shpg. Wt. 52 lbs.

HEATHKIT W-5M **$59.75**

Top-Flight Performance for the Critical Listener

25-WATT HI-FI AMPLIFIER KIT

Considered top value in its power class by leading independent research organizations, the W-5M incorporates all the design features required by the super critical listener. Features include a specially designed Peerless output transformer and KT66 tubes. The circuit is rated at 25 watts and will follow instantaneous power peaks of a full orchestra up to 42 watts. A "tweeter saver" suppresses high frequency oscillation and a new type balancing circuit facilitates adjustment of the "dynamic" balance between output tubes. Frequency response is ±1 db from 5 CPS to 160,000 CPS at 1 watt and within 2 db from 20 to 20,000 CPS at full 25 watts output. Harmonic distortion is less than 1% at 25 watts and IM distortion is 1% at 20 watts (60 and 3,000 CPS, 4:1). Hum and noise are 99 db below 25 watts for truly quiet performance. Rich black and gold colored styling. Shipped express only. Shpg. Wt. 31 lbs.

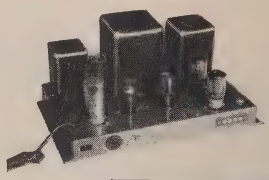

HEATHKIT W4-AM **$39.75**

Faithful Sound Reproduction with Minimum Investment

20-WATT HI-FI AMPLIFIER KIT

This fine amplifier will amaze you with its outstanding performance. It features a true Williamson circuit with extended frequency response, low distortion, and low hum levels. Enjoy true hi-fi with only a minimum investment compared to other units on the market. 5881 tubes and a special Chicago-Standard output transformer are employed to give you full fidelity at minimum cost. Frequency response extends from 10 CPS to 100 kc within ±1 db at 1 watt assuring you of full coverage of the audio range. Clean, clear sound amplification takes place in circuits that hold harmonic distortion at 1.5% and IM distortion below 2.7% at full 20 watt output. Hum and noise are 95 db below full output. Taps on the output transformer are at 4, 8 or 16 ohms to match the speaker system of your choice. An outstanding performer, this investment will bring you years of listening enjoyment. Shipped express only. Shpg. Wt. 28 lbs.

All basic amplifiers recommended for use with model WA-P2, SP-1 or SP-2 preamplifiers

...When You Buy Heathkits

HEATHKIT

"BOOKSHELF" 12-WATT AMPLIFIER KIT

The model EA-2 combines eye-pleasing style and color with many extra features for high quality sound reproduction. This fine amplifier provides full range frequency response from 20 to 20,000 CPS within ±1 db. Harmonic distortion is less than 1% at full 12 watt output over the entire range (20-20,000 CPS). IM distortion is less than 1.5% at 12 watts with low hum and noise. Miniature tubes are used throughout the advanced circuitry, including EL84 output tubes in a push-pull tapped-screen output circuit using a special designed output transformer. Transformer has taps at 4, 8 and 16 ohms. The model EA-2 has its own built-in preamplifier with provision for three separate inputs, mag phono, crystal phono and tuner. The mag phono input features RIAA equalization. Separate bass and treble controls are provided with boost and cut action. A special hum-balance control assures quiet operation. The luxury styled cabinet has a smooth simulated leather texture in black with inlaid gold design and is constructed of vinyl plastic bonded to steel. It resists scuffing, wear, abrasion, and chemicals. The front panel features brushed-gold trim and buff knobs with gold inserts for a very pleasing appearance. An amber neon pilot lamp indicates when the amplifier is on. Cabinet measures 12½" W. x 3$\frac{3}{16}$" D. x 4⅜" H. making it suitable for use on a bookshelf, end table, etc. High quality is emphasized throughout for performance matching amplifiers costing many times more. Shpg. Wt. 15 lbs.

HEATHKIT EA-2 **$27.95**

Combines beauty, style and quality

★ LESS THAN 1% DISTORTION AT FULL OUTPUT OVER ENTIRE AUDIO RANGE.

★ BUILT-IN PREAMPLIFIER

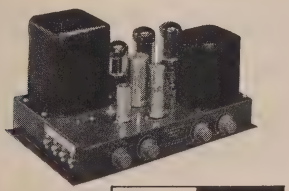

HEATHKIT A9-C **$35.50**

A Bargain Package of Power and Performance

GENERAL-PURPOSE 20-WATT AMPLIFIER KIT

The A9-C combines a preamplifier, main amplifier and power supply all on one chassis providing a compact unit to fill the need for a good high fidelity amplifier with a moderate cash investment. Designed primarily for home installations, it is also capable of fulfilling P.A. requirements. The preamplifier section features four separate switch selected inputs. Separate bass and treble tone controls offer 15 db boost and cut. A true high fidelity performer, the A9-C covers 20 to 20,000 CPS within ±1 db. Front panel is detachable, and can be installed on the outside of a cabinet where the chassis comes through, for custom installations. A fine unit with which to start your hi-fi system. Shpg. Wt. 23 lbs.

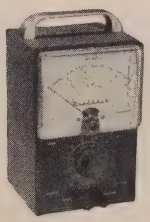

HEATHKIT AV-3 **$29.95**

Invaluable for Hi-Fi Testing

AUDIO VTVM KIT

Critical AC voltage measurements are made easy with this high quality vacuum tube voltmeter which emphasizes stability, broad frequency response and sensitivity. Features large 4½" 200 microampere meter, with increased damping in the meter circuit for stability in low frequency tests. Extremely high voltage range handles measurements from a low value of 1 millivolt to a maximum of 300 volts. AC (RMS) voltage ranges are: 0-.01, .03, .1, .3, 1, 3, 10, 30, 100 and 300 volts. Db ranges cover −52 to +52 db. Employs 1% precision multiplier resistors for maximum accuracy. High input impedance (1 megohm at 1,000 CPS). Frequency response is essentially flat from 10 CPS to 200 kc. Shpg. Wt. 6 lbs.

HEATHKIT AW-1 **$29.50**

Measure Exact Power Output

AUDIO WATTMETER KIT

Here is a fine meter to accurately measure output wattage. Five power ranges cover 0-5 mw, 50 mw, 500 mw, 5 w and 50 w full scale. Five switch selected db ranges cover −10 db to +30 db. All indications are read directly on the large 4½" 200 ua meter. Frequency response is ±1 db from 10 CPS to 250 kc. External or internal load resistors are selected with convenient front panel switch. Non-inductive load resistors are built in for 4, 8, 16 or 600 ohms impedance. Precision multiplier resistors are used for high accuracy and incorporates a crystal diode bridge for wide-range frequency response. Modern styling and convenient front panel design. Cabinet is ventilated to allow efficient cooling of load resistors. Shpg. Wt. 7 lbs.

HEATH COMPANY • a subsidiary of Daystrom, Inc. • **Benton Harbor 20, Mich.**

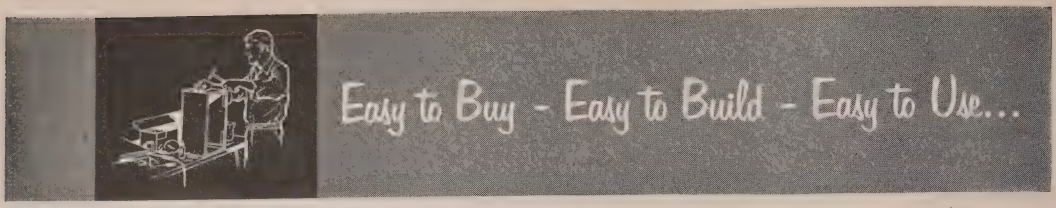

HEATHKIT
CE-1
$43.95 each

CONTEMPORARY
Model CE-1B Birch
Model CE-1M Mahogany

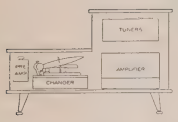

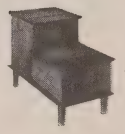

TRADITIONAL
Model CE-1T Mahogany

Combine all your Hi-Fi equipment in this attractive cabinet

CHAIRSIDE ENCLOSURE KIT

This Chairside Enclosure lets you combine all of your hi-fi equipment into one compact control center and, at the same time add a beautiful piece of furniture to your home. The CE-1 is designed to house the AM and FM tuners (BC-1A and FM-3A) and the WA-P2 preamplifier along with the majority of record changers which will fit into the space provided. Adequate room is available in the rear of the unit to house any of the Heathkit amplifiers designed to operate with the WA-P2. The enclosure is flexible enough to give you a large choice in component installation. If only one tuner and the preamplifier are used, the two units can be installed in the tilt-out drawer, or if more convenient, either unit can be placed in the space provided in front of the changer compartment. The tilt-out shelf can be installed on either right or left side and the lift-top lid is similarly designed to lift from either side depending on your choice during construction. Good ventilation is achieved through appropriately placed slots in the bottom and back of the enclosure. Overall dimensions are 18"W. x 24" H. x 35½" D. The changer compartment measures 17¾" L. x 16" W. x 9⅝" D. All parts are precut and predrilled for easy assembly and attractive hardware is supplied to match each style. The contemporary cabinet is available in either mahogany or birch and the traditional cabinet is available in mahogany only. Furniture grade plywood can be finished to your taste. Shpg. Wt. 46 lbs.

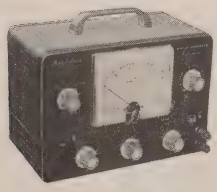

HEATHKIT
AG-9A **$34.50**

Your own source of Hi-Fi audio signals

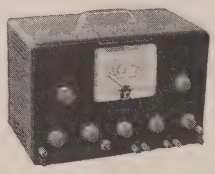

HEATHKIT
AA-1 **$49.95**

3 Audio test instruments in one compact unit

HEATHKIT
HD-1 **$49.50**

Check amplifier distortion quickly

AUDIO SIGNAL GENERATOR KIT

The model AG-9A is "made to order" for high fidelity applications, and provides quick and accurate selection of low-distortion signals from 10 CPS to 100 kc. Three rotary switches select two significant figures and a multiplier to determine audio frequency. Incorporates step-type and a continuously variable output attenuator. Output indicated on large 4½" panel meter, calibrated in volts and db. Attenuator system operates in 10 db steps, corresponding to meter calibration, in ranges of 0-.003, .01, .03, .1, .3, 1, 3 and 10 volts RMS. "Load" switch permits use of built-in 600-ohm load, or external load of different impedance. Output and frequency indicators accurate to within ±5%. Distortion less than .1 of 1% between 20 and 20,000 CPS. Shpg. Wt. 8 lbs.

AUDIO ANALYZER KIT

Complete high fidelity testing facilities are yours in the AA-1. It combines the functions of three separate instruments; an AC VTVM, audio wattmeter and a complete IM analyzer with filters and high and low frequency oscillators built in. VTVM ranges are: 0-.01, .03, .1, .3, 1, 3, 10, 30, 100 and 300 volts (RMS). Db scale reads from −65 to +52 dbm. Wattmeter ranges are: .15 mw, 1.5 mw, 15 mw, 150 mw, 1.5 w, 15 w and 150 w. IM scales are 1%, 3%, 10%, 30% and 100% full scale. Provides internal load resistors of 4, 8, 16 or 600 ohms. Combining and consolidating functions reduces the number of test leads and controls required for the same test. Complete instructions are provided for easy assembly, also valuable information on use of instrument. Shpg. Wt. 13 lbs.

HARMONIC DISTORTION METER KIT

Valuable in both designing and servicing of audio circuits, the HD-1 used with an audio signal generator, will accurately measure harmonic distortion at any or all frequencies between 20 and 20,000 CPS. Distortion is read on panel meter in ranges of 0-1, 3, 10, 30 and 100% full scale. Full scale voltage ranges of 0-1, 3, 10 and 30 volts are provided for the initial reference settings. Signal-to-noise ratio is measured on a separate meter scale calibrated in db. Features high input impedance (300,000 ohms) and 1% precision resistors in the VTVM voltage divider circuit for excellent sensitivity and accuracy. High quality components insure years of dependable service. Complete instructions provided for easy assembly and operation. Shpg. Wt. 13 lbs.

Heathkits are Your Best Dollar Value

HEATHKIT

TRANSISTOR PORTABLE RADIO KIT

The overwhelming sales of this outstanding transistor portable have made a substantial price reduction possible . . . in addition, an all new plastic molded case adds the finishing touch to the exceptional circuitry. Six name-brand (Texas Instrument) transistors are used for extra good sensitivity and selectivity. The 4" x 6" PM speaker with heavy magnet provides excellent tone quality. Use of this large speaker and roomy chassis make it unnecessary to crowd components adding greatly to the ease of construction. Transformers are prealigned so it is ready for service as soon as construction is completed. A touchup in alignment is easily accomplished on a station by following simple instructions in manual. Alignment tool furnished. Has built-in rod-type antenna for reception in all locations. Six standard size "D" flashlight cells are used for extremely long battery life (between 500 and 1000 hours) and they can be purchased almost anywhere. Cabinet is two-tone blue molded plastic with pull-out carrying handle. Dimensions are 9½" L. x 7¼" H. x 4" D. Shpg. Wt. 6 lbs.

Model XR-1-L: Identical to XR-1-P except in genuine leather case. Rich, warm sun-tan tone. Leather carrying strap included. Shpg. Wt. 7 lbs.

Leather Case: can be purchased separately if desired. Fits all XR-1P's and XR-1's. No. 93-1. Shpg. Wt. 3 lbs. $6.95.

MODEL XR-1-L
$34.95

HEATHKIT **XR-1-P** **$29.95**

Newly designed plastic case . . . new low price!

★ 4" X 6" SPEAKER FOR "BIG SET" TONE
★ LONG BATTERY LIFE (500 to 1000 Hours)

HEATHKIT **CT-1** **$7.95**

Test condensers right in the circuit

HEATHKIT **DF-1** **$54.95**

Pin-point your exact location

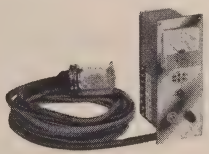

HEATHKIT **FD-1** **$35.95 each**
(6 volt model FD-1-6)
(12 volt model FD-1-12)

Detects gas fumes

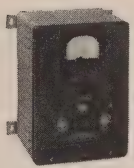

HEATHKIT **MC-1** **$42.95**

Save your boat batteries

IN-CIRCUIT CAPACI-TESTER KIT

Check most capacitors for "open" or "short" right in the circuit with this handy kit. Detects open capacitors from about 50 mmf up, not shunted by an excessively low resistance value. Checks shorted capacitors up to 20 mfd (not shunted by less than 10 ohms). (Does not detect leakage nor check electrolytic condensers.) Employs a 60-cycle frequency for the short test and a 19 megacycle frequency for the open test. Uses electron beam "eye" tube for quick indication. Test leads included. Shpg. Wt. 5 lbs.

TRANSISTOR RADIO DIRECTION FINDER KIT

This transistor radio compass will double as a portable radio. Covers the standard broadcast band from 540 to 1600 kc. Ideal for use aboard boats and also on land by hunters, hikers, etc. A directional high-Q ferrite antenna rotates from the front panel to obtain a fix on a station. A 1 ma meter serves as null and tuning indicator. Prealigned IF transformers—six transistor circuit. Powered by tiny 9-volt battery with spare included. Dimensions 7½" W. x 5⅛" H. x 5⅛" D. Shpg. Wt. 5lbs.

FUEL VAPOR DETECTOR KIT

Protect your boat and passengers against fire and explosion with one of these fuel vapor detector kits. Indicates the presence of fumes on a three-color "safe-dangerous" meter scale and immediately shows if it is safe to start the engine. A pilot lamp shows when the detector is operating. Easy to build and install, even by one not having previous experience. Operates from your boat battery. The kit is complete with heavy-duty neoprene insulated cable and includes spare detector unit. Shpg. Wt. 4 lbs.

MARINE CONVERTER KIT

Charge 6 or 12 volt batteries with this marine converter and battery charger. A panel mounted 25 ampere meter continuously monitors the charging current. Moisture and fungus proofed for rugged marine use. Convection cooling prevents unsafe temperature rise. The MC-1 has no moving parts, tubes nor blowers to wear out or break. Mounting brackets are supplied for easy installation on any boat. Ideal for keeping batteries fully charged or to supply extra current for appliances. Shpg. Wt. 16 lbs.

HEATH COMPANY • a subsidiary of Daystrom, Inc. • Benton Harbor 20, Mich.

New Styling - New Features...

HEATHKIT TX-1 **$229.50**

Complete Versatility for Top-Notch Amateur Communications

★ NEWLY DESIGNED VFO—ROTATING SLIDE RULE DIAL
★ MODERN STYLING—PROVISION FOR SSB ADAPTER

"APACHE" HAM TRANSMITTER KIT

Fresh out of the Heath Company laboratories, the brand-new "Apache" model TX-1 ham transmitter features modern styling and the latest in circuitry for extra fine performance. The "Apache" is a high quality transmitter operating with a 150 watt phone input and 180 watt CW input. In addition to CW and phone operation, built-in switch selected circuitry provides for single-sideband transmission through the use of a plug-in external adapter. These SSB adapters will be available in the near future. A compact, stable and completely redesigned VFO provides low drift frequency control necessary for SSB transmission. A slide rule type illuminated rotating VFO dial with vernier tuning provides ample bandspread and precise frequency settings. The bandswitch allows quick selection of the amateur bands on 80, 40, 20, 15 and 10 meters. (11M with crystal control). This unit also has adjustable low level speech clipping and a low distortion modulator stage employing two of the new 6CA7/EL-34 tubes in push-pull class AB operation. Time sequence keying is provided for "chirpless" break-in CW operation. The final amplifier is completely shielded for greater TVI protection and transmitter stability. Die-cast aluminum knobs and front panel escutcheons add to the attractive styling of the transmitter. Pi network output coupling matches antenna impedances between 50 and 72 ohms. Shpg. Wt. 115 lbs.

$50.00 deposit required on C.O.D. orders. Shipped motor freight unless otherwise specified.

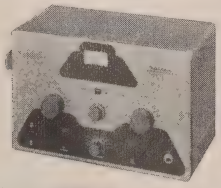

HEATHKIT DX-20 **$35.95**

An Ideal Code Transmitter

DX-20 CW TRANSMITTER KIT

Designed especially for CW work, the DX-20 features high efficiency at low cost. An ideal rig for the novice or advanced-class CW operator. Plate power input is 50 watts, and covers 80, 40, 20, 15, 11 and 10 meters with single knob bandswitching. Features a single 6DQ6A tube in the final amplifier stage and a 6CL6 as a crystal oscillator. Pi network output circuit matches various antenna impedances between 50 and 1000 ohms and reduces harmonic output. Top-quality parts are featured throughout, including "potted" transformers, etc., for long service life. Complete shielding to minimize TVI. Removable metal pull-out plug on left end of cabinet provides access for crystal changing. Very easy to build with complete instructions supplied. Shpg. Wt. 19 lbs.

HEATHKIT DX-100 **$189.50**

You'll be Proud to Own This Outstanding Performer

DX-100 PHONE AND CW TRANSMITTER KIT

Well known for its high quality and fine performance the DX-100 features a built-in VFO, modulator, and power supply, complete shielding to minimize TVI, and a pi network coupling to match impedances from 50 to 600 ohms. RF output is in excess of 100 watts on phone and 120 watts on CW, for clean strong signals on all ham bands from 10 to 160 meters. Single knob bandswitching and illuminated VFO dial and meter face add real operating convenience. RF output stage uses a pair of 6146 tubes in parallel, modulated by a pair of 1625's. High quality components are used throughout, such as potted transformers, silver-plated or solid coin silver switch terminals, aluminum-heat dissipating caps on the final tubes, copper plated chassis, etc. Shpg. Wt. 107 lbs.

$50.00 deposit required on C.O.D. orders. Shipped motor freight unless otherwise specified.

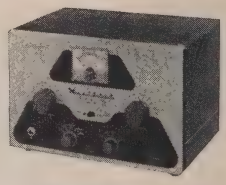

HEATHKIT DX-40 **$64.95**

Phone & CW Facilities at Low Cost

DX-40 PHONE AND CW TRANSMITTER KIT

An outstanding buy in its power class the DX-40 provides both phone and CW operation on 80, 40, 20, 15, 11 and 10 meters. A single 6146 tube is used in the final amplifier stage to provide full 75 watt plate power input on CW, or controlled carrier modulation peaks up to 60 watts for phone operation. Modulator and power supplies are built in and single-knob bandswitching is combined with the pi network output circuit for complete operating convenience. Complete shielding to minimize TVI. Provision is made for three crystals. A four-position switch selects any of the three crystals or a jack for external VFO. Crystal sockets are reached through access door in rear of cabinet. High quality D'Arsonval movement panel meter. Shpg. Wt. 25 lbs.

For Real Ham Enjoyment

HEATHKIT

"MOHAWK" HAM RECEIVER KIT

Here is a ham receiver that any radio operator would be proud to own. The "Mohawk" has all the functions required for high quality communications with clear, rock-steady reception on all bands. This 15-tube receiver features double conversion with IF's at 1682 kc and 50 kc and covers all of the amateur frequencies from 160 through 10 meters on seven bands with an extra band calibrated to cover 6 and 2 meters using a converter. Receiver accommodations are provided for these converters which will be available in Heathkits soon. The "Mohawk" is specially designed for single-sideband reception with crystal controlled oscillators for upper and lower sideband selection. A completely preassembled, wired and aligned front end coil assembly assures ease of construction and top performance of the finished unit. Other features include five selectivity positions from 5 kc to 500 CPS, bridged T-notch filter for maximum heterodyne rejection, and a built-in 100 kc crystal calibrator. The set provides a 10 db signal-to-noise ratio at less than 1 microvolt input. Front panel features S meter, separate RF, IF and AF gain controls, T-notch tuning, T-notch depth, ANL, AVC, BFO, bandswitch, tuning, antenna trimmer, calibrate set, calibrate on, CW-SSB-AM, receive-standby, upper-lower sideband, selectivity, phone jack and a wide band rotating slide rule type vernier tuning dial with easy to read calibrations. Shpg. Wt. 90 lbs.

$50.00 required on C.O.D. orders. Shipped motor freight unless otherwise specified.

HEATHKIT RX-1 **$274.95**

Now in Kit Form a Top Quality Ham Band Receiver

★ PREWIRED AND ALIGNED FRONT END COIL ASSEMBLY.
★ CRYSTAL CONTROLLED OSCILLATORS FOR DRIFT-FREE RECEPTION.

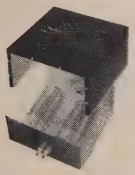

HEATHKIT B-1 **$8.95**

Get Proper Match Between Transmitter and Antenna

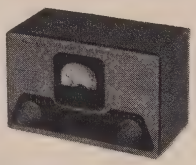

HEATHKIT AM-2 **$15.95**

Measure Standing Wave Ratio

HEATHKIT VX-1 **$23.95**

Eliminates Hand Switching

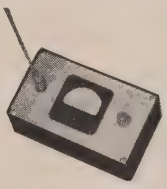

HEATHKIT PM-1 **$14.95**

Quick Check of Transmitter Operation

BALUN COIL KIT

Unbalanced coax lines used on the most modern transmitters can be matched to balance lines of either 75 or 300 ohms impedance by using the model B-1 Balun Coil Kit. Can be used with transmitters and receivers without adjustment over the frequency range of 80 through 10 meters, and will handle power inputs up to 200 watts. Cabinet size is 10" square by 5" D. and may be located any distance from the transmitter or antenna. A protective cover is supplied to prevent damage in outdoor installations. Shpg. Wt. 4 lbs.

REFLECTED POWER METER KIT

The match of your antenna transmission system can be checked by measuring the forward and reflected power or standing wave ratio from 1:1 to 6:1 with this fine unit. Designed to handle a peak power of well over 1 kilowatt of energy the AM-2 may be left in the antenna system feed line at all times. Band coverage is 160 meters through 2 meters. Input and output impedances for 50 or 75 ohm lines. No external power required for operation. Cabinet size is 7⅜" x 4⅛" x 4⅝". Shpg. Wt. 3 lbs.

ELECTRONIC VOICE CONTROL KIT

This unique device allows you to switch from receiver to transmitter merely by talking into your microphone . . . you get the advantage of "telephone-type conversation" as in single sideband but with regular AM transmission. The unit is adjustable to all conditions by sensitivity controls provided. A variable time delay control changes the "hold" time. Provision is made for receiver and speaker connections and also for a 117 volt antenna relay. Built-in power supply. Complete instructions provided. Shpg. Wt. 5 lbs.

RF POWER METER KIT

This self contained unit requires no power for operation. You simply place it close to the transmitter antenna to sample the RF field which is then indicated on the panel meter. Operates with any transmitter having an output frequency between 100 kc and 250 mc, regardless of power. Sensitivity is 0.3 volts RMS full scale, and a special control on the panel allows for further adjustment of the sensitivity. Measures 3¾" W. x 6¼" L. x 2" D. An easy way to put your mind at ease concerning transmitter operation. Shpg. Wt. 2 lbs.

HEATH COMPANY • a subsidiary of Daystrom, Inc. • Benton Harbor 20, Mich.

Choose from a wide variety of Heathkits

DUAL-CHASSIS 20 WATT HI-FI AMPLIFIER KIT

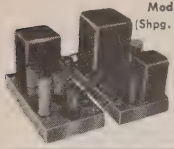

Model W3-AM
(Shpg. Wt. 29 lbs.)
$49.75

12" UTILITY SPEAKER

Model 401-6
(Shpg. Wt. 7 lbs.)
$7.50

ALL-BAND RADIO KIT

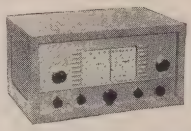

Model AR-3
(Shpg. Wt. 12 lbs.)
$29.95
(less cabinet)

CRYSTAL RADIO KIT

Model CR-1
(Shpg. Wt. 3 lbs.)
$7.95

BROADCAST BAND RADIO KIT

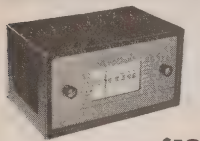

Model BR-2
(Shpg. Wt. 10 lbs.)
$18.95
(less cabinet)

ELECTRONIC CROSSOVER KIT

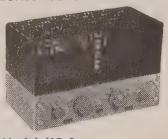

Model XO-1
(Shpg. Wt. 6 lbs.)
$18.95

"Q" MULTIPLIER KIT

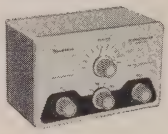

Model QF-1
(Shpg. Wt. 3 lbs.)
$9.95

"AUTOMATIC" CONELRAD ALARM KIT

Model CA-1
(Shpg. Wt. 4 lbs.)
$13.95

GRID DIP METER KIT

Model GD-1B
(Shpg. Wt. 4 lbs.)
$21.95

VIBRATOR POWER SUPPLY KIT

6 volt Model VP-1-6
12 volt Model VP-1-12
(Shpg. Wt. 4 lbs.)
$7.95 ea.

VARIABLE FREQUENCY OSCILLATOR KIT

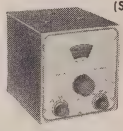

Model VF-1
(Shpg. Wt. 7 lbs.)
$19.50

PROFESSIONAL RADIATION COUNTER KIT

Model RC-1
(Shpg. Wt. 8 lbs.)
$79.95

ISOLATION TRANSFORMER KIT

Model IT-1
(Shpg. Wt. 9 lbs.)
$16.50

ELECTRONIC SWITCH KIT

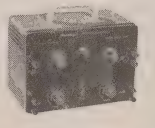

Model S-3
(Shpg. Wt. 8 lbs.)
$21.95

REGULATED POWER SUPPLY KIT

Model PS-3
(Shpg. Wt. 17 lbs.)
$35.50

VOLTAGE CALIBRATOR KIT

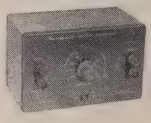

Model VC-3
(Shpg. Wt. 4 lbs.)
$12.50

DIRECT-READING CAPACITY METER KIT

Model CM-1
(Shpg. Wt. 7 lbs.)
$29.50

TUBE CHECKER KIT

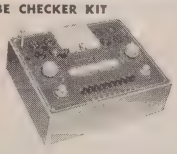

Model TC-2
(Shpg. Wt. 12 lbs.)
$29.50

EASY TIME PAYMENTS

AVAILABLE FOR YOUR CONVENIENCE . . .

Any order totaling $90 or more can be paid for in small monthly payments (send for complete details).

RESISTANCE SUBSTITUTION BOX KIT

Model RS-1
(Shpg. Wt. 2 lbs.)
$5.50

CONDENSER SUBSTITUTION BOX KIT

Model CS-1
(Shpg. Wt. 2 lbs.)
$5.50

CATHODE RAY TUBE CHECKER KIT

Model CC-1
(Shpg. Wt. 10 lbs.)
$24.95

LABORATORY RF GENERATOR KIT

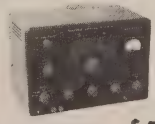

Model LG-1
(Shpg. Wt. 16 lbs.)
$48.95

"Q" METER KIT

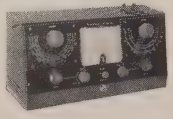

Model QM-1
(Shpg. Wt. 14 lbs.)
$44.50

DECADE CONDENSER KIT

Model DC-1
(Shpg. Wt. 3 lbs.)
$16.50

DECADE RESISTANCE KIT

Model DR-1
(Shpg. Wt. 4 lbs.)
$19.50

...to Fill Your Exact Needs

HEATHKIT

PORTABLE TUBE CHECKER KIT

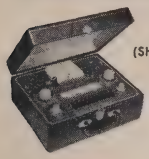

Model TC-2P
(Shpg. Wt. 15 lbs.)

$34.50

TV PICTURE TUBE TEST ADAPTER* FOR TC-2 AND TC-2P

Model 355
(Shpg. Wt. 1 lb.)

$4.50

BINDING POST KIT

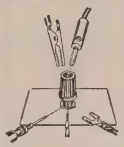

Model 362
(Shpg. Wt. 1 lb.)

$4.00

BATTERY TESTER KIT

Model BT-1
(Shpg. Wt. 2 lbs.)

$8.50

ELECTRONIC IGNITION ANALYZER KIT

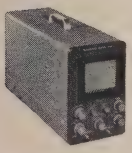

MODEL IA-1
(Shpg. Wt. 20 lbs.)

$59.95

SCOPE PROBES

Scope Demodulator Probe Kit
Model 337-C
(Shpg. Wt. 1 lb.)

$3.50

Low Capacity Probe Kit
Model 342
(Shpg. Wt. 1 lb.)

$3.50

VTVM PROBES

30,000 Volt DC HV
Probe Kit No. 336
Shpg. Wt. 2 lbs. **$4.50**

Etched Circuit RF
Probe Kit No. 309-C
Shpg. Wt. 1 lb. **$3.50**

Peak-to-peak Voltage
Probe Kit No. 338-C
Shpg. Wt. 2 lbs. **$5.50**

ENLARGER TIMER KIT

Model ET-1
(Shpg. Wt. 3 lbs.)

$11.50

IMPEDANCE BRIDGE KIT

Model IB-2A
(Shpg. Wt. 12 lbs.)

$59.50

"LOW RIPPLE" BATTERY ELIMINATOR KIT

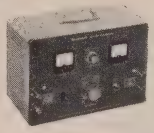

Model BE-5
(Shpg. Wt. 21 lbs.)

$39.95

ELECTRONIC ANALOG COMPUTER KIT

Full Computer Group C

$945.00

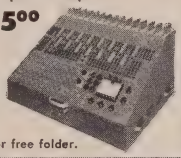

Write for free folder.

Free Catalog

Send for this informative booklet describing these and many other do-it-yourself kits.

ORDER DIRECT BY MAIL . . . from the WORLD'S LARGEST MANUFACTURER

OF ELECTRONIC INSTRUMENTS IN KIT FORM

Save ½ or more over equivalent ready-made products by buying direct and assembling them yourself. You gain priceless knowledge through complete and informative construction manuals.

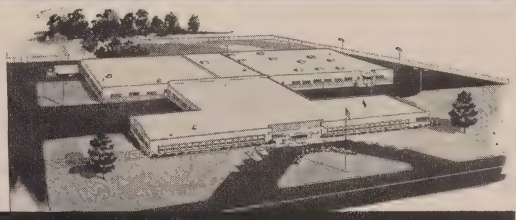

HEATH COMPANY A Subsidiary of Daystrom, Inc. **BENTON HARBOR 20, MICH.**

ORDER BLANK

NOTE: All prices and specifications subject to change without notice.

Enclosed find ( ) check ( ) money order for_____
Please ship C.O.D. ( ) postage enclosed for_____pounds.

On Express orders do not include transportation charges—they will be collected by the express agency at time of delivery.

On Parcel Post Orders include postage for weight shown. All prices are NET F.O.B. Benton Harbor, Michigan, and apply to Continental U.S. and Possessions only.

Name_____

Address_____

City & Zone_____State_____
(PLEASE PRINT)

SHIP VIA
☐ Parcel Post
☐ Express
☐ Freight
☐ Best Way

QUANTITY	ITEM	MODEL NO.	PRICE
		POSTAGE	
	☐ SEND FREE Heathkit Catalog	TOTAL	

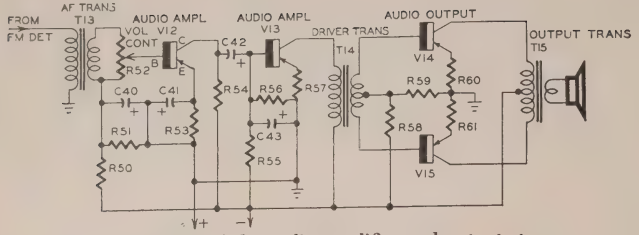
FROM FM DET
AF TRANS T13
AUDIO AMPL VOL CONT V12
AUDIO AMPL V13
DRIVER TRANS T14
AUDIO OUTPUT V14 V15
OUTPUT TRANS T15
R50 R51 R52 R53 R54 R55 R56 R57 R58 R59 R60 R61
C40 C41 C42 C43

Fig. 6—Circuit of the audio amplifier and output stages.

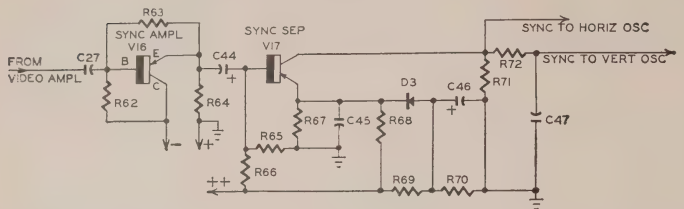

Fig. 7—The sync separator uses two p-n-p transistors and a crystal diode to do its job.

(*Continued from page* 59)

for home use (such as large consoles).

The circuit of a typical audio amplifier section is given in Fig. 6. This amplifier consists of two common-emitter "gain" stages driving a common-emitter push-pull output amplifier which, in turn, drives a PM speaker. All transistors are p-n-p units.

In operation, the audio signal obtained from the ratio detector is coupled through impedance-matching transformer T13 to V12's input circuit. Potentiometer R52, across T13's secondary winding, serves as a *volume* control. Base bias for the first stage is supplied by voltage divider R50-R51, bypassed by C40. Emitter resistor R53, bypassed by C41, insures stable operation. R54 is V12's collector load.

The amplified audio signal appearing across R54 is coupled through capacitor C42 to V13's base. This stage's base bias current is supplied by voltage divider R55–R56, bypassed by C43. An unbypassed emitter resistor, R57, is provided to do a threefold job—it stabilizes stage operation, reduces distortion by introducing a small amount of degeneration and increases V13's input impedance. Driver transformer T14 matches V13 to the push-pull output stage. A stepdown turns ratio is used here.

Transistors V14 and V15, together, form the power output stage. Base bias current for these transistors is furnished by voltage divider R58–R59. Small unbypassed emitter resistors R60 and R61 minimize the effects of differences between V14 and V15 and thus insure balanced operation. Finally, the amplified output signal is coupled through output transformer T15 to the loudspeaker's voice coil.

Sync separator

Many types of transistor pulse-shaping, clipping and amplifying circuits have been developed for use in military equipment and in electronic computers. Thus, the problem of sync-pulse separation is a relatively minor one. Chances are that a commercially manufactured TV receiver will employ a one- or two-stage sync separator, using high-speed switching or rf transistors in these stages. The schematic of a typical sync separator is given in Fig. 7. This circuit includes an impedance-matching common-collector amplifier (V16) and common-emitter sync separator (V17). Both stages use p-n-p's.

In operation, the video signal obtained from the video amplifier is coupled through dc blocking capacitor C27 to V16's base circuit (waveform is shown in Fig. 8). Base bias current for this stage is provided by voltage divider R62–R63, with resistor R64 acting as the emitter load. The use here of a common-collector amplifier minimizes loading on the video amplifier. As the reader may recall, a common-collector circuit, in contrast to the more popular common-emitter configuration, has a *high* input impedance. The signal appearing across R64 (see Fig. 9) is coupled through dc blocking capacitor C44 to V17's base input circuit.

V17 is biased so that it is driven to collector-current saturation by the peaks of the applied video signal. This establishes the amplitude of the peak pulses developed across collector load resistor R71 at a relatively fixed value and, to some extent, clips off noise peaks of greater amplitude than the sync pulses. This saturating action is achieved, even with comparatively weak input signals, by using a combination bias voltage which includes fixed and variable components. A fixed bias is applied by voltage divider R65–R66, and a variable bias is developed in the emitter circuit, appearing across R67. The latter bias, in turn, depends on collector current and the ratio of bleeder resistor R68 and emitter resistor R67, R69, R70, C46 and D3 improve the circuit's immunity to noise signals while, at the same time, providing optimum separation of vertical sync pulses.

To see how this noise-immunity circuit works, let us first consider the circuit's operation when handling normal (noise-free) sync pulses. Under these conditions, emitter current biases diode D3 in its low-resistance (or conducting) direction, permitting R69, R70 and C46 to become part of the emitter-to-ground circuit. In effect, C46, a fairly large capacitor, is shunted across C45, and the emitter bias circuit has a fairly long time constant. This permits optimum separation of the broad, low-frequency vertical sync pulses.

If a high-amplitude noise signal is applied to the stage, D3 is still biased in its forward (conducting) direction and the action is as before. However, under these conditions, C46 can charge to a peak voltage higher than that to

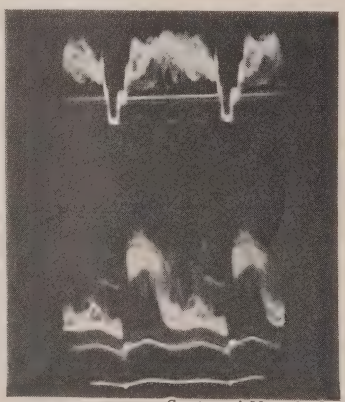

Courtesy of Motorola, Inc.

Fig. 8—Waveforms at V16's base; (top) 60-cycle sweep; (bottom) 15,750-cycle sweep.

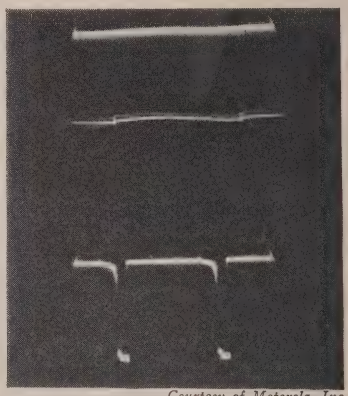

Courtesy of Motorola, Inc.

Fig. 9—In some transistor receivers, this waveform will be present at V16's base; (top) 60-cycle sweep; (bottom) 15,750-cycle sweep.

BUILD YOUR OWN JBL ACOUSTICAL ENCLOSURE FROM DETAILED PRODUCTION PRINTS

get the greatest thrill high fidelity can give you...

full range, rich, clean sound from precision JBL Signature loudspeakers mounted in an acoustical enclosure you make with your own hands. Reward your painstaking craftsmanship with speakers designed for the perfectionist. JBL Signature units, such as the Model D130, are acknowledged by foremost authorities to be the finest made. The D130 is the only 15" extended range speaker made with a 4" voice coil. It is unsurpassed in efficiency and transient-handling ability. The JBL Model 175DLH gives you smooth, crisp reproduction of frequencies above 1200 cps. The 175DLH is equipped with an acoustical lens, an exclusive JBL development, for even distribution of highs over a 90° solid angle. Any speaker, if it is to give you accurate bass reproduction, must be mounted in a properly engineered acoustical enclosure.

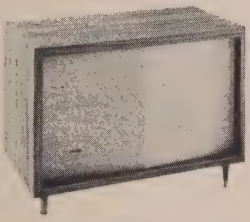

THE HARKNESS Model C40

BUILD A JBL BACK-LOADED FOLDED HORN

Designed specifically for the JBL D130, the JBL back-loaded folded horn is probably the most widely-used enclosure of its type ever manufactured. The cabinet is relatively small—less than 40" in its greatest dimension—and yet, ingeniously folded within, is an exponentially tapered horn path with an effective length of six feet. The horn adds an octave of accurate, clean, deep down bass. There are two versions of the horn: Model C34 stands vertically and may be placed in a corner, although corner placement is not required. Model C40, the Harkness, is a low-boy folded horn that is independent of wall or corner for proper functioning. Prints are designed for direct, simple, clear instruction, and time-saving construction. Cost is three dollars per set.

Model C34

USE THIS FORM TO ORDER YOUR PLANS

Now you can build this most popular JBL enclosure from detailed production prints which include a complete list of materials, all dimensions, and instructions for assembly.

JBL

JAMES B. LANSING SOUND, INC.
3249 Casitas Avenue, Los Angeles 39, California
Gentlemen:
Enclosed find $_____ for
_____ Model C34 Production Prints @ $3.00 per set.
_____ Model C40 Production Prints @ $3.00 per set.
Please print clearly or type your name and complete address:
Name_____
Address_____

3 Million Transistor Portables

Mean Big Battery Business and Bigger Dealer Profits

That's a lot of transistor portables that are going to be needing batteries this year . . . nearly three times as many as a year ago, and the figure is still growing.

For this skyrocketing new market, Mallory offers a complete line of transistor and portable radio batteries.

Mercury batteries, pioneered by Mallory, last longer, give steadier volume than ordinary batteries. Mallory Zinc-Carbon batteries are dependable and economical—meet all the requirements of today's modern portable radio sets, and flashlights as well.

Mallory Battery Company
A Division of
P. R. MALLORY & CO. Inc.
MALLORY
P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

In Canada, Mallory Battery Company of Canada Limited, Toronto 4, Ontario

• Capacitors • Vibrators • Resistors • Controls • Switches • Filters
• Rectifiers • Power Supplies • Mercury and Zinc-Carbon Batteries

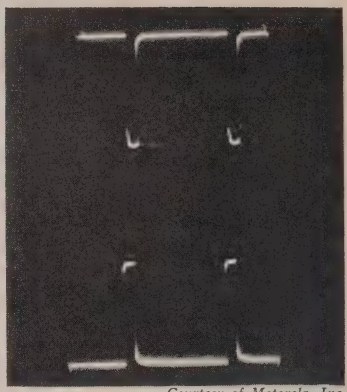

Courtesy of Motorola, Inc.

Fig. 10—Waveforms at V17's output; (top) at the collector, 15,750-cycle sweep; (bottom) at the emitter, 15,750-cycle sweep.

which it is charged by the average sync pulses. When this occurs, the voltage across C46 is such as to place a *reverse* bias on D3, and C46 is effectively removed from the emitter-to-ground circuit. Thus, the time constant of the emitter biasing circuit changes from a large to a relatively small value (C45 is *much* smaller than C46). This lets the sync separator recover from noise pulses more quickly and allows a normal separation of horizontal sync pulses.

The stage continues to operate with a short time constant in its emitter biasing circuit until C46 discharges through R70. Then normal operation is resumed. This C46–R70 time constant is long enough to insure good noise immunity, but not so long as to interfere with the circuit's recovery in time to separate the next vertical sync impulse.

The sync pulses separated by V17 and appearing across R71 (see Fig. 10) are fed to the horizontal and vertical sweep oscillator circuits. R72 and C47 form an integrating network for the vertical sync pulses.

Sweep and high-voltage circuits

As in vacuum-tube TV receivers, the sweep oscillators may employ any of a variety of basic circuits—multivibrators, blocking oscillators, various types of relaxation oscillators and so on. In addition to the basic oscillator types available to vacuum-tube circuit designers, many specialized semiconductor oscillators suitable for use in sweep oscillator circuitry employ special-purpose devices such as G-E's Unijunction transistor, IBM's "thyratron" transistor and Shockley's bi-stable diode.

Transistor deflection circuits are, in a way, easier to design than vacuum-tube sweeps. For one thing, CRT deflection yokes are, in general, low-impedance devices. Vacuum tubes are high-impedance devices. Thus, considerable effort must be expended simply to match the output of a high-impedance

tube to a low-impedance yoke winding.

This problem is exemplified by the circuitry used in the horizontal output stages of most commercially available TV receivers. This stage alone generally requires a medium-power vacuum tube and may consume as much as 40 watts (three times as much as a complete transistor TV receiver may need). Theoretically, however, almost *zero power* is required to deflect a CRT's electron beam. The high power required of a typical horizontal output stage is used almost entirely to make up for circuit losses.

While we can expect much better efficiency from transistor deflection amplifiers, typical deflection circuits will probably use one or more power transistors. Such transistors are needed to supply the high peak deflection currents required, but probably will not be used at their maximum power ratings. In many cases, the deflection yoke windings may be direct-coupled to their respective sweep output stages; the output impedance of a power transistor and the input impedance of a yoke are on the same order of magnitude.

The high dc voltage needed for the CRT's anode may be obtained in much the same way as in vacuum-tube TV sets. That is, autotransformer action might be used to step up the pulse developed during the horizontal deflection circuit's retrace (or "flyback"), with this new pulse rectified by appropriate semiconductor rectifiers. Voltage-doubler or -tripler circuits may be used if necessary.

High voltage also can be obtained by using transistor rf or pulse type power supplies. In such circuits, one or more additional power transistors would be employed in the receiver's circuit, together with a suitable oscillator transformer, and rectifier and filter components.

A typical *horizontal deflection* and *high-voltage* circuit is shown in schematic form in Fig. 11. This circuit includes a relaxation oscillator (V18), a common-emitter sweep amplifier (V19) and a voltage-doubler high-voltage rectifier (D5 and D6).

In operation, a Unijunction transistor, V18, is used as the oscillator. The circuit's basic repetition rate (frequency) is determined by the R-C time constant of R74, R73 and charge–discharge capacitor C49. Of these components, R74 is variable and acts as the horizontal hold control. The sync pulses from the sync separator are applied to V18's emitter circuit through dc blocking capacitor C48.

The negative-going pulses developed across load resistor R75 connected to V18's B2 electrode, are fed through coupling capacitor C50 to V19's base circuit. This p-n-p transistor is biased almost to cutoff by the small direct current delivered by voltage divider R77–R76 and acts as a switch, conducting heavily when pulses are applied to its base but remaining "off" at other times.

With a strong negative pulse applied to V19's base, this transistor conducts, charging C51 through the horizontal deflection yoke and starting the horizontal trace. At the same time, C52 is charged through T16, storing energy in both the transformer's winding and the capacitor. During this time, D4 is biased in its high-resistance (nonconducting) direction.

Once the initial pulse has passed, C52 can discharge through D4 and the

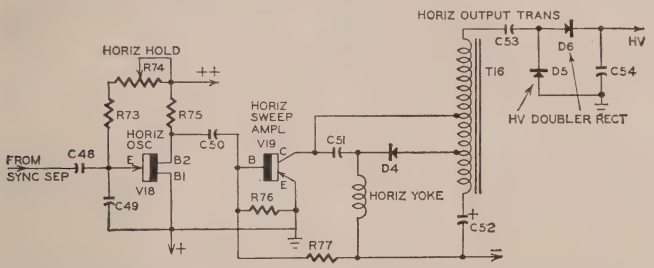

Fig. 11—Horizontal oscillator, horizontal output and high-voltage stages. A doubler rectifier and autotransformer are the major components in the high-voltage supply.

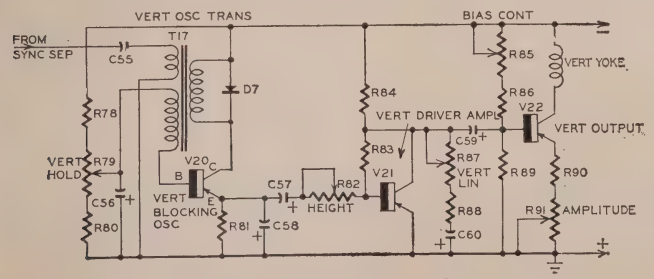

Fig. 12—The vertical sweep stages.

HOW TO BUILD A

Transistorized 40-watt supply

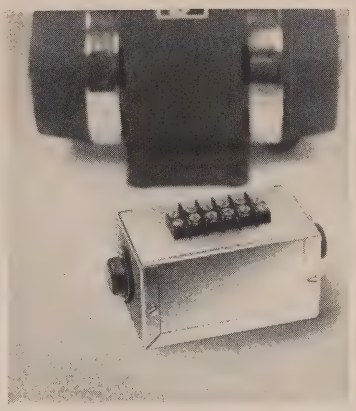

Easy to build, this modern power supply is as big in performance as it is little in size. Two CBS 2N256 power transistors, operating from a 12-volt battery, deliver 450 and 250 volts simultaneously. Combined output is 40 watts continuous service.

Features: compact and light . . . 85% efficient . . . instant-starting . . . cool-running . . . long-lived. No moving parts . . . vibrationless, noiseless and troublefree. You'll find this supply ideal for mobile or portable transmitter and/or receiver, sound system, etc.

Free Bulletin E-279 gives complete how-to-build-it details. Get it today with your 2N256 transistors from your CBS Tube distributor.

2N256...$1.50
2N255...$1.35

CBS-HYTRON

Semiconductor Operations, Lowell, Mass.
A Division of
Columbia Broadcasting System, Inc.

SHIPPED ON APPROVAL
NO MONEY WITH ORDER
NO C.O.D.

Model TD-55 — TUBE TESTER . . . Total Price $26.95 — Terms: $6.95 after 10 day trial, then $5.00 per month for 4 months.

Model TW-11 — TUBE TESTER . . . Total Price $47.50 — Terms: $11.50 after 10 day trial, then $6.00 per month for 6 months.

Model TV-12 — TRANSCONDUCTANCE TUBE TESTER . . . Total Price $72.50 — Terms: $22.50 after 10 day trial, then $10.00 per month for 5 months.

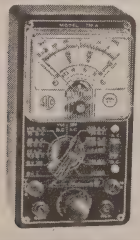

Model 770-A — VOLT-OHM-MILLIAMMETER . . . Total Price $15.85 — Terms: $3.85 after 10 day trial, then $4.00 per month for 3 months.

Superior's New Model TD-55
EMISSION TYPE TUBE TESTER

FOR { **The Experimenter or Part-time Serviceman,** who has delayed purchasing a higher priced Tube Tester.
The Professional Serviceman, who needs an extra Tube Tester for outside calls.
The busy TV Service Organization, which needs extra Tube Testers for its field men.

Speedy, yet efficient operation is accomplished by: 1. Simplification of all switching and controls. 2. Elimination of old style sockets used for testing obsolete tubes (26, 27, 57, 59, etc.) and providing sockets and circuits for efficiently testing the new Noval and Sub-Minar types.

You can't insert a tube in wrong socket
It is impossible to insert the tube in the wrong socket when using the new Model TD-55. Separate sockets are used, one for each type of tube base. If the tube fits in the socket it can be tested.

"Free-point" element switching system
The Model TD-55 incorporates a newly designed element selector switch system which reduces the possibility of obsolescence to an absolute minimum. **Checks for shorts and leakages between all elements**
The Model TD-55 provides a supersensitive method of checking for shorts and leakages up to 5 Megohms between any and all of the terminals.

Elemental switches are numbered in strict accordance with R.M.A. Specifications.
The 4 position fast-action snap switches are all numbered in exact accordance with the standard R.M.A. numbering system. Thus, if the element terminating in pin No. 7 of a tube is under test, button No. 7 is used for that test.

$26.95 NET

Complete with carrying case.....

Superior's New Model TW-11
STANDARD PROFESSIONAL TUBE TESTER

• Tests all tubes, including 4, 5, 6, 7, Octal Lockin, Hearing Aid, Thyratron, Miniatures, Sub-miniatures, Novals, Sub-minars, Proximity Fuse Types, etc.

• Uses the new self-cleaning Lever Action Switches for individual element testing. **All elements are numbered according to pin-number in the RMA base numbering system.**

• Model TW-11 does not use combination type sockets. Instead individual sockets are used for each type of tube. Thus **it is impossible to damage a tube by inserting it in the wrong socket.**

• Free-moving built-in roll chart provides complete data for all tubes. Printed in large easy-to-read type.

NOISE TEST: Phono-jack on front panel for plugging in either phones or external amplifier detects microphonic tubes or noise due to faulty elements and loose internal connections.

EXTRAORDINARY FEATURE
SEPARATE SCALE FOR LOW-CURRENT TUBES
Previously, on emission-type tube testers, it has been standard practice to use one scale for all tubes. As a result, the calibration for low-current types has been restricted to a small portion of the scale. The extra scale used here greatly simplifies testing of low-current types.

$47.50 NET

Housed in hand-rubbed oak cabinet

Superior's New Model TV-12
TRANS-CONDUCTANCE TUBE TESTER

★ **Employs improved TRANS-CONDUCTANCE circuit.**
An in-phase signal is impressed on the input section of a tube and the resultant plate current change is measured. This provides the most suitable method of simulating the manner in which tubes actually operate in Radio & TV receivers, amplifiers and other circuits. Amplification factor, plate resistance and cathode emission are all correlated in one meter reading.

★ **NEW LINE VOLTAGE ADJUSTING SYSTEM.**
A tapped transformer makes it possible to compensate for line voltage variations to a tolerance of better than 2%.

★ **SAFETY BUTTON**—protects both the tube under test and the instrument meter against damage due to overload or other form of improper switching.

EXTRA FEATURE
Model TV-12 Also Tests Transistors!
A transistor can be safely and adequately tested only under dynamic conditions. The Model TV-12 will test all transistors in that approved manner, and quality is read directly on a special "transistor only meter scale.

$72.50 NET

Housed in hand-rubbed oak cabinet

Superior's New Model 770-A
POCKET-SIZED VOLT-OHM MILLIAMMETER

USING THE NEW "FULL VIEW" METER
71% MORE SCALE AREA

Occupies exactly the same space used by the older standard 2½" Meters, yet provides 71% more scale area. As a result, all calibrations are printed in large easy-to-read type.

• Housed in round-cornered, molded case. Beautiful black etched panel.

6 A.C. VOLTAGE RANGES: 0-15/30/150/300/1500/3000 Volts • **6 D.C. VOLTAGE RANGES:** 0-7.5/15/75/150/750/1500 Volts • **2 RESISTANCE RANGES:** 0-10,000 Ohms, 0-1 Megohm • **3 D.C. CURRENT RANGES:** 0-15/150 Ma., 0-1.5 Amps. • **3 DECIBEL RANGES:** —6 db to +18 db, +14 db to +38 db, +34 db to +58 db.

$15.85 NET

Complete with test leads.....

USE APPROVAL FORM ON NEXT PAGE

We invite you to try before you buy any of the models described on this and the following page. If after a 10 day trial you are completely satisfied and decide to keep the Tester, you need send us only the down payment and agree to pay the balance due at the monthly indicated rate.

NO INTEREST OR FINANCE CHARGES ADDED!

If not completely satisfied, you are privileged to return the Tester to us, cancelling any further obligation.

TRY FOR 10 DAYS

before **you buy!**

then **if satisfactory pay in easy, interest free, monthly payments. See coupon below.**

Superior's New Model 77

VACUUM TUBE VOLTMETER

WITH NEW 6" FULL-VIEW METER

Compare it to any peak-to-peak V. T. V. M. made by any other manufacturer at any price!

- Model 77 completely wired and calibrated with accessories (including probe, test leads and portable carrying case) sells for only $42.50.
- Model 77 employs a sensitive six inch meter. Extra large meter scale enables us to print all calibrations in large easy-to-read type.
- Model 77 uses new improved SICO printed circuitry.
- Model 77 employs a 12AU7 as D.C. amplifier and two 9006's as peak-to-peak voltage rectifiers to assure maximum stability.
- Model 77 uses a selenium-rectified power supply resulting in less heat and thus reducing possibility of damage or value changes of delicate components.
- Model 77 meter is virtually burn-out proof. The sensitive 400 microampere meter is isolated from the measuring circuit by a balanced push-pull amplifier.
- Model 77 uses selected 1% zero temperature coefficient resistors as multipliers. This assures unchanging accurate readings on all ranges.

AS A DC VOLTMETER: The Model 77 is indispensable in Hi-Fi Amplifier servicing and a must for Black and White and color TV Receiver servicing where circuit loading cannot be tolerated.

AS AN AC VOLTMETER: Measures RMS values if sine wave, and peak-to-peak value if complex wave. Pedestal voltages that determine the "black" level in TV receivers are easily read.

AS AN ELECTRONIC OHMMETER: Because of its wide range of measurement leaky capacitors show up glaringly. Because of its sensitivity and low loading, intermittents are easily found, isolated and repaired.

SPECIFICATIONS

• **DC VOLTS** — 0 to 3/15/75/150/300/750/1,500 volts at 11 megohms input resistance. • **AC VOLTS (RMS)** — 0 to 3/15/75/150/300/750/1,500 volts. • **AC VOLTS** (Peak to Peak) — 0 to 8/40/200/400/800/2,000 volts. • **ELECTRONIC OHMMETER** — 0 to 1,000 ohms/10,000 ohms/100,000 ohms/1 megohm/10 megohms/100 megohms/1,000 megohms. • **DECIBELS** —10 db to + 18 db, + 10 db to + 38 db, + 30 db to + 58 db. All based on 0 db = .006 watts (6 mw) into a 500 ohm line (1.73v). • **ZERO CENTER METER** — For discriminator alignment with full scale range of 0 to 1.5/7.5/37.5/75/150/375/750 volts at 11 megohms input resistance.

Model 77 comes complete with operating instructions, probe and test leads. Use it on the bench — use it on calls. A streamlined carrying case, included at no extra charge, accommodates the tester, instruction book, probe and leads. Operates on 110-120 volt 60 cycle. Only ..... **$42.50 NET**

Model 77 — VACUUM TUBE VOLTMETER . . . Total Price $42.50 — Terms: $12.50 after 10 day trial, then $6.00 per month for 5 months.

Superior's New Model 76

ALL PURPOSE BRIDGE

IT'S A CONDENSER BRIDGE IT'S A RESISTANCE BRIDGE IT'S A SIGNAL TRACER IT'S A TV ANTENNA TESTER

Specifications

CAPACITY BRIDGE SECTION
4 Ranges: .00001 Microfarad to .005 Microfarad; .001 Microfarad to .5 Microfarad; .1 Microfarad to 50 Microfarads; 20 Microfarads to 1000 Microfarads. Will also measure the power factor of all condensers from .1 to 1000 Microfarads.

RESISTANCE BRIDGE SECTION
2 Ranges: 100 ohms to 50,000 ohms; 10,000 ohms to 5 megohms.

SIGNAL TRACER SECTION
With the use of the R.F. and A.F. Probes included with the Model 76, you can make stage gain measurements, locate signal loss in R.F. and Audio stages, localize faulty stages, locate distortion and hum, etc.

TV ANTENNA TESTER SECTION
Loss of sync., snow and instability are only a few of the faults which may be due to a break in the antenna, so why not check the TV antenna first? Locates a break in any TV antenna and measures the location of the break in feet from the set terminals. *Complete with R.F. and A.F. probes and test leads* ..... **$26.95 NET**

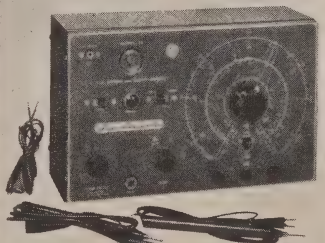

Model 76 — ALL PURPOSE BRIDGE . . . Total Price $26.95 — Terms: $6.95 after 10 day trial, then $5.00 per month for 4 months.

Superior's New Model TV-50

GENOMETER

7 Signal Generators in One!

- R.F. Signal Generator for A.M.
- R.F. Signal Generator for F.M.
- Audio Frequency Generator
- Bar Generator
- Cross Hatch Generator
- Color Dot Pattern Generator
- Marker Generator

R.F. SIGNAL GENERATOR: 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics
VARIABLE AUDIO FREQUENCY GENERATOR: Provides a variable 300 cycle to 20,000 cycle peaked wave audio signal.
BAR GENERATOR: Pattern consists of 4 to 16 horizontal bars or 7 to 20 vertical bars.
CROSS HATCH GENERATOR: The pattern consists of non-shifting horizontal and vertical lines interlaced to provide a stable cross-hatch effect.

DOT PATTERN GENERATOR (FOR COLOR TV): The Dot Pattern projected on any color TV Receiver tube by the Model TV-50 will enable you to adjust for proper color convergence.
MARKER GENERATOR: The following markers are provided: 189 Kc., 262.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc., (3579 Kc. is the color burst frequency.) *Complete with shielded leads . . .* **$47.50 NET**

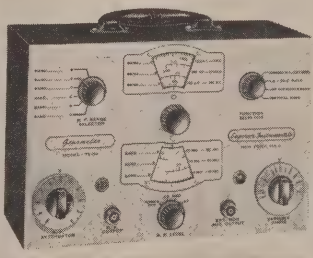

Model TV-50 — GENOMETER . . . Total Price $47.50 — Terms: $11.50 after 10 day trial, then $6.00 per month for 6 months.

MOSS ELECTRONIC DISTRIBUTING CO., INC.
Dept. D-475, 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked on approval. If completely satisfied I will pay on the terms specified with no interest or finance charges added. Otherwise, I will return after a 10 day trial positively cancelling all further obligation.

Name .....

Address .....

City .....Zone....State.....

All prices net, F.O.B., N.Y.C.

- ☐ **Model TD-55** .....**Total Price $26.95 $6.95 within 10 days. Balance $5.00 monthly for 4 months.**
- ☐ **Model TW-11** .....**Total Price $47.50 $11.50 within 10 days. Balance $6.00 monthly for 6 months.**
- ☐ **Model TV-12**.....**Total Price $72.50 $22.50 within 10 days. Balance $10.00 monthly for 5 months.**
- ☐ **Model 770-A** .....**Total Price $15.85 $3.85 within 10 days. Balance $4.00 monthly for 3 months.**
- ☐ **Model 77**.....**Total Price $42.50 $12.50 within 10 days. Balance $6.00 monthly for 5 months.**
- ☐ **Model 76**.....**Total Price $26.95 $6.95 within 10 days. Balance $5.00 monthly for 4 months.**
- ☐ **Model TV-50**.....**Total Price $47.50 $11.50 within 10 days. Balance $6.00 monthly for 6 months.**

win a dream trip for two

to the

RK-22

BRUSSELS WORLD'S FAIR!

win other exciting prizes... in the big, new Rek-O-Kut contest!

Rek-O-Kut's exciting, new contest is a music-lover's delight! You can win a trip for two to the Brussels World's Fair via Sabena Belgian World Airlines... magnificent Rondine turntables... and turntable arms... just by listening to a Rek-O-Kut demonstration. Simply stop in at your high fidelity dealer, ask him to demonstrate high fidelity reproduction on a Rondine turntable, and fill out an entry blank. There are no puzzles to solve — no jingles to write — no coupons to clip — nothing to buy! You'll be eligible for one of the big contest prizes... and you'll have enjoyed music reproduction at its finest — on a Rondine! Prices from $59.95.

Selected for display at the American Pavilion, Brussels World's Fair!

For the high fidelity dealer nearest you, write:

REK-O-KUT COMPANY, INC.
38-19 108th Street, Corona 68, New York

TELEVISION

horizontal yoke, continuing the horizontal trace. The transistor (V19) is *not* conducting at this time and, for practical purposes, is no longer part of the circuit. Finally, as C52 is discharged, the energy stored in T16 is suddenly released as the magnetic field built up during the initial current surge collapses. This strong pulse, applied to the deflection yoke, develops the necessary retrace signal. The circuit then receives another pulse from V18 and the action is repeated.

The retrace pulse developed by T16 is stepped up by autotransformer action and fed through C53 to a voltage-doubling rectifier circuit consisting of high-voltage semiconductor diodes D5 and D6 and filter capacitor C54. The high dc voltage developed across C54 is, in turn, applied to the CRT.

The circuit for a vertical sweep circuit is given in Fig. 12. This section consists of a blocking oscillator (V20), a driver amplifier (V21) and a vertical output stage (V22). All three use p-n-p transistors in the common-emitter configuration.

In operation, T17 is the blocking oscillator transformer. Two windings provide feedback between collector and base circuits to start oscillation, while a third winding is used to inject the sync-pulse signal obtained from the sync separator. The vertical sync pulse is applied to the third winding through dc blocking capacitor C55.

The blocking oscillator's basic repetition rate is determined by its base bias current and by the R-C time constant in its base circuit. The circuit's time constant is determined by the setting of R79, by R80 and by C56. R79's setting also determines base bias and hence this potentiometer becomes the vertical hold control.

Diode D7, across T17's primary, bypasses the unwanted half cycle of the blocking oscillator's pulse.

A sawtooth signal is developed across C58 as this capacitor is charged rapidly through V20 and discharged slowly through R81. This signal is coupled through C57 and R82 to the base electrode of the driver amplifier (V21). R82 provides a basic amplitude adjustment and thus serves as a height control. Base bias for this stage (V21) is supplied through collector load resistor R84 and base resistor R83.

The amplified and inverted signal appearing across R84 is coupled through capacitor C59 to output amplifier V22. The network consisting of potentiometer R87, fixed resistor R88 and capacitor C60 is included to provide a linearity adjustment; R87 is the circuit's vertical linearity control.

Base bias for the output amplifier is furnished by a voltage divider made up of potentiometer R85 and fixed resistors R86 and R89. R85 can be adjusted to provide optimum bias for the output stage whenever it is necessary to replace the vertical output transistor (V22). Unbypassed emitter

TRIO'S 1958 ZEPHYR FAMILY OF ANTENNAS

FOR DISTANCE

FOR EXTREME DISTANCE

FOR THE MAXIMUM

U.S. PATENT No. 2,772,413
CANADIAN PATENT No. 541,670

EXTENDED "WING" DIPOLE
"WING" DIRECTOR
COLLINEAR DIRECTOR
STAGGER - TUNED

TRIO® Manufacturing Company
GRIGGSVILLE, ILLINOIS

Export Sales Div.,
Scheel International Inc.,
5909 N. Lincoln Ave., Chicago, U.S.A.
Cable Address: HARSCHEEL

resistors R90 and R91 help stabilize circuit operation. One of these resistors (R91) is made adjustable and serves as an additional amplitude control.

The vertical deflection yoke is direct-coupled to V22 and is its collector load. In this application, V22 is operated as a class-A power amplifier. As a result, the vertical deflection signal includes a large dc component which would normally shift the CRT's raster far to one side. This shift is corrected by placing small ceramic recentering magnets longitudinally in the vertical yoke's window.

To sum up

The transistor TV circuits we have discussed are based on circuits which have been investigated theoretically, studied experimentally and, in some cases, used in experimental transistor television receivers. They do not necessarily represent the final circuits which will be used when such sets are in full production. The development and manufacture of new types of semiconductor devices could result in considerable changes in basic circuit philosophy.

For example, the invention of an extremely high-gain high-frequency transistor could reduce the number of stages needed in the video if and video amplifier sections. Similarly, the development and manufacture of a semiconductor picture-reproducing device which could be used in place of a cathode-ray tube would require entirely different sweep circuitry and probably would eliminate the need for a high-voltage supply.

Finally, there are the day-to-day changes in television broadcasting. With the increased interest in color television, there is the real possibility that the first commercially produced all-transistor TV receivers will be color sets. There is also the possibility that some manufacturer, taking advantage of the sales appeal and public interest in transistors, may introduce a partially transistorized (or hybrid) set well in advance of an all-transistor reciever. END

Bibliography

Application Notes on the Surface Barrier Transistor. Sprague Electric Co.

Transistors I. RCA Laboratories.

Joseph Chernof, "Design Features of a Transistor Sweep Circuit," *Electronic Equipment*, July, 1957.

Flory, Gray, Morgan and Pike, "Miniature ITV Camera Uses Drift Transistors," *Electronics*, January, 1957.

Louis E. Garner, Jr., *Transistor Circuit Handbook* (Sams).

Louis E. Garner, Jr., "Using the Unijunction," RADIO-ELECTRONICS, July, 1957.

Walter B. Guggi, "CRT Deflection Circuit Has High Efficiency," *Electronics*, April 1, 1957.

D. W. Baker, "High-Frequency Circuits Use Meltback Tetrodes," *Electronics*, June 1, 1957.

M. J. Hellstrom, "Design Considerations in Transistor Vertical Deflection," *Electronic Equipment*, June, 1957.

Lloyd P. Hunter, *Handbook of Semiconductor Electronics* (McGraw-Hill).

Richard B. Hurley, "Designing Transistor Circuits – Video Amplifiers," *Electronic Equipment*, May, 1957.

W. Palmer and G. Schiess, "Transistorized Vertical Deflection System," *Electrical Design News*, May, 1957.

Richard F. Shea, *Transistor Circuit Engineering* (Wiley).

Just 2 settings on the NEW

Model FC-2

FAST-CHECK TUBE TESTER

tests over 600 tube types completely, accurately ... AND IN SECONDS!

SIZE:
H: 11¼"
W: 14⅝"
D: 4⅜"

• NO MULTIPLE SWITCHING
• NO ROLL CHART CHECKING

NEW Special compartment to accommodate line cord and CRT Test Adapter cable

CANNOT BECOME OBSOLETE

Engineered to accommodate all future tube types...new tube listings furnished periodically.

TRY THE FC-2 BEFORE YOU BUY IT!

Shipped on approval for FREE 10 day trial... No obligation to buy

EASY TO BUY IF YOU'RE SATISFIED!

Pay in small monthly payments at net cash prices... no financing charges

MODEL FC-2—housed in rugged oak carrying case complete with CRT adapter, tube listings..... only $69.50 Net

GUARANTEED FOR 1 FULL YEAR

This extremely low price is made possible only because YOU ARE BUYING DIRECT FROM THE MANUFACTURER

The FAST-CHECK enables you to save valuable time and eliminate unprofitable call backs. You earn extra money and win confidence by showing your customer the actual condition and life expectancy of the tube on the large meter scale of the FC-2. The extra tubes you will sell each day will pay for the FAST-CHECK in a very short time.

WIDE RANGE OF OPERATION

- Checks quality of over 600 tube types ... more than 99% of all TV and radio tubes, including the newest series-string TV tubes, auto 12 plate-volt tubes, OZ4s, magic eye tubes and gas regulators.
- Checks inter-element shorts and leakage.
- Checks for gas content.
- Checks for life expectancy.

IMPORTANT FEATURES

✓ Checks each section of multi-section tubes and even if only one section is defective the tube will read "Bad" ✓ 41 long lasting phosphor-bronze tube sockets accommodate all present and future tube types—cannot become obsolete ✓ Less than 10 seconds required to test any tube ✓ Large D'Arsonval type meter is extremely sensitive yet rugged—is fully protected against accidental burn-out ✓ Line isolated ✓ 7-pin and 9-pin straighteners conveniently mounted on panel ✓ Quick reference tube chart lists over 600 tube types ✓ Line voltage compensation

NEW A specially designed PICTURE TUBE ADAPTER cable is now part of the FC-2 ... making it a highly efficient CRT Tester-Rejuvenator. This feature eliminates the need of carrying extra instruments and makes the FC-2 truly an all-around tube testet. The adapter enables you to check all picture tubes (including the new short-neck 110 degree picture tubes) for cathode emission, shorts and life expectancy .... also to rejuvenate and restore cathode emission of weak picture tubes.

WHAT SERVICEMEN* are SAYING ABOUT THE FC-2

"You've really made tube testing a snap" ... "I've almost got the cost of the Fast-Check paid off with the extra money I've made, and it's only 2 weeks since I received it" ... "It's easier to use than you said" ... "I wouldn't ever want to be without it" ... "I use it in the shop and take it along on every call".

*Names on request

MAIL COUPON NOW—NO MONEY REQUIRED WITH ORDER

CENTURY ELECTRONICS CO., INC.

111 Roosevelt Avenue
Dept. 106, Mineola, N.Y.

Please rush the new Model FC-2 FAST-CHECK TUBE TESTER for a 10 day trial period. If I am not completely satisfied I will return the instrument within 10 days without further obligation. If fully satisfied I agree to pay the down payment within 10 days and the monthly installments as shown. No financing charges are to be added. Should I fail to make payment when due, the unpaid balance shall become due and payable at once.

☐ BUDGET TERMS: Pay $14.50 within 10 days after receipt of instrument. Balance $11.00 monthly for 5 months, plus shipping charges.

☐ PREPAID TERMS: Enclose $69.50 with coupon as payment in full and Century will pay all shipping costs. 10 day money-back guarantee.

Name.....

Address.....

City.....State.....

ABSOLUTELY NO RISK ON YOUR PART

New look in indoor antennas

Electrical tuning, a 72–300-ohm matching network and small size are featured in this indoor TV antenna

By LARRY STECKLER
ASSISTANT EDITOR

(Top) Antenna elements are partially raised after the case has been opened. Tuning is adjusted with the little lever in the front. Bottom view shows the tuned coils and four-conductor matching network.

A NEW type of indoor TV antenna is now on the retailer's shelves. Called Vi-Fi (short for *Video-Fidelity*), it is different in both design and appearance—even has a flip-top box.

At the heart of this antenna are two coils wound on a common form and spaced about 3 inches apart. The inductances of these coils are simultaneously varied by an adjustable ferrite core. This electrically compensates for any variation from the theoretical element length. With previous types of indoor antennas, the length of the elements had to be adjusted or a multiple-position switch set to bring in the best picture.

The Slide Rule tuner (adjustable ferrite core) in the Amphenol Vi-Fi antenna permits adjustment without touching the elements, a major problem with some types of indoor antennas. When you touch the elements, the added body capacitance may result in an improper adjustment of antenna length. When you remove your hand, the picture fades away or distorts in one way or another. None of this takes place with the Vi-Fi. Coil matching also allows shorter elements—only 27 inches when extended.

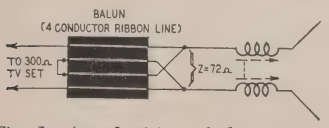

Fig. 1—Actual wiring of the antenna, matching network and tuning coils.

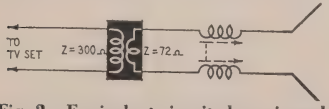

Fig. 2—Equivalent circuit shows impedance transformation from 72–300 ohms.

Another problem is matching the antenna to the set. The natural impedance of a dipole is approximately 72 ohms. The usual input impedance at a TV receiver's antenna-input terminals is 300 ohms. For best results the antenna's impedance must match the set's.

There are two ways to do this—either the dipole must be folded, increasing its impedance to 300 ohms, or some kind of matching network or transformer must be used. As a folded dipole is impractical and a matching transformer is bulky and expensive, a simple matching network is employed.

This network consists of a length of four-conductor ribbon line, which due to its construction transforms the dipole's 72-ohm impedance to 300 ohms. The actual wiring of this network is shown in Fig. 1 and the effective circuit in Fig. 2.

When tested in several metropolitan locations, the results were very satisfactory. It pulled in sharp, ghost-free signals with a high signal-to-noise ratio. Simply adjusting the Slide Rule tuner cleared up ghosts and snow in many instances.

The primary or local area for television reception is rapidly expanding due to increased station power output and improved receiver sensitivity. In many areas, the outdoor antennas, which pioneered the way for television, are fast becoming old and dilapidated. In many of these instances the old roof antenna can be replaced by a new indoor unit with excellent results. The Vi-Fi was designed to fit these conditions.

Since the elements of an indoor antenna need be extended only when in use, the antenna housing is designed so that the elements can be collapsed and folded down into the case when not in use. A roll-up type dust cover (flip-top box) was added so the case could be closed, and the antenna takes on the appearance of a cigarette or jewelry box.

As an aid to orientation, the element sockets are the ball joint type, allowing 360° rotation. Two angle brackets, provided with the antenna, permit back-of-the-set installation. Since back-of-the-set mounting is not always feasible, plastic feet are fastened to the bottom cover so the antenna can also be used on top of the set. The housing comes in three decorative colors, one of which will blend with your color scheme. END

To AVOID amplifier and speaker WASTE... choose from

4 University WIDE-ANGLE SPEAKERS

For uniform dispersion of sound over a wide area

CHOICE OF 5 DRIVERS FOR CLH OR COBREFLEX

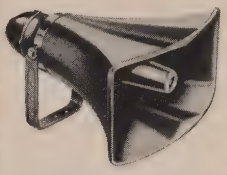

CLH 4½ ft. air column. Exclusive omni-directional bell and mounting bracket helps "tune out" reverberation and "dead spots." $44.50 list.

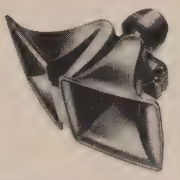

COBREFLEX All die-cast aluminum one piece construction resists a life-time of physical abuse. 2½ ft. air column. $38.33 list.

CIB Built-in hermetically sealed driver. Excellent for "talk-back." Exclusive Positive-Lok omni-directional mounting bracket. $42.00 list.

CMIL Smaller than CIB, perfect for voice. Built-in driver packs mighty wallop at low input power. Ideal for close quarter installations. $29.75 list.

MA-25 $27.50 list
85-6500 cps. 25 W.

SA-HF $36.00 list
80-10,000 cps. 30 W.

SA-30 $47.50 list
built-in matching trans.
80-10,000 cps. 30 W.

PA-HF $47.50 list
70-10,000 cps. 50 W.

PA-50 $57.50 list
built-in matching trans.
70-10,000 cps. 50 W.

Only University gives you the choice of speakers you need to ensure greatest economy of amplifier power, equipment and installation costs. No wasteful, "cure-all, do-all" compromises here. Each speaker is designed to do its specific kind of job most efficiently and reliably, with plenty of room for future expansion. Each speaker incorporates many *exclusive* features to fulfill every possible application. The chart below graphically shows the relative differences between these four speakers in terms of sound output, input power, and low frequency response. Simply choose the intended application and determine the appropriate speakers. Or, depending upon existing operating prerequisites, select the speaker(s) capable of doing the job. That's all there is to it.

NOW AVAILABLE—Free Product Catalog. Or send $1 for the *NEW* 64-page University TECHNILOG, the complete speaker system planning manual. Desk J-4, University Loudspeakers, Inc., 80 S. Kensico Ave., White Plains, N.Y.

Background Noise Level in db	Average Typical Application (CHART A)
90	FACTORY (Very Noisy)
	MACHINE SHOP (Average)
80	PRINTING PRESS
	BALLROOMS
	RESTAURANT (Noisy)
	NOISY ASSEMBLY DEPT.
	FACTORY (Average)
75	R.R. WAITING ROOM
	AUDITORIUM (Average)
	ASSEMBLY PLANT (Quiet)
70	
	SHIPPING-REC. (Average)
	OFFICE (Busy)
65	DEPT. STORE (Average)
	AUDITORIUM (Quiet)
60	RESTAURANT (Average)
	STORE (Quiet)
	OFFICE (Quiet)
	GARAGE
	HOTEL LOBBY—HOSPITALS
55	CHURCH—FUNERAL PARLOR

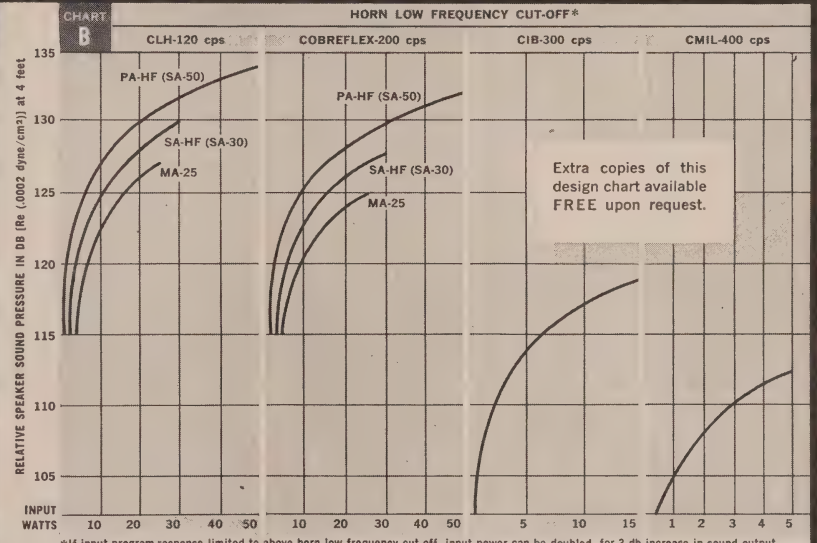

*If input program response limited to above horn low frequency cut-off, input power can be doubled, for 3 db increase in sound output.

HOW TO USE THIS CHART

1. Determine sound pressure needed by finding noise level from Chart A, add loss of db in Table C and add adjusting factor in Table D.
2. Draw horizontal line across Chart B corresponding to the db figure just calculated. This now establishes which speakers can be considered.
3. A vertical line drawn to the base of Chart B shows the input power needed for each qualifying speaker.
4. Now, further selection may be based upon frequency response necessary (see Horn Cut-Off, Chart B), initial cost, operating economy and reserve power desired.
5. The CIB and CMIL may also be used in high noise levels by employing several throughout the listening area.

Example: Factory — noise level 90 db, 320,000 cu. ft., live acoustics, music and speech
90+25+5=120 db required

Qualifying speakers are CLH or Cobreflex, with any of the drivers. Final choice is determined by driver characteristics and installation problems. (Send for TECHNILOG or Product Catalog.)

TABLE C	INDOORS			OUTDOORS	
ROOM VOLUME	DB LOSS			FURTHEST	
CU. FT.	LIVE	NEUTRAL	DEAD	DISTANCE FT.	DB LOSS
1,000	0	3	6	4	0
3,200	5	8	11	8	6
10,000	10	13	16	16	12
32,000	15	18	21	32	18
100,000	20	23	26	64	24
320,000	25	28	31	128	30
1,000,000	30	33	36	256	36

TABLE D		INDOORS DB	OUTDOORS DB
PROGRAM ADJUSTING FACTOR	SPEECH	4	7
	MUSIC	6	11
	MUSIC & SPEECH	5	9

LISTEN *University® sounds better*

COMMERCIAL—INDUSTRIAL

FACTS and FALLACIES in COLOR TV SERVICE

by ROBERT G. MIDDLETON

Some things we have learned carefully just ain't so!

The Fallacy	The Fact	Discussion
Color burst can be observed on a narrow-band scope if a demodulator probe is used.	**The burst signal is not displayed.**	The test fails because the *demodulating capability* of conventional demodulating probes is limited. Such probes are OK for sweep-frequency tests of chroma circuits, in which the modulation envelope has a 60-cycle repetition rate. However, they fail in burst-signal tests in which the modulation envelope has a 15,750-cycle repetition rate and a low duty cycle. *Use a wide-band scope with a low-capacitance probe.*
A scope is unsuitable for color TV service if it uses peaking coils in the vertical amplifier.	**Chroma waveform displays are unaffected by peaking coils.**	Wide-band scopes which use series and shunt peaking coils in the vertical amplifier are much less costly than those using distributed amplifiers. The assumption that a scope which uses peaking coils is unsuitable for color TV tests arises from the fact that such a scope will *ring* on square-wave signals that have a *very fast rise*. All chroma waveforms have a relatively *slow rise time* and *a wide-band scope with series and shunt peaked amplifiers is completely satisfactory for color TV tests.*
Individual cycles in the burst can be counted if a good scope is applied at the picture detector output.	**It is usually impossible to display the individual cycles of the burst signal at the output of the picture detector.**	The inability to display individual cycles of the burst signal at the output of the picture detector results from signal degradation by noise, cross-modulation with the sound signal, crosstalk with the sweep circuits and residual hum voltage. *Individual cycles of the burst signal can be counted only when the output from a color bar generator is viewed directly, prior to passage through the receiver signal circuits.*
Only a volt-ohmmeter is necessary for service in chroma circuits in a color TV receiver.	**A volt-ohmmeter provides only preliminary test data. Good generators and scopes are essential for testing and adjusting chroma circuits properly.**	Correct color reproduction depends greatly upon careful alignment of the chroma bandpass amplifier, burst amplifier, quadrature transformer and reactance tube circuits. For this purpose a good (crystal-controlled) color bar generator, wide-band scope, sweep generator with *flat* signal output and accurate (crystal-calibrated) marker generator are essential. The sweep generator must provide extended low-frequency output down to at least 40 kc, and preferably to 15 kc.
A white dot generator must also provide cross-hatch output to be useful in convergence procedures.	**An equally good convergence job can be accomplished whether cross-hatch output is available or not.**	Cross-hatch output is a *convenience* in preliminary convergence adjustments. For example, it is somewhat easier to adjust the vertical columns into parallel lines, and the horizontal rows into parallel lines when cross-hatch is used, because incidental displacement of *dots* may be a confusing situation to the beginner. *Final* convergence, however, *must* be accomplished upon the basis of a *dot* pattern. Cross-hatch *complicates* these final adjustments.
Good color reception can be obtained only if the antenna is very accurately oriented.	**Extremely accurate orientation is not required. However, it is often helpful to use an antenna rotator if color programs are available on more than one channel.**	The assumption that highly accurate antenna orientation is required for color reception arises from the fact that ghosts are more objectionable in color than in black-and-white. To the extent that an antenna rotator will minimize ghost signals, it will be found valuable in color TV reception.

The Fallacy	The Facts	Discussion
Impedance matching is mostly a joke and does not need to be considered in practical work.	Impedance matching is often a serious problem in color reception and a poor match may result in complete loss of color.	Careless routing of the lead-in, branching of the lead-in to two or more receivers, faulty lightning arresters, a break in one side of the lead-in or faulty input circuits to the front end will often attenuate the color burst to such an extent that color sync drops out and color reproduction cannot be obtained.
Any antenna that provides good black-and-white reception is OK for color reception.	Often untrue. If the black-and-white signal is analogous to the bass notes on a piano, the color burst and signal are analogous to the treble notes. Both low and high frequencies must be accommodated.	Sharply tuned high-gain antennas, such as single-channel multi-element Yagis are least likely to provide good color reception although they are good for black-and-white. *Broad-band* Yagis, on the other hand, usually provide good color reception. Any antenna with *flat* response over the received channel, plus a noise-free signal, will deliver a good color picture.
If there are standing waves on the lead-in, the line can be cut to a critical length to obtain color reception.	True for one channel. If more than one color station is to be provided for, this expedient often fails to give satisfactory reception on *both* channels.	When standing waves are present on the lead-in, causing the length of the line to become a critical factor, the proper procedure is to repair or replace the front end to obtain proper impedance match to the lead-in. Remember that discontinuities in the lead-in *installation* can cause the line length to become critical, in spite of the fact that the front end may be accurately matched to the line impedance.
The bandwidth of the chroma bandpass amplifier in an (R − Y) (B − Y) receiver can be broadened beyond 0.5 mc to obtain more color detail in the picture.	The assumption is true but the adjustment is a compromise of conflicting factors. (See discussion.)	When the response of the chroma bandpass amplifier is increased substantially beyond 0.5 mc in an (R − Y) (B − Y) receiver, it will be noted that although chroma detail improves the trailing edges of objects in the picture (during color reception) develop horizontal streaks or spikes. These spurious spikes are due to crosstalk between the Y and chroma channels.
If the color-phasing control is adjusted correctly for reception on one channel, it will not require readjustment on other channels.	True only in special cases. In general, it is necessary to readjust the color-phasing control when the receiver is switched to another channel.	Readjustment is usually required because the antenna may have an upward-sloping characteristic on one channel and a downward-sloping characteristic on another. Discontinuities in the lead-in and impedance mismatch to the tuner often cause a change in the standing-wave pattern on the lead-in from channel to channel. The frequency response of the tuner may also differ from channel to channel. These variations cause a *phase shift* in the chroma signal, which may require readjustment of the color-phasing control to compensate for the shift.
The color picture tube is so sensitive to stray magnetic fields that setup adjustments must always be made if the receiver is moved to another place in the room.	Sometimes true but not necessarily so. Whether purity is greatly affected depends upon local conditions.	The amount of variation in stray magnetic fields about a room may be small or large in different situations. Some buildings contain extensive steel construction, while others have practically none. Stray magnetic fields are usually found in the vicinity of iron pipes, conduit, steam radiators and floor furnaces. No hard-and-fast rule can be laid down concerning stray magnetic fields in residences or shops.
Color TV is developing so fast that test equipment available today may become obsolete tomorrow.	True only for certain special types of instruments. No matter what receiver designs are adopted, 90% of present-day equipment will always be essential.	The vast majority of test instruments are designed for the NTSC signal, which *all* receivers process in one manner or another. Accordingly, the wide-band (4-mc) scope, NTSC color bar generator and standard sweep alignment equipment cannot possibly become obsolete. However, the white dot generator could become unnecessary if a one-gun color picture tube is finally perfected.
It is so difficult to learn about color TV that it is best to have nothing to do with it.	A very short-sighted attitude. Operators of horseshoeing shops sometimes took a similar attitude toward the automobile back in 1912.	It is no more difficult for a technician versed in black-and-white TV servicing to become proficient in color service than it was for radio technicians to master the new conceptions presented by black-and-white TV. Some who have cleared the new hurdle say that it is actually easier.
You can save yourself a lot of headaches by talking down color TV to your customers.	This business practice is aptly termed "knocking yourself out." You might as well spend time each day tossing money out the window.	Color TV servicing is a new high-profit market. People expect to pay more for color service. They expect the receivers to require more frequent attention. And surprisingly enough, in the present market, customers are not highly critical of reception quality. The only headache is the time and effort required to learn the new technology. *Don't be a buggy-whip peddler in the automobile era.* END

AEROVOX MICA CAPACITORS

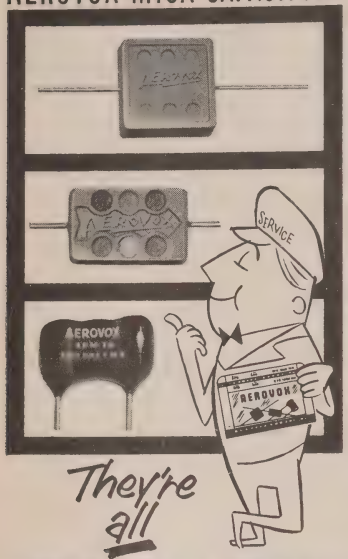

They're all

"TROUBLE-FREE"

CAPACITORS

Smart servicemen refuse to take risks . . . That's why technicians everywhere use and depend on Aerovox mica capacitors for "trouble-free" operation. Your local Aerovox Distributor stocks the complete line of Aerovox mica capacitors including all the popular types commonly used in service work.

POSTAGE STAMP MICAS

Types 1468LS and 1469 for those general applications are the smallest axial lead micas available. Ideal for critical applications such as horizontal or vertical oscillators. All units are color-coded and stamped with capacity value.

HIGH VOLTAGE MICAS

Types 1468LS-HV and 1467LS-HV are designed especially for TV and low power transmitters and power amplifier applications. These units feature the highest voltages available in these case sizes. Units are marked with capacity and working voltage and are tested at double the rated voltage to insure long-life.

PLASTIC-COATED, DIPPED-MICAS

Types ADM-15, 19 & 20 are superior in many instances to conventional molded units. High operating temperatures, excellent long-life characteristics, ideal for printed-wiring assemblies. Smaller physical sizes with unsurpassed performance and stability features.

AEROVOX CORPORATION

DISTRIBUTOR DIVISION

NEW BEDFORD MASSACHUSETTS

tv dx

By ROBERT B. COOPER, JR.

IT took a little while, but it finally happened. F2 skip made the big jump across the United States, bringing what is probably the first reception of this type ever recorded on a transcontinental basis. The period of Jan. 1–9, 1958, saw transcontinental skip between such places as Nova Scotia, Maine, New York, Montreal, Pennsylvania and the western United States —Washington, Oregon and northern California. Although most reception consisted of video only, channel 2, some northern California dxers did manage to sneak in a few minutes of audio at reception peaks.

Eddie Albright of Medford, Ore., reports his first F2 on Jan. 9, between 1100 and 1430 PST of what appeared to be CKCW, Nova Scotia. The audio portion of Eddie's channel 2 was completely obliterated by amateur 6-meter stations in Ohio, New York, Pennsylvania and New England. Some of the longest 6-meter TVI we have heard of!

James Scalvini of Ferndale, Calif., fared somewhat better, noting channel 2 reception like clockwork every day Jan. 1–9, excepting Jan. 2, between 0900 and 1100 PST. Reception would last 15 minutes to over an hour. Video reception was very distorted with multiple ghosting, continually changing phase relationships, all of which made viewing bad.

Going from West Coast observers to Nova Scotia, Canada, dxer Ronald Boyd of Truro, Nova Scotia, has had some very good luck in logging a Russian channel 2 station, BBC channel 3 (on our channel 2) and many tentatively identified stations from Germany, France, Italy and elsewhere. Dx was peaking nicely during the first three days of this year, but dropped off considerably around the middle of January. Such reception is gone for US and Canadian observers until next fall.

From the looks of current sunspot count information, the best F2 TV dxing for the current 11-year sunspot cycle should have occurred during November, 1957, and January, 1958. The peak average spot count appears to have been reached and a gradual descent is expected for the next few years. European reception should be very good again this fall, however. Skip is reported to have reached as high as 70 mc between Europe and parts of the Atlantic coast on two occasions this past fall, the highest values ever recorded (see chart).

Looking from the other end, we have on hand a report from Murilo Rodrigo Marques Lopes, employed at Radio Free Europe, in Portugal. During the first weeks of November, 1957, Murilo reports strong but badly ghosted reception from what appears to have been WCBS-TV, New York; WGR-TV, Buffalo, and WGBH-TV, Boston, Mass. Dxer Lopes uses a dx setup worthy of the name, with complete switchable gear for all known world standards.

During the summer of 1957, frequent daily reception was noted from many European countries (on E skip), lots of good trops and now some F2. We hope to have Es reports from him this summer for a comparison between Es conditions on the two continents.

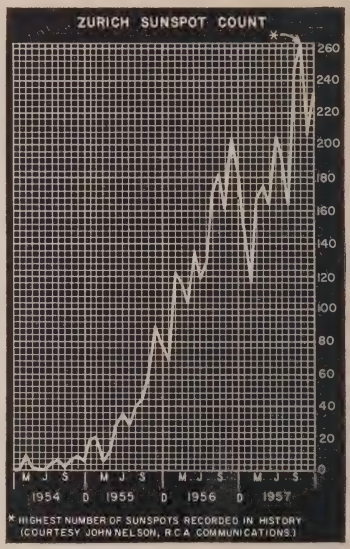

The Zurich number is compiled at the Federal Swiss Observatory and is a weighted figure representing the daily average number of sunspots observed each month.

E skip: Winter, 1958

Not to be left out, some E skip was reported during the first two months of this year, occurring for the most part during January. Jan. 3 appears to have been very good throughout the country. Dxer Ronald Boyd notes Jan. 3 as being on a par with anything seen at his location during the summer months. Es got as short as 430 miles for Ron (to Boston) while on the West Coast, KBOI-TV, channel 2, Boise, Idaho, was seen in Medford, Ore., by Eddie Albright, a short 330 miles for E skip. Such short skip is known as an occa-

sional summer-time phenomenon, and is seldom noted in the winter.

February, 1958, has produced only one reported opening, occurring over a very southerly path from Malibu, Calif., to Harlingen, Tex., and Mexico City, Mexico. Mr. Jack F. Harris reports this skip during the evening of Feb. 8.

Although many brilliant auroral displays have been noted by visual observers, auroral dx on the television channels has been conspicuous by its absence. Again turning to Nova Scotia, Ronald Boyd of Truro notes identification of WSYR-TV, channel 3, Syracuse, N.Y., several times on Dec. 31, actually lasting all day from early morning (0630) till late evening. Another observation of daytime aurora (something which cannot be seen visually but must be tracked by radio reflection) occurred in the early morning of Jan. 1. CBFT, Montreal, was logged several times, with another patch of auroral skip around midnight. WBBM-TV, channel 2, Chicago, popped through on what appears to have been aurora-Es at midnight on the first. This picture was strong, although accompanied by violent fading and bad ghosting. We are still soliciting detailed reports of similar east–west hauls made during aurora.

A brilliant visual display on the evening of Feb. 10 and the morning of the 11th was reported as far south as Miami, Mexico, and Los Angeles. The same disturbance was also active in the southern hemisphere producing an Aurora Australis, seen over wide areas in the South Pacific. Dx reports for this period do not show any TV effects however.

Meteor-scatter dx

Ed Prond, Dolton, Ill., and John Cody, Middleton, Conn., are two dxers who don't quit just because E skip ceases to be a daily occurrence or trops drop below par. Both managed to add to their station totals during January. Dxer Prond added 4 stations and Cody a whopping 11 new stations, all logged via meteor scatter. If you are new to the dxing game, we suggest you consult back copies of the TV DX column for more information on meteor-scatter dxing.

In our January listing of total number of stations logged by dxers, and the *Over 50 TV DX Club*, some confusion has been reported by readers. When first writing to this column, please include a list of your totals, broken down channel by channel, of every station logged by you in your dxing career. Dates and times of these back loggings are not required, although helpful to us. Your initial report, to which we add your monthly reports, is kept on file. If you keep your monthly reports coming in on schedule, listing all dx seen over the 30-day period, your totals will automatically appear up to date and be complete in the once-a-year-totals listing.

In counting a station which has changed call letters, channels, locations, etc., we find the following method best. If the station in question changes channels (thus creating a new set of interference conditions), it is permissible to count the station as a new logging. Moving the transmitter location 10 miles or more also allows you to add the station to your log again. But mere changes in call letters, power increases, etc. do not constitute a new station.

Predictions

With the normal E-layer skip occurring in May and June, the chances for high-band burst reception (channels 7–13) is greatly increased when we have a strong E-skip opening coinciding with a strong meteor shower. With skip running as high as channel 6 (88 mc) over a 1,200-mile path, a meteor shower entering the E layer during the skip session may push burst reception into channels 7–13 with amazing frequency.

Before this reaches the newsstands, E-layer skip should be occurring on a fairly regular basis, providing dxers with frequent reception of low-band channels 500–1,500 miles distant. During the first two weeks of May, E skip is likely to occur from 1600–2100 local time. Moving on toward the end of May, Es follows no set pattern, occurring most anytime during the day and night. Watch vacant channels or those with fringe reception for signs of stations or interference from antenna headings not normally productive of a station. Reception via multihop E skip should be possible to Venezuela, Puerto Rico and Brazil during the second and third weeks of May, around 1700–2000 local time (channels 2–4). June and E skip are almost synonymous. Any time, any direction, any of the low-band channels the rule, not the exception.

Ground-wave reception increases greatly as the warmer months approach. With temperature inversions occurring almost daily, in the early morning and around sundown, general reception will probably increase 100 miles on low-band vhf, 150 miles on high-band vhf and 50–100 miles on uhf. Extra special long-range ground-wave conditions are usually signaled by approaching warm, moist fronts, moving eastward following a high-pressure area of dry air. Early morning and late evening are again the best periods of the day to try your hand at unusual extended ground-wave reception. East–west paths are normally most productive.

Report forms

This column, through RADIO-ELECTRONICS Magazine, provides free TV dx report forms or logging sheets to any observers requesting them. Your use of these forms will insure that we get all the essential information for each of your dx loggings. Simply address a 2-cent postcard to TV Dx Column, RADIO-ELECTRONICS Magazine, 154 W. 14th St., New York 11, N.Y. New report forms are sent upon receipt of completed monthly sets from you, the dxer. END

THE PAUSE THAT PROTECTS YOUR RECORDS

exclusive feature of
GLASER-STEERS GS-77
high fidelity changer

Now, the original brilliant performance of your records can be preserved for hundreds of additional plays. This requires an automatic record changer that handles records with a gentleness not yet achieved by any other changer on the market. The changer that accomplishes this... the new GLASER-STEERS GS-77.

TURNTABLE PAUSE is one dramatic reason why the GS-77 handles records more gently than any other automatic record playing mechanism. During the record-change cycle, the GS-77 turntable comes to a complete halt, and doesn't resume motion until the stylus has come to rest in the run-in groove of the next record. This completely eliminates the grinding action which occurs where records are dropped onto a moving turntable or disc.

The GS-77 TONE ARM affords further protection. Improved mass distribution and low pivot friction have so minimized arm resonance and tracking error that these flagrant causes of groove and stylus wear are now virtually eliminated. In addition, the arm has been so designed that stylus pressure between the first and top records in a stack does not vary more than 0.9 gram.

SPEEDMINDER goes still further – for by simply setting the appropriate stylus into play position, the GS-77 automatically plays at the correct record speed, and in the microgroove position, intermixes 33⅓ and 45 rpm records regardless of their sequence in the stack.

The GS-77 is the perfect high fidelity record changer. It combines traditional turntable quality with modern automatic conveniences – and it does this with incredible mechanical simplicity. No wonder

...audiophiles are switching to the new
GLASER-STEERS GS-77

$59.50 less cartridge and base
(base illustrated, $9.60)

RE-6
GLASER-STEERS CORP.
20 Main Street, Belleville 9, N. J.
Please send me complete information on the GS-77.
NAME_____
ADDRESS_____
CITY_____ZONE____STATE_____

TV Service CLINIC

conducted by

By ROBERT G. MIDDLETON
TELEVISION CONSULTANT

WE are getting many requests for data on dc restorers and how to add one to a TV receiver. Because of the interest shown in this circuit, we are presenting the basic facts here.

There are two types of TV receivers. One has dc coupling from the picture detector to the picture tube. This type of receiver does not use a dc restorer. Dc restoration is inherent in dc coupling. Most receivers fall into the second category and are ac-coupled from the picture detector to the picture tube. These receivers require dc restorers for good reproduction of dark night and bright daylight scenes. Without dc restoration, night scenes appear too bright and day scenes too dark. Moreover, dark lettering on white backgrounds and light lettering on dark backgrounds appear with severe background distortion and smear.

A dc restorer clamps the horizontal sync tips to a preset level determined by the setting of the brightness control and *reinserts the dc component* of the composite video signal. *It also does much more than this.* It restores all ac frequencies in the video signal from dc to 15,750 cycles.

Hence, the name dc restorer is an ultra-conservative term. It is like saying that a rich man smokes 50-cent cigars. He also drives a Cadillac and drinks vintage wines. A better name for a dc restorer would be a *low-frequency recovery device.* Note that dc is a very low frequency (zero frequency, to be exact). Hence, if we call a dc restorer a low-frequency recovery device, we include its function of reinserting the dc component—moreover, we recognize the ac recovery function of this modestly named device.

A basic dc restorer is arranged as shown in Fig. 1. It holds the horizontal sync tips at some dc voltage value. It does this on the basis of the low forward resistance of the restorer diode, which conducts on the sync tips. The restorer charges capacitor C, which then discharges slowly. So, the capacitor always shows a charge which is practically the same as the horizontal sync voltage during vertical retrace time. At this time, the peak-to-peak voltage of the sync pulses gives the actual dc level. Because the time constant of the R-C circuit is long, the horizontal sync does not "slump" or "grow" between vertical retrace intervals. This is clamp action. A "slump" or a "growth" in sync-tip level corresponds to distortion frequencies from zero to 15,750 cycles. Clamping eliminates this distortion.

The 100,000-ohm resistor in Fig. 1 reduces the restorer diode's load on the video signal lead. It works because it passes the 15,750-cycle sync pulses. The 100,000-ohm resistor works into the input capacitance of the diode. Accordingly, it gives a low-pass filter action where needed. The high video frequencies are not found across the diode. The restorer operates only on low video frequencies.

You will find elaborations of the Fig. 1 configuration, depending upon the

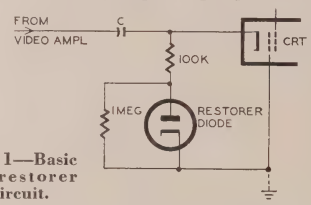

Fig. 1—Basic dc restorer circuit.

details of the picture tube input circuit. However, the basic principle is always as shown in Fig. 1. If you will take the time to understand its action, you will understand all dc restorer circuits.

Mixed-up colors

On an RCA CT-100 color receiver, large areas of red show as green, though small red objects appear OK. Afc and matrix are adjusted properly. Any suggestions will be appreciated.—J. H. C., Willowdale, Ont., Canada.

Your report does not describe the symptoms in detail. However, it would seem that the picture tube is not tracking. Tracking means the adjustment of screen and background controls so that a neutral gray screen is maintained over the normal signal range of a black-and-white picture. A gray screen must be maintained at any usable settings of the brightness and contrast controls.

Here are the important rules:

1. To correct a highlight tint, adjust the blue and green background controls.

2. To correct a lowlight tint, adjust the blue and green screen controls.

Two-set coupling

Two receivers are being operated from a coupler which seems to be defective. Horizontal bar interference appears on one of the receivers.—R. N. S., Crystal City, Mo.

If a receiver radiates considerably, the coupler must have sufficient attenuation to kill the interference. A coupler made up from four 150-ohm resistors as shown in Fig. 2 is sometimes sufficient. However, if you still have noticeable interference, you must add H-pads in the receivers' lead-ins as in Fig. 3.

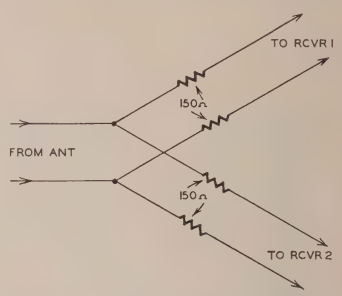

Fig. 2—This type of 2-set coupling reduces interference caused by radiation.

Vertical roll

A Zenith 23G22 has a tendency to roll vertically. I have replaced numerous components in the vertical oscillator and sync section, with no effect. The vertical hold is very touchy. What can you suggest?—B. S., Baltimore, Md.

Your report does not state whether the picture rolls up or down or both ways at different times. If the picture rolls down, the trouble is in the vertical oscillator. But, if the picture rolls up, the trouble can be in either the integrator section or the oscillator. When the oscillator drifts too far off frequency, even a strong vertical sync pulse cannot lock the sweep. On the other hand, a weak vertical sync pulse will not hold sync when the oscillator drifts slightly. This is a job for a scope. Check the vertical sync waveforms for

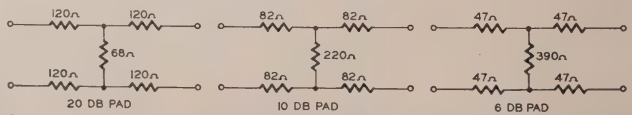

Fig. 3—H pads may be needed when coupling 2 sets to a single TV antenna to attenuate interference-causing radiation.

peak-to-peak voltage. If these are correct, investigate the resistors and capacitors in the vertical-oscillator section—particularly those in the grid circuit.

Snowy picture

In a Philco 22B4002, code 140 TV receiver the picture is snowy on all channels. The antenna checks good, the tuner has been cleaned and appears to be normal, as well as the other stages in the receiver. Can you suggest the cause of this trouble?—D. S., Jr., College Park, Md.

There is a point in the early signal circuits at which the incoming signal is greatly attenuated and falls down to the noise level. Once this happens, subsequent amplification is useless, and all pictures become snowy. It is fairly easy to localize this type of trouble by pulling tubes and watching the picture. Start by tuning the receiver to a vacant channel. Turn up the contrast and volume controls to place considerable snow in the raster and noise in the sound. Then disconnect the lead-in. If there is little or no change in the noise level, the trouble is in the antenna. Try a pair of rabbit ears, or other antenna, for comparison. If there is a very noticeable drop in noise, the antenna is OK. Leave the antenna disconnected for the next tests. Pull the mixer. If there is a big drop in noise, the mixer is OK and the trouble is in the rf amplifier. But if there is little or no change in noise level, there is trouble in the mixer circuit. We know the oscillator is OK because you can get pictures. In exceptional cases, the trouble will be found in the first if amplifier stage.

Vertical instability

An Admiral 20X5B has intermittent vertical instability caused by a slight hum in the video which is not noticeable in the sound. Hum bars are noticeable only when the picture is momentarily off and carrier is on. Horizontal pulling varies from time to time. A scope shows 60-cycle hum as far back as the second if. I suspected that the lead-in cable might be picking up some ac, but another receiver works OK on the same cable. Overriding the agc bias with battery voltage does not help. I have checked the power supply. I'm about out of ideas on this one.—H. E. S., Bryan, Tex.

Since the hum is at 60 cycles, we can go immediately to the heater system. This is a job which should be done with a scope at the output of the video amplifier, to check the hum level while unplugging tubes right down the line from the front end. This will probably localize the trouble and simplify location of the faulty circuit. However, if you can unplug all the tubes and still have the hum, the heater voltage is getting into the signal through a leak. It could be a leak across a socket from heater to grid. This can be localized by disconnecting the heater line step by step, leaving the scope at the output of the video amplifier. END

Yours FREE!

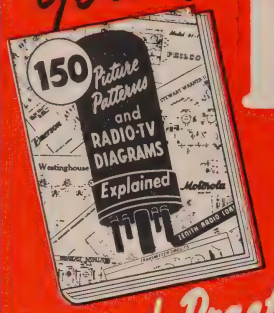

This Big Valuable Book Given Just For Examining Coyne's New 7-Volume Set "Applied Practical Radio-Television"

ON 7 DAY FREE TRIAL!

Yes, you get our big Diagrams book, absolutely FREE! It's like a valuable road-map that shows you the way to easier Radio-TV repair. Needed by every serviceman. Complete 11 x 22" Schematic Diagrams on many radio and television sets help cut your servicing time. Includes simple instructions on how to use the diagrams and picture patterns. This helpful book is yours FREE for asking to see Coyne's great new 7-book set, "Applied Practical Radio-Television!"

At Last! Money-Making "Know-How" on Transistors, Color TV and Servicing!

Coyne's great new 7-volume set gives you all the answers to servicing problems—quickly! For basic "know-how" that is easy to understand, you'll find everything you want in volumes 1 to 5 which contain over 5000 practical facts and data. They cover every step from fundamentals to installing, servicing and trouble-shooting, all types of radio and TV sets. Includes COLOR TV, UHF and TRANSISTORS. All this plus Coyne's New TECHNICAL DICTIONARY with over 4000 definitions of latest terms, symbols and abbreviations.

EXTRA! 868-Page TV CYCLOPEDIA Included

For speedy on-the-job use, you get Vol. 6—famous Coyne CYCLOPEDIA. Quick answers to problems on servicing, alignment, installation in ABC order. *NEW! Each book in the set has bright, modern, washable covers!* Use this 7-volume TV-RADIO LIBRARY FREE for 7 days; get Servicing Book FREE!

SEND NO MONEY

Just mail coupon for 7-volume set on 7 days free trial. We'll include book of 150 TV-Radio Patterns & Diagrams. If you keep the set, pay $3 in 7 days and $3 per month until $24.50 plus postage is paid. (Cash price $22.95.) Or you can return the library at our expense in 7 days and owe nothing. YOU BE THE JUDGE. *Either way, the book of TV-Radio Patterns and Diagrams is yours FREE to keep!* Offer limited. Act NOW!

COYNE ELECTRICAL SCHOOL
500 So. Paulina Street
Dept. 68-T1, Chicago 12, Ill.

OVER 2850 PAGES OF FACTS

VOL. 1—Application of Television-Radio Principles: 300 pages—resonance, tuning, amplifiers, oscillators, etc.

VOL. 2—Radio, Television & FM Receivers: 403 pages—rectifiers, high frequency, short wave, FM, antennas, etc.

VOL. 3—Radio-TV Circuits: 336 pages—power tubes, decoupling, distortion, phototubes, phase inverters, etc.

VOL. 4—Latest Instruments For Servicing: 368 pages—all types of testing instruments.

VOL. 5—TV Servicing & Trouble Shooting Manual: 437 pages—all types of TV sets, UHF, boosters, color TV, etc.

VOL. 6—TV CYCLOPEDIA: 868 pages—quick answers to all TV problems in A-B-C order. Cross indexed.

VOL. 7—Technical Dictionary: 152 pages—over 4000 definitions of terms, symbols, abbreviations.

FREE! 5 YEARS OF VALUABLE SUPPLEMENTS

Coyne's FREE Annual Supplement Service keeps your set up-to-date on everything that will be new in the field of Radio-TV, electronics and electricity for the next 5 years.

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL, Dept. 68-T1
500 S. Paulina St., Chicago 12, Ill.

YES! Send 7-volume "Applied Practical Radio-Television" for 7 days FREE TRIAL, per your offer. Include TV-Radio Patterns & Diagram Book FREE.

Name..... Age.....

Address .....

City..... Zone..... State.....

Where Employed.....

☐ Check here if you want library sent COD. You pay postman $22.95 plus COD postage on delivery. 7-day money-back guarantee.

SQUARE-WAVE GENERATOR

Simple 2-tube instrument delivers square waves at all frequencies between 10 and 180,000 cycles

By T. W. DRESSER

THE quickest and easiest way to check the performance of any amplifier (video, scope or audio) is by squarewave analysis. The method is rapidly increasing in popularity, but has been held back by the relatively high price of a suitable generator.

While circuits for home-built instruments have appeared, they usually do not extend beyond about 20 kc, limiting their use to audio amplifiers. For scope or video amplifiers, a range extending to 100 kc or more is a must.

This inexpensive unit will cover from 10 or 12 cycles up to 180 kc and can be built by the average technician. It has four ranges: 12–180 cycles, 140–1,800 cycles, 1.4–18 kc, and 14–180 kc. The generated square wave has a rise time of slightly over 0.5 μsec and a 12-volt peak-to-peak amplitude.

The circuit (Fig. 1) is essentially a cathode-coupled multivibrator. Components were chosen with a view to limiting the amplitude of the plate waveform. A dual triode is used rather than two separate tubes to obtain better symmetry of characteristics. The multivibrator's output is coupled to a 6AQ5 amplifier which provides both high- and low-impedance outputs.

I used a 10 x 5 x 2-inch chassis, but there is no reason why the unit could not be built into a small metal cabinet. A power supply delivering 200 volts dc at 50 ma and 6.3 volts at 2 amps is required. Calibration depends to some extent on the B-voltage and the unit's frequency range may vary if the B-supply voltage is different.

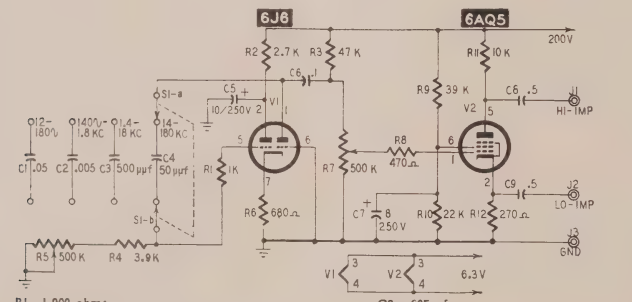

R1—1,000 ohms
R2—2,700 ohms
R3—47,000 ohms
R4—3,900 ohms
R5, 7—pot, 500,000 ohms
R6—680 ohms
R8—470 ohms
R9—39,000 ohms
R10—22,000 ohms
R11—10,000 ohms
R12—270 ohms
All resistors ½ watt, 10%
C1—.05 μf
C2—.005 μf
C3—500 μμf
C4—50 μμf
C5—10 μf, 250 volts, electrolytic
C6—0.1 μf
C7—8 μf, 250 volts, electrolytic
C8, 9—0.5 μf
All capacitors 600 volts unless noted
J1, 2, 3—banana jacks
S1—2-pole 4-position rotary
V1—6J6
V2—6AQ5
Miscellaneous hardware

Fig. 1—Generator circuit. An external power supply is needed.

Square-wave generators can be divided into two types—those using a sine-wave generator followed by a clipper and amplifier, and the multivibrator type working as a relaxation oscillator. Any form of square-wave generator should have a balanced waveform—duration of pulses equal to time between pulses—so it can be used for beam switching on oscilloscopes and other purposes. Both types of generators will provide this, but a complicated circuit or carefully matched time-constant components are required.

Take extra care while wiring and see that all capacitors are kept well away from the chassis to keep stray capacitance down. Leads should be as short as possible and well away from the chassis. Mount the time-constant capacitors (C1, C2, C3, C4) directly on switch S1. Use the smallest-size capacitors available and on no account use metal-cased units. The potentiometers are carbon or composition types.

When wiring is finished and the circuit has been checked for errors, you are ready to check the generator. Connect its output to the vertical input terminals of a good oscilloscope—one that has reasonably flat response at high frequencies and a fast rise time—otherwise it will be impossible to make accurate tests.

Switch on the generator and scope. Now vary the sweep until only 2 or 3 cycles are visible on the screen. Then adjust R1 until a balanced trace (see Fig. 2) is obtained. Then check at with the generator set at 50 cycles, 10 kc and 100 kc. At these points the square wave should be a perfect figure without tilt, rounding or overshoots.

In use, the generator's output is connected to the input of the amplifier under test and a scope is placed across the amplifier's output. Departures from a square wave at the output are noted and the cause found and repaired.

In video amplifiers, if there is a falloff of lower frequencies or phase

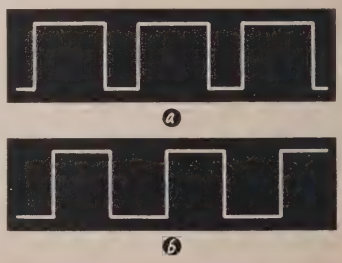

Fig. 2—Waveshapes at generator's output: a—unbalanced wave; b—balanced wave.

It's Newly Revised And Brought Up-To-Date!

Send for this FREE Booklet today!

• *See what can be yours in the rapidly expanding field of . . .*

ELECTRONICS

including: GUIDED MISSILES • RADAR
• INSTRUMENTATION • COMPUTERS
• AUTOMATION • ASTRONAUTICS
• SERVOMECHANISMS
• AERONAUTICAL ELECTRONICS
• TELEMETERING • COMMUNICATIONS
• MANUFACTURING • TELEVISION
• BROADCASTING

Electronics offers you a

- BETTER JOB
- BETTER PAY
- PROMOTION
- GREATER SECURITY
- GREATER CONFIDENCE
- BETTER LIVING FOR YOU AND YOUR FAMILY

All these benefits can be yours if you act now! Take that first step this minute—No obligation whatsoever! Write

CAPITOL RADIO ENGINEERING INSTITUTE

Dept. 146-Y, 3224-16th St. N. W. Washington 10, D.C.

TAKE A MINUTE TO MAIL THIS COUPON FOR FREE BOOKLET!

CAPITOL RADIO ENGINEERING INSTITUTE

ECPD Accredited Technical Institute Curricula—Founded 1927

Dept. 146-Y 3224 16th St., N.W., Washington 10, D.C.

Please send me your course outline and FREE illustrated Booklet "Your Future in the New World of Electronics" . . . describing opportunities and CREI home study courses in Practical Electronic Engineering Technology. **HI**

CHECK FIELD OF GREATEST INTEREST

- ☐ Radar, Servo and Computer Engineering Technology
- ☐ Electronic Engineering Technology
- ☐ Broadcast (AM, FM, TV) Engineering Technology
- ☐ Television Engineering Technology
- ☐ Aeronautical Electronic Engineering Technology

Name.....Age.....

Street.....

City.....Zone.....State.....

Check: ☐ Home Study ☐ Residence School ☐ Korean Veteran

NOT FOR BEGINNERS.
If you have had a high school education, and experience in electronics—and realize the need of high-level technical knowledge to make good in the better electronic jobs—you can qualify for CREI home study training. (Electronic experience is not required for admission to CREI Residence School).

Please fill in the following information:

EMPLOYED BY .....

TYPE OF PRESENT WORK.....

EDUCATION: YEARS HIGH SCHOOL.....

YEARS COLLEGE.....

ELECTRONICS EXPERIENCE .....

For my Money XCELITE Tools are the Finest!

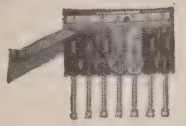

. . . Superbly made and designed for Radio, T.V. and Electronic Technicians. *See your Distributor* . . . only one quality . . . the finest — whether you choose individual items or the handy kits . . .

Use the Tools the Professionals use!

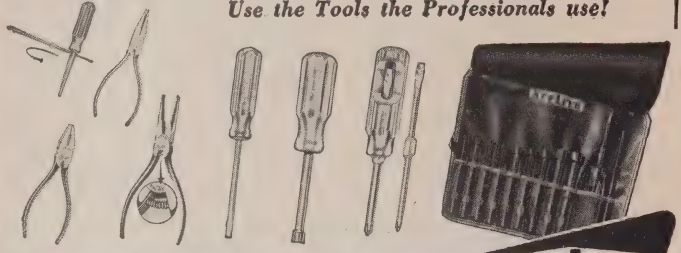

XCELITE, INCORPORATED
ORCHARD PARK, NEW YORK
Canada: Charles W. Pointon, Ltd., Toronto

XCELITE *Quality Hand Tools*
PREFERRED BY THE EXPERTS

Another Sencore Time-Saver

NEW IMPROVED SENCORE LC3 Leakage Checker

Check these outstanding New Features

Now — For the first time . . .

Checks 130 different tube types — more than any other "grid circuit" type checker. Includes UHF and latest type tubes.

Checks picture tubes without removing tube from cabinet or chassis.

New Roll Chart prevents obsolescence — just dial the tube type and save time. Chart is easily replaced at no extra cost.

Dynamic Filament checks including heater to cathode leakage & shorts — no need for a second filament tester.

Two spare preheating sockets to cut down testing time.

Capacitor checks simplified.

$28.95 DEALER NET *Really Whips Tough Dogs*

The LC3 provides all these new improved features in addition to those employed in earlier leakage or "grid circuit" testers. A must for any TV service technician.

SERVICE INSTRUMENTS CORP.
171 Official Rd • Addison, Ill.

In stock at your local parts distributor

Cut out this ad now for further information

BIGGEST BUYS OF '58!

Regency

ALL-TRANSISTOR Vest-Pocket RADIO READY TO PLAY!

$14.95 Including 1000-hour batteries and phone!

Lektron scoops the field with the "hottest" pocket transistor radio since the advent of the transistor! Designed and built by Regency, one of America's great names in radio. Uses an exclusive circuit with RF, DET and AMP stages. SMALLER THAN A PACK OF CIGARETTES!—only 3 x 2 x 1". NO EXTERNAL ANTENNA OR GROUND—no hanging wires! Amazing sensitivity, volume and selectivity. Attractively designed two-tone styrene case. Variable tuning covers 540 to 1500 kcs. READY TO PLAY when you receive it! 1000-hour batteries and ultra-sensitive phone included in this fabulously low price! Gift packed. Wt. 1 oz. Postpaid.

SATISFACTION GUARANTEED!

20,000 OHMS/VOLT MULTI-TESTER

LOWEST PRICE IN U.S.A.! $17.99

Ready to go! 5⅛ x 3⅝ x 2¼". Test leads incl. Ranges: AC & DC V.: 0 to 1200, 600, 120, 30, 6. 20K ohms/volt DC; 10K ohms/volt AC; DC mils: 0 to 300, 12, 1.2; DC micro-amps: 0 to 60; DC ohms: 0 to 10K, 100K, 1 meg, 10 megs; DB: 20 to +17; CAPACITANCE: .0005 to .01; INDUCTANCE: 30 to 3,000 henrys. Ship wt. 5 lbs. Please include postage with this item; excess returned.

WRITE FOR NEW SUMMER BARGAIN FLYER!

LEKTRON

131 EVERETT AVE. CHELSEA 50, MASS.

TEST INSTRUMENTS

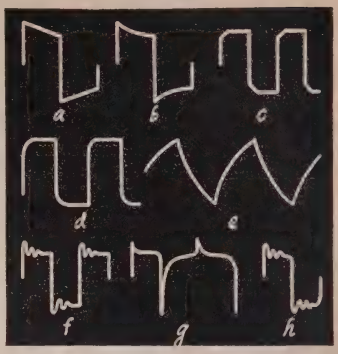

Fig. 3—Waveforms observed in amplifier troubleshooting: a, b, c—indicate a falloff of lower frequencies or phase shift with regard to higher frequencies; d—falloff in frequency response above 800 kc; e—falloff in frequency response around 200 kc; f, g, h—resonant peaks caused by misadjusted peaking coil, high wiring inductance or high-frequency leakage.

shift with regard to higher harmonics, the top of the wave, instead of being flat, will lean over and may even be concave as in Figs. 3-a, -b and -c. Fig. 3-d indicates a falloff in frequency response above 800 cycles and Fig. 3-e shows a similar condition at a lower frequency, around 200 cycles.

Resonant peaks result in the patterns shown in Figs. 3-f, -g and -h. This frequently indicates a misadjusted peaking coil, high wiring inductances or high-frequency leakages through gain controls or faulty capacitors.

While the unit is small and easy to build, don't think of it as a toy or something only for amateurs. It is intended for serious work and is probably as good for this purpose as many higher-priced more complicated equipment. It will have many uses in checking video and scope amplifiers and will prove just as valuable when that defective hi-fi amplifier comes into the shop. END

50 Years Ago

In Gernsback Publications

HUGO GERNSBACK, *Founder*

Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some larger libraries still have copies of Modern Electrics on file for interested readers.

In June, 1908, *Modern Electrics*

Modern Electric Tubes, by H. Gernsback.

The Poulsen Wireless Station at Lyngby.

A Silicon Detector, by A. C. Austin, Jr.

The Construction of a Tuning Coil, by A. C. Austin, Jr.

An Unusual Oscillation Detector, by John L. Hogan, Jr.

Typesetting By Wireless, by the Paris Correspondent.

See The Best Before You Build!

SEE THE AMAZING

ALLIED knight-kits®

IN THE WORLD'S LEADING ELECTRONIC SUPPLY CATALOG

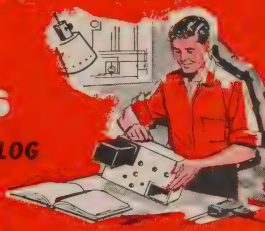

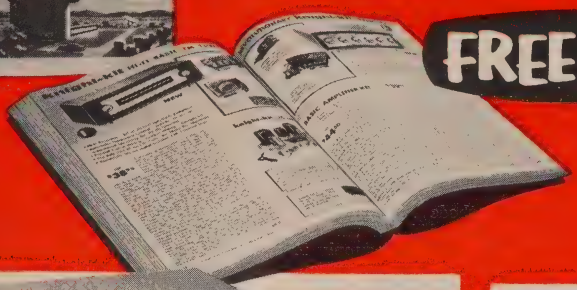

FREE! send for it now

THERE'S A knight-kit FOR EVERY NEED

- LOWEST COST
- EASIEST TO BUILD
- FATEST DESIGN
- FINEST QUALITY

Do-It-Yourself: SAVE UP TO 50%

knight-kits: BEST BUY HI-FI KITS

- 18-Watt Amplifier
- 30-Watt Amplifier
- 25-Watt Amplifier
- 20-Watt Amplifier
- 10-Watt Amplifier
- FM-AM Tuner
- FM Tuner
- Preamplifier
- 2-Way Speaker System
- 3-Way Speaker System

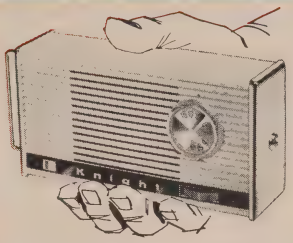

knight-kits: BEST BUY HOBBY KITS

- "Space-Spanner" Radio
- "Ocean-Hopper" Radio
- "Ranger" AC-DC Radio
- 2-Way Intercom
- Electronic Lab Kits
- Crystal Set
- Wireless Broadcaster
- 5-Transistor Portable
- 2-Transistor Pocket Radio
- Transistor Lab Kit
- 1-Transistor Radio
- Photoelectronic System
- Electronic Photoflash
- Phono Oscillator

knight-kits: BEST BUY INSTRUMENT KITS

- Capacitor Checker
- R/C Tester
- Transistor Checker
- Flyback Checker
- Battery Eliminator
- 5" Oscilloscopes
- Vacuum Tube Voltmeter
- Tube Tester
- VOM's
- RF Signal Generator
- Signal Tracer
- Audio Generator
- Sweep Generator
- R/C Substitution Boxes
- Voltage Calibrator

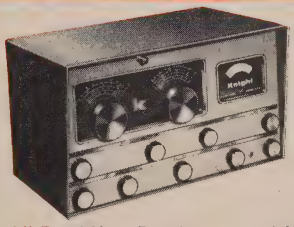

knight-kits: BEST BUY AMATEUR KITS

- All-Band Ham Receiver
- Self-Powered VFO
- 100 kc Crystal Calibrator
- 50-Watt Transmitter
- RF "Z" Bridge
- Code Practice Oscillator

ALLIED RADIO

404-PAGE ALLIED CATALOG FREE!

Send for this value-packed catalog featuring the complete ALLIED KNIGHT-KIT line, as well as the world's largest stocks of everything in Electronics. You'll want this valuable, money-saving Buying Guide.

WRITE FOR YOUR FREE COPY TODAY

ALLIED RADIO CORP., Dept. 122-F8
100 N. Western Ave., Chicago 80, Ill.

☐ Send FREE 1958 ALLIED 404-Page Catalog

Name_____

Address_____

City_____ Zone____ State_____

® Registered Trade Mark—Allied Radio Corp.

SPOT-O-MATIC

With this signal generator, a flick of a switch spots the frequency you want—between 15 and 100,000 cycles

By I. QUEEN
EDITORIAL ASSOCIATE

THE R-C type of audio oscillator is well adapted to home construction because it is easily assembled and calibrated. This one has novel features not found in previous designs. Using only two tubes and no variable capacitors, it is easy to construct and takes up little space. It covers 15 cycles to 100 kc with plenty of output and low distortion. The most important feature is spot tuning, which makes many fixed frequencies available at the throw of one or more switches.

Fig. 1 is the complete circuit. V2 feeds back voltage to V1's grid through an R-C network. Oscillations occur at the frequency of the network. V2 is a cathode follower capable of high output at a low output impedance. Note how direct coupling eliminates components and, of course, improves frequency response. V2's cathode is well above ground, but so is its grid and there is no bias problem. The power supply is conventional and needs no description. It is a full-wave type that delivers about 135 volts at 20 ma to the oscillator.

From TV receivers we know that switch tuning is quick and convenient and that it eliminates human error. If you have occasion to use several frequencies during a test run or hi-fi measurement, you will appreciate this feature. It means that you can switch from one frequency to others and always return to the precise value you originally had.

There are three frequency switches, for 15, 25 and 60 cycles. Fortunately we are not limited to a single frequency per switch. Actually, combinations of the three may be switched in, the resultant being the sum frequency. For example, operating the first two switches (15 and 25 cycles) gives a 40-cycle output. With the three basic frequencies there are seven spot frequencies per decade. They are 15, 25, 40, 60, 75, 85 and 100 cycles, making a good distribution throughout the decade. The oscillator has a multiplying switch for ×1, ×10, ×100 and ×1,000; so you have a total of 28 spot frequencies, the highest being 100 kilocycles.

The frequency-coupling network is a bridged-T (see Fig. 2). Bridged-T oscillators generally have lower distortion than those based on the Wien bridge. Also, hum is lower because there is a common ground for both input and output.

Capacitors C_a and C_b control the

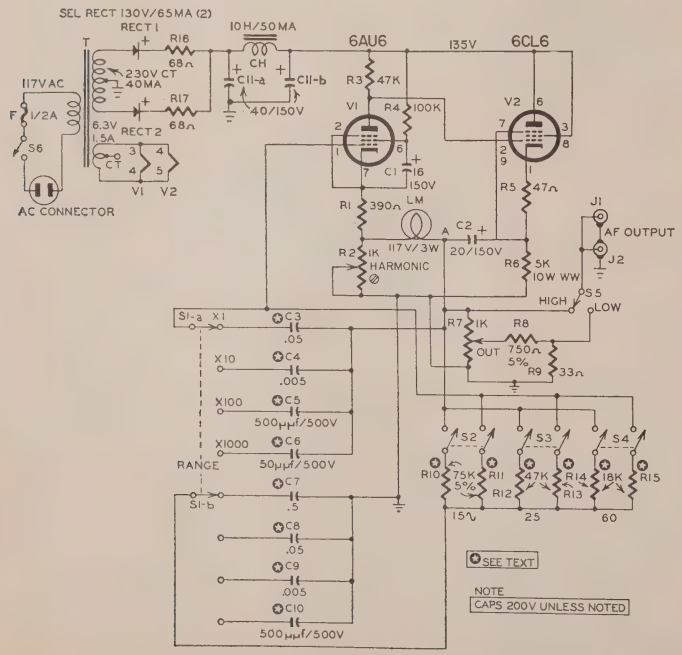

Fig. 1—Circuit of the two-tube Spot-O-Matic.

R1—390 ohms
R2—pot, 1,000 ohms, screwdriver adjust
R3—47,000 ohms
R4—100,000 ohms
R5—47 ohms
R6—5,000 ohms, 10 watts ww
R7—pot, 1,000 ohms
R8—750 ohms, 5%
R9—33 ohms
R10, 11—75,000 ohms, 5%
R12, 13—47,000 ohms
R14, 15—18,000 ohms
R16, 17—68 ohms
All resistors ½-watt 10% unless noted
C1—16 μf, 150 volts, electrolytic
C2—20 μf, 150 volts, electrolytic
C3, 8—.05 μf, paper
C4, 9—.005 μf, paper
C5, 10—500 μμf, mica, 500 v
C6—50 μμf, mica, 500 v
C7—0.5 μf, paper
C11—40-40 μf, 150 volts, electrolytic
All capacitors 200 volts unless noted
CH—filter choke, 10 h, 50 ma, 500 ohms (Triad C-3X or equivalent)
F—½-amp fuse
J1, 2—phono jacks
RECT 1, 2—selenium rectifiers, 65 ma, 130 volts (Federal 1002 or equivalent)
S1—2-pole 5-position rotary (1 position unused) (Centralab PA-1003 or equivalent)
S2, 3, 4—dpdt toggle
S5, 6—spst toggle
T—power transformer: primary, 117 volts; secondary, 230 volts ct, 40 ma; 6.3 volts, 1.5 amps (Triad R-29A or equivalent)
V1—6AU6
V2—6CL6
LM—3-watt 117-volt candelabra screw-base lamp (Allied Radio 52E354, GE type 356 or equivalent)
Socket, candelabra screw
Socket, 7-pin miniature with shield
Socket, 9-pin miniature with shield
Chassis, 2 x 7 x 7 inches
Fuse holder
Miscellaneous hardware

CHART OF CAPACITANCES USED BY THE AUTHOR

Capacitor	Value and connection
C3	.05 μf
C4	.022 μf in series with .005 μf
C5	500 μμf
C6	47 μμf
C7	0.5 μf
C8	.05 μf in parallel with .001 μf
C9	.005 μf
C10	500 μμf in parallel with 36 μμf mica trimmer adjusted for optimum

frequency *range* which may be ×1, ×10, ×100 or ×1,000. C_b is always 10 times larger than the corresponding C_a. When the switch is thrown to the next higher range, the respective capacitors are one-tenth the value of those for the previous range. For any given range, resistors R_a and R_b are equal, and they select the actual frequency.

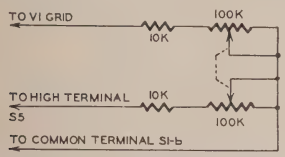

Fig. 2—The basic bridged-T frequency-determining R-C network.

A lower resistance means higher frequency. For the three spot frequencies we need three pairs of identical resistors.

Building the oscillator

The instrument is built into a 7 x 7 x 2-inch aluminum chassis. There is plenty of space for all components without crowding. The HARMONIC control is above the chassis, all others are on the front panel. The output jacks are mounted on the right of the chassis.

First mount the tubes, HARMONIC control, transformers, etc. Then assemble the power supply and check it.

Now you are ready for the frequency networks. Since the frequencies are fixed, it pays to spend a lot of time here to obtain accuracy. Commercial instruments are often rated at 5% maximum error but, if you have the time and patience, you can do much better. The plan is to go through your resistor and capacitor supplies and select the correct values by actual frequency measurement. The values designated on the schematic will provide the required frequencies quite closely, but if you have access to an oscilloscope, you can *select* components for higher precision.

Few experimenters have access to a good capacitance bridge, and it is not needed. Use paper or mica capacitors throughout, not ceramic or electrolytic. The resistor pairs should be checked with an ohmmeter.

For the ×1 range, you need a 0.5- and a .05-μf capacitor. (At this stage of the game it is wise to connect all components with clip leads, leaving the soldering until you have made the final selection.)

Using your ohmmeter, select a matched pair of resistors of approximately 18,000 ohms. Upon completing the network and connecting it to the oscillator, your scope should show a frequency of 60 cycles.* If the frequency is too high, larger resistors are needed or the value of the capacitors may be increased. That's why it is a good idea to have three or four capacitors and

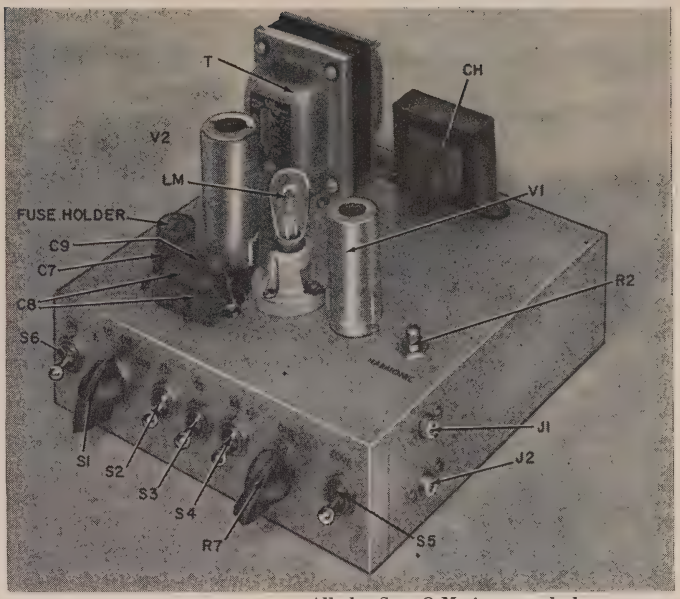

All the Spot-O-Matic controls but one are mounted on the instrument's front panel.

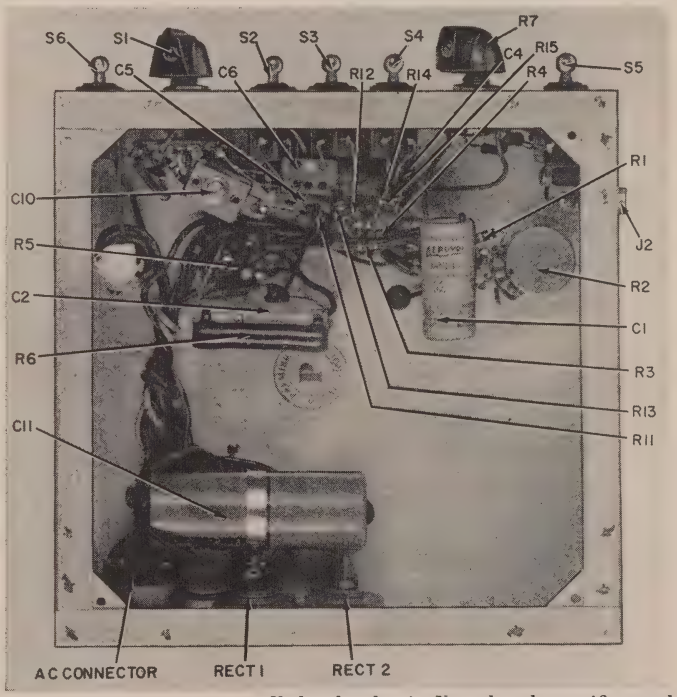

Under the chassis. Note that the rectifiers and power supply filter capacitor are mounted away from the rest of the oscillator's circuitry.

*George Zwick, *Oscilloscope*, page 122 (Gernsback Library).

resistors of each indicated value on hand. Select the units that give greatest accuracy.

Now pick a matched pair of 75,000-ohm resistors. Try various units from those you have to get as close to 15 cycles as possible. Repeat this with 47,000-ohm resistors to obtain 25 cycles. If this frequency does not make an easily recognized pattern when compared with line frequency, try switching on 15 and 25 together. The 40-cycle pattern is easier to recognize. If the 15 and 40 networks are accurate, the 25 must also be.

Select a .05- and a .005-μf capacitor for the $\times 10$ range. Don't forget that the larger unit is always C_b and connects to switch S1-b. With these capacitors the frequency must be 10 times larger and the amplitude must remain unchanged. Be guided by these facts: If one or both capacitors are too large, your new frequency will be lower than it should be. If the amplitude is too high, the *ratio* of C_b to C_a is too great.

Amplitude adjustments

For example, suppose we have completed the $\times 1$ range. Switch in any desired frequency in the band, say 40 cycles. Connect to the scope and set the sweep so that a single cycle appears. Thus, the sweep frequency is also 40 cycles. Now switch to the $\times 10$ range. You should observe 10 complete cycles on the scope. Furthermore, the amplitude of the range-2 pattern should be *identical* with range-1 signal.

Let us say that you are not too lucky (or perhaps you are very fussy). You feel that the range-2 amplitude is larger than that of the first. Furthermore, the frequency is a little too low and you want improvement. To raise the frequency we need lower capacitance (the resistors have been selected once for all ranges and should not be disturbed). The larger amplitude of range 2 shows that the ratio C_b/C_a is too large. Therefore, we select another (*smaller* value) for C_b. For extra-high precision you may even have to make a new selection for *both* capacitors.

Your labor can be eased with the help of another oscillator to compare frequency. Otherwise, simply set your scope for a complete cycle on one range, and look for 10 complete cycles on the next higher range. Use a minimum (preferably zero) sync signal during this measurement. For high accuracy, the patterns should remain stationary *without* aid of sync.

To arrive at the correct value of capacitance or resistance, you can add units in parallel or series as required. The chart shows the particular shunt and series capacitor arrangements I used. The same method applies, of course, to the resistors. I find that heat applied to a resistor can often raise its resistance several percent. If you have a resistor that is slightly low, apply a hot soldering iron to its leads. The resistance will rise appreciably, and in most cases will fall on cooling but leave a net rise. For this reason keep hot soldering irons away from the resistors once you have the correct value.

Note that C7, C8, and C9 are mounted above the chassis. The other capacitors are below.

Final steps

After completing the instrument, connect its output to an oscilloscope. Note that J1 and J2 are tied together. Thus you may use one as signal source for an amplifier, and the other may be used for monitoring voltage or waveform. As the HARMONIC control (R2) is set toward zero resistance, no oscillation will occur. At maximum a distorted wave will be observed and, as the resistance is lowered toward midrange, the wave clears up. At about a 3-volt output, it should be a good sine wave but distortion will be still lower as R2 is decreased further.

S5 controls the output amplitude. In one position the *maximum* is about 3 volts (depending upon R2's setting). In the low position, the *maximum* is about 100 mv. R7 is a variable output control.

Because of low output impedance, the voltage does not drop much when a load is connected. For example, if you adjust for 2 volts open-circuit, a 600-ohm load will reduce it to 1.5 volts.

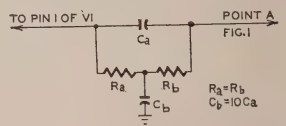

Fig. 3—A few additional parts and you've added a useful variable frequency circuit to the unit.

If you wish to add other basic frequencies or perhaps to substitute frequencies for those listed, the resistances must be changed. The required resistance may be calculated from the following simple formula:

$$\frac{f}{1{,}100} = R$$

where R is in thousands of ohms and f is the basic frequency (in the lowest range). Capacitors are as specified previously. Thus, for 55 cycles you need a pair of resistors, each 20,000 ohms. Of course this is the *approximate* value. The exact resistance is indicated by your oscilloscope as already described, and it requires careful selection of resistors.

Also, you may wish to add variable tuning. Since capacitance is fixed for any given range, the resistance must be varied. For the variable element use a dual potentiometer, each unit 100,000 ohms with logarithmic taper (see Fig. 3). The fixed resistors are limiting elements. To use the variable tuning, switch off all fixed frequencies and switch in the dual potentiometer instead. This feature was actually included in an earlier model of the Spot-O-Matic, but was abandoned in favor of greater simplicity. END

NOW...
stereophonic
HIGH FIDELITY
components
by
Pilot

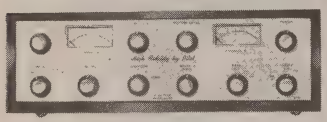

SP-215
Stereo Preamplifier
$189.50

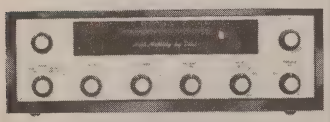

SM-244
Stereo Preamp
and Amplifier
$189.50

PRICES SLIGHTLY HIGHER IN WEST

For complete details,
mail this coupon today.

RQ-6
Pilot Radio Corporation
37-06 36th St., L. I. C. 1, New York
Please send literature covering Pilot Stereo Components.
NAME_____
ADDRESS_____
CITY_____ZONE____STATE_____
Manufacturer in electronics for over 39 years

An Inexpensive Scope Calibrator

A range of .01 to 100 volts peak-to-peak with an accuracy of 5% makes this unit a valuable addition to your test equipment

By JOSEPH CHERNOF

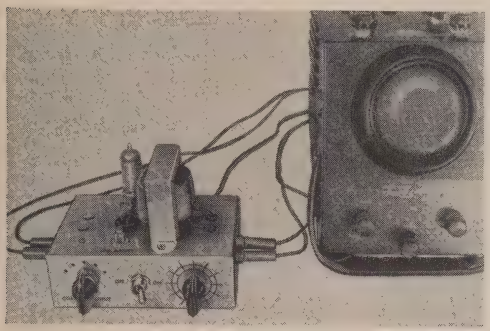

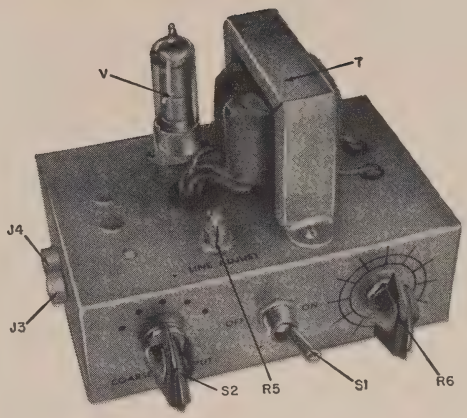

Top view

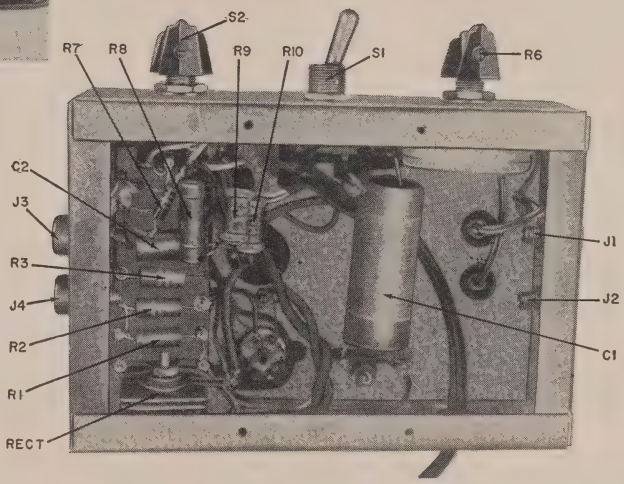

With a little crowding size could be cut in half.

IF amateurs and experimenters were polled as to what they consider the most important single difference between an inexpensive oscilloscope and its high-priced laboratory brother, the hands-down winner would probably be a built-in calibrator circuit. To be truly useful, the calibrator should provide a continuously variable output over a wide range with a reasonable degree of accuracy. It should also be small and compact so it can be used with a scope without increasing workbench clutter. Such a unit is described in this article.

The scope calibrator operates from the 117-volt line. It has a useful output from below .01 volt to 100 volts peak to peak. With normal values of ac line voltage, output voltage accuracy should hold to within 5% after calibration. Accuracy depends on the care used in selecting the voltage-dividing resistors used in the COARSE OUTPUT switch network.

There are three front-panel controls. One, the COARSE OUTPUT switch, is a decade attenuator that provides four ranges of output voltage. The second, the OUTPUT VOLTS control, provides a continuous linear adjustment of the calibrator output voltage. The third control is an ON–OFF switch. Two pairs of banana jacks on the unit's side panels provide input and output terminals. The signal input terminals replace the scope's vertical input terminals for all test-lead connections. The signal output terminals are connected to the scope's vertical input terminals. For normal use of the scope, the fifth position of the output attenuator control provides a direct

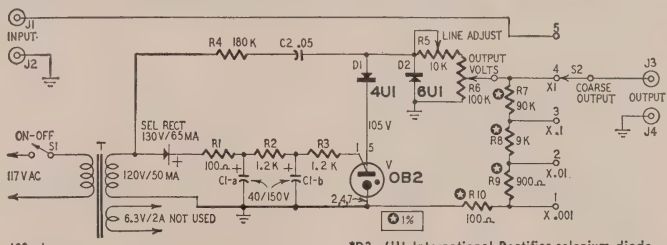

R1—100 ohms
R2, 3—1,200 ohms
R4—180,000 ohms
R5—pot, 10,000 ohms, screwdriver adjust with locknut
R6—pot, 100,000 ohms, linear taper
R7—90,000 ohms, 1%
R8—9,000 ohms, 1%
R9—900 ohms, 1%
R10—100 ohms, 1%
All resistors ½ watt
C1—40-40 μf, 150 volts, electrolytic
C2—.05 μf
*D1—4U1, International Rectifier selenium diode
*D2—6U1 International Rectifier selenium diode (D1, D2 mounted under terminal board.)
J1-4—Banana jacks
RECT, selenium 130 volts, 65 ma
S1—spst toggle
S2—1-pole 5-position rotary
T—Power transformer: primary, 117 volts; secondary 120 volts, 50 ma; 6.3 volts, 2 amps (Merit P-3045)
V—0B2
Case, 6 x 6 x 4 inches, socket, 7-pin miniature
miscellaneous hardware

** Available from: Radio Shack, 167 Washington St., Boston 8, Mass.*

Circuit of the scope calibrator.

ADDS INCOME 2 WAYS
1. Tests and Repairs Picture Tubes
(110° Tubes and Color Tubes too, with new C40 Adapter)
2. Makes New Tube Sales Easier
CATHODE REJUVENATOR TESTER

CRT 400 PROVES REAL MONEY-MAKER

Thousands of servicemen today make money and keep customer good-will by checking and correcting b&w picture tube troubles with the famous B&K CRT 400, right in the home without removing tube from set. Restores emission and brightness. Repairs inter-element shorts and open circuits. Checks leakage. Indicates picture quality customer can expect. Life Test checks gas content and predicts remaining useful life of picture tube. Makes new picture tube replacement sales easier!

Model 400 (without adapter).....Net, **$59.95**

New C40 Adapter for 110° Tubes and Color Tubes

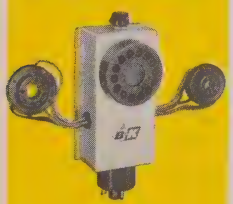

NEW MODEL C40 ADAPTER DOUBLES VALUE OF B&K CRT

Designed for use with all B&K Models 400 and 350 CRT's. Makes it easy to test and rejuvenate TV color picture tubes and 110° picture tubes. Isolates and detects difficult color troubles. Tests and rejuvenates each gun of the color picture tube separately the same way as a black & white tube.

Model C40 Adapter.....Net, **$9.95**

See your B&K distributor, or write for Bulletin AP12-E

Makers of CRT, DYNA-QUIK, DYNA-SCAN and CALIBRATOR

B & K MANUFACTURING CO.

3726 N. Southport Ave. · Chicago 13, Illinois

B&K

NEVER BEFORE AT THIS LOW PRICE!

Precision, battery-operated transistorized portable

TAPE RECORDER

$29.95 ppd

Send for it today!

Weighs only 2 lbs. 8"x7"x2"

(imported from West Germany)

Precision-engineered—Records, plays back, erases. Variable speed controls. Operates on 4 ordinary C-batteries. Uses standard ¼" 1-mil or ½-mil tape. Playback time about 15 min. Patented motor mount provides for forward and reverse winding; stopping with instantaneous braking action, taking up all slack tape; preventing tape from spilling. Voice can be dubbed and superimposed on music or other voice recording (and vice versa). Fine, durable, high-quality components. Complete instructions.

Servicemen—Dealers! Every service call an easy sale after a simple demonstration. Renders same functions as machines costing many times as much.

Your cost for sample, only **$29.95.** Suggested retail selling price, $39.95! On your re-order for two or more, earn an additional 10% discount. Hurry—be the first in your area with this sure-fire item! Everyone will buy! Rush order now!

Unconditionally guaranteed for 90 days against mechanical defects. 10-day money-back guarantee.

FILNOR PRODUCTS CO. Dept. RE-5 **1 Park Ave., N.Y. 16, N. Y.**

TEST INSTRUMENTS

connection between the input and output terminals. This effectively removes the calibrator from the scope's input so a signal from a circuit under test can be observed. Additional utility and flexibility can easily be incorporated by adding an extra pair of input terminals connected to a sixth position of the output attenuator switch. (You would need a six-position rotary switch instead of the five-position unit used.) This would let you monitor two separate circuits without moving test leads around.

The unit's circuit is shown in the diagram. A rectified dc output voltage is filtered through R1, R2, R3, C1-a and C1-b. R1 is a current-limiting resistor, included to prevent damage to the selenium rectifier by the initial surge of charging current drawn by C1. Resistors R1, R2 and R3 are also used in conjunction with V1, an OB2, to provide a regulated 105-volt dc output.

Clipped output

The transformer's 120-volt output is also applied to the calibrator's voltage-dividing resistors. Diodes D1 and D2 limit the applied voltage to a 105-volt peak-to-peak value. D1's cathode is biased with 105-volt regulated dc from V1 so that it will conduct when voltages exceeding 105 are applied to its plate. Thus, peak voltages higher than 105 are effectively clipped. Likewise, D2's plate is connected directly to ground so that all negative values of instantaneous ac voltage will also be clipped. The output of these clipping circuits is a semi-square wave with a constant 105-volt peak-to-peak value.

This constant output voltage is applied to the output attenuating circuits, consisting of potentiometer R5, potentiometer R6, and the COARSE OUTPUT switch resistors R7, R8, R9 and R10. Values for these resistors have been chosen so that the variable output voltage from R6 can be multiplied by attenuation factors of 1, 0.1, .01 and .001. R7, R8, R9 and R10 should be held to tolerances of 1% for best calibration accuracy.

The initial calibration procedure is short and sweet. Connect an accurate vtvm to output terminals J3 and J4, turn the calibrator unit on and set OUTPUT VOLTS potentiometer to the maximum voltage setting. Set COARSE OUTPUT switch to its ×1 position. The vtvm should indicate approximately 105 volts peak to peak. Vary R5 until the output voltage reads exactly 100 peak to peak. Tighten the shaft locknut.

The unit is now ready to use. It can be mounted on top of your scope or bolted to its side. The components will fit into a much smaller case if size and portability are important. If the unit is mounted on top of the oscilloscope, size would not be a major factor, and a 6 x 4 x 4-inch metal case, finished to match your oscilloscope, will provide an attractive housing for the calibrator. END

New Tubes & Semiconductors

THIS month has turned out a large group of new units. Among them are two MADT transistors, a test picture tube for 110° deflection systems, a high-fidelity output tube and a group of 50-watt power transistors.

2N499

A micro-alloy diffused-base germanium transistor intended for use as a power oscillator or power amplifier at frequencies up to 100 mc. Polarities are similar to those of p-n-p transistors. Power gain is typically 10 db at 100 mc. Typical power oscillator output at 100 mc. is 35 mw.

The maximum ratings of this Philco transistor are:

V_{CB}	− 30
V_{CE}	− 18
V_{EB}	− 0.5
I_C (ma)	− 50
P_c (mw)	75

2N499
2N504

2N504

The 2N504 is a hermetically sealed germanium MADT (*M*icro-*A*lloy *D*iffused-base *T*ransistor) field-flow transistor designed for use in if amplifiers. Its maximum frequency of oscillation is at least 50 mc. Polarities are similar to those of p-n-p junction transistors.

Maximum ratings of this Philco unit are:

V_{CB}	− 35
V_{CE} (I_B = 0)	− 25
V_{EB}	− 1
I_C (ma)	− 50
P_c (at 25°C) (mw)	50

8YP4

This lightweight (2-pound) 8-inch rectangular picture tube is designed as a universal check tube for TV receivers

using 110° picture tubes. The tube has a conventional base and comes with an adapter to match the button base of most 110° tubes. It has a 6.3-volt 600-ma heater which is also designed to operate satisfactorily in 450 ma heater strings. It is made by Sylvania.

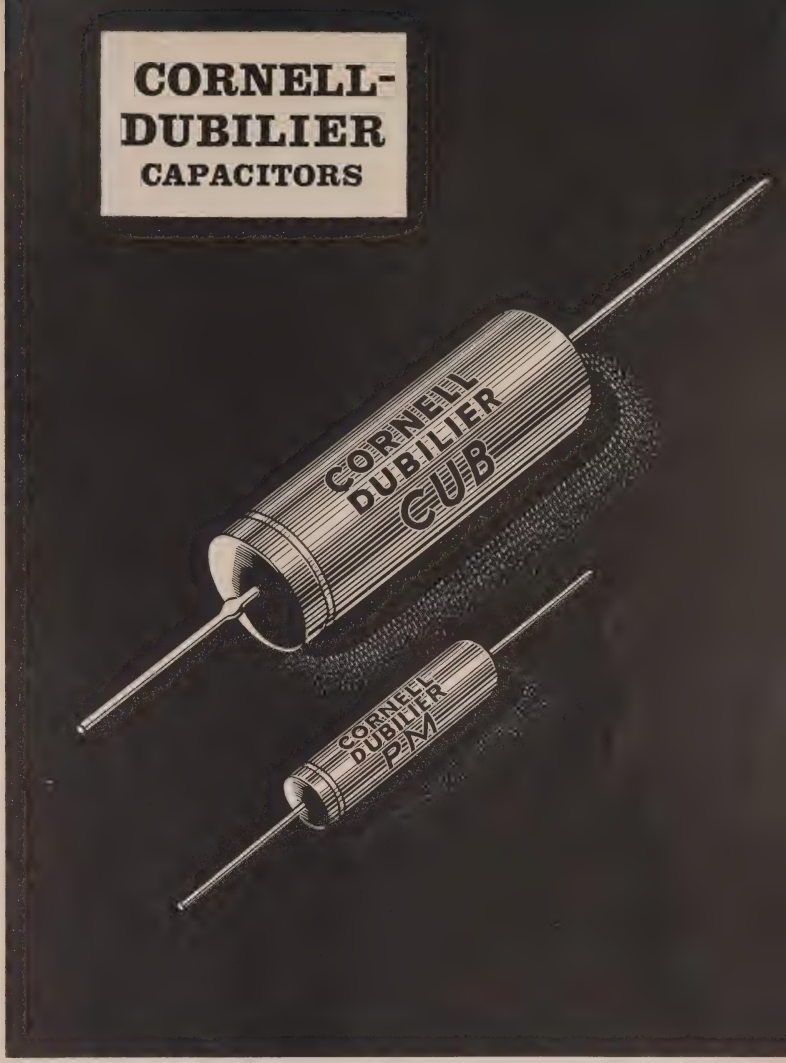

Thoroughbreds when the heat's on

Here are two types of C-D tubulars so thoroughly entombed in high-grade plastic that they're virtually unaffected by heat, cold and humidity. And, because they employ superior dielectrics, these capacitors have a 15%-25% greater voltage breakdown margin. That makes them the ideal replacement capacitors on all servicing jobs.

The C-D CUB, shown, is available with HT COMPOUND or DYKANOL "C" dielectric. The C-D PM utilizes the superior dielectric qualities of DUPONT "MYLAR." Both types maintain excellent electrical characteristics at high temperatures.

For a lasting service job, use C-D CUBS or PM'S. Your local C-D distributor carries complete stocks. For full data, ask for catalog 200D-3, or write Cornell-Dubilier Electric Corporation, South Plainfield, New Jersey, Dept. RE-6.

CORNELL-DUBILIER CAPACITORS

Old Hands at Dependability

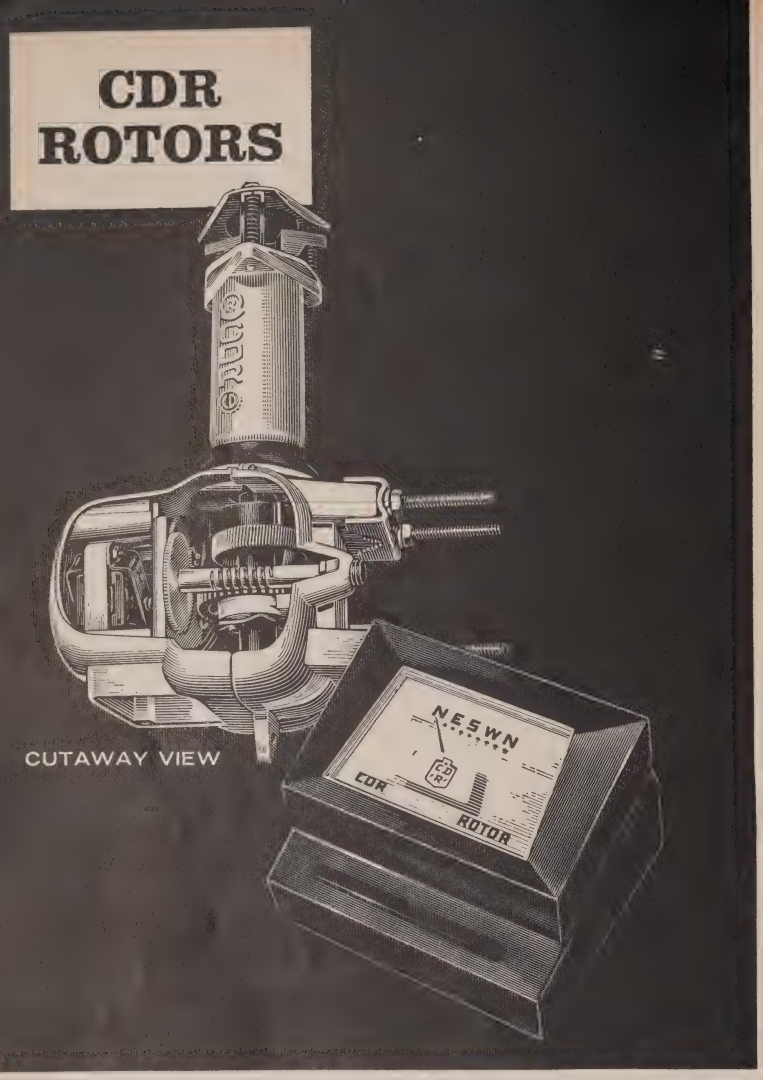

All new features

Completely designed from the ground up, CDR Model TR-15 and TR-16 Rotors have features never before available in the popular price range. Check these refinements and you'll see why: Quick mounting mast collet . . . speedy installation (no loose parts to assemble) . . . self-centering sawtooth clamps take masts up to 1½" O.D. . . . instant locking prevents drift . . . mechanical brake releases magnetically . . . instantly reversible . . . makes complete revolution in 45 seconds . . . meets JAN salt water test . . . great strength thrust bearing support . . . low weight . . . completely weather-sealed . . . fits standard towers . . . streamlined to reduce wind resistance . . . mahogany or blonde finish control box. Get full details today from your local CDR distributor.

CORNELL-DUBILIER ELECTRIC CORP.
South Plainfield, New Jersey

THE RADIART CORPORATION
Indianapolis, Indiana

CDR
Antenna Rotors

Old Hands at Dependability

2N623

A high-frequency diffused-base germanium transistor that enables high gain at frequencies ideal for television if amplifiers, radio rf amplifiers and vhf oscillators. Featuring a 200-mc typical maximum frequency of oscillation and a 90-mc typical alpha-cutoff frequency, this p-n-p transistor delivers

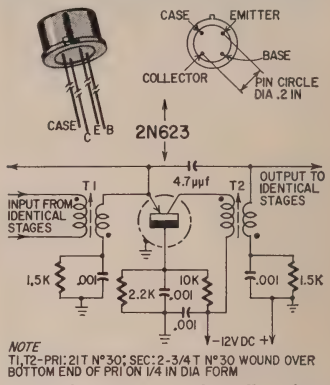

NOTE
T1,T2-PRI: 21T N°30; SEC: 2-3/4 T N°30 WOUND OVER BOTTOM END OF PRI ON 1/4 IN DIA FORM

50-db gain at 1 mc and 13-db gain at 50 mc. In the 43-mc if amplifier circuit (see diagram) the Texas Instruments 2N623 provides 15-db typical gain and 20-mw output.

Maximum ratings of the unit are:

V_{CBO}	− 30
V_{CEO}	− 15
V_{EBO}	− 1
P_{total} (mw)	40

7027

A high-perveance beam power tube designed specifically for use in push-pull power amplifier circuits of high-fidelity audio equipment. Featuring high power sensitivity and high stability, the 7027 can deliver high power at low distortion. Double-base pin connections for both grids 1 and 2 provide for flexibility of circuit arrangement and cool operation of the grids, which minimizes reverse grid current.

7027

Typical operating values using this RCA tube in an Ultra-Linear output circuit are:

V_P	410
V_{G2}	see note
Cathode bias resistor (ohms)	220
Peak af (g1 − g1) (volts)	68
Zero-signal cathode current (ma)	134
Maximum-signal cathode current (ma)	155
Effective load resistance plate to plate (ohms)	8,000
Total harmonic distortion (%)	1.6
Maximum-signal power output watts	24

NOTE: g2 voltage is obtained from taps on the primary winding of the output transformer. The

taps are located on each side of the center tap so as to apply 43% of the plate signal voltage to g2 of each tube.

2N394, 395, 396, 397

These germanium p-n-p alloy-junction high-frequency switching transistors are intended for military, industrial and data-processing applications where

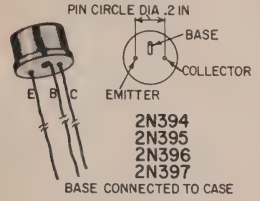

high reliability and extreme stability of characteristics are of prime importance.

Maximum rating of these General Electric transistors at 25°C are:

	2N394	*395*	*396*	*397*
V_{CE}	− 10	− 15	− 20	− 10
V_{CB}	− 10	− 15	− 20	− 10
V_{EE}	− 10	− 10	− 10	− 10
I_C (ma)	− 200	− 200	− 200	− 250
$P_{average}$ (mw)	150	150	150	150
Alpha-cutoff freq (mc)	5.5	7	7	10

2N627, 628, 629, 630

Germanium p-n-p alloy junction power transistors capable of handling high wattages at high voltage. Collector electrode is connected to the case. Units are designed for high-current switching and audio applications.

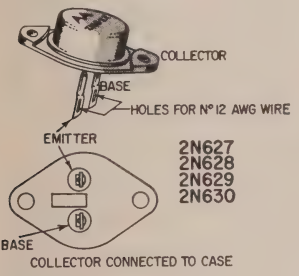

Maximum ratings of these Motorola transistors are:

	2N627	*628*	*629*	*630*
V_{CB}	40	60	80	100
V_{CE}	30	45	60	75
I_C (dc) (amps)	10	10	10	10
P_C (base temp 30°C) (watts)	50	50	50	50

END

"OK! So I am chicken!"

RADIART VIBRATORS

Consistently dependable power

Next time an auto-radio vibrator replacement is called for, try Radiart. There's a complete line for all 6-volt and 12-volt applications. And no waiting for the type you want, because your local Radiart Distributor maintains a full stock for your convenience. Ask him for your free copy of the Radiart Vibrator Replacement Guide, or write to Dept. S-1, The Radiart Corporation, Indianapolis 5, Indiana.

RADIART TOBE Vibrators

Old Hands at Dependability

new Devices

HAM RECEIVER KIT, *Mohawk model RX-1.* Wide-band slide-rule type vernier tuning. Covers amateur bands from 160–10 meters. External receiver-powered converter accommodates cover 6 and 2 meters. Front end preassembled, wired and aligned. Double-conversion if at 1682

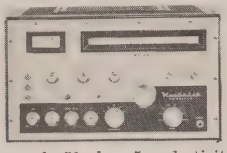

kc and 50 kc. 5 selectivity positions from 5 kc to 500 cycles. Bridged T-notch filter for maximum rejection. Built-in 100-kc crystal calibrator. 10-db signal-to-noise ratio at less than -1 μu input. 15 tubes. —**Heath Co.,** Benton Harbor 20, Mich.

INDOOR ANTENNA, *Perma-Tena.* Two continuous foil strips are glued to ceiling and connected to an antenna wall out-

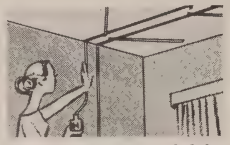

let. Elements are extended from both sides of ceiling strips and secured with conductive cement. When painted over, antenna becomes invisible. Kit includes compass for proper orientation, conductive paint and materials, wall outlet, wall and conductive cement, applicator and other necessary material.—**K & K Research Development Co.,** P.O. Box 925, Hawthorne, Calif.

FRINGE-AREA TV ANTENNA, *Satellite-Helix.* 28 elements. Front-to-back voltage ratios:

15 to 1 (low band), 18 to 1 (high band). 300-ohm impedance, balanced sleeve dipole system.—**JFD Electronics Corp.,** 6101 16th Ave., Brooklyn 4, N. Y.

TV ANTENNA, *Dura-Gold Corvette.* Deep fringe-area, all-channel type (2–13). Metal ele-

ments covered with vinyl plastic to protect against corrosion.—**Clear Beam Antenna Corp.,** Canoga Park, Calif.

ANTENNA TOWER, *No. 25.* General-purpose communications and heavy-duty TV type. 12 ½-inch equilateral triangular design. Uses 1¼-inch heavy-gauge tubing for side rails and zig-zag solid steel cross bracing. Self-supporting to 50 feet or

guyed to 150 feet. Hot-dipped galvanized or enamel finish.—**Rohn Manufacturing Co.,** 116 Limestone, Bellevue, Peoria, Ill.

LOW-LOSS SWITCH, for antenna systems, *TACO model 823.* Miniaturized unit 1¾ x 1¾ inches. Mounted in gold anodized case. Slide switch presents 300-ohm impedance for maximum energy transfer. Dpdt type unit used for switching between two antennas at receiver.—**Technical Appliance Corp.,** Sherburne, N. Y.

AUTO RADIO ANTENNA, *model JA-7 Bullet.* Chrome, die-cast swivels for vertical or 45°, angle mounting. 3-section telescoping mast extends to 57

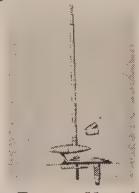

inches.—**Tenna Manufacturing Co.,** 7580 Garfield Blvd., Cleveland 25, Ohio.

STYLUS-USE TIMER, *Hi-Fi-Eye.* When connected in parallel with record changer or turntable, automatically indicates how many hours it has been in use. Lets you know when to

change stylus.—**Electronic Instruments Service,** 8907 S. Vermont Ave., Los Angeles 44, Calif.

VARIABLE ATTENUATORS. *Model AV-50* (illustrated) has

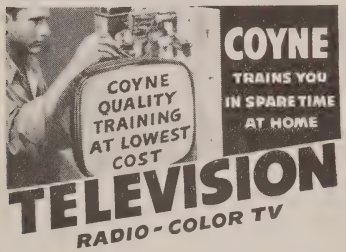

Only from famous COYNE do you get this modern up-to-the minute TV Home Training. Easy to follow instructions—fully illustrated with 2150 photos and diagrams. Not an old Radio Course with Television tacked on. Includes *UHF* and *COLOR TV*. Personal guidance by Coyne Staff. *Practical Job Guides* to help you EARN MONEY QUICKLY IN A TV-RADIO SALES AND SERVICE BUSINESS—**part time or full time.** COSTS MUCH LESS—pay *only for training—no costly "put together kits."*

SEND COUPON FOR FREE BOOK

SEND COUPON BELOW for *Free Book* and full details including EASY PAYMENT PLAN. NO COST OR OBLIGATION—NO SALESMAN WILL CALL.

B. W. COOKE, Jr., Pres. **COYNE ELECTRICAL SCHOOL** FOUNDED 1899

A TECHNICAL TRADE INSTITUTE OPERATED NOT FOR PROFIT
500 S. Paulina, Dept. A8-H5, Chicago 12, Illinois

COYNE ELECTRICAL SCHOOL
Television Home Training Div.
500 S. Paulina St., Chicago 12, Ill., Dept. A8-H5

Send FREE BOOK and details of your Television Home Training offer.

Name_____

Address_____

City_____ State_____

NEW ULTRON UNIT PROVIDES

SONIC REALISM

THE MODEL U-2 REVERBERATION UNIT

MAKES YOUR MUSIC SYSTEM REPRODUCE NATURAL QUALITIES OF LIVE SOUND

"PRESENCE" AT LOW COST

APPLICATION OF REVERBERATION PRINCIPLES GIVES EFFECT OF STEREO WITHOUT REQUIRING MULTIPLE PROGRAM SOURCE

Ultron Company's Model U-2 Reverberation Unit will link any supplementary amplifier-speaker combination to your basic monaural system so as to provide realistic sound reproduction from a single source of program material. Music through a U-2 equipped system acquires a depth and sparkle known only to those accustomed to more expensive stereo installations. Hook-up is a simple matter covered in full by installation instructions accompanying each unit. Dimensions are approximately 2 x 3 x 5¼ inches.

ORDER NOW

OR SEND FOR FURTHER DETAILS

Purchase price will be refunded if unit is not as claimed and is returned undamaged within ten days of purchase.

ULTRON COMPANY
Dept. R-1, 7943 Haskell Ave., Van Nuys, Calif.

☐ Send free descriptive folder

☐ Send _____ U-2 Units @ $18.75

(Calif. residents add 4% sales tax.)

☐ C.O.D. ☐ Postpaid (check enclosed)

Name_____

Address_____

City & State_____

ALWAYS SPECIFY

HUSH®

Chemically engineered for tuners and switching mechanism

Hush comes in a 6 oz. pressure can with sufficient pressure to reach all contacts to wash away that dirt, leaving clean and positive contacts, protected with a lasting lubricant film.

$2.25 Net

Hush also available in 2 oz., 8 oz. and 32 oz. containers.

EVER-QUIET®

Since 1949 the Original Volume Control and Contact Restorer

EVER-QUIET is a free-flowing liquid that leaves no powder residue. Scientifically designed to seep around the shaft and penetrate the control or potentiometer, cleaning the contacts and leaving a safe protecting film.

2 oz. 79c Net

See your distributor or write to

CHEMICAL ELECTRONIC ENGINEERING, INC.
Matawan New Jersey

50-ohm characteristic impedance; *AV-75* has 75-ohm characteristic impedance. Both provide 0–62.5-db attenuation in 0.5-db steps. Operates from dc–500 mc.—**Jerrold Electronics Corp.,** 23rd & Chestnut Sts., Philadelphia 3, Pa.

UHF CONVERTER, *model 99R.* 3-section tuner with dual input section. Single-knob tuning of

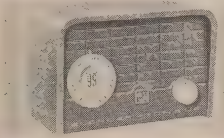

channels 14–83. 300-ohm impedance.—**Blonder-Tongue Laboratories Inc.,** 9-25 Alling St., Newark 2, N. J.

AM–FM TUNER, *model LT-25.* FM section: response within 1 db from 20–20,000 cycles; output

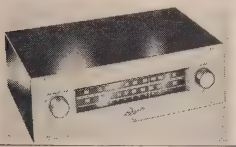

level for 100% modulation is 2.5 volts; afc and afc defeat; Armstrong circuit with limiter and Foster-Seeley discriminator. AM response 20–5,000 cycles, within 3 db. Built-in AM and FM antennas.—**Lafayette Radio,** 165-08 Liberty Ave., Jamaica 33, N. Y.

REVERBERATION UNIT, *model U-2.* Used as link between basic amplifier output and input

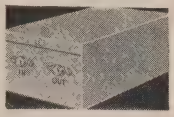

of any auxiliary amplifier and speaker combination. Gives illusion of presence without necessity for two sources of program material.—**Ultron Co.,** 7943 Haskell Ave., Van Nuys, Calif.

TRANSISTOR INTERCOM, *Centrum.* Two 4.5-volt batteries power unit. Standard set consists of master station, substa-

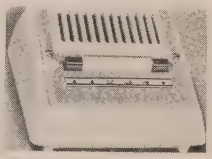

tion and 20 yards of cable. Up to 3 additional substations may be added.—**Reeves Equipment Corp.,** 10 E. 52 St., New York.

HI-FI PHONO CARTRIDGE.

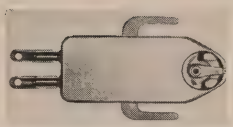

Magneto-dynamic type. Moving magnet armature made of ferrite material and magnetized perpendicularly to its axis. Response from 10–20,000 cycles within 2 db. Output 3.5 mv at 10 cm/sec velocity. Lateral compliance greater than 5×10^{-6} cm/dyne. Vertical tracking force 5 grams.—**North American Philips Co. Inc.,** High Fidelity Products Div., 230 Duffy Ave., Hicksville, N. Y.

SPEAKER ENCLOSURES. *Model RJ/8* (illustrated), de-

signed for 8-inch speakers, fits in single shelf of standard bookcase. *RJ/12-S:* double-shelf model for 12-inch speakers. *RJ/12-F:* floor model for 12-inch speakers. *RJ/Super 8:* ready-to-play system consisting of RJ/8 enclosure equipped with Wharfdale Super 8/FS/AL speaker. Unfinished birch and finished in mahogany, walnut or blond.—**R-J Audio Products Inc.,** 80 Shore Rd., Port Washington, N. Y.

FLEXICONE. Helps improve speakers. Lowers cone resonance 10–40 cycles. Gives soft, permanently flexible, outer-edge cone suspension. Comes in do-

it-yourself kit with instructions.—**Howard Re-Cone Service,** 824 Kennedy St. NW, Washington 11, D. C.

12-WATT AMPLIFIER, *model LA-22.* Response 30–20,000 cycles

within 1 db at rated output. Less than 1½% IM distortion. Hum level 60–80 db below full output. 5 inputs including tape head. Equalization, loudness, treble and bass controls.—**Lafayette Radio,** 165-08 Liberty Ave., Jamaica 33, N. Y.

30-WATT AMPLIFIER, *HF-32,* kit or wired. Response within

DX-16 Super Deluxe TV KIT

70° or 90°—operating all 17", 21", 24" and 27" PICTURE TUBES

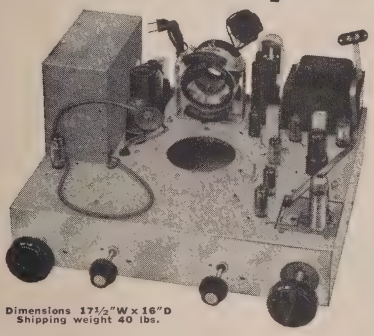

Dimensions 17½"W x 16"D
Shipping weight 40 lbs.

NEW IN DESIGN—*Mounts Horizontally, Vertically or Sideways.*

★ Produces a Superior 16-Tube Chassis with 30-Tube performance.
★ Latest advanced Intercarrier Circuitry and Multi-section Tubes.
★ Standard Cascode Tuner for Selectivity and Fine Definition.
★ 5 Microvolts Video Sensitivity (20 volts peak to peak at CRT grid).
★ Fast Action AGC for Drift Free, Steady and Clear Pictures.
★ 3 Hi-gain Video I.F. Stages for excellent Contrast and Details.
★ AGC Level and Area Control, for adjusting reception to signal area.
★ All Video and I.F. Coils factory pre-aligned and tuned.
★ Horizontal Sweep Circuit is the famous RCA Synchroguide Network.
★ Large 250 ma Power Transformer.
★ Large 12" Concert-tone Speaker.

Sold on the Easy-Payment-Plan—$2.49 starts you off. You receive LIFE-SIZE step-by-step Building Instructions . . . just buy a few dollars worth of parts at a time . . . or buy it complete at the low price shown below.

COMPLETE KIT WITH SET OF Westinghouse **TUBES** 4—6CB6 and 6U8, 6T8, 6C4, 12BH7, 6SN7, 6BQ6, 6W4, 1X2B, 5U4. 6J6 and 6BQ7 included in the Tuner. (less CRT)..... **$79.97**

BUILD YOUR OWN TV CABINET FOR ANY TV CHASSIS Comparable to the type that Top Mfrs. use on their higher priced TV sets.

CABINET KIT with 90% of the job done, includes—

FRONT SECTION complete as pictured in Solid Mahogany, Walnut or Blond Korina.

TOP, SIDES, BACK with **CRT CUP, MASK, SAFETY GLASS, ETC.** and Easy-to-follow Instructions.

Front, Top and Sides supplied in a beautiful Piano Finish ● ● ● Knob panel undrilled (or drilled on receipt of your template) ● ● ● For matching Mask specify type of CRT used. Same price for Mahogany, Walnut or Blond.

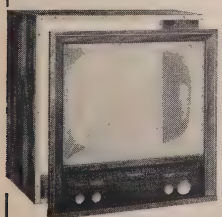

Worth $60 when completed, only takes a few hours to assemble

21" CABINET KIT 26"H, 25"W, 22"D **$24.95**
(Also available for 17"CRT)

Worth $65 when completed, only takes a few hours to assemble

24" or 27" CABINET KIT 30"H, 28½"W, 22"D **$36.47**
Maximum Shipping weight 48 Lbs.

FRONT SECTION for WALL INSTALLATIONS Includes Mask, Safety Glass, Decals and Illustrated Instructions. 21".. **$17.45** | 24" or 27".. **$22.97**

(only) Same price on Mahogany, Walnut or Blond or in Natural (unfinished) for your own color application.

BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N.Y.

BUILD 16 RADIO CIRCUITS at Home with NEW *DELUXE* 1958 PROGRESSIVE RADIO "EDU-KIT"

Now $22.95 Reg. U.S. Pat. Off.

A COMPLETE RADIO COURSE

★ No Knowledge of Radio Necessary
★ No Additional Parts or Tools Needed
★ EXCELLENT BACKGROUND FOR TV
★ School Inquiries Invited
★ Attractively Gift Packed

Now Includes

★ TRANSMITTER
★ SIGNAL TRACER
★ SIGNAL INJECTOR
★ CODE OSCILLATOR

FREE EXTRAS

• SET OF TOOLS • RADIO & ELECTRONICS TESTER • ELECTRIC SOLDERING IRON • TESTER INSTRUCTION MANUAL • MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE • HI-FI GUIDE • QUIZZES • TV BOOK • FCC AMATEUR LICENSE TRAINING • RADIO BOOK • PRINTED CIRCUITRY • PLIERS-CUTTERS • ALIGNMENT TOOL • WRENCH SET

NO NEED TO SPEND HUNDREDS OF DOLLARS FOR A RADIO COURSE

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction, servicing, basic Hi-Fi and TV repairs, code, FCC amateur license requirements.

You will learn how to identify radio symbols, how to read and interpret schematics, how to mount and lay out radio parts, how to wire and solder, how to operate electronic equipment, how to build radios. You will receive a basic education in radio, worth many times the small price you pay, only $22.95 complete.

THE KIT FOR EVERYONE

The Progressive Radio "Edu-Kit" was specifically prepared for any person who has a desire to learn Radio. The "Edu-Kit" has been used successfully by young and old in all parts of the world, by many Radio Schools and Clubs in this country and abroad. It is used for training and rehabilitation of Armed Forces Personnel and Veterans throughout the world.

The Progressive Radio "Edu-Kit" requires no instructor. All instructions and parts are included. Every step is carefully explained. You cannot make a mistake.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore, you will construct radio circuits, perform jobs and conduct experiments to illustrate the principles which you learn.

You begin by examining the various radio parts included in the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set, you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble shooting. Then you build a more advanced radio, learn more advanced circuits, gradually, in a progressive but easy manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are sixteen Receiver, Transmitter, Code Oscillator, Signal Tracer, and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

In order to provide a thorough, well-integrated and easily-learned radio course, the "Edu-Kit" includes practical work as well as theory; troubleshooting in addition to construction; training for all, whether your purpose in learning radio be for hobby, business or job; progressively-arranged material, ranging from simple circuits to well-advanced topics in Hi-Fi and TV. Your studies will be further aided by Quiz materials and our well-known FREE Consultation Service.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 16 different radio and electronics circuits, each guaranteed to operate. Our Kit contains tubes, tube sockets, variable, electrolytic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book.

TROUBLE-SHOOTING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of troubles in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the Dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

J. Stataitis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend $240 for a Course but I found your ad and sent for your Kit."

——UNCONDITIONAL MONEY-BACK GUARANTEE——

ORDER FROM AD—RECEIVE FREE BONUS RESISTOR AND CONDENSER KITS WORTH $7.00

☐ Send "Edu-Kit" Postpaid. I enclose full payment of $22.95.
☐ Send "Edu-Kit" C.O.D. I will pay $22.95 plus postage.
☐ Send me FREE additional information describing "Edu-Kit."

Name .....

Address .....

PROGRESSIVE "EDU-KITS" INC. 497 Union Avenue, Dept. 1416, Brooklyn 11, N.Y.

NEW DEVICES *(Continued)*

0.1 db from 15–30,000 cycles at any level from 1 mw–and 30 watts. Harmonic distortion below 1% within 1 db of 30 watts. 4, 8 and 16-ohm outputs. Inputs for magnetic phono, tape head, mike, high level (TV, tuner, aux). Equalization, level, loudness, bass, and treble controls. Rumble and scratch filters.—**Electronic Instrument Co., Inc., EICO,** 33-00 Northern Blvd., Long Island City 1, N. Y.

DUAL-CHANNEL AMPLIFIER, *Dual-Amp.* Input separated by electronic divider circuits into low-frequency and high-frequency components. Variable

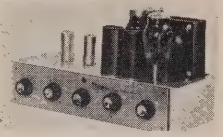

crossover between 100 and 4,000 cycles. Low-end amplifier rated at 24 watts, high end at 6 watts. Separate volume controls for each.—**Transvision Inc.,** New Rochelle, N. Y.

HI-FI AMPLIFIER, *Mini-Fi model KN-510.* 10 watts. Response within 1 db from 20–20,000 cycles at full output. Harmonic distortion less than 2%, IM distortion less than 3%. Inputs for magnetic phono, crystal or ceramic phono, tuner,

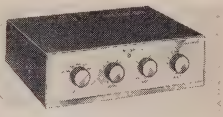

auxiliary equipment and tape head. Bass, treble, volume, equalization selector and rumble filter. Outputs for 4-, 8- or 16-ohm speakers and high-impedance output for tape recorder.—**Allied Radio Corp.,** 100 N. Western Ave., Chicago 80, Ill.

STEREO AMPLIFIER, *model SR 17-17.* Combines 2 preamps and 2 power amplifiers on single chassis. Power output 17 watts each section. Harmonic distortion less than 0.5% at rated output. IM distortion less than 1.5% at rated output. Hum and noise 60–70 db below rated out-

put. Response within 1 db from 20–15,000 cycles. Inputs for tape decks, tape recorders, phono cartridges and auxiliary. Compensation, balance, bass, treble, volume and contour controls.—**Sargent-Rayment Co.,** 4926 E. 12th St., Oakland, Calif.

FM–AM TUNER AMPLIFIER, *model AT-130.* Sensitivity: FM, 5 μv for 20-db quieting; AM, 25 μv per meter. Selectivity: FM, 220 kc at 3 db point; AM, 9 kc at 6-db point, Hum level 60 db below maximum output. Amplifier response within 0.5 db from 20–20,000 cycles. Harmonic distortion: FM, 1%; AM, 2.5%. Built-in antennas. Treble, bass, loudness, function selector, and tuning controls. Tuning indicator. Inputs for tape or phone. Multiple speaker outputs.—**Granco Products Inc.,** 36-07 20th Ave., Long Island City 5, N. Y.

STEREO MASTER CONTROL UNIT, *model 400:* 16 inputs, arranged in 8 pairs.—Low level, tape, mike, monitor, tuner, aux 1 and aux 2. 4 outputs. Push-button input selector, equalization and output selectors, volume, balance, loudness, bass and treble controls. Response uniform from 20–25,000 cycles.

Distortion less than 0.15% for 2-volt output. Crosstalk, 60 db down.—**Fisher Radio Corp.,** 21-21 44th Dr., Long Island City 1, N. Y.

ADJACENT-CHANNEL TRAP, *Filter Matic.* Hi-Q traps and bandpass filters remove adjacent-channel TV interference. Units for all vhf channels available.— **Benco Television**

Associates Ltd., 27 Taber Rd., Rexdale, Ontario, Canada.

PANEL MOUNTING KIT. Accessory kit to be used with the Dynakit preamp. Includes brass escutcheon plate, pair of nickel-plated mounting brackets and hardware. Lets user mount preamp on panels up to 1⅛ inches thick.—**Available from Dynakit distributors.**

MULTIPURPOSE PLIER, *Channellock No. 426.* 6½ inches long with thin jaws. For use in hard-to-get-at places. 5 adjustments with jaw capacity up to ⅞ inch in parallel position. Drop-

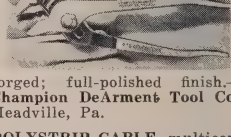

forged; full-polished finish.—**Champion DeArment Tool Co.,** Meadville, Pa.

POLYSTRIP CABLE, multiconductor flat cable for use in electrical and electronic equipment. Available in widths up to 51 conductors. Consists of flat copper ribbon .0015 inch thick and

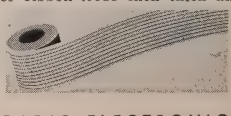

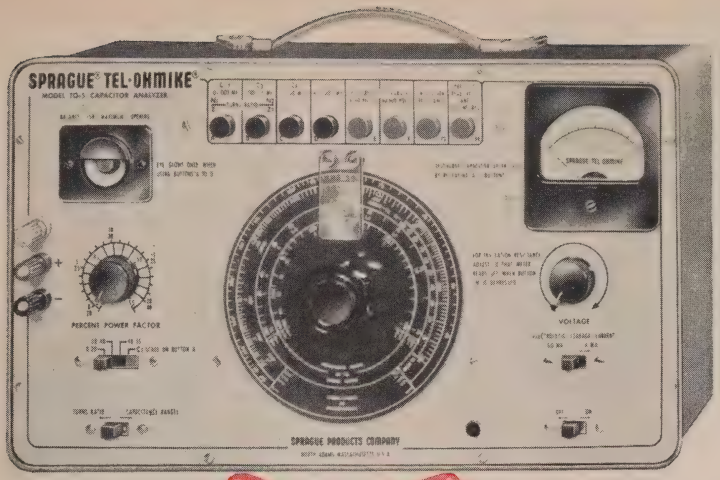

NEW TO-5 TEL-OHMIKE® capacitor analyzer

measures all 4 . . . plus

1 CAPACITANCE	2 POWER FACTOR	3 LEAKAGE CURRENT	4 INSULATION RESISTANCE	extra feature TURNS RATIO
Measures up to 2000 μf in five overlapping ranges . . . including an accurate 1 to 100 μμf range, exclusive with Sprague.	Power factor of electrolytic capacitors is measured by the highly accurate bridge method. Reads up to 55% in three ranges for convenience in measurement.	Leakage current of electrolytics is measured directly on the meter, with exact rated voltage up to 600 v. applied from continuously adjustable power supply. Two ranges—0-6-60 ma.	Insulation resistance of paper, ceramic, and mica capacitors is read directly on meter . . . up to 20,000 megohms.	In addition to its function as a complete capacitor analyzer, the TO-5 also measures the turns ratio of power and audio transformers.

The NEW TO-5 TEL-OHMIKE Capacitor Analyzer is one of the fastest and surest ways of measuring . . . capacitance, power factor, leakage current, insulation resistance, and turns ratio. This compact, easy-to-use instrument has the highest accuracy of any instrument of its type available to the service trade.

New jumbo dial makes meter reading easy. Special color-keyed pushbuttons permit instant range selection . . . and allow automatic safety discharge of capacitors after testing. Magic-eye tube simplifies bridge balancing for capacitance and power factor measurements.

SEE THE NEW TO-5 TEL-OHMIKE IN ACTION . . . AT YOUR DISTRIBUTOR!

This 4-in-1 test instrument is only 8⅞" high, 14⅝" wide, and 6½" deep . . . weighs a mere 12½ pounds. The complete price for . . .

MODEL TO-5 (115 VAC/50-60 cy) . . Only **$83.90 net**

Also available: Model TO-5X for 115-230 V/25-60 cy. . . $89.90 net
Model TP-5RM for rack mounting . . . . . $93.90 net

SPRAGUE®
world's largest capacitor manufacturer

SPRAGUE PRODUCTS COMPANY, DISTRIBUTORS' DIVISION OF SPRAGUE ELECTRIC COMPANY, NORTH ADAMS, MASS.

let RCA train you in

Advanced Electronics

This is the college-level training you need to work with professional engineers on research, development or production projects in such fields as: automation, guided missiles, radar, television, computers and other advanced electronic applications. RCA Institutes Resident School in New York City offers this comprehensive course that prepares you for any field of electronics you may choose.

It's the blue ribbon course at RCA Institutes Resident School—among several to suit your inclination and ambition. Other courses in TV & General Electronics, Radio & TV Servicing, and Radio Telegraph Operating.

Classes start four times each year. Applications now being accepted. *Approved for Veterans*

RCA INSTITUTES, INC.
School of Television and Electronic Technology
A Service of Radio Corporation of America

RCA Institutes, Inc., Dept. RER-68
350 W. Fourth St., N. Y. 14, N. Y.

Please send me your FREE catalog of Resident School courses in N. Y.

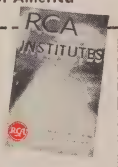

Name.....
Please print

Address.....

City..... Zone....State.....

For Home Study Courses see ad on opposite page.

.030 inch wide encased in plastic insulation. Each conductor rated at 1 amp.—**International Resistance Co.**, 401 N. Broad St., Philadelphia 8, Pa.

TUNABLE RF COILS. Encapsulated units cover a range of 0.1–10,000 μh. *Series 1*, 13/32-inch diameter, ⅞ inch long, 0.1

to 22 μh. *Series 2*, 17/32-inch diameter, 1 inch long, 33–10,000 μh. *Series 3*, 11/32-inch diameter, ⅝ inch long, 0.1–15 μh.—**Vanguard Electronics Co.**, 3384 Motor Ave., Los Angeles 34, Calif.

POTENTIOMETER KIT, *Trimit.* 25-turn pots; screwdriver-adjust; self-locking shaft. For vertical and horizontal hold circuits. Gives service technician greater range of adjustment. Introductory kit contains 5 assorted carbon elements, 5 clip-on adapters which fit chassis holes, and instruction sheet.—**Bourns Laboratories, Inc.**, P. O. Box 2112, Riverside, Calif.

REPLACEMENT FLYBACKS. *HVO 100* replaces G-E RTO-161. *HVO-160* for Zenith S-24978. *HVO-162* for G-E RTO-183.—**Merit Coil & Transformer Corp.**, 2027 Sherman St., Hollywood, Fla.

RF SIGNAL GENERATOR KIT, *model G-30.* 8 bands cover 160 kc-240 mc. To 120 mc in fundamentals. Rf output exceeds 100,000 μv. 400-cycle audio output approximately 15 volts. — **Paco Electronics Co.**, Div. Precision Apparatus Co., Inc., 70-31 84th St. Glendale, L. I., N. Y.

SIGNAL-TRACER KIT, *model Z-80.* Handles all receiver or amplifier signal levels, rf or af. High-gain amplifier for rf and af investigation. High sensitivity for direct pickup of broadcast signals at receiver antenna input terminals. Fine and coarse

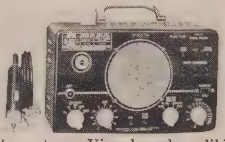

attenuators. Visual and audible signal indicators and output terminals for use with scope or vtvm. Noise test, wattmeter and test amplifier circuits. — **Paco Electronics Co., Inc.** Div. of Precision Apparatus Co. Inc., 70-31 84th St., Glendale 27, N. Y.

DC SCOPE KIT, *model OP-1.* Dc-coupled amplifiers and dc-coupled C-R tube unblanking. Triggered sweep circuit operates on either internal or external signals and may be ac- or dc-coupled. Sweep frequencies provided by switch-selected base rates of 2 and 0.2 msec/cm, and 20, 2 and 1 μsec/cm in conjunction with continuously variable 10-to-1 multiplier. 5ADP2 flat-face scope tube. Edge-lighted grid screen. Vertical attenuator has 12 positions and is calibrated in volts per cm. Horizontal sweep calibrated in time per

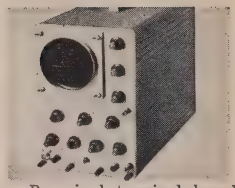

cm. Pre-wired terminal boards used for critical circuits. — **Heath Co.**, Benton Harbor 20, Mich.

CADDY TESTER has tube and rectifier checker built into tube and tool caddy. Leatherette-covered case with compartments

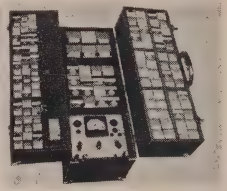

for tubes and tools.—**Vis-U-All Products Co.**, 303 Fuller Ave. NE, Grand Rapids, Mich.

AUTOMATED TUBE TESTER, *Cardamatic model 121.* Uses prepunched cards to set up tester for tube to be tested. Checks

for mutual conductance, gas, grid emission, interelement shorts and leakages. Comes with cards for approximately 325 tubes. — **Hickok Electrical Instrument Co.**, 10531 Dupont Ave., Cleveland 8, Ohio.

TUBE TESTER, *Fast-Check model FC-2.* Two controls to set. Checks for quality, interelement shorts and leakage, gas content

and life expectancy. 7-pin and 9-pin straighteners mounted on panel.—**Century Electronics Co. Inc.**, 111 Roosevelt Ave., Mineola, N. Y.

POCKET TESTER, *Electro-Probe.* Checks for live outlets and determines if voltage is present at fuses, sockets, switches, lines and terminals. Use on all voltages between 110

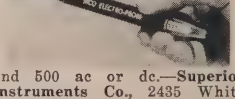

and 500 ac or dc.—**Superior Instruments Co.**, 2435 White Plains Road, New York 67, N. Y.

END

All specifications given on these pages are from manufacturers' data.

RCA INSTITUTES offers you the finest of home study training. The equipment illustrated and text material you get with each course is yours to keep. Practical work with very first lesson. Courses for the beginner and the advanced student. Pay-as-you-learn. You need pay for only one study group at a time.

Send for this FREE Book Now

[RESIDENT SCHOOL courses in New York City offer comprehensive training in Television and Electronics. Day and evening classes start four times each year.
Detailed information on request]

RCA INSTITUTES, Inc. Home Study Dept. RE-68
A Service of Radio Corporation of America
350 West Fourth Street, New York 14, N. Y.

Without obligation, send me FREE 52 page CATALOG on Home Study Courses in Radio, Television and Color TV. No salesman will call.

Name.....
please print
Address.....
City.....Zone.....State.....
Korean Vets! Enter discharge date.....

CANADIANS — Take advantage of these same RCA courses at no additional cost. No postage, no customs, no delay. Send coupon to:
RCA Victor Company, Ltd., 5001 Cote de Liesse Rd., Montreal 9, Quebec
To save time, paste coupon on postcard.

For resident school courses see ad on opposite page

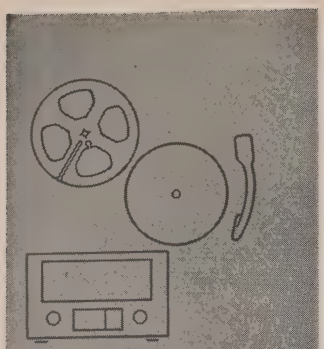

ALL STEREO LEADS TO MADISON FIELDING

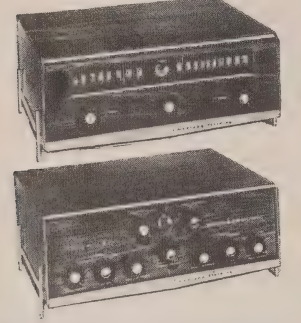

Whatever the choice may be — tape, record, or good old fashioned AM/FM radio, straight or multiplexed — Madison Fielding is the design center of any stereo system. Complete control and amplifier facilities for both monaural and stereophonic sound are built into the perfectly matched Series 330 AM/FM Stereophonic Tuner and Series 320 40-watt Stereophonic Amplifier.

Series 330 Tuner:

Two complete ultra-sensitive tuners on one compact chassis for either AM or FM reception individually, or, with a turn of a switch, both signals can be made available simultaneously. Multiplexed output is provided for by use of one adapter.

Series 320 40-watt Amplifier:

In addition to individual controls for each channel, the unit features a Master Volume Control, which controls both levels simultaneously for stereo. When used monaurally, it will serve as a complete electronic crossover system to feed separate woofer and tweeter.

For further information, write to:

Madison Fielding Corp.
5 Lorimer Street
Brooklyn, New York

The center of your stereo system.

Technicians' News

NEW ASSOCIATION FORMED

A group of television technicians have banded together to form the Television Electronic Service Association of Central Missouri. Officers of the association are: Vernon Towner, Towner Radio & TV, Jefferson City, president; Al Idle, A & B Radio & TV, Jefferson City, vice president; John Reinsch, TV Service Center, Jefferson City, secretary-treasurer; Dennison Houghton, Peoples Radio Co., Columbia, director. Additional directors are to be appointed.

LESA FORMS

West Branch, Iowa, reports the organization and incorporation of the Linn Electronic Servicemen's Association (LESA).

The group plans to promote and maintain a high standard of ethics among retail electronic service technicians and dealers.

LESA officers are: Dick Reeder, president; Marvin Kirkpatrick, vice president; Tom Cours, secretary; George Rizzio, treasurer, and Louis Guetzko, Ralph Brink and Eugene Stick, directors.

LICENSE SUSPENDED

In the first action of its kind, the TV Board of Examiners of the City of Long Beach, N. Y., suspended the TV technician licenses of Norman Litman, Samuel Kaperstein and Bart Randazzo, operators of Melody Mart.

The board's decision states that these licensees had deceived and misled the complainant, Mrs. Harold Miller, by failing to give information to the complainant as to the condition of the TV set—warranting the set to be worth the expenditure for repairs, when in fact knowing that the cathode-ray tube was in poor condition and needed a booster, and by giving customer bill which did not reflect the true items of material used in repair.

The suspension was to have ended Feb. 28. However, an application for a new license to take effect on that date was denied.

TESA–MISSOURI VOTES

At a recent meeting in Columbia, Mo., of the Television Electronic Service Association of Missouri (TESA–Mo) a seminar on service business operations was conducted by Wayne Lemons and a technical discussion on servicing instrument development by David Doss.

New officers of the group are: Ed

"ONE DOLLAR" buys

As much as $15 worth — Everything Brand New and sold to you with a money back guarantee.

DEDUCT 10% ON ANY ORDER OF $10 OR OVER

Plus a FREE SURPRISE PACKAGE

☐ 100 – ASSORTED FUSES popular sizes.....$1
☐ 100 – ASST. ½ WATT RESISTORS some 5%..$1
☐ 70 – ASSORTED 1 WATT RESISTORS.....$1
☐ 35 – ASSORTED 2 WATT RESISTORS.....$1
☐ 50 – ASST. TUBULAR CONDENSERS.....$1
☐ 10 – 6' ELECTRIC LINE CORDS with plugs....$1
☐ 5 – TV CHEATER CORDS with both plugs.....$1
☐ 4 – 50' SPOOLS HOOK-UP WIRE 4 colors.....$1
☐ 50 – STRIPS ASST. SPAGHETTI best sizes....$1
☐ 100 – ASST. RUBBER GROMMETS best sizes..$1
☐ 100' – TWIN LEAD-IN WIRE 300Ω heavy duty..$1
☐ 50' – FLAT 4-CONDUCT. WIRE many purposes..$1
☐ 25'—INSULATED SHIELDED WIRE $1
☐ 1 – $7 INDOOR TV ANTENNA hi-gain 3 section..$1
☐ 20 – ASST. TV KNOBS, ESCUTCHEONS, Etc..$1
☐ 3 – ASST. TOGGLE SWITCHES spst, dpdt, etc..$1
☐ 6 – ASST. SLIDE SWITCHES spst, dpdt, etc....$1
☐ 4 – BAKELITE KNIFE SWITCHES dpdt $1
☐ 15 – ASST. ROTARY SWITCHES $15 worth....$1
☐ 100' – FINEST NYLON DIAL CORD best size...$1
☐ 200 – SELF TAPPING SCREWS #8 x ½" $1
☐ 35 – ASST. RADIO KNOBS screw and push-on...$1
☐ 100 – KNOB SPRINGS standard size ⅜" x ½"..$1
☐ 100 – ASSORTED KNOB SET-SCREWS.....$1
☐ 25 – ASSORTED CLOCK RADIO KNOBS.....$1
☐ 400 – ASST. H'DWARE screws, nuts, rivets, etc..$1
☐ 50 – ASST. SOCKETS octal, noval and miniature..$1
☐ 20 – ASSORTED TUBE SHIELDS best sizes.....$1
☐ 50 – ASST. MICA CONDENSERS some in 5%..$1
☐ 50 – ASST. CERAMIC CONDENSERS.....$1
☐ 10 – ASST. VOLUME CONTROLS less switch...$1
☐ 5 – ASST. VOLUME CONTROLS with switch...$1
☐ 4 – VOLUME CONTROL HEX NUTS.....$1
☐ 20 – ASST. PILOT LIGHTS popular types.....$1
☐ 10 – PILOT LIGHT SKTS. bayonet type, wired...$1
☐ 50 – ASST. TERMINAL STRIPS 1, 2, 3, 4 lug ..$1
☐ 10 – ASST. RADIO ELECTRO. CONDENSERS.$1
☐ 5 – ASST. TV ELECTROLYTIC CONDENSERS.$1
☐ 15 – ASST. TV COILS sync. peaking, width, etc. ..$1
☐ 25 – ASST. MICA TRIMMER CONDENSERS..$1
☐ 50 – TUBULAR CONDENSERS .001–600v.....$1
☐ 15 – TUBULAR CONDENSERS .047–600v $1
☐ 50 – TUBULAR CONDENSERS .01–400v.....$1
☐ 2 – ELECTROLYTIC COND. 40/40–450V.....$1
☐ 2 – ELECTROLYTIC COND. 40/10/10–450v....$1
☐ 30 – FP CONDENSER MOUNTING WAFERS..$1
☐ 3 – ELECTROLYTIC COND. 80–450v.....$1
☐ 3 – ELECTROLYTIC COND. 50/30–150v.....$1
☐ 15 – TUBULAR CONDENSERS .015–1600v.....$1
☐ 10 – HV TUBULAR CONDENSERS .006–1600v..$1
☐ 10 – HV TUBULAR CONDENSERS .001–6000v..$1
☐ 10 – HV TUBULAR CONDENSERS .005–6000v..$1
☐ 35 – MICA COND. 20–100 mmf & 15–270 mmf.....$1
☐ 35 – MICA COND. 20–470 mmf & 15–680 mmf.....$1
☐ 35 – MICA COND. 20–820 mmf & 15–1000 mmf $1
☐ 35 – CERAMIC COND. 20–5 mmf & 15–10 mmf....$1
☐ 35 – CERAMIC COND. 20–25 mmf & 15–47 mmf...$1
☐ 35 – CERAMIC COND. 20–56 mmf & 15–82 mmf ...$1
☐ 35 – CERAMIC COND. 20–100 mmf & 15–150 mmf..$1
☐ 35 – CERAMIC COND. 20–270 mmf & 15–470 mmf..$1
☐ 35 – CERAMIC COND. 20–1000 mmf & 15–1500 mmf..$1
☐ 35 – CERAMIC COND. 20–2000 mmf & 15–5000 mmf..$1
☐ 50 – 100Ω ½ WATT RESISTORS 5%.....$1
☐ 75 – 470KΩ ½ WATT RESISTORS 10%.....$1
☐ 50 – 15KΩ 1 WATT RESISTORS 10%.....$1
☐ 50 – 470KΩ 1 WATT RESISTORS 10%.....$1
☐ 25 – 2.2Ω 2 WATT RESISTORS 5%.....$1
☐ 25 – 100KΩ 2 WATT RESISTORS 10%.....$1
☐ 10 – ASST. WIREW'ND RES. 5, 10, 20 watts...$1
☐ 3 – AUDIO OUTPUT TRANS. 50L6 type $1
☐ 3 – AUDIO OUTPUT TRANS. 6K6 or 6V6 type...$1
☐ 3 – I.F. COIL TRANSFORMERS 456 kc.....$1
☐ 3 – I.F. COIL TRANSFORMERS 10.7 mc FM ...$1
☐ 4 – OVAL LOOP ANTENNAS asst'd hi-gain types ..$1
☐ 3 – LOOPSTICK ANT. new ferrite adjustable.....$1
☐ 12 – RADIO OSCILLATOR COILS 456 kc.....$1
☐ 3 – ½ MEG VOLUME CONTROLS with switch ..$1
☐ 5 – 50K VOLUME CONTROLS less switch.....$1
☐ 10 – SURE GRIP ALLIGATOR CLIPS.....$1
☐ 1 – GOLD GRILLE CLOTH 14"x14" or 12"x18"..$1
☐ 1 – 5" PM SPEAKER alnico #5 magnet.....$1
☐ 5 – SETS SPEAKER PLUGS wired $1
☐ 10 – SETS PHONO PLUGS and PIN JACKS..$1
☐ 2 – $2.50 SAPPHIRE NEEDLES 4000 playings...$1
☐ 5 – DIODE CRYSTALS 2–IN21 2–IN23 1–IN64 ..$1
☐ 2 – SELENIUM RECTIFIERS 1–65 ma & 1–150 ma $1
☐ 1 – TV VERT. OUTPUT TRANS. 10 to 1 ratio ...$1
☐ 5 – TV CRT. SOCKETS with 18" leads.....$1
☐ 5 – HI-VOLT. ANODE LEADS with 18" leads....$1
☐ 1 – TV RATIO DETECTOR TRANS. 4.5 mc. ...$1
☐ 1 – SET TV KNOBS standard type incl. decals $1
☐ 1 – LB SPOOL ROSIN CORE SOLDER 40/60...$1
☐ 6 – SPIN TIGHT SOCKET SET 3/16" to 7/16"..$1
☐ 3 – TV ALIGNMENT TOOLS 5", 7", 12" $1
☐ $15 – "JACKPOT" TELEVISION PARTS.....$1

HANDY WAY TO ORDER—Simply tear out advertisement and pencil mark items wanted (X in square is sufficient); enclose with money order or check. You will receive a new copy of this ad for re-orders.

ON SMALL ORDERS—Include stamps for postage, excess will be refunded. Larger orders shipped express collect.

BROOKS RADIO & TV CORP.
84 Vesey St. Dept. A, New York 7 N.Y.

Engle, Crystal City, president; Dennison Houghton, Columbia, northeast vice president; M. C. Crane, St. Joseph, northwest vice president; W. A. Pryer, Mountain Grove, southwest vice president; E. Carroll, Cabool, southeast vice president; Carrol King, Lamar, secretary, and Carl Adcock, Aurora, treasurer. To the board of directors for two years: Robert Matteson, Florissant; Howard J. Freiner, St. Louis; Wayne Lemons, Buffalo, and Arrent Patterson, Springfield.

ATLANTA ELECTION

The Radio–Television Service Association of Greater Atlanta Inc., at their annual election meeting in Atlanta, Ga., elected Kermit M. Smith, Decatur Radio & Television Service, as their new president. L. J. Webber, Webbers Radio & Appliance Co., became first vice president; W. H. Steed, Radio Doctor, second vice president; M. Daniels, Fulton Appliance Service, third vice president; Pierce McGee, McGee's Television & Radio Service, secretary, and Joe Mull, Mull Television Co., treasurer.

Elected chairman of the board of directors was Red Tarsa, Riteway Television Co. Board members are Marvin Cochran, Atlanta Electronic Service; W. T. Edwards, Edwards Radio-Television Co., and Arthur Powell, Powell Electronics.

KCTSA MEETING

A program outlining how to avoid taking of "NSF" and "no account" checks was presented by the National Check Protection Service at a regular meeting of the King County Television Service Association Inc. (KCTSA). The meeting was held at the Stewart Hotel in Seattle, Wash.

At the annual meeting held earlier this year, Clayton Faller was elected president for the coming fiscal year. Other members voted to office were: Loyal Gudel, vice president, and Jim Humphrey, secretary-treasurer. Among the new directors are Connie Jenkins, Robert Kelly and Frank Shelton. Holdover directors are Paul Morvee, Clinton Cox and Carl Pitman. Harold Hart, last year's president, will automatically serve on the board this year. END

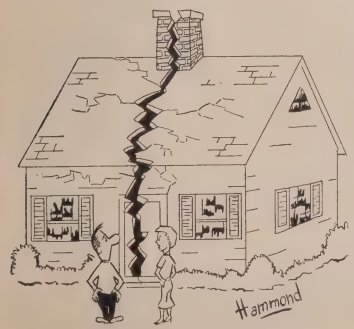

"The Hi-Fi has got to go."

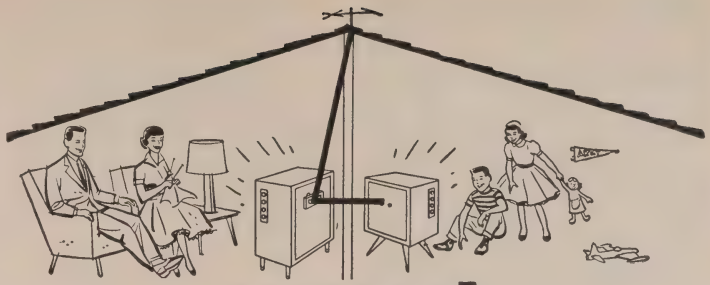

NOW!

sharper, clearer pictures on 1, 2 or 3 tv sets with 1 antenna

NEW B-T LABS B-23 TWO-SET BOOSTER

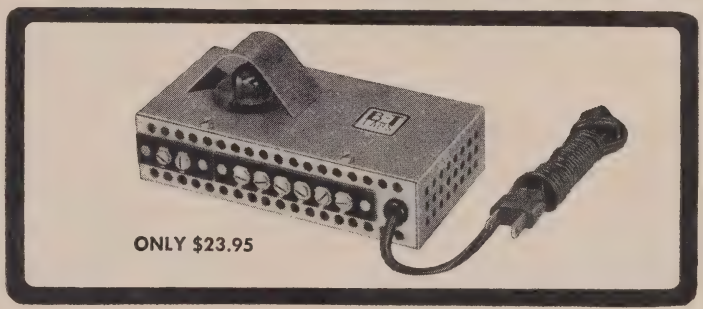

From B-T comes the most important step forward in better TV reception for 1958 – a broadband TV amplifier that boosts signal strength on all VHF channels 2-13 and operates 1 or 2 or 3 TV sets with one antenna. No tuning is required.

combines two functions in one

A single B-23 –

● **BOOSTS** signal strength on 1 or 2 or 3 TV sets – up to 6 db gain operating two TV sets from one antenna.

● **COUPLES** 2 or 3 TV sets – using the present antenna. Outperforms non-powered couplers in any reception area by more than 2 to 1.

check these B-23 features:

● Ideal for color – add a color TV set and keep present black-and-white set, use the same antenna – the result, sharper, clearer pictures on both sets.
● Low noise figure – designed to work with new VHF sets.
● Reduces interference.
● Easily installed at antenna terminals of set. Can be mounted out of sight at the rear of the receiver.
● Automatically amplifies channels 2-13.
● Ideal small TV system (motels, multiple dwellings, TV showrooms).

FOR OPERATING 3 TO 8 TV SETS, USE THE B-T LABS DA8-B – MORE THAN 10 DB GAIN ON ALL VHF CHANNELS.

The DA8-B Distribution Amplifier is a broadband, all-channel unit that requires no tuning, impedance matching devices, pre-amps or other special fittings. Ideal for all small TV systems including garden apartments, motels, TV showrooms serving more than 3 sets. Approved for color. only $94.50.

The B-23, the DA8-B, and a host of other B-T quality engineered products to improve television reception,are available at electronic parts distributors.

For further information, use coupon.

B-T LABS BLONDER-TONGUE LABS., INC.
9 Alling Street, Newark 2, New Jersey

Please send me literature covering:
☐ *B-T B-23* ☐ *B-T TV Accessories*

Name_____
Address_____
City_____ Zone___ State_____
RE-6

POWERING
4 OUT OF 5
of the world's
greatest amplifiers

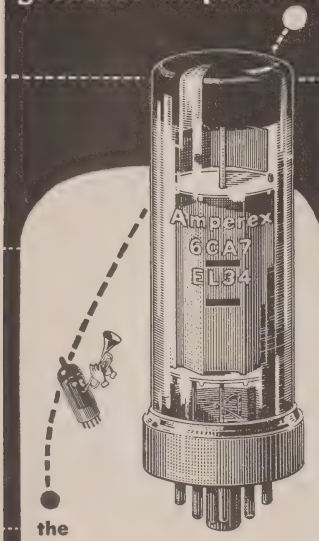

the
Amperex
6CA7/EL34

HIGH-POWER OUTPUT PENTODE

High-fidelity authorities are not in agreement as to which is "best" among the handful of genuinely great power amplifier designs available today. But one thing they know for sure—at least 4 out of 5 of the contenders have 6CA7/EL34's in the output stage. No other comparable tube combines to the same degree the 6CA7's exceptional linearity, high power dissipation and low drive-voltage requirements. It is a true pentode design, with a separate suppressor grid that controls the space charge, resulting in greater linearity on reactive speaker loads than is possible with competitive beam-power tetrodes. A single pair of 6CA7's in push-pull has been successfully used in power amplifiers delivering up to 100 watts undistorted output.

OTHER **Amperex TUBES** FOR HIGH-FIDELITY AUDIO APPLICATIONS:

EL84/6BQ5 9-pin power pentode; 17 W PP
EF86/6267 Low-noise high-μ pentode
ECC81/12AT7 Low-noise medium-μ dual triode
ECC82/12AU7 low-noise low-μ dual triode
ECC83/12AX7 Low-noise high-μ dual triode
GZ34 Cathode-type rectifier; 250 ma.
EZ80/6V4 9-pin rectifier; cathode; 90 ma.
EZ81/6CA4 9-pin rectifier; cathode; 150 ma.

At All Leading Electronic Parts Distributors

Amperex
ELECTRONIC CORP.
230 Duffy Ave., Hicksville, Long Island, N.Y.

Patents

PASSIVE RESPONDER

Patent No. 2,812,428

Karl Rath, New York, N. Y. (Assigned to Radio Patents Co., New York, N. Y.)

A conventional radio transmitter needs power to operate it. However a remote station can be set up to pick up rf from another station, modulate it, then retransmit it, so no local power is required. The master station is shown at the right of the diagram. It is a simple superregenerator, self-quenched at about 50 kc. The carrier may be 50 mc which is radiated from A1 to the remote antenna A2. The output of a superregenerator circuit is composed of pulses of rf.

The receiver tank is tuned to the same carrier and is shunted by a resonant quartz crystal. Like any vibrating device, the crystal absorbs power one instant, returns it the next. Thus, after a short delay, the crystal generates rf of the same frequency as that received, and power is radiated from A2. The microphone (when spoken into) modulates the rf. Due to time delay by the crystal, the pulses received at A1 arrive between intervals of superregenerator pulses.

When a modulated signal is picked up by a superregenerator, the receiver oscillations are similarly modulated. For that reason it is possible for an unauthorized listener to tune to A1 and receive the messages from A2. To avoid this possibility, a local scrambling oscillator is added as shown. The same scrambling process is also applied to the incoming audio signal to cancel out the interference. Therefore the reproduced signal is free of interference, yet secrecy is preserved so far as other stations are concerned.

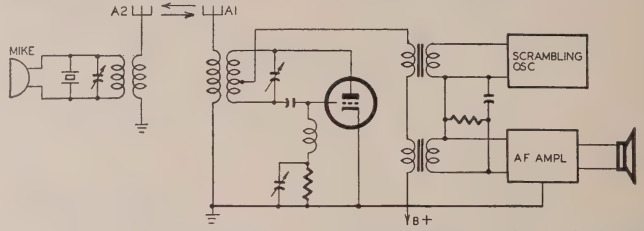

AUTOMATIC TELEPHONE DIALING

Patent No. 2,813,931

Lee de Forest, Los Angeles, Calif.

This invention eliminates dialing errors and expedites dialing calls. It is attached to one side of a dial telephone and has a hinged drive mechanism that drops down on the dial. The mechanism swings up so the dial can be operated manually. When the arm is lowered, a large gear locks on the dial so that both turn for automatic dialing.

A punched card is needed for each phone number. To make a call, the desired card is moved (on its pivot) from the storage to the operating position. See diagram. A metal plate over the card holds it in place.

A switch starts the motor. A set of gears drives the rack R together with a crossbar and a set of seven metal fingers. The fingers start to move from the top of the card, and each can complete a circuit upon contacting the metal plate (through punch holes in the card). Each finger is synchronized by a rotary switch so it is in the circuit in sequence.

As R moves downward, the first finger moves beneath the card until it contacts the metal plate through the U perforation in the card (which is punched for UL 1-2345). At this time the dial has reached letter U also. The contact releases the gear mechanism through solenoid action. R flies back to its starting position, and the dial returns to its resting place. Then R advances again, this time with the second finger connected into the circuit. When this metal part reaches the perforation in letter L, contact is again made and the gear train returns to its starting position. Of course, L has now been dialed. In this way the five digits are dialed in turn.

Interested readers are referred to the patent specification for complete details. END

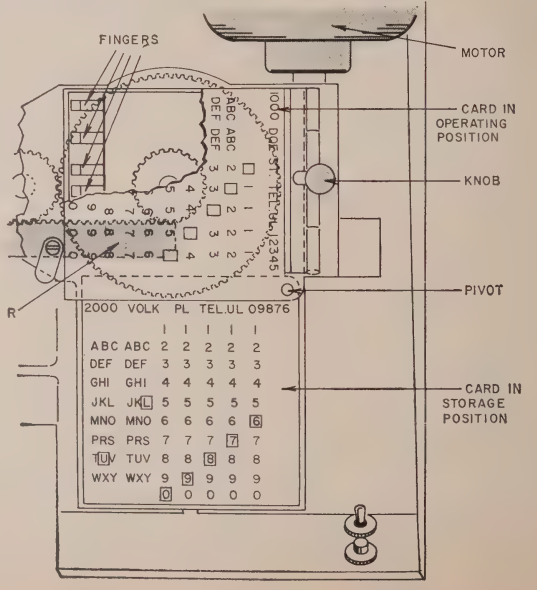
FINGERS
MOTOR
CARD IN OPERATING POSITION
KNOB
PIVOT
CARD IN STORAGE POSITION
R
2000 VOLK PL TEL.UL 09876
ABC ABC 2 2 2 2 2
DEF DEF 3 3 3 3 3
GHI GHI 4 4 4 4 4
JKL JKL 5 5 5 5 5
MNO MNO 6 6 6 6 6
PRS PRS 7 7 7 7 7
TUV TUV 8 8 8 8 8
WXY WXY 9 9 9 9 9
0 0 0 0 0

radio-electronic Circuits

SPHERICAL TWEETER

The ideal pulsating sphere of all acoustics textbooks is cleverly approximated by K. H. Becker in an arrangement which appeared in *Funkschau, 11-56.*

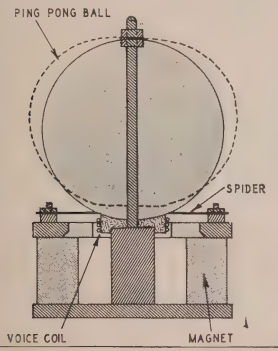

The high-frequency directivity of the ordinary cone loudspeaker is very marked, and the usual remedies are diffusing contraptions or multiple-speaker arrangements.

The loudspeaker represented in the diagram replaces the cone by a spherical, ellipsoidal or ovoidal body. One pole or end is clamped and the other pole glued to the moving coil.

To improve its elasticity, it is recommended that slots be cut along the meridians between the two poles.

The displacement of the moving coil alternately expands and contracts the pulsating sphere. The sound is radiated toward the sides and upward.

The best practical results have been obtained using a ping-pong ball, with two diametrically opposed axial slots. The frequency range then extends from 2,000 to 15,000 cycles.—*A. V. J. Martin*

30–50-MC BOOSTER

Some of the less-expensive FM receivers for monitoring fire, police and similar radio services in the 30–50-mc band do not have enough gain for good quieting when receiving weak mobile stations. This low-noise cascode booster will improve these receivers.

L2 and L3 are Cambridge Thermionic Corp. (CTC) type LS3 30-mc inductors. L1 and L4 are antenna and output coupling coils. Each should be adjusted for maximum signal. Use hookup wire and start with about six turns around

all new edition
VOL. III. NO. 1
up-to-date component prices
PLUS
the quick easy way to figure service charges
Dave Rice's
OFFICIAL PRICING DIGEST
Flat rate and hourly service charges, based on and showing regional and national averages, plus up-to-date list or resale prices on over 63,000 components. Arranged alphabetically by manufacturers and products, numerically by part number. Compact, convenient size fits in tube caddy, toolbox or pocket. $2.50 per copy from your distributor.
ELECTRONIC PUBLISHING COMPANY, INC.
180 N. WACKER DRIVE, CHICAGO 6, ILL.

Another Sencore Time-Saver
SENCORE FILAMENT CHECKER
MODEL FC-4
★ COMPLETELY NEW
★ MORE VERSATILE
★ LOWER COST
Quickly finds any open filament. Especially handy for servicing series filament TV sets and radios; only checker that checks all octals, loctals, 7 and 9 pin miniatures automatically.
Continuity and voltage tester — no switches, merely plug in test leads.
Only $29.95
DEALER NET WITHOUT LEADS $2.75
POPULAR SENCORE PRODUCTS
• Transistor Tester
• Leakage Checker
• Filament Tester
• Voltage Regulator
• Bias Supply
AT LEADING DISTRIBUTORS EVERYWHERE
Mfg by SENCORE SERVICE INSTRUMENTS CORP.
171 OFFICIAL RD., ADDISON, ILL.

THIS IS THE WAY A GREAT TAPE RECORDER IS BUILT...

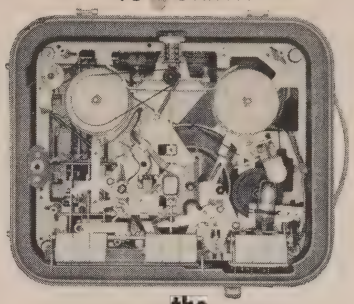

the new imported
NORELCO®
'CONTINENTAL'
world's most advanced all-in-one portable
TAPE RECORDER
Engineered by Philips of the Netherlands, world pioneers in electronics
Precision-crafted by Dutch master technicians
Styled by the Continent's top designers
Three speeds (7½, 3¾ and 1⅞ ips)... twin tracks...pushbutton controlled
Special narrow-gap (0.0002 in.) head for extended frequency response
Built-in wide-range Norelco speaker
Also plays through external hi-fi set
For the name and address of your nearest Norelco dealer,

NORTH AMERICAN PHILIPS CO., INC.
High Fidelity Products Division
230 DUFFY AVENUE, HICKSVILLE, L.I., N. Y.

DYNAKIT
PREAMPLIFIER

ACCLAIMED AS THE FINEST AVAILABLE—BY LABORATORY TEST OR CRITICAL LISTENING—IN MONEY-SAVING KIT FORM!

This handsome new control unit gives crystal clear, noise-free reproduction from *any* modern program source. Its unique all feed back design by David Hafler sets a new standard of preamplifier performance. The design of the Dynakit preamplifier is a synthesis of outstanding features which produce smoother, more natural sound. Compare these features with any other units regardless of price.

★ Unequalled performance

Actually less than .1% *distortion* under all normal operating conditions: *Response* ±.5 db 6 cps to over 60 kc. Distortion and response unaffected by settings of volume control. Superlative square wave performance, and complete damping on any pulse or transient test.

★ Easiest assembly

All critical parts supplied factory-mounted on XXXP printed circuit board. Eyeleted construction prevents damage to printed wiring. This type of construction cuts wiring time by 50% and eliminates errors of assembly. Open simplified layout offers complete accessibility to all parts.

★ Lowest noise

Integral dc heater supply plus low noise components and circuitry bring noise to less than 3 microvolt equivalent noise input on RIAA phono position. This is better than 70 db below level of 10 millivolt magnetic cartridge.

★ Finest parts

1% components in equilization circuits to insure accurate compensation of recording characteristics. Long life electrolytic capacitors and other premium grade components for long trouble-free service.

★ High flexibility

Six inputs with option of extra phono, tape head, or mike input. Four AC outlets. Controls include tape AB monitor switch, loudness with disabling switch, full range feedback tone controls. Takes power from Dynakit, Heathkit, or any amplifier with octal power socket.

★ Outstanding appearance

Choice of bone white or charcoal brown decorator colors to blend with any decor. Finished in indestructible vinyl coating with solid brass escutcheon.

★ Best buy

Available from your Hi-Fi dealer at only $34.95 net (slightly higher in the West), and yet the quality of performance and parts is unexcelled at any price.

Descriptive brochure available on request. Pat. Pending

The Dynaco Pre-Amplifier has been selected for display at the Brussels Worlds Fair as representative of highest quality American High-Fidelity equipment!

DYNACO INC.

617 N. 41st St., Philadelphia, Pa.

Export Division:
25 Warren St., New York 7, N.Y.

the bottom ends of L2 and L3. Neutralizing coil L^n should be approximately 40 turns of No. 24 enameled wire wound on a ¼-inch form. Vary the number of turns and the spacing for minimum noise.

The tuned circuits can be aligned

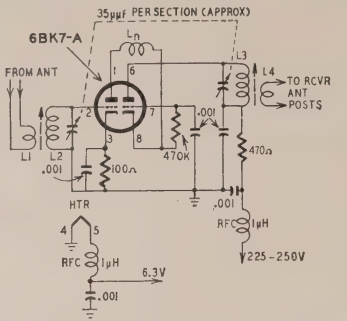

so they track reasonably well by carefully adjusting the slugs in L2 and L3. Tracking can be adjusted more precisely by connecting a small trimmer of around 5 $\mu\mu$f across each section of the tuning capacitor and varying their settings along with those of the tuning slugs for optimum performance.

TRANSISTOR CODE OSCILLATOR

Two transistors, a resistor, a capacitor, a loudspeaker, a telegraph key and a 1.5-volt penlight cell are all that are required for this simple and reliable code-practice oscillator. Volume is sufficient for classroom use, especially with an efficient loudspeaker. A direct-coupled positive-feedback circuit is used

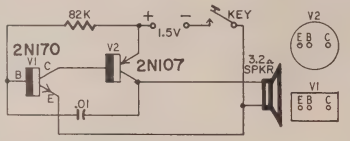

with one n-p-n transistor and one p-n-p transistor.

Don't reverse the transistors or the voltage source polarity. The oscillator frequency can be lowered by using more capacitance, more resistance, or both. With the circuit constants given, the frequency is between 600 and 800 cycles. If one of the widely advertised 89c surplus telegraph keys and 99c manufacturer's surplus speakers are used, total cost will be less than $5. Keying is clean and crisp if key contacts are not dirty. Total battery drain is less than 4 ma, low enough for obtaining many ham tickets before the first penlight cell is exhausted!—*Harold Balyoz, W6YBP.* END

HEARING RANGE

By Jeanne DeGood

Since Hi-Fi gives me any tone
That any human hears,
What sounds are there I might have known
If they'd improved my ears?

OPPORTUNITY ADLETS

Rates—50c per word (including name, address and initials). Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount, 10% for 12 consecutive issues. Misleading or objectionable ads not accepted. Copy for August issue must reach us before June 15, 1958.

RADIO-ELECTRONICS,
154 West 14 St., New York 11, N. Y.

"SHURE-TRAK" Liquid rubber-conditioner for phono drives, recorder belts, idler wheels. Cleans, restores, maintains traction. Unconditionally guaranteed. $1. BROWN'S, Box 4124, Philadelphia 44, Pa.

HIGH-FIDELITY SPEAKERS REPAIRED. AMPRITE Speaker Service, 70 Vesey St., New York 7, N.Y. BA 7-2580.

CASH PAID! Sell your surplus electronic tubes. Want unused, clean transmitting, special purpose, receiving, TV types, magnetrons, klystrons, broadcast, etc. Also want military & commercial lab test and communications gear. We swap too, for tubes or choice equipment. Send specific details in first letter. For a fair deal write, wire or telephone: BARRY, 512 Broadway, New York 12, N.Y. Walker 5-7000.

RECORDERS, Hi-Fi, Tapes. Free Wholesale Catalogue. CARSTON, 215-T East 88th St., New York 28, N.Y.

Ampex, Concertone, Crown, Ferrograph, Presto, Tandberg, Pentron, Bell, Sherwood, Rek-O-Kut, Dynakit. Others. Trades. BOYNTON STUDIO, 10RE Pennsylvania, Yonkers, N. Y.

START A FAST GROWING, money making business. Operate a self-service tube tester route spare or full time. No selling. Stores make money for you every open hour. Send for FREE booklet describing this proven business. CENTURY ELECTRONICS, 111-J Roosevelt Ave., Mineola, N. Y.

LABORATORY QUALITY equipment and Military Surplus Electronics bought, sold. ENGINEERING ASSOCIATES, 434 Patterson Road, Dayton 9, Ohio.

DIAGRAMS FOR REPAIRING RADIOS $1. Television $2. Give make, Model. DIAGRAM SERVICE, Box 672-RE. Hartford 1, Conn.

DISCOUNTS up to 50% on hi-fi Amplifiers, tuners, speakers, tape recorders; individual quotations only; NO CATALOGS. CLASSIFIED HI-FI EXCHANGE, RE 2375 E. 65 St., Brooklyn 34, N.Y.

ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING equipment repaired. HAZELTON INSTRUMENT Co., 128 Liberty Street, New York, N.Y.

TELEVISION Tuner Repairs. DAN'S TELEVISION LABORATORY, 619A Sunrise Highway, Babylon, N.Y.

BUILD YOUR OWN printed circuits. Instructions, projects—$1. CIRCUIT LABORATORIES, Box 52RE, Norwalk, Conn.

DEBTS COLLECTED everywhere or no charge. GRANT AGENCY, 34 Park Row, New York 38, N. Y.

WORLD RENOWNED Hartley Speakers now available to Dealers, Servicemen, custom installers lowest franchise requirements in High Fidelity industry write to HARTLEY PRODUCTS COMPANY 521 East 162nd St., New York 51, N.Y.

DISCOUNTS TO 50%, recorders, tapes, hi-fi components, consoles, photograph equipment. Request specific prices only. LONG ISLAND AUDIO & CAMERA EXCHANGE, 3 Bay 26th St., Brooklyn 14-R, N.Y.

DELAYED LIGHT SWITCHES, home or automobile. Free Literature. KUHN & CO., 1212 Detroit St., Flint 3, Mich.

5-inch TV Test Tube. Model 5FP7. Brand-new, using an improved plug-in harness converter. See article "Economy Test Tube," Radio-Electronics, March, 1958, page 57. Essential for vertical chassis-non-ion. Guaranteed. $3, postpaid. LION PRODUCTS, Box 205, Brooklyn 15, N. Y.

DIAGRAMS! Repair Information! Radios—Amplifiers—Recorders $1 Televisions $1.50. Give make, model, chassis. TV MILTIE, Box 101EA, Hicksville, N.Y.

SELF-SERVICE TUBE TESTERS, $25 to $50. Used-reconditioned complete with signs and floor model cabinets. Get into a profitable business with a minimum investment. Write, ED MOERKE, P.O. Box No. 264, Zion, Ill.

HIGH-PAYING JOBS, opportunities; foreign, USA. All Trades. Companies pay fare. For information, write Dept. 57U, National Employment Information, 1020 Broad, Newark, N.J.

PROFESSIONAL Electronic Projects—Organs, Timers, Intercoms, Counter, etc. $1 each. List Free. PARKS, Box 1665, Lake City Station, Seattle 55, Wash.

MIDGET radio kit $1 plus postage. SMITH, Box 98, Frank, Pa.

SAVE MONEY! Get our price list on all types Radio and TV tubes at Mfrs. prices! 100% guaranteed, all brand new and unused, no mechanical or electrical rejects, not washed or rebranded! 24 hour service! Write United Radio Company, 58 Market St., Newark. N.J.

How Many Hours Have You Used Your Stylus? (Phono Needle)

HI-FI EYE—THE RECORD PROTECTOR—can answer this honestly, **CAN YOU?** A worn stylus **WITH ONLY ONE PLAYING** can wipe all the highs from your valuable records. A simple glance at **HI-FI EYE** tells you the total hours your stylus has been in use. Use this simple means to protect your valuable records. Easily installed. Operation automatic. Designed to sell for $24.95. **SPECIAL INTRODUCTORY OFFER $14.95.** Don't delay, order today. Guaranteed. 6 months warranty. **No C.O.D.'s. California** add 4%. Distributed by.

Hi-Fi Eye Co.
Box 44739 Hancock Station
Los Angeles 44, Calif.

Please mention
RADIO-ELECTRONICS
when answering advertisements

30 Watt Hi-Fi Super Lin Kit
AMP-PREAMP with TRANSISTORIZED FRONT END
FREQUENCY RESPONSE: ± 1 db 10-40,000 cps.; TUBES: uses (1) 6AU6, (1) 12AT7, (1) 12AU7, (2) EL84's, (1) 5Y4-GB. SHIPPING WEIGHT 26 lbs. FL-30
Sale Price..... **$42.00** F.O.B. N.Y.
Send for Free Catalogue
CUTICK ELECTRONICS HI-FI RADIO TV PARTS
171 Washington St., (Dept. R-E), New York 7, N.Y.

TAPE RECORDERS
HI FI COMPONENTS
Tapes—Accessories
UNUSUAL VALUES
Send for Free Catalog
DRESSNER
69-02 RE: 174 St.
Flushing 65, N.Y.
MERITAPE Low Cost, High Quality Recording Tape—in boxes or cans.

TAPE RECORDERS
WHOLESALE PRICES
HI-FI COMPONENTS
NATIONAL BRANDS
WRITE FOR FREE CATALOGUE
CARSTON 215-TD E. 88 ST. NEW YORK 28, N.Y.

July
RADIO-ELECTRONICS
on sale
JUNE 24

ENGINEERING
Prepare for unlimited opportunities of the Electronic Age!
B. S. DEGREE IN 27 MONTHS
Earn your B.S. DEGREE IN 27 MONTHS in Aeronautical, Chemical, Civil, Electrical or Mechanical Engineering; in 36 MONTHS in Mathematics, Chemistry, Physics. Intensive, specialized courses. Comprehensive training in electronics, television, advanced radio theory and design, math, nuclear physics and elec. eng. Engineering Science preparatory courses. Low rate. Graduates in demand. Spacious campus; 20 bldgs., dorms, gym, playing field. Earn part of your expenses in Fort Wayne. G.I. approved. Enter June, Sept., Dec., March. Catalog.
INDIANA TECHNICAL COLLEGE
1768 E. Washington Blvd., Fort Wayne 2, Indiana
Please send me free information on B.S. ENGINEERING DEGREE IN 27 MONTHS as checked.
☐ Electronics ☐ Chemical ☐ Aeronautical
☐ Civil ☐ Mechanical ☐ Electrical
B.S. DEGREE IN 36 MO. in: Math.☐ Chem.☐ Physics☐
Name.....
Address.....

try This one

SHOP HINTS

When more sensitive means aren't available, use a voltage regulator tube as a handy rf indicator. Tubes like the OB3/VR90 or OD3/VR150 serve well. For low power, touch terminal 2 or 5 to the rf source and the gas inside will glow. For higher power, hold the glass envelope in the rf field and the gas inside the tube will glow. The more rf, the brighter the glow in the tube, so that a resonance point is indicated by maximum glow—*S. Clark*

SOLDER AIDS DRILLING

To drill a hole in a metal radio or TV chassis, you must usually center-punch a pilot hole to give the drill an accurate start. The usually deforms the metal around the hole and gives the chassis and its many vibration-sensitive components a severe jolt.

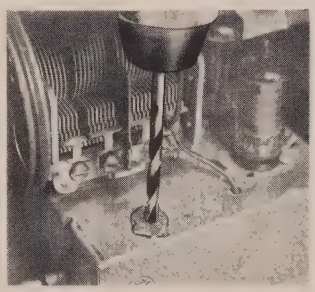

To prevent this, form a thin layer or pool of solder over the spot where the hole will be drilled. The drill won't have any trouble eating into the soft solder and it will enter the chassis surface accurately without a center-punched pilot hole.—*J. C. Alexander*

DRINKING-STRAW SPAGHETTI

It recently occurred to me that wire insulating spaghetti is commonly sold for another purpose at the grocer and five-and-dime stores. Not only is it available at these stores, but it comes in a variety of colors and sizes! I'm referring, of course, to plastic drinking straws. They make ideal wire insulating spaghetti. I often pick up a pack of them right along with my weekly groceries. They're inexpensive too.—*John A. Comstock*

FUSE-CLIP BURNISHER

I clean and brighten the metal clips of tubular fuse holders with a 1½-inch wide strip of fine abrasive cloth wrapped around the ¼-inch shank of a screwdriver. The abrasive cloth is

DYNAKIT
Amplifier Kits
A great amplifier circuit of superb listening quality in money-saving kit form!

MARK III 60 watts **79.95*** net

The new Mark III includes all the sensational attributes of the popular Mark II plus these outstanding deluxe features

★ 60 watts at less than 1% distortion. Instantaneous peak power of 140 watts. IM less than .05 at average listening levels.
★ Choke filtering and low noise circuitry reduce hum and noise to 96 db below 60 watts.
★ New rugged KT-88 tubes and other heavy duty parts used conservatively.

MARK II 50 watts **69.75*** net

The Mark II is the best buy in high power high fidelity kits

★ Ease of assembly due to uniquely simple circuitry and printed circuit construction with factory-mounted parts.
★ Highest stability using patented stabilizing networks with minimum number of phase shifting stages. Suitable for all loudspeaker systems including electrostatic.
★ Dyna Biaset (patent pending) for simplified adjustment and complete freedom from effects of unbalanced components. No balancing adjustments required to meet published specifications.
★ Dynaco Super-Fidelity output transformer with patented para-coupled windings. This is the finest available transformer of its type for the most critical audio uses.

Available from leading Hi-Fi dealers everywhere *Slightly higher in West
Descriptive brochure available on request.

The Dynaco Amplifier has been selected for display at the Brussels Worlds Fair as representative of highest quality American High-Fidelity equipment!

DYNACO INC.
617 N. 41st Street, Philadelphia, Pa.
Export Div.: 25 Warren St., N.Y. 7, N.Y.

SATELLITES
ROCKETS
MISSILES
SPACE PROJECTS
ELECTRONICS—AERONAUTICS TECHNOLOGY

Prepare Now at
NORTHROP
for a brilliant career in the TECHNOLOGICAL WORLD of *Today and Tomorrow!*

This is the Technological Age — the time when men with Engineering Know-how can write their own ticket — pick their own field of specialization in Electronics and Aeronautics. YOU can EARN HIGH SALARY — and have an unlimited future — if you decide NOW to prepare for an ENGINEERING TECHNOLOGY CAREER.

AT NORTHROP INSTITUTE

— one of the country's leading institutions of technological education — you can complete your training in JUST TWO SHORT YEARS.

Recognized throughout the AVIATION and ELECTRONICS INDUSTRIES as an "industry" school, and with thousands of successful graduates now employed by Industry — you owe it to yourself to get complete information about what Northrop Institute can offer you.

Approved for Veterans

Northrop
Aeronautical Institute
An Accredited Technical Institute
1189 W. Arbor Vitae Street
Inglewood 1, California

Mail Coupon for Complete Information

NORTHROP AERONAUTICAL INSTITUTE
1189 W. Arbor Vitae Street, Inglewood 1, Calif.
Please send me immediately the Northrop catalog, employment data, and schedule of class starting dates. I am interested in:

- ☐ Electronic Engineering Technology
- ☐ Aeronautical Engineering Technology
- ☐ Aircraft Maintenance Engineering Technology
- ☐ Master Aircraft and Engine Mechanic
- ☐ Jet Engine Overhaul and Maintenance

Name..... Age..
Address .....
City..... Zone.. State.....
Veterans: Check here ☐ for Special Veteran Training Information.

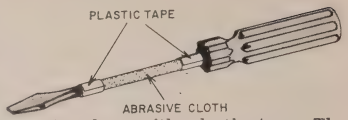

held in place with plastic tape. The fuse-size shank is an almost perfect fit and just a few turns of the handle makes fast work of burnishing the clip's inner surfaces. Since I came across a few really bad cases of high contact resistance due to slip corrosion, I've made it a habit to clean fuse-clip contacts every time I replace a tubular fuse.—*Scott Mack*

BATTERY TO SPEAKER CONNECTIONS

When discarding a dead portable battery, cut out and save any snap-on battery connectors. Many of these can be matched to each other. Next time you want to put connections onto a PM speaker just solder the snap-on clips to the speaker leads.—*A. Von Zook*

TIGHTENING DIAL CORDS

After considerable use, dial cables have a tendency to stretch and to slip on the tuning shafts. There are several ways to remedy slipping dial cables. You can apply nonslip compound to the cable where it goes around the shaft or, if possible, move the cable spring to a place on the drum where it puts more pull on the cable or shorten the cable or replace the old cable with a new one. However, I feel that my method is one of the simplest and most effective.

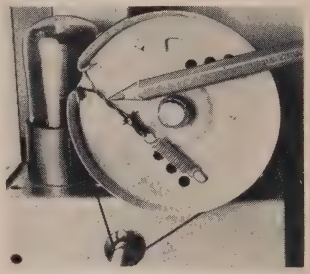

If the cable is in good condition, but simply slips on the tuning shaft, you can tighten it easily. Simply remove the bottom end of the cable spring from the lug of the drum, give the cable a few twists at the place pointed out in the photo, and hook the spring back on the drum lug again. The twists shorten the cable so the spring puts more tension on it. Experiment with the number of twists needed.—*Art Trauffer*

KEEPING THE IRON CLEAN

I keep the tip of my soldering iron clean and free of scale by occasionally holding it against a revolving wire brush. The stiff wire bristles of the brush remove all traces of scale and solder. Then the iron can be readily tinned.—*John A. Comstock* END

MAKE SURE IT FITS!

OXFORD
SPEAKERS

You obtain the finest sound reproduction when you select the proper speaker for the specific application. Each OXFORD SPEAKER is "tailor-designed" to actually "fit the need."

Specify OXFORD when you next require quality speakers. Remember: Oxford quality has consistently been superior for over thirty years.

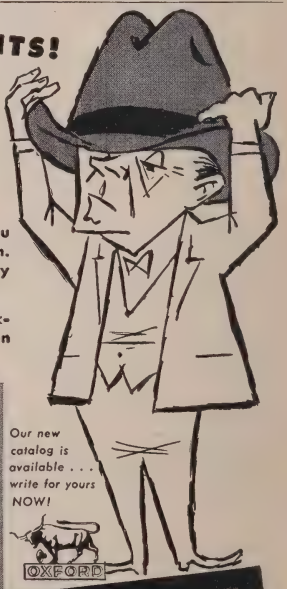

RADIO & TV SPEAKERS
OXFORD Speakers are used by more original set manufacturers — find out why!

OUTDOOR SPEAKERS
For rugged, steady performance under any conditions, OXFORD Weatherproof speakers will meet the need.

DUAL CONE HI-FI SPEAKERS
Oxford's newest development to provide maximum performance. For Hi-Fi and rear deck applications.

PORTABLE RADIO SPEAKERS
More Oxford speakers are used in portable sets than ever before . . . there must be reasons!

Our new catalog is available . . . write for yours NOW!

OXFORD Components, Inc.
Subsidiary of Oxford Electric Corp.
556 West Monroe Chicago 6, Ill.
Export: Reburn Agencies, New York City
In Canada: Atlas Radio Corp., Ltd., Toronto

Technotes

WATERLOGGED AUTO ANTENNA

Sometimes the insulation at the bottom of an auto antenna wears or breaks, allowing water to leak down the antenna, grounding it out. A fast, temporary remedy is to slip a boot from the end of an auto-brake master cylinder over the antenna and down to the cowl, forming an effective seal.—*E. Mayover*

DEFECTIVE BAR GENERATOR

This complaint concerned a color bar generator. When the generator was used to drive known good color TV receivers, only gray bars were produced, with no visible color.

It was a Telechrome generator, using the output circuit shown in the diagram. We started checking waveforms and found a normal signal at the grid of the tube. Evidently, high-frequency attenuation was taking place in the plate circuit.

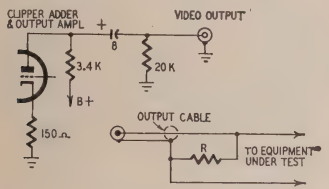

It was apparent from the circuit diagram that the plate load (3,400 ohms) was much too high to obtain high-frequency output. However, the output cable is a branch of the ac plate load. We checked the cable and found no terminating resistor (R)—it had evidently been removed by someone who thought that it didn't make any difference or something. We connected a 75-ohm resistor across the cable's terminals and presto—we were back in the color business.—*Robert G. Middleton*

MOTOROLA TS-539

Symptom: No agc, picture comes in momentarily after channel selection, then blanks out.

Measure the agc voltage at the tuner's agc terminal with no signal present. There should be 1 volt at this point. If no agc is present and the 6AU6 agc tube checks good, try replacing the 6DQ6 horizontal output. If this tube is shorted (and this has happened several times without noticeably affecting brightness or blowing the fuse), no agc will be developed. On one particular receiver, the symptoms

NEW—JUST OFF THE PRESS!

ELECTRONIC PUZZLES AND GAMES

By Matthew Mandl
Gernsback Library
Book No. 70
128 pages
Paper-cover edition only $1.95

More fun than a CIRCUS

Make your own
ELECTRONIC PUZZLES and GAMES

Now build, plan and play your own electronic games. Anyone from Cub Scout to engineer can do it and enjoy it. This new Gernsback Library book shows you how to make all of them—from a simple knife-switch to a complicated space-travel game. A wonderful book to start a boy off on electronics. All you need is a soldering iron, wire, batteries, flashlight bulbs and a few simple tools. Layout drawings outline each puzzle or game and there are photographs of each basic type. Kids from 8 to 80 will love this book. It's more fun than a circus. Order your copy today!

You can make these games . . .

- Knife switch puzzle
- Double indicator puzzle
- Street light puzzle
- River crossing puzzle
- Little thinker
- Twenty one
- Hide-and-seek
- Trip to the Shore
- Jet plane game
- Cross-country race
- Space-travel game
- Mystery safe puzzle
- Adding machine puzzle
- Magic number puzzle
- Prospecting puzzle
- Hidden word puzzle
- Satellite game
- Tri-target game
- Basket-catch game
- Horse race game

Plus a complete index

OTHER NEW GERNSBACK BOOKS

69—Electronic Hobbyists' Handbook	$2.50
68—TV and Radio Tube Troubles	2.90
67—Elements of Tape Recorder Circuits	2.90
65—Servicing Color TV	2.90
64—Understanding Hi-Fi Circuits	2.90
63—Transistor Circuits	2.75
62—TV—It's a Cinch	2.90
61—Transistor Techniques	1.50
60—Rapid TV Repair	2.90

SEE YOUR DISTRIBUTOR OR MAIL THIS COUPON TODAY

Gernsback Library, Inc. Dept. 68
154 West 14th St., New York 11, N. Y.

☐ No. 70—Electronic Puzzles and Games
☐ 69 ☐ 68 ☐ 67 ☐ 65 ☐ 64 ☐ 63 ☐ 62 ☐ 61 ☐ 60

My remittance of $..... is enclosed.
Please send me the books checked, postpaid.

Name.....
please print
Street.....
City.....Zone.....State.....

GET INTO ONE OF THESE TOP OPPORTUNITY FIELDS

ELECTRICITY
—Electronics or TELEVISION
—Radio-Color TV

TRAIN IN THE GREAT SHOPS OF

COYNE OLDEST, BEST EQUIPPED SCHOOL OF ITS KIND IN U. S.

Veterans and Non-Veterans—Prepare for a better job *NOW* that *offers a real future, too!* Get practical training in TELEVISION—RADIO—ELECTRICITY—ELECTRONICS—(Refrigeration & Electric Appliance Repair can be included). Learn on real equipment—no advanced education or previous experience needed. Lifetime employment service to graduates.

Finance Plan—enroll now, pay most of tuition later. Part time employment help to students.

FREE BOOK Clip coupon for Big Free Illustrated Book. No salesman will call. Act NOW.

B. W. COOKE, JR., President
COYNE ELECTRICAL SCHOOL FOUNDED 1899
A TECHNICAL TRADE INSTITUTE OPERATED NOT FOR PROFIT
500 S. PAULINA St., CHICAGO, Dept. A8-5C
ELECTRICITY • TELEVISION • RADIO • REFRIGERATION • ELECTRONICS

B.W. COOKE, JR., Pres., COYNE ELECTRICAL School
500 S. Paulina St., Chicago 12, Ill., Dept. A8-5C
Send FREE BOOK and details on:
☐ TELEVISION-RADIO
☐ ELECTRICITY-ELECTRONICS

NAME.....
ADDRESS.....
CITY.....STATE.....

NEW! IMPROVED!
SENCORE
TRC4
TRANSISTOR CHECKER

Another Sencore Time-Saver

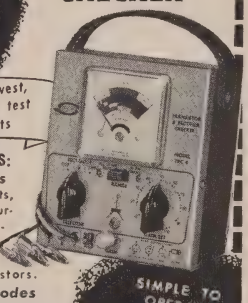

America's newest, most popular test instruments

NOW CHECKS:

★ ***Transistors*** for opens, shorts, leakage and current gain. Includes new gain test on power transistors.

★ ***Crystal Diodes*** checks forward to reverse current ratio on all diodes.

★ ***Selenium Rectifiers*** checks forward and reverse currents.

Controls are accurately set for each transistor by referring to replaceable set-up chart on rear. Test leads or socket provides for fast hook-up.

SIMPLE TO OPERATE
ONLY $17.95 Dealer Net
Cannot become obsolete. Approved by leading manufacturers.

See your parts distributor.

SENCORE Mfg by **SERVICE INSTRUMENTS CORP.**
171 OFFICIAL RD., ADDISON, ILL.
Cut out this ad now for further information

did not point to a defective 6DQ6 because brightness and width were perfectly normal.—*John B. Ledbetter*

PHILCO 49-1002

Complaint was a wormy (grainy) picture. A clue to the trouble was found by moving a grounded metal plate around the chassis. The improvised

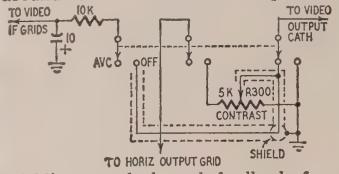

shielding wand showed feedback from the wire connecting the center arm of the contrast control (R300, 5,000 ohms) to the manual avc switch.

This video feedback was eliminated by running the lead in a shielded cable whose outer braid was grounded at both ends.—*A. R. Clawson*

MAGNAVOX CTA440AA

The set was suffering from critical vertical sync. To solve the problem, the sync pulse delivered to the PC integrator was increased by making the modification shown in the diagram.

The vertical takeoff was across the 220-ohm portion of the cathode resistance (R311). This was changed to 470 ohms. The horizontal feed from the cathode of the phase splitter must be

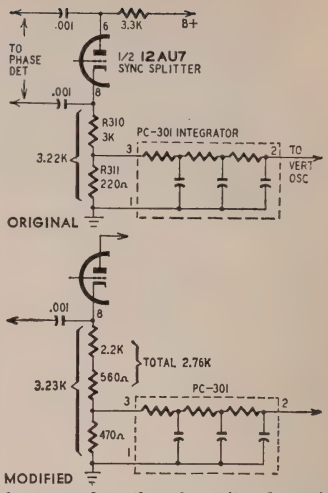

about equal to that from its plate circuit. To make the cathode resistance nearly the same, R310 (3,000 ohms) was replaced with two resistors, 2,200 and 560 ohms. Total cathode resistance of the 12AU7 is now 3,230 ohms in place of the original 3,220 ohms. Locking and interlace are better.—*Eugene Rollins.* END

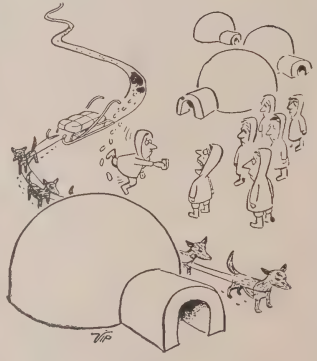

"SERUM? Heck, we thought it was our order of JENSEN NEEDLES arriving."

TRANSISTOR RADIO REPAIRS NOW EASY!

with this NEW Howard W. Sams BOOK

"SERVICING TRANSISTOR RADIOS"

COMPLETE ANALYSIS OF 70 POPULAR TRANSISTOR RADIO MODELS

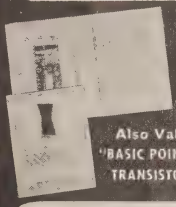

Includes new General Motors (Delco) Transistorized Auto-Portable Radio

Also Valuable Section—"BASIC POINTERS ON SERVICING TRANSISTORIZED RADIOS"...

COVERS LATEST MAKES AND MODELS

This book helps you earn big profits on Transistor Radio repairs—gives you complete, time-saving information—helps you become an expert on transistorized radios! Complete data on 70 latest models is based on actual lab analysis of each set. You get the famous Sams Standard Notation schematics—accurate, big, legible; full photo views of each chassis, with all components identified; complete alignment instructions; complete parts lists with full replacement data—everything you need to be successful in fast-growing transistorized radio servicing. Here's a "must" book for your bench. Order it now!

152 pages; 8¼ x 11" PRICE ONLY..... $2.95

SEE THIS BOOK AT YOUR SAMS DISTRIBUTOR OR MAIL COUPON

FREE TRIAL COUPON

Howard W. Sams & Co., Inc., Dept. 2-FF8
2201 E. 46th St., Indianapolis 5, Ind.

Send me Sams "Servicing Transistor Radios" for 10 days FREE examination. In 10 days I will pay for the book, plus few cents delivery cost, or return postpaid.

We pay delivery costs if you remit with this coupon; same return privilege.

Name_____

Address_____

City_____ Zone____ State____

(Outside U.S.A. priced slightly higher)

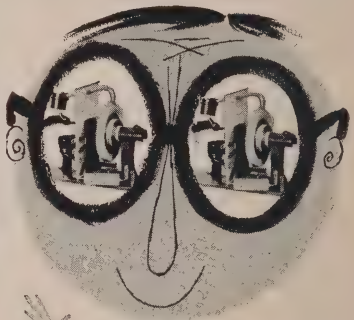

Seeing Double?

SURE . . . THEY LOOK ALIKE BECAUSE THEY ARE EXACTLY ALIKE

Each Merit product of the same type is exactly the same as another—both in construction and appearance.

COMPARE IT WITH MERIT

Take a Merit product off the shelf. Compare it with any other similar product on the market. You'll find Merit *is* superior!

COMPARE IT WITH MERIT

MERIT COIL & TRANSFORMER CORP.

MERIT PLAZA, HOLLYWOOD, FLORIDA

Business and People

J. R. Whiteside, executive vice president of Simpson Electric Co., Chicago, was named president.

George S. Bond, joined Howard W. Sams & Co., Indianapolis, Ind., as assistant to the chairman of the board, Howard W. Sams. Bond comes from P. R. Mallory where he was advertising and sales promotion manager.

Helen Staniland Quam of Quam Nichols Co., was elected president of the Association of Electronic Parts & Equipment Manufacturers Inc., the

first woman to head a major electronics industry trade group. **Gail S. Carter** (left) Merit Coil & Transformer Corp., was elected first vice president, and **Robert E. Svoboda,** Amphenol Electronics Corp., was elected second vice president. **Kenneth Hathaway,** Ward Leonard, was re-elected treasurer, and **Kenneth C. Prince,** executive secretary.

Victor Mucher, president of Clarostat Manufacturing Co., Dover, N. H., was honored on his 49th birthday by the Dover Rotary Club of which he is president. Friends, relatives and business associates surprised him in a takeoff of the TV program "This Is Your Life."

Photo shows Vic Mucher, seated, with his wife (right) and two sisters. Standing (left to right) are his two brothers, William and George; Austin C. Lescarboura, head of the agency which has handled Clarostat advertising for over 32 years, and Charles Golenpaul, vice president of Aerovox, an old friend.

INFRARED SNIPERSCOPE TELESCOPE & PARTS

See in the dark—without being observed. War surplus Sniperscope M-2. Contains the famous IP25A Image Tube. Govt cost about $1200. Used for industrial plant security; research lab experiments; infrared photography; spectroscopy, etc. Instrument complete, ready to use. Includes Power Pack, infrared light source. Will operate from 6 V auto battery. Battery or transformer available.

Stock No. 85,053-EK.....Shipping weight approx. 12 lbs..... **$150.00** f.o.b. Barrington, N. J.

Send check or M.O.—money-back guarantee!

Save still more money! Build your own Sniperscope! We will furnish instructions—parts, including: Power Packs, 1P25A image tubes, light units, filters, etc. For details—request FREE Catalog "EK."

SPECIAL! SPECIAL!
INFRARED 1P25A IMAGE TUBE

Stock No. 70,127-EK.....**$9.95 pstpd.**

Send check or money order, money-back guarantee

COLOR TV TUBESCOPE

Saves time, effort in alignment of color dot pattern.

Stock No. 50,139-EK.....22 power.....**$24.50 pstpd.**

Send check or money order, money-back guarantee

GET FREE CATALOG "EK"

America's No. 1 source of supply for experimenters, hobbyists. World's largest variety of Optical Items. Bargains galore. . . . War Surplus—Imported—Domestic! Microscopes, Telescopes, Satellitescopes, Color TV Tubescopes, Infrared sniperscopes and Parts, Prisms, Lenses, Reticles, Mirrors and dozens of other hard-to-get Optical Items.

WRITE FOR FREE CATALOG EK

EDMUND SCIENTIFIC CO.
BARRINGTON, NEW JERSEY

the ALL NEW SENCORE Align-O-Pak TV BIAS SUPPLY

Another Sencore Time-Saver

For **BLACK and WHITE and COLOR**

Just Dial any DC Voltage from 0 to 18 volts positive or negative—For AGC trouble shooting and alignment—Do away with messy bias batteries.

Completely isolated. Recommended by TV manufacturers. Wire wound control for calibration accuracy. For AGC trouble shooting, connect to AGC buss and vary voltage from 0 to 18 volts negative. If picture stabilizes at any voltage, AGC is defective. Complete with test leads.

MODEL BE3
$78.95
Dealer Net
Leather Carrying Case...$2.95

Mfg by
SERVICE INSTRUMENTS CORP.
171 OFFICIAL RD. ADDISON, ILL.

POPULAR SENCORE PRODUCTS
- Transistor Tester
- Leakage Checker
- Filament Tester
- Handy "36"
- Vibra-Dapter

SELF-SERVICE TUBE TESTER
$25 to $50

Used-reconditioned complete with signs and floor model cabinets. Get into a profitable business with a minimum investment. Write, Ed Moerke, P. O. Box No. 264, Zion, Ill.

LEARN WHILE YOU SLEEP

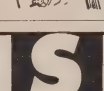

100 page fact-filled illustrated instruction book tells all. How to do it... what it costs ...results obtained...plus hundreds of time-saving hints. Price $2.00. Satisfaction guaranteed. Sleep-Learning Research Ass'n. Box 24-H, Olympia, Washington.

TELEVISION

AT HEALDS YOU LEARN BY DOING IN MODERN ELECTRONICS LABORATORIES

HEALD
ENGINEERING COLLEGE
Established 1863
Van Ness at Post, RE
San Francisco, Calif.

Never before in American history has the need been so great for Trained Engineers and Technicians. No other type of training can compare with actual shop practice you get at Healds under expert instructors.

Bachelor of Science Degree, 27 Months

- ☐ Radio-TV Technician including Color TV (12 Months)
- ☐ Electronics Technician (12 Months)
- ☐ Industrial Electronics Technician (12 Months)
- ☐ Electronics Engineering (B.S. Degree)
- ☐ Electrical Engineering (B.S. Degree)
- ☐ Mechanical Engineering (B.S. Degree)
- ☐ Civil Engineering (B.S. Degree)
- ☐ Architecture (B.S. Degree)

Heald College ranks FIRST West of the Mississippi in "Who's Who in America"

Approved for Veterans
DAY AND EVENING CLASSES
Write for Catalog and Registration Application.
New Term Starting Soon.

Your Name .....
Address .....
City .....
State .....

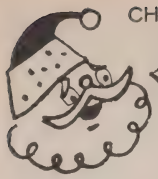

CHRISTMAS IN JUNE!

SEMI-ANNUAL
DOUBLE BONUS OFFER!

BONUS #1
Your Choice of any
POLY-PAK®
Listed Below

BONUS #2
Our Choice
$5 WORTH
Assorted
RADIO PARTS

BOTH FREE WITH $10 ORDER!

UNTIL JUNE 30
Our Usual $1 POLY-PAKS®
88¢ EACH

- ☐ 100 CERAMIC CONDENSERS. 2 lbs.
- ☐ 30 DISC CONDENSERS
- ☐ 40 PRECISION RESISTORS. 1 lb.
- ☐ 10 TIMING MECHANISMS. 2 lbs.
- ☐ WIRE STRIPPER-CUTTER.
- ☐ 7 SCREWDRIVERS w/RACK.
- ☐ 60 HI-Q RESISTORS. 1 lb.
- ☐ PIC TUBE BRIGHTENER, parallel.
- ☐ 20 FERRITE TUNED COILS. 2 lbs.
- ☐ 5 BALLPOINT PENS. ½ lb.
- ☐ 50-FT. "ZIP" CORD. 2 lbs.
- ☐ 5 25' ROLLS "MICRO" WIRE.
- ☐ 250-FT. HOOKUP WIRE. 3 lbs.
- ☐ 115/1/60 FAN MOTOR.
- ☐ SIGMA 10,000 ohm RELAY.
- ☐ MEN'S CIGARETTE LIGHTER.
- ☐ 40 MOLDED CONDENSERS.
- ☐ 150 RESISTORS. 2 lbs.
- ☐ 2 TRANSISTOR XFMRS.
- ☐ 20 PRINTED CIRCUITS.
- ☐ 4 G-E 1N69 DIODES.
- ☐ 6 AC-DC Cord sets
- ☐ 5 DIAL-LITE ASSEMBLIES.
- ☐ VEEDER-ROOT COUNTER. 0-9999.
- ☐ 40 TUBE SOCKETS. 2 lbs.
- ☐ MIDGET CRYSTAL MIKE.
- ☐ 4 POWER FILTER CHOKES. 2 lbs.
- ☐ "MICRO" MOTOR, 1½ VDC.
- ☐ 20 RAYTHEON KNOBS. 1 lb.
- ☐ 6 TRANSISTOR SOCKETS. w/plate
- ☐ 1000 PCS. HARDWARE. 2 lbs.
- ☐ 6 SILICON DIODES.
- ☐ 8 GERMANIUM DIODES.
- ☐ 10 POWER SWITCHES, asstd. 115 VAC
- ☐ 40 PRINTED CIRCUIT PARTS.
- ☐ 60 COILS & CHOKES. 2 lbs.
- ☐ 2 SUB-MINI SOLENOIDS. 2 oz.
- ☐ 20 VOLUME CONTROLS. 2 lbs.
- ☐ 15 ROTARY SWITCHES. 3 lbs.
- ☐ 50 PLUGS, RECEPTACLES. 2 lbs.
- ☐ 6 FERRI-LOOPSTICK CORES. 1½ lbs.
- ☐ SUN BATTERY, hundreds uses.
- ☐ 40 POWER RESISTORS. 2 lbs.
- ☐ 60 TUBULAR CONENSERS. 2 lbs.
- ☐ 60 TERMINAL STRIPS, BOARDS.
- ☐ 1 MINI-METER, 1¾ rd. 0-6 Amp. AC
- ☐ 40 HI-Q CONDENSERS.
- ☐ 8-PC. NUTDRIVER SET. 1 lb.
- ☐ TV MIRROR. 1 lb.
- ☐ 50 ASSORTED KNOBS. 2 lbs.
- ☐ 10 "POLY" BOXES.
- ☐ 100 RADIO PARTS. 3 lbs.
- ☐ 75-PC. RESISTOR SPECIAL. 1 lb.
- ☐ 2 PNP TRANSISTORS.
- ☐ 65 mfd. CONDENSER SPCL. 2 lbs.
- ☐ 70 MICA CONDENSERS. 1 lb.
- ☐ 15-PC. TWIST DRILL SET.
- ☐ 40 SUB-MINI RESISTORS.
- ☐ 10 ELECTROLYTICS. 3 lbs.

AUTO SPEAKER KIT
☐ Rear deck 5 x 7" PM spkr. Switch, grille, hardware. **$3.98**
☐ 6 x 9" SPEAKER KIT . . . only **$4.44**

12" COAX HI-FI SPKR.
☐ 40 to 15,000 cycles range, 12" woofer, built-in extended range tweeter & crossover. 8-8 ohm. V.C. Hvy Alnico magnet. Wt. 5 lbs. Reg. $19.95 **$8.88**

3-SPEED PICKUP
☐ With turnover cartridge, 2 sapphire needles. High output hi-fi type. Reg. $8 **$2.99**

WORLD'S SMALLEST RADIO
☐ KIT. 2½ x 1¾ x ¾" w/permeability tuner, diode, all parts, directions. Reg. $3.50 **$1.19**

3-TUBE AC-DC AMPLIFIER
☐ Fully wired, ready for use. Reg. $5. Separate volume and tone controls. Lowest price ever! **$2.99**

TUBES, $1.91 EXTRA

"MICRO" METER SALE!
50-70% OFF!
In orig. boxes
EACH ONLY 1⅝" SQUARE

- ☐ 0-15 VDC $4.44
- ☐ 0-30 VDC 4.44
- ☐ 0-200 VDC 4.44
- ☐ 0-500 VDC 4.44
- ☐ 0-15 VAC 4.44
- ☐ 0-150 VAC 4.44
- ☐ 0-1 ma 4.44
- ☐ 0-100 ma 4.44
- ☐ 0-200 ma 4.44
- ☐ 0-500 ma 4.44
- ☐ 0-50 microamps 6.88
- ☐ 0-100 microamps .. 6.50
- ☐ 0-200 microamps .. 5.99
- ☐ 0-500 microamps .. 4.99

POCKET MULTI-TESTER
☐ 3½ x 2 x 1½" bakelite case. 100 ohms/volt. Readings: 0/15/150/1000 AC & DC V; 0/150 ma; 0/100,000 ohms. W/test leads & battery. $12 value **$6.99**

HOW TO ORDER Check items wanted. Return entire ad w/check or M.O. including sufficient postage; excess returned. C.O.D. orders, 25% down; rated, net 30 days. Print name, address, amount money enclosed, in margin. (Canada postage, 45c 1st lb., 28c ea. addl. lb.) EXPORT ORDERS INVITED.

LEKTRON 131 Everett Ave. CHELSEA 50, MASS.

Joseph R. Owen was appointed manager of advertising and sales promotion for the General Electric Specialty Electronic Components Dept., Auburn, N. Y. He will be responsible for promotion activities on the department's high-fidelity audio components and specialized electronic materials and devices. He had been in charge of sales promotion in the G-E Television Receiver Dept.

Bob Mueller (left) and **Leon Ungar** (right), partners in Ungar-Mueller Sales Co., Southern California repre-

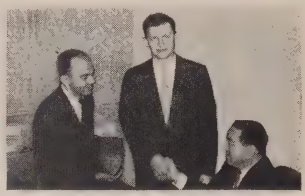

sentatives for General Cement Manufacturing Co., Rockford, Ill., were presented with the Salesman of the Year Award by W. H. Dean (center), Western Sales Manager for General Cement, for outstanding achievement in total volume and largest percentage increase in distributor sales in the Western division.

Business

Raytheon Manufacturing Co. Receiving Tube and Semiconductor Operations, Newton, Mass., was honored with the NATESA Friends of Service Management Award. In the photo, Frank Moch, executive director of NATESA, is shown

presenting the award to Norman B. Krim, vice president and general manager of Raytheon's receiving tube and semiconductor operations, while (left to right) F. B. Simmons, E. I. Montague, F. E. Anderson and J. A. Hickey, Raytheon executives look on.

Cornell-Dubilier, South Plainfield, N. J., is promoting the sale of its Mylar tubular capacitors by merchandising them in a clear plastic dispenser which holds 80 of the most popular units.

In the April issue this column reported that Lewis J. Shioleno had been named vice president and general manager of Erie Resistor Corp., Erie, Pa. Actually Mr. Shioleno was promoted to general manager of the Electronics Division. **Byron B. Minnium** is vice president and general manager of Erie Resistor Corp.

WILL YOUR REPLACEMENT "Fuse" "Resistor" BURN OUT AGAIN?

Another Sencore Time-Saver

Not if you use—
The NEW SENCORE "FUSE-SAFE" CIRCUIT TESTER

Save costly call backs by testing the circuit *before replacing* fuse, fuse resistor or circuit breaker.

Individual scale for each value fuse resistor — no interpretation, just read in red or green area

★ Measures line current and up to 1100 watts of power at 115 volts using line cord and socket.

★ Two convenient current ranges — 0 to 2 amps and 0 to 10 amps. Test leads clip in place of fuse or fuse resistor.

★ 5 ohm, 10 watt resistor prevents TV circuit damage and simulates operating conditions.

$8.95 DEALER NET
MODEL FS-3
AC-DC or both as needed for Fuse Resistor Circuits

As Recommended by Leading Manufacturers

SENCORE
Mfg by **SERVICE INSTRUMENTS CORP.**
171 OFFICIAL RD., ADDISON, ILL.

Cut out this ad now for further information

STEREO LAYS AN EGG

Stereo can be wonderful **but** it just doesn't come naturally by the use of two of everything in sound. Unfortunately, this is what too many are realizing after substantial investments in this glamour child of high fidelity.

Stereo actually requires still higher fidelity than single channel systems due to the highly critical timing sequences which must be maintained until the separate signals reach each of the listeners' ears. Probably the most difficult problem in this regard is in the speaker system which now must reproduce and radiate these signals in the exact sequence required.

If this requirement is not met, and we have a virtual dissection of the input signals combined with random phasing and haphazard blending topped off by highly directive radiation, "stereo will most surely lay an egg," regardless of the cost involved.

We have a pair of the patented Karlson Enclosures and a couple of good wide range speakers, all these complicated requirements are automatically realized and you can have the very best in stereo at the most modest prices.

These enclosures are designed for 8, 12, 15 inch speakers and are available in kit, unfinished, and finished form at prices you can afford ranging from $18.60 to $174.00. Special models are also available for obtaining more optimum phasing with large multiple speaker systems.

Write to Karlson Associates, Inc., Dept. RE8X, 433 **Hempstead Ave., West Hempstead, L. I., N. Y.** for free catalog.

Rek-O-Kut Co., Corona, N. Y., is offering a trip for two to the Brussels World's Fair and to Paris as the grand prize in a new dealer–consumer contest. In the photo, Cliff Shearer, marketing director of Rek-O-Kut, is being greeted

by Al Gross of Sabena Belgium Airlines and by Avery Yudin, Rek-O-Kut sales manager, on returning from Brussels where he arranged the trip.

Clark Gibb (right), president of The Paul Bunyan Chapter is welcomed back to The Representatives by Jules Bress-

ler, national president. The application of the Minnesota group was approved by the board of governors.

General Cement Manufacturing Co. purchased Microphone Division of Elgin National Watch Co. and will move the operation to Rockford, Ill., where it will function as American Microphone Manufacturing Co., a division of GC-

Textron Inc. The present sales organization remains intact. Photo shows Stanley B. Valiulis (seated right), president of General Cement, signing the contract as Elgin and General Cement executives look on. END

CORRECTIONS

In our *New Records* on page 129 of our February, 1958 issue, the line "Vox L-3 (16⅔ rpm)" was misplaced; it should have appeared between "Borodin: Polovetsian Dances" and "Round the World, Round the Clock" and not at the top of the listing.

In the April issue (page 42) we announced a number of articles planned as features in the May Special Transistor Issue. Unfortunately, last-minute publishing difficulties and technical bugs prevented publication of all the articles. We deeply regret this and assure you these interesting articles on transistors will appear in early issues.

Eliminate Battery Troubles with the all new

BATTERY INSURANCE COMPUTER

The revolutionary new electronic discovery—the BATTERY INSURANCE COMPUTER—attaches to the generator of your present car, controls your regulator and generator to give a quick charge or trickle charge to your present automotive battery automatically. Your present battery should serve you indefinitely with the aid of this all new concept of maintaining an adequate charge—

Computer controlled model $7.50
Specify make and year of car—12 or 6 volt system

MacFARLANE INDUSTRIES
P.O. Box 33 Redondo Beach, Calif.

COLOR from your positive transparencies **PRINTS 25¢** 2½ x 3½

Direct from laboratory to you—by mail
Custom quality – money back guarantee

COLOR FILM PROCESSING	COLOR PRINTS & DUPES
Anscochrome, Ektachrome, or Super Anscochrome—	3½ x 5 ..... $ .45
	8 x 10 ..... 2.00
35mm 20 exp.,2¼,mtd $1.25	35mm duplicates .25
Kodachrome-20 exp . 1.50	Sorry we do not ship COD

Write today for free mailer and complete price list!

Colorfax Authorized Ansco Color Laboratory laboratories • inc

1160-F Bonifant Street • Silver Spring, Maryland

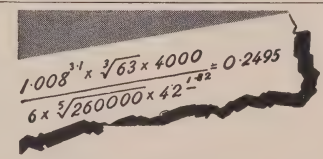

A 66-inch Slide-rule for your pocket

Slide Rule Open

The GENIAC® Calculator carries 66-inch spiral scales yet measures only ten inches fully extended and six inches when closed. Four to five figure accuracy can be relied on. It is indispensable to the scientist, research worker and student. Administrative staff and business men will find it of tremendous value for a host of estimating and checking calculations.

The GENIAC® Slide Rule solves multiplication, division, percentage calculation and gives 5 place logarithms.

You may use it for 30 days and if you are not satisfied repack and mail it back.

What our users say:

"It does all you claim—four or five figure accuracy without eyestrain or magnifiers. Half an hour's study is ample for its use." A.E.B. . . .

"I use the GENIAC Calculator for all my slide rule work and need the extra digit which normal slide rules cannot give. I had to get one of my customers a GENIAC Slide Rule last month, after using mine in his office." E. & G.H. Textile Manufacturers.

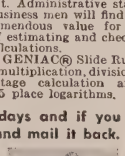

Slide Rule Closed

Send for yours now—Only $19.95 postpaid.

Oliver Garfield Co., Inc., RE-68
108 East 16th Street, New York 3, N.Y.

COMPLETE TRAINING

FOR BETTER RADIO-TV SERVICE JOBS

Radio-TV RECEIVER CIRCUITRY and OPERATION
Radio-TV TROUBLESHOOTING and REPAIR
ONLY $13 for the complete 2-volume course
3 MONTHS TO PAY

Let these two world-famous Ghirardi training books teach you to handle all types of AM, FM and TV service jobs by approved **professional methods—and watch your efficiency and earnings soar!**

Completely modern, profusely illustrated and written so you can easily understand every word, these books pave the way to fast, accurate service on any type of home radio-TV-electronic equipment ever made. Each book contains the latest data on the latest methods and equipment —NOT a rehash of old, out-of-date material. Each is co-authored by A. A. Ghirardi whose famous RADIO PHYSICS COURSE and MODERN RADIO SERVICE were, for 20 years, more widely used for military, school and home study training than any other books of their type!

THE NEW Ghirardi

RADIO-TV SERVICE LIBRARY

Almost 1500 pages and over 800 clear illustrations show step-by-step how to handle every phase of modern trouble-shooting and servicing.

1—Radio and Television Receiver
TROUBLESHOOTING & REPAIR

A complete guide to profitable professional methods. For the novice, it is a comprehensive training course. For the experienced serviceman, it is a quick way to "brush up" on specific jobs, to develop improved techniques or to find fast answers to puzzling service problems. Includes invaluable "step-by-step" service charts. 820 pages, 417 illus., price $7.50 separately. See combination offer!

2—Radio and Television Receiver
CIRCUITRY AND OPERATION

This 669-page volume is the ideal guide for servicemen who realize it pays to know what really makes modern radio-TV receivers "tick" and why. Gives a complete understanding of basic circuits and circuit variations; how to recognize them at a glance; how to eliminate guesswork and useless testing in servicing them. 417 illus. Price separately $6.75.

New low price . . . You Save $1.25!

If broken into lesson form and sent to you as a "course," you'd regard these two great books as a bargain at $50 or more! Together, they form a complete modern servicing library to help you work faster, more efficiently and more profitably.

Under this offer you buy them both for only $13.00. You save $1.25 on the price of the two books—and have the privilege of paying in easy installments while you use them.

10-DAY FREE TRIAL

Dept. RE-68, RINEHART & CO., Inc.
232 Madison Ave., New York 16, N.Y.

Send book(s) below for 10-day FREE EXAMINATION. In 10 days, I will either remit price indicated (plus postage) or return books postpaid and owe you nothing.

☐ Radio & TV Receiver **TROUBLESHOOTING & REPAIR**, (Price $7.50 separately)

☐ Radio & TV Receiver **CIRCUITRY & OPERATION** (Price $6.75 separately)

☐ **Check here for MONEY-SAVING COMBINATION OFFER . . . Save $1.25.**

Send both of above big books at special price of only $13.00 for the two (Regular price $14.25) . . . you save $1.25. Payable at rate of $4 (plus postage) after 10 days if you decide to keep books and $3 a month thereafter until $13 has been paid.

Name.....

Address.....

City, Zone, State.....

Outside U.S.A.—$8 for TROUBLESHOOTING & REPAIR; $7.25 for CIRCUITRY & OPERATION; $14 for both. Cash with order only, but same 10 day return privilege.

"TAB" Tubes Tested, Inspected, Boxed

New and used Gov't & Mfrs.
6 Mos. Guarantee! Surplus! No Rejects
Receiving types orders $10 or more, ppd., 48 states

0A2	.80	6BJ6	.72	12AT6	.59	117Z3	.69
0B2	.72	6BK7	.99	12AT7	.89	117Z6	1.10
0C3	.84	6BL7	1.95	12AU6	.63	434A	2.00
0D3	.80	6BN6	1.08	12AU7	.69	2C51	2.65
0Z4	.50	6BQ6	1.19	12AV7	.79	2D21	.68
1A7	1.00	6BZ7	1.25	12BA6	.65	3D23	5.00
1B3	.78	6C4	.49	12BA7	.99	717A	5/$1
1R5	.78	6C5	.69	12BD6	.59	4-125	29.00
1S4	.78	6CB6	.80	12BE6	.59	4-250	35.00
1T4	.78	6CD6	1.49	12BF6	.59	4E27	7.00
1U4	.68	6H6	.59	12BH7	.99	4PR60	29.50
1U5	.89	6J5	.59	12BY7	1.00	4X150	19.00
1X2A	.68	6J6	.59	12BZ7	.99	4X250	35.00
3Q4	.68	6K6	.59	12CU6	1.45	4X500	38.00
3Q5	.86	6K7	.79	12SA7	.69	5BP1	3.98
3S4	.68	6L6	1.19	12SQ7	.89	5BP4	1.98
3V4	.99	6S4	.59	12SH7	.89	35Z4	4.00
5R4	1.25	6S8	.99	12SJ7	.75	100T	7.00
5U4	.59	6SA7	.69	12SK7	.75	250T	20.00
5V4	.89	6SB7	1.19	12SQ7	.69	388A	1.00
5Y3	.59	6SC7	.89	19BG6	2.15	418A	14.00
6AB4	.59	6SG7	.79	19T8	1.19	450T	43.00
6AC7	.79	6SA7	.69	25BQ6	1.39	807	1.10
6AG7	.89	6SJ7	.69	25L6	.72	808	1.00
6AH6	.99	6SK7	.72	25Y4	.77	809	3.00
6AK5	.69	6SL7	.89	25Z5	.72	810	10.00
6AL5	.59	6SN7	2/$1	25Z6	.75	811	3.00
6AQ5	.66	6SQ7	.74	EL34	3.49	813	3.00
6AS7	3.00	6SR7	.79	EL37	2.49	813	9.00
6AT6	.49	6T8	.98	35L6	.59	814	2.45
6AU4	1.29	6U8	.98	35W4	.52	815	2.50
6AU5	1.19	6V6	1.39	35Y4	.69	829B	8.00
6AU6	.79	6W4	.79	35Z5	.89	832A	7.00
6AX4	.79	6W6	.89	50A5	.89	866A	1.60
6BA6	.59	6X4	.39	50B5	.69	6146	4.00
6BA7	1.00	6X5	.49	50C5	.69	5879	1.20
6BD6	.69	6Y6	.89	50L6	.69	5881	2.70
6BE6	.59	7N7	.89	KT66	3.29	6550	3.90
6BG6	1.50	12AL5	.59	75	.89	5842	11.00
6BH6	.79	12AQ5	.75	80	.59	5654	1.00

Write for Complete Tube List! Discounts to Qty. Buyers
TUBES WANTED! WE BUY! SELL & TRADE!

FINEST HI-FI RECORDING TAPE

1200 Ft.—7" Reel **$1.45** *Lots of 3*
Money Back Gtd.

Highest quality controlled plastic base tape made by new "Erin" process. Precision coated & Slit. Gtd. Constant output. Splice Free. Freq. 7½ IPS 40-15KC Oxide Wnd. In.
New 1st Quality "Mylar" 2400 Ft.—7" Reel Ferro "Erin" Gloss Process Recording tape....$4.49, 3 for $12

NEW VRII "GE" PHONO CARTRIDGES

Postpaid 48 States!
4G061/LP or 4G063/78 DIAMOND.....$16
4G050/LP&78 TRI-PLAY SAPPHIRE.....$8.59
4G052/LP&78 TRI-PLAY DIAMOND & SAP.....$18
4G053/LP&78 TRI-PLAY DIAMONDS.....$26

DIAMOND PHONO-NEEDLES! *Postpaid 48 States!*
REGISTERED ONE YR. GUARANTEED BY THE MFGR!
ALL MAKES LP&78—ONE DIAMOND $7; TWO DIAMONDS $14; DIAMOND & SAPPHIRE $8.
PLEASE SEND CARTRIDGE NAME & NUMBER

INFRARED RECEIVER ASSEMBLY USN/ US/AM-R1400, DIRECT VIEWING TELESCOPE UNIT, CHANGES INVISIBLE INFRA-RED ENERGY INTO A VISIBLE IMAGE ON AN INBLT SCREEN INCLUDES INFRARED FILTER & RADIOACTIVE CHARGING SYSTEM. NAVY COST $216 INCLUDES INST. CASE & DATA. SPECIAL $21.

Write for BONUS CATALOG

NEW GTD RADIO & T.V. RECTIFIERS

35MA 40¢ @, 6 for $2; 65MA 45¢ @, 5 for $2; 75MA 49¢ @, 5 for $2; 100MA 59¢ @, 6 for $3; 150MA 70¢ @, 8 for $5; 250MA 79¢ @, 6 for $4; 300MA 88¢ @, 5 for $4; 350MA $1.00 @, 8 for $7; 400MA $1.10 @, 5 for $5; 500MA $1.35 @, 4 for $5; 25MA/260V $1.10 @, 5 for 55; 100MA/260V $1.25 @, 9/$10; 100MA/156V 95c @; 300MA/156V $1.75, 3/$5. *Order $10, Postpaid 48 States!*
MFGRS. & DSTRBTRS. WRITE FOR QTY. PRICES
NEW SILICON 500MA/100°C/140 V/400 PIV Rectifier Hmt Sealed with clip $1.45, 8 for $11.00, 25 for $30.00.

NEW "TEKSEL" SELENIUM BRIDGE RECTIFIERS. ONE YEAR GTD!

FULL WAVE BRIDGE • *WRITE for CATALOG*

CURR. CONT.	18VAC 14VDC	36VAC 28VDC	72VAC 56VDC	144VAC 118VDC
1AMP	$ 1.30	$ 2.00	$ 4.00	$ 9.45
2AMP	2.15	3.00	5.25	12.00
3AMP	2.90	4.00	8.60	16.75
6AMP	4.15	8.00	18.75	36.15
10AMP	6.10	12.15	26.30	48.90
15AMP	9.90	19.00	40.00	66.60
24AMP	15.00	29.45	57.50	108.45

HAMS NEW TRANSISTORIZED "TABPAK"

D.C. Power Supply!!! Kit or Assembled. Filtered. Small in size! Quiet! Light Wgt.! Input 6 to 14VDC. (Low Idle Current.) Output 450 & tap @ 250 VDC at up to 150 ma/65 watts.
"TABPAK" Assembled TR39CB.....$35
"TABPAK" Kit TR39CK.....$30

DC POWER for TRANSISTORS!

Transistors! Filtered Power Supply Kit used to power transistor circuits, amplifiers etc. Delivers 12VDC at 2AMPS filtered less than 0.5% ripple or 28VDC at 1A TPSK2 Kit $18. TPS2W assembled & wired $24. 115VAC Inpt Transformer & Full Wave Bridge Rectifier for 12VDC @ 2AMPS. or RECTRAN KIT RT1K.....$4.50
RT1W Assembled & Wired.....$8.50
RT2K Kit 12 or 18VDC at 6 AMPS.....$9.00
RT2W Assembled & Wired.....$14.75

KITS! "TAB" *THE BEST* KITS!

All Kits Contain Most Popular Values & Sizes

Kit 35 Precision Resistors	Kit 35 Power Resistors
Kit 18 Switches	Kit 75 Mica Cond's
Kit 3 Transistor Transf.	Kit 8 Crystal Diodes
Kit 150 Carbon Resistors	Kit 4x50 ft. Hookup Wire
Kit 33 Panel Lamps	Kit 100 Fuses
Kit 12 Electrolytic Cond's	Kit 100 Ceramic Cond
Kit 15 Volume Controls	Kit 18 Rotary Switches
Kit 36 Tube Sockets	Kit 6 Crystals & Holders
Kit 50 Tubular Cond's	Kit 65 Inductors & Coils
Kit 500 Lugs & Eyelets	Kit 5 Microswitches
Kit 10 Xmit Mica Cond's	Kit 10 Wheat Lamps
Kit 5 Lbs. Suprise Kit	Kit 40 Insulators
Kit 10 Xmit Mica Cond's	Kit 85 Insulated Resist.
Kit Encapsulation Fluid	Kit TV Knobs
Kit Volume Control Fluid	Kit GE Glypt & Varn.

BUY 10 KITS GET ONE FREE! EACH KIT **99c**

"TAB" TERMS: Money Back Guarantee! Our 14th year. $2 min order F.O.B. N.Y.C. Add shpg charges or for C.O.D.. 25% Dep. Prices shown subject to change.
111JG LIBERTY ST., N. Y. 6, N. Y.
PHONE: RECTOR 2-6245
Write for Bonus Catalog

technical Literature

Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears. UNLESS OTHERWISE STATED, ALL ITEMS ARE GRATIS. ALL LITERATURE OFFERS ARE VOID AFTER SIX MONTHS.

TELEVISION PICTURE TUBES, with complete physical and electrical specifications, are listed in this handy booklet. Monochrome, color and aluminized types are included.—**Raytheon Manufacturing** Receiving & Cathode-Ray Tube Operations, 55 Chapel St., Newton 58, Mass.

SILICON RECTIFIER HANDBOOK, *catalog No. 67,* deals exclusively with this manufacturer's line of silicon rectifiers. Theory of operation, manufacturing processes, characteristics and uses are shown.—**Sarkes Tarzian Inc.,** Rectifier Div., 415 N. College Ave. **$1. Free to** RADIO-ELECTRONICS readers.

ELECTRONIC COMPONENTS, *1958 catalog.* 16-page 2-color booklet describes this manufacturer's complete line of electronic test instruments and high-fidelity equipment in both kit and wired forms. Vtvm's, vom's, oscilloscopes, Geiger counter, preamplifier, amplifiers and speaker systems are included.—**Electronic Instrument Co. Inc., EICO,** 33-00 Northern Blvd., Long Island City, N.Y.

TEST INSTRUMENTS *bulletin AP12* describes and illustrates the TV analyst, tube checkers and test instruments for in-the-home service and shop use.—**B & K Manufacturing Co.,** 3726 N. Southport Ave., Chicago 13, Ill.

VARIABLE TRANSFORMER CATALOG, *bulletin P258G.* This 100-page book is filled with product information, engineering data, outline drawings, connections, ratings, and charts and illustrations of all standard 50/60-cycle Powerstats as well as some special-use types.—**Superior Electric Co.,** Dept. P258G, Bristol, Conn.

HIGH-FIDELITY COMPONENTS are offered in an illustrated 12-page catalog. Tuners, amplifiers, speakers and speaker systems are presented.—**Altec Lansing Corp.,** 1515 S. Manchester Ave., Anaheim, Calif.

REACTANCE SLIDE RULE solves problems such as resonant frequency, capacitative reactance, inductive reactance and coil Q, and dissipation factor. Useful for solving problems of filter design, oscillator tank circuits, trans-

What articles would you like to see published in RADIO-ELECTRONICS? Maybe you're the man to write them. Ask for an author's guide.

RADIO-ELECTRONICS

154 West 14th Street New York 11, N. Y.

SPECIAL INTRODUCTORY OFFER!

VACO Red Cap *"At Your Service"*

Screw Drivers

Here's your chance to get a beautiful 5-piece screw driver set at a true bargain price! All the most popular sizes (including No. 2 genuine Phillips) *plus* —a FREE tool hanger board complete with patented, adjustable hanger hooks for holding your most frequently used tools. Here's how:

FREE Tool Hanger Board and Patented Hanger Hooks
Just mail in the coupon enclosed in the RC 15 Boxed Set and VACO will send you this 12" x 24" perforated masonite panel and set of hanger hooks at no charge.

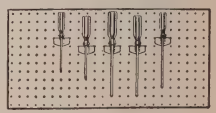

See Your Jobber, *Today!*

VACO PRODUCTS CO., 317 E. Ontario St., Chicago 11, Ill.
In Canada: Atlas Radio Corp., Toronto 19, Ontario

former and amplifier design.—**Shure Brothers Inc.**, 222 Hartrey Ave., Evanston, Ill. **75c.**

TERMINALS AND CONNECTORS for high-temperature applications are detailed in *catalog section HT*. Comprehensive specifications are presented for each type.—**AMP Inc.**, Harrisburg, Pa.

SILICON RECTIFIER HANDBOOK, tells how they are made, gives theory of operation, engineering design notes, and basic rectifier circuits in the first section of an illustrated 64-page *catalog 111*. In the second section numerous types of these units with specifications and circuits are described. —**Audio Devices Inc.**, Rectifier Div., 620 E. Dyer Rd., Santa Ana, Calif. **$1.**

RECORDING TAPE. An illustrated folder *"Which Tape Type are You?"*, offers general information on magnetic recording tape and helps you select the type tape that best suits your needs.—**Minnesota Mining & Manufacturing Co.**, 900 Bush St., St. Paul 6, Minn.

CRYSTAL FILTERS, *bulletin XT-455*, is a 2-color 4-page brochure outlining a line of stock and special miniaturized quartz crystal filters. Technical data, typical and representative curves of the filters are shown. Symmetrical bandpass, wide-band, narrow-band, and asymmetrical or single-sideband filters are described.—**Burnell & Co. Inc.**, 10 Pelham Parkway, Pelham Manor, N. Y.

HI-FI TRANSFORMERS made by Partridge are presented in a 4-page leaflet. 20- and 30-watt models are offered. Complete specifications are included.—**M. Swedgal**, 259 Broadway, New York 7, N. Y.

APPLICATION NOTES for using silicon junction rectifiers to protect sensitive current devices are presented in Vol. 1, No. 1 of *Semi-conductor Application Notes*. This issue illustrates how the nonlinear characteristics of silicon diodes, in both the forward and Zener operating regions, make them ideally suited to protecting ac and dc measuring instruments.—**Hoffman Electronics Corp.**, Semiconductor Div., 930 Pitner Ave., Evanston, Ill.

TRANSFORMERS AND COILS, *catalog 630*, lists the entire line of transformers, coils and components for radio TV, industry, amateur, transistor and military applications produced by this firm. Fully illustrated, 24 pages.—**Thordarson - Meissner Manufacturing Co.**, 7th and Belmont, Mt. Carmel, Ill.

VHF–UHF EQUIPMENT including instruments and accessories for signal and pulse generation, impedance measurement, detection, modulation, attenuation and transmission through shielded coaxial lines detailed in this illustrated booklet.—**General Radio Co.**, 275 Massachusetts Ave., Cambridge 39, Mass. END

RADIO-ELECTRONICS pays $3.00 for good cartoon ideas and $15 and up for finished work.

RADIO-ELECTRONICS

154 West 14th St., New York 11, N.Y.

DIGITAL COMPUTER KIT

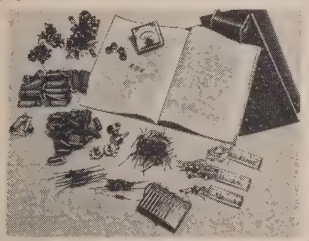

Build 100 transistor computer circuits and work with them! Basic units can be built within hours. Assemble them into computers and operate. The language of computers is explained and projects included. You will receive 22 transistors and 200 electrical parts. $59.50 plus postage. Twelve other kits available.

Partial list of courses:
- ☐ C1 Elementary relay brains $12.50
- ☐ C2 Elementary digital computers $24.50
- ☐ C3 Elementary analog computers $19.50
- ☐ C14 Computer Master 50 lessons and projects (digital voltmeter, digital ohmmeter)
- ☐ C15 Electronics, 40 lessons and 3 text books. $22.50 down and $10 for 5 months.
- ☐ Complete catalog.

EBE Inc., 1015 Atkin Ave.
Salt Lake City 6, Utah
- ☐ Send one transistor computer kit
- ☐ Enroll me in course.....
- ☐ Enclosed $.....

Name and address attached

SENCORE

Another Sencore Time-Saver

Handy "36" R-C Substitution Unit

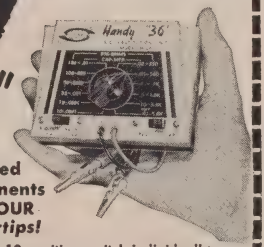

"36" Most Often Needed Components At YOUR *Fingertips!*

3 pole, 12 position switch individually selects one of the "36" components for direct substitution.

Contains:
- ★ 12—1 watt 10% resistors from 10 ohms to 5600 ohms
- ★ 12—½ watt 10% resistors from 10K ohms to 5.6 megohms
- ★ 10—600 volt capacitors from 100-mmfd. to .5mfd.
- ★ 1—10mfd., 450V Electrolytic
- ★ 1—40mfd., 450V Electrolytic
- ★ For Shop, Lab, or outside service

ONLY $12.75 DEALER NET

Completely isolated

AVAILABLE AT ALL PARTS DISTRIBUTORS!

SENCORE SERVICE

INSTRUMENTS CORP.

171 OFFICIAL RD., ADDISON, ILL.

POPULAR SENCORE PRODUCTS
- Transistor Tester
- Leakage Checker
- Filament Tester
- Voltage Regulator
- Bias Supply

Cut out this ad now for further information.

Examine FREE

Prentice-Hall ELECTRONICS & UHF LIBRARY

Edited by W. L. EVERITT

5 VOLUMES 1662 ILLUSTRATIONS

Pay Easy Installments If You Keep the Set

Turn to this new, up-to-date Library with complete confidence, for dependable facts on any phase of modern electronic theory and practice. These volumes, by outstanding authorities, give you thorough guidance—clearly written, logically arranged, profusely illustrated.

Electronic Fundamentals and Applications
By Prof. John D. Ryder,
Dean, College of Engineering, Michigan State University

Complete, logical, easy-to-follow treatment of (a) physical principles underlying electron tubes, (b) characteristics of vacuum tubes, (c) all basic tube circuits. Includes: Electron Ballistics, Cathode-Ray Tubes, Emission of Electrons, Space Charge in Vacuum Tubes, Diode Rectifiers, Triodes, Multi-Element Tubes, Small-Signal Amplifier Circuits, Audio-Frequency Amplifiers, Radio-Frequency Amplifiers, Oscillator Circuits, Modulation Systems, Wave-Shaping Circuits, Gaseous Conduction, Gas Diodes, Gas Control Tubes and Circuits, Photoelectric Cells, Solid-State Electronics.

Electromagnetic Waves and Radiating Systems
By Prof. Edward C. Jordan,
Head, Dept. Electrical Engineering, Univ. of Illinois

Covers entire field of electromagnetic engineering. Includes propagation as well as radiation and wire transmission. Full treatment of UHF transmission lines, wave guides, antennas, slot antennas, radiation and diffraction, ground-wave and sky-wave propagation.

Ultra High Frequency Engineering
By Thomas L. Martin
Head, Dept. of Electrical Engineering, Univ. of Arizona

Theory and technique of ALL the new fields of electronic engineering: Radar, Telemetering, Electronic computing, Facsimile, Television, Blind landing systems, Pulse-time modulation, Ionosphere measurements . . . and the others.

Networks, Lines and Fields
By Prof. John D. Ryder,
Dean, College of Engineering, Michigan State University

Network transformations and theorems, Resonance, Impedance transformation and coupled circuits, Filters, General transmission line, High-frequency line, Equations of the electromagnetic field, Radiation, Transmission and reflection of plane waves at boundaries, Guided waves between parallel planes, Wave guides.

Elements of Television Systems
By George E. Anner, University of Illinois

Complete basic theory, plus current practice, covering: Closed TV systems, Commercial Telecasting Systems, Color TV Systems. Gives clear exposition of all phases of picture transmission, including the new technique of dot interlace.

SEND NO MONEY—EXAMINE FREE

Just mail coupon below to get complete 5-Volume Set on 10 DAYS' FREE TRIAL. If not completely satisfactory, return in ten days and owe nothing. Or keep the set and pay only $7.50 down and $8 a month for five months until full price of $47.50 is paid. Decide for yourself—without risk or obligation—just mail coupon to examine Library ten days free.

Prentice-Hall, Inc., Dept. 5744-H1
Englewood Cliffs, N.J.

Send me the Prentice-Hall **ELECTRONICS & UHF LIBRARY** (5 Volumes) for ten days' free examination. If fully satisfied in ten days I will send you $7.50 plus few cents postage and then $8 a month for five months until full price of $47.50 is paid. Or I will return the Library in ten days and owe nothing.

Name.....

Address.....

City and State.....

NOW H. A. Hartley offers you a complete practical guide to audio design. . .

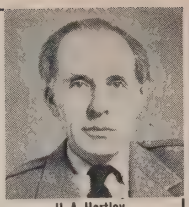

H. A. Hartley

Popular author of articles in RADIO-ELECTRONICS and RADIO & TV NEWS. Hailed on both sides of the Atlantic as a brilliant audio engineer.

H. A. Hartley's new book -- AUDIO DESIGN HANDBOOK saves you the time of wading through masses of technical data to ferret out the core of practical design information you're searching for. He steers you away from the shoals of tricky common mistakes and misconceptions. Hartley shows you how audio design can be done easily and simply! He tells you how to avoid blind alleys by first determining WHAT YOU WANT—and then building within the limits of your own goal. The book covers amplifiers, feedback, power supplies, speakers and enclosures, dividing networks, measurements and testing, plus a few salty personal observations on the wrong directions hi-fi has taken. Easily the most stimulating and helpful book on audio designing ever written!

You can get this deluxe, beautifully-bound $5 book—the latest addition to the G/L Audio Hi-Fi Book Club—for only $3.75! Read how you can join the club, get this book and save money.

HOW THE G/L AUDIO HI-FI BOOK CLUB CAN HELP YOU

- Shows you the way to more pleasure in hi-fi if it's your hobby—more profits if it's your profession.
- Offers you the benefits of the knowledge and experience of top writers like Crowhurst, Hartley, Dorf, Marshall and others.
- You can build a complete hi-fi library in easy stages—on the NO-RISK INSPECTION PLAN.
- You SAVE $1.25–25%–ON EACH BOOK YOU BUY!

HOW TO ENROLL

- Select the book you want on the coupon below.
- SEND NO MONEY NOW—we send you the book on a NO-RISK inspection plan.
- If you like the book you keep it and pay—not the $5.00 retail price—but the SPECIAL MEMBER'S RATE OF ONLY $3.75—and we pay postage.
- If you don't want the book, simply send it back—no fuss, no obligation, no high pressure—AND NO SALESMAN WILL CALL.
- You receive a new book on the same NO-RISK INSPECTION PLAN every four months.
- You need take a minimum of only four books during the whole membership period. No time limit—no long term contract. You may cancel anytime after that.

Each book handsomely bound with a deluxe gold-leaf stamped cloth cover.

OTHER BOOKS ALREADY PUBLISHED

Order Audio Design Handbook or any other book.

ELEMENTS OF TAPE RECORDER CIRCUITS
By Herman Burstein and Henry C. Pollak
Answers all the questions a hi-fi fan would ask about tape recorder circuits. Includes a chapter on design for modifying your own equipment.

UNDERSTANDING HI-FI CIRCUITS
By Norman H. Crowhurst
Mr. Hi-Fi himself tells you how to get hi-fi tailored to your own needs. Tells you which type of components to choose for the system you want and can afford.

BASIC AUDIO COURSE — By Donald Carl Hoefler. Complete coverage of theory and fundamentals from the physics of sound to advanced techniques, including amplifiers, feedback, power supplies, distortion, attenuators, speaker systems, and so much more it is impossible to list all here.

MAINTAINING HI-FI EQUIPMENT — By Joseph Marshall. Now for the first time—learn the techniques necessary to recognize and repair hi-fi troubles. Covers acoustic as well as electronic, electrical and mechanical faults. A must for the professional hi-fi man—or any audiophile who really cares about his hi-fi system.

Other books are in preparation

MAIL THIS COUPON TODAY

SEND NO MONEY

NO-RISK COUPON

GERNSBACK LIBRARY, Inc., Dept. 68C
154 West 14th St., New York 11, N.Y.

Enroll me in the G/L Audio Hi-Fi Book Club. Begin my membership with the book checked below.

- ☐ AUDIO DESIGN HANDBOOK
- ☐ UNDERSTANDING HI-FI CIRCUITS
- ☐ BASIC AUDIO COURSE
- ☐ MAINTAINING HI-FI EQUIPMENT
- ☐ ELEMENTS OF TAPE RECORDER CIRCUITS

Name_____

Street_____

City_____ Zone____ State_____

Books

ALL ABOUT ELECTRICITY, by Ira M. Freeman. Random House, Inc., 457 Madison Ave., New York 22, N.Y. 7 x 9¼ inches, 141 pages. $1.95.

This is one of an "all-about" series that includes birds, flowers, stars, etc. It is intended for "readers of 10 to 15" but perhaps not for youngsters who already happen to experiment with transistors, build portable radios or operate ham stations.

With helpful illustrations, the book is simple, effective and as clear as possible for such a topic. Principles of the telephone, battery, electromagnetism, power transmission and radio are skillfully treated in a way to attract the interest of future scientists. Color TV appears briefly, and transistors are also mentioned.

For the benefit of young minds, the author has dramatized the basic discoveries of Franklin, Galvani, Oersted, Bell, Marconi and others. These stories introduce the reader to the principles and applications that follow.—*IQ*

SYLVANIA SERVICE INFORMATION, Vol. 2. Sylvania Electric Products Inc., Radio & Television Div., Service Dept., Batavia, N.Y. 11 x 17 inches, 138 pages. $3.50.

A comprehensive manual of service information, schematic diagrams, production changes, test and alignment points and parts lists for Sylvania radio, TV and audio equipment produced between May, 1954, and December, 1957.—*RFS*

UNDERSTANDING ELECTRONICS, by John Lewellen. Thomas Y. Crowell Co., 432 4th Ave., New York, N. Y. 5½ x 8¼ inches. 213 pages. $2.75.

This most recent of a series of books intended to give the nontechnical beginner an insight into some of the involved mechanics of the modern world presents a fascinating picture of electronics. Starting off with "Can you imagine anything changing its direction 500,000 times a second?" the author takes the reader through a tour of basic electricity, magnetic fields, how electrons behave, how the parts of radio work and even describes transistors. For the layman who wants to know what makes things tick.—*LS*

MOST-OFTEN-NEEDED 1958 TELEVISION SERVICING INFORMATION. Compiled by M. N. Beitman. Supreme Publications, 1760 Balsam Rd., Highland Park, Ill. 8½ x 10½ inches, 192 pages. Price $3.

SCHOOL DIRECTORY

ENGINEERING DEGREES

E.E.
Option Electronics or Power

Earned through
HOME STUDY
Residence Classes Also Available

PACIFIC INTERNATIONAL UNIVERSITY
(Operating as a College of Engineering only at present)
5719-M, Santa Monica Blvd., Hollywood 38, Calif.

PACIFIC INTERNATIONAL UNIVERSITY

CODE SENDING RECEIVING SPEED

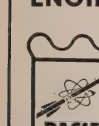

Be a "key" man. Learn how to send and receive messages in International Morse code. Communicate with operators around the globe. Learn at home quickly through famous Candler System. Used by best operators. Qualify for Amateur or Commercial License. Write for FREE BOOK.

CANDLER SYSTEM CO.
Dpt. 3-G, Box 9228, Denver 20, Colo. USA

GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic and advanced courses in theory and laboratory. Assoc. degree in electronics in 29 mos. B.S. in electronic engineering obtainable. ECPD accredited. G.I. approved. Graduates in all branches of electronics with major companies. Start September, February. Dorms, campus. High School graduate or equivalent. Catalog.

VALPARAISO TECHNICAL INSTITUTE
Dept. C Valparaiso, Indiana

ELECTRONICS

Prepare for unlimited opportunities in electronics!

ENGINEERING DEGREE IN 27 MONTHS

B.S. degree in 27 months, mathematics, electrical engineering, TV, advanced radio theory and design. Modern labs. Low tuition, earn board. Also Aero., Chemical, Civil, Electrical, Mech. Engineering. B.S. degree in 36 mo. in Math., Chem., Physics. Also prep courses. G.I. appr. 20 bldgs., dorms., gym. Enter June, Sept., Dec., March. Catalog. Keeping Pace With Progress.

INDIANA TECHNICAL COLLEGE
1568 E. Washington Blvd., Fort Wayne 2, Ind.

college grads get ahead faster!

. . . have higher incomes . . . advance more rapidly. Grasp your chance for a better life. Share rewards awaiting college men. Important firms visit campus regularly to employ Tri-State College graduates. Start any quarter. **Approved for Vets.**

Bachelor of Science Degree in 27 months

Complete Radio Engineering courses (TV, UHF, FM, Electronics). Also Mechanical, Civil, Electrical, Chemical, Aeronautical Engineering *in 36 months* a B.S. in Business Administration (General Business, Accounting, Motor Transport Management Majors). Superior students faster. More professional class hours. Small classes. Enrollment limited. Beautiful campus. Well-equipped labs. Prep courses. Enter June, Sept., Jan., Mar. Earnest, capable students (whose time and budget require accelerated courses and modest costs) are invited to *write Jean McCarthy, Director of Admissions for Catalog and "Your Career in Engineering and Commerce."*

TRI-STATE COLLEGE
2468 College Avenue, Angola, Indiana

ELECTRONICS

PREPARE FOR A GOOD JOB!
BROADCAST ENGINEER
RADIO SERVICING AUTOMATION
TELEVISION SERVICING
BLACK & WHITE—COLOR

APPROVED FOR VETERANS AND SURVIVORS OF VETERANS
BUILDING AIR CONDITIONED
SEND FOR FREE LITERATURE

BALTIMORE TECHNICAL INSTITUTE
1425 EUTAW PLACE, BALTIMORE 17, MD.

Be an ENGINEERING TECHNICIAN

FREE BOOK

EARN HIGH SALARY Big demand for trained men in *ELECTRONICS ... RADIO-TV!* A. S. Degree in just 24 months at resident school; or complete first year by home study. Also radio-TV servicing, broadcasting, airline training. Nation-wide placement service. G. I. approved. Low tuition. *Resident Home Study* Write NOW for FREE illustrated catalog.

CENTRAL TECHNICAL INSTITUTE *(Est. 1931)*
Dept. Y-68, 1644 Wyandotte Street, Kansas City 8, Missouri

ENGINEERING Home Study Courses

COURSES written by world authorities in all branches of engineering. Step-by-step instructions using methods proved successful by thousands of our graduates. One hour each day in your spare time will start you off to higher pay, security, prestige. Check the course you are interested in and we will send you a complete outline of the course with a booklet describing the Institute and our advanced methods of teaching. Send to: Canadian Institute of Science and Technology Ltd., 683 Century Bldg., 412, 5th St. N.W., Wash., D.C.

- Civil Eng.
- Surveying
- Architecture
- Forestry
- Mining
- Structural
- Mechanical Eng.
- Industrial Eng. & Management
- Refrigeration
- Heating
- Drafting
- Plastics
- Electrical Eng.
- Radio
- Electronics
- Television
- Aeronautical Eng.
- Aircraft Engineer
- Navigation
- General Education
- Chemical
- Mathematics
- Journalism
- Accounting

NAME.....

ADDRESS.....

CITY..... STATE.....

Course Interested In.....

Canadians: Send to Canadian Institute of Science & Technology Limited, 683 Garden Bldg., 263 Adelaide St. West, Toronto, Ont.

Your choice of school is highly important to your career in

INDUSTRIAL ELECTRONICS

RADIO-TELEVISION

ELECTRONICS COMMUNICATIONS

Become an
ELECTRICAL ENGINEER
or an
ENGINEERING TECHNICIAN
at
MSOE *in Milwaukee*

Choose from courses in:

ELECTRICAL ENGINEERING

Bachelor of Science degree in 36 months—
Communications of Electrical Power.

ENGINEERING TECHNOLOGY

Associate in Applied Science degree in 18 months—
Electronics Communications.
Electrical Power, or Computers.

MSOE — located in Milwaukee, one of America's largest industrial centers—is a national leader in electronics instruction—with complete facilities, including the latest laboratory equipment, visual aid theater, amateur radio transmitter—offers 93 subjects in electrical engineering, electronics, radio, television, electrical power, and electricity.

Advisory committee of leading industrialists. Courses approved for veterans. Over 50,000 former students. Excellent placement record. Previous educational, military, and practical experience is evaluated for advanced credit.

QUARTERS BEGIN SEPTEMBER, JANUARY, MARCH, JULY

Choose wisely — your future may depend on it. Mail coupon today!

MILWAUKEE SCHOOL OF ENGINEERING

Dept. RE-658, 1057 N. Milwaukee St.
Milwaukee, Wis.

Please send free illustrated career booklet
(please print)

I'm interested in.....

Name..... Age.....

Address.....

City..... State.....

☐ I am ☐ I am not eligible for veterans benefits

..... (discharge date)

STAN-BURN

CATHODE RAY TUBE SPECIALS

ONE YEAR GUARANTEE

G.E.	Type	STAN BURN	G.E.	Type	STAN BURN
$15.80	10BP4	$10.00	24.75	17LP4	$18.00
19.10	12LP4A	13.95	37.00	19AP4A	24.00
	12QP4	11.50	28.35	20CP4A	18.95
20.35	12UP4	15.00	33.60	20CP4B*	21.95
20.75	14CP4	13.75	36.00	21AP4	25.00
	15DP4	14.50	29.75	21EP4A	20.15
33.75	16AP4	18.50	34.85	21EP4B*	23.25
32.20	16DP4A	15.25	30.90	21FP4	21.15
33.75	16GP4	18.75	37.00	21MP4	26.25
23.50	16KP4	15.75	29.75	21YP4	22.00
28.40	16KP4A*	18.75	34.85	21YP4A*	25.00
31.50	16LP4A	16.25	28.30	21ZP1	21.00
31.50	16WP4	16.25	33.60	21ZP1B*	24.00
33.50	17BP4	15.75	100.00	24AP4	56.00
28.40	17BP4B*	18.75		(6 mos. guar.)	
30.75	17CP4	20.50	48.40	24CP4A*	38.00
33.90	17GP4	21.50	50.00	24DP4A*	39.00

*ALUMINIZED—INQUIRE FOR ANY TUBE TYPE NOT LISTED. STAN-BURN CRT TUBES ACA LICENSED. MFD. BY LINCOLN. All orders of 6 or more STAN-BURN CRT are subject to additional 10% discount. PRICES SUBJECT TO CHANGE WITHOUT NOTICE.

WHY PAY MORE? HI-FI COMPONENTS • KITS • RECORD PLAYERS • TAPE RECORDERS • TUNERS • AMPLIFIERS • SPEAKERS • ELECTRONIC PARTS & TUBES • Etc.

Top brand nationally adv. merchandise in this and other Radio & TV mags. is yours at low, low cost. Send us your list. Give Mfr's name and Model No. of item. Write for '58 catalogs to Dept. RE-6 today.

GENERAL ELECTRIC RECEIVING TUBES

Brand New—1 Year Guarantee—Boxed

0Z4	.83	6K6GT	1.13	12SA7	1.45
1B3GT	1.38	6SN7GT	1.25	12SK7	1.33
5U4GA	.95	6V6GT	1.03	12SQ7	1.18
6AQ5	1.25	6W4GT	1.15	35W4	.68
6AU6	1.00	12AU7	1.18	35Z5GT	.90
6BQ6GA	2.08	12BA6	.95	50C5	1.03
6BG6GA	3.10	12BE6	1.03	50L6GT	1.15

ADDITIONAL 10% DISCOUNT IN LOTS OF 10 ASSORTED!

WRITE FOR COMPLETE PRICE LIST

SAVE UP TO $100 A YEAR ON TV REPAIRS

Amazing new book "How To Keep Your Own TV Set" gives you everything you have to know to spot TV trouble. Shows how to fix it "presto." Everything in easy-to-understand language and step-by-step diagrams. Latest up-to-date information on tube changes, antennas, tube location charts, trouble shooting guide, etc., plus list of tube types and prices. Only $1.00 plus 10c for postage.

HI-FI DIAMOND NEEDLES—1 Yr. Guar.

Diamond needles reduce record wear and needle noise thus retaining full frequency response and tonal qualities of your records for a longer period of time.

SINGLE DIAMOND needle.....$7.95
DIAMOND SAPP dual needle.....8.95
Shipment PPD. (specify cartridge make)

RECORD CHANGERS

COLLARO TC-340 4 speed changer...$36.75
COLLARO RC-440 4 speed changer... 40.67
COLLARO TC-540 4 speed changer... 45.57
GARRARD RC-88 4 speed changer.... 53.41
GARRARD RC-98 4 speed changer.... 66.15

FREE wood mounting base, record wiping cloth and 45 RPM spindle with all orders for Collaro and Garrard changers, while this last.

VM 4 SPEED HI-FI CHANGER—Model 1210 with Ronette or Astatic flip-over cartridge.....$22.95

MONARCH Model UA8U 4 SPEED AUTO. INTERMIX CHANGER less cartridge...$19.95

WEBCOR 4 SPEED CHANGER with turn-over cartridge.....$23.95

RONETTE (phono fluid) cartridge flip-over type.....$2.98

SONOTONE cartridge, flip-over.....$2.98

45 RPM SPINDLE for V.M. or Monarch..$1.98

WOOD MOUNTING BASE for V.M. or Monarch.....$3.95

MOUNTING BOARD unfinished for V.M. or Monarch.....$1.50

NEW GENERAL ELECTRIC HI-FI VARIABLE RELUCTANCE CARTRIDGE. Replaces discontinued RPX050 type. Full range reproduction 20-20,000 cycles. Four gram tracking force for minimum record and stylus wear.
4G050—Dual Sapphire needles.....$8.77
4G052—Diamond, Sapphire needles...$18.99

KITS!

We stock the following manufacturers' complete line of kits—see reference pages.

EICO see pages 25-26	DYNACO see pages 114-115
QUALITY see page 126	ARKAY
PRECISE	ELECTRO-VOICE
BOGEN	Inside Back Cover
GROMMES	CABINART
	TECHMASTER

All domestic orders will be shipped prepaid. Send us your list. Order by Mfr. and Model No. of item.

$20 WORTH OF ELECTRONIC PARTS IN GRAB-BAG consisting of: Porcelains, coils, speaker, transf., resis, cond. ONLY.....$1.98 (plus 50c postage)

YOU NAME IT—WE HAVE IT

Complete line of T.V. & Radio receiving tubes, coils, transf., controls, antennas & accessories—No Minimum Order—DEALER DISCOUNTS! Thousands of satisfied Hi-Fi enthusiasts and dealers will vouch that STAN-BURN GIVES THE BEST DEAL POSSIBLE!

EXPORT INQUIRIES AND OFFERS INVITED.
Terms: 20% with order. Balance C.O.D. All prices F.O.B. NEW YORK Warehouse.
Write for our latest price list and Hi-Fi Catalog RE-6. All Prices Subject to Change Without Notice.

STAN-BURN RADIO and ELECTRONICS CO.
558 CONEY ISLAND AVE. • B'KLYN 18, N. Y.

BOOKS *(Continued)*

A compilation of original manufacturers' service information covering nearly 520 models of television receivers produced by 11 firms.

TRANSISTOR ELECTRONICS, by David DeWitt and Arthur L. Rossoff. McGraw-Hill Book Co., Inc., 330 W. 42 St., New York 36, N. Y. 6 x 9 inches, 381 pages. $8.

According to these authors, the purpose of this book is to teach. This it should do very well, for there is a good balance between basic theory and practical circuit design. The text is the result of a successful technical course, and it is written at the level of the senior student or graduate engineer.

The first chapters touch on crystal structure and junction theory. Following are discussions of transistors for low frequency, audio power, high frequency, switching, mixing, radio reception, etc. Chapters are divided into small sections with suitable subheadings for convenience in locating a desired topic.

The text is easy to follow if the reader knows his college math. Equivalent circuits and useful diagrams show how gain, power and impedance may be be controlled and varied. The circuits are basic, leaving specific component values unlisted. Final chapters cover special transistor types, some not yet in wide commercial use, and the important subject of transistor noise.—*IQ*

COMMERCIAL RADIO OPERATOR'S LICENSE GUIDE, by Martin Schwartz. American Electronics Co., 1203-05 Bryant Ave., New York 59, N.Y. 6 x 9 inches. Elements 1 and 2, 48 pages, 75c. Element 3, 122 pages, $1.75.

Study guides to prepare candidates for commercial radiotelephone first- and second-class licenses and radiotelephone third-class permits to pass Elements 1 (Basic Law), 2 (Basic Operating Practice) and 3 (Basic Radiotelephone) of the FCC examination. The guides contain study questions with clear simple answers to each. They present all diagrams and types of problems likely to be required on the exam. Each element concludes with a sample FCC type test with answers.

RADIO AMATEUR'S HANDBOOK. American Radio Relay League, Inc., W. Hartford, Conn. 35th Edition, 6½ x 9½ inches, 746 pages. $3.50 in US, $4 in possessions, $4.50 elsewhere.

The radio bible has been brought up to date with new information on transistors, antennas, receivers and auxiliary equipment. Whatever your need—Conelrad device, optimum spacing for beam elements, help in learning the code, or review of theory—simply consult the index and turn to the indicated page.

As always, emphasis is on build-it-yourself apparatus. Photos, schematics, charts and detailed instructions all help to make it easier. A must for the engineer, technician and ham.—*IQ* END

BE QUALITY WISE . . BUY QUAL-KITS!

HI-FI AMP. KIT
Complete 6 tube-10 watt amplifier Push-pull beam power output, built-in pre-amp. 5 position selector switch, 3 position record equalization, LP, RIAA, Eur. Response ½ db. 20-20,000 cps. Output 10 watts at less than 2% IM. Low noise level and harmonic distortion. **$28.50**

Every kit complete with 28 page fully illustrated instruction and assembly manual. Cover and legs optional.

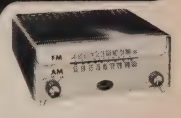

HI-FI AM-FM TUNER KIT
Advanced 7 tube circuit plus Rectifier for full sensitivity and selectivity. Distortion less than 1%. Sensitivity is 5 uv for 30 db quieting on FM, 25 uv AM. Armstrong FM Circuit with limiter. Foster-Seeley Discriminator. 20-20,000 cps response. Full AFC control — no drift. Easy assembly. **$28.95***

Write for FREE catalog and name of nearest dealer carrying these remarkable units.

*Add 10 percent for new federal tax

QUALITY-ELECTRONICS
319 Church St. Dept. RE-6 New York 13, N. Y.

ORDER by MAIL and SAVE!
TV PICTURE TUBES

10BP4	$ 7.95	17BP4	$10.95	21AMP4	$19.95
12LP4	8.95	17CP4	17.00	21ATP4	20.95
14B/CP4	9.95	17GP4	17.60	21AUP4	20.95
16DP4	14.95	17HP4	13.60	21EP4	14.95
16EP4	15.90	17LP4	13.60	21FP4	15.95
16GP4	15.90	17QP4	11.95	21WP4	17.30
16KP4	10.95	17TP4	19.30	21YP4	15.95
16LP4	10.95	19AP4	19.30	21ZP4	14.95
16RP4	10.95	20CP4	13.90	24CP4	23.95
16WP4	15.20	20HP4	17.95	24DP4	26.95
16TP4	10.95	21AP4	22.10	27EP4	39.95
17AVP4	15.20	21ALP4	20.95	27RP4	39.95

27"—6 month guarantee—all others 1 year. Aluminized Tubes $5.00 more than above prices. These prices are determined to include the return of an acceptable similar tube under vacuum.

ALL PRICES FOB CHICAGO, ILLINOIS. Deposit required, when old tube is not returned, refundable at time of return. 25% required on COD shipments. Old tubes must be returned prepaid. We ship anywhere.

WRITE FOR COMPLETE LIST.

—PICTURE TUBE OUTLET—
3032 Milwaukee Ave., Chicago 18, Ill.
Dickens 2-2048

CRYSTAL CONTROLLED CONVERTERS

POLICE • FIRE • COMMERCIAL

- Precision—Stability
- Sensitivity
- Easy Installation

$32.50

• A compact converter supplied with commercial tolerance crystals, self contained automatic noise limiter. Also models with squelch. Ideal for mobile or home use.

TUNERS

Enjoy FM Programs While You Drive.

- FM BROADCAST
- 30-50 MC
- 108-176 MC

from $22.50

WRITE FOR LITERATURE

KUHN ELECTRONICS
20 GLENWOOD CINCINNATI 17, OHIO

ADVERTISING INDEX

Radio-Electronics does not assume responsibility for any errors appearing in the index below.

Aerovox Corp. 88
Allied Radio Corp....15, 95
Amperex Electronic Corp....112

B & K Manufacturing Co....100
Barry Electronics Corp....127
Bell Telephone Labs....21
Benco Television Associates Ltd. 20
Blonder-Tongue Labs....111
Brooks Radio & Television Corp. 105, 110

CBS-Hytron....22, 79
Capitol Radio Engineering Institute....13, 93
Carston Studios 115
Centralab Div. of Globe Union.... 6
Century Electronics Co., Inc.... 83
Chemical Electronic Engineering Inc. 104
Cleveland Institute of Radio Electronics 11
Colorfax Laboratories, Inc....121
Cornell-Dubilier Electric Corp. 101, 102
Coyne Electrical School..91, 104, 117
Cutick Electronics 115

DeVry Technical Institute.... 7
Dressner 115
Dynaco Inc. 114-115

EBE Inc. 123
Edmund Scientific Co....119
Electro-Sonic Labs.... 20
Electro-Voice, Inc. ....Inside Back Cover
Electronic Instrument Co. (EICO)....25, 26
Electronic Publishing Co., Inc....113

Filnor Products 100

Garfield (Oliver) Co....121
Gernsback Library Inc....117, 124
Glaser-Steers Corp.... 89
Grantham School of Electronics.. 17

Heald Engineering College....119
Heath Co....60-75
Hi-Fi Eye Co....115

Indiana Technical College....115

Jensen Industries 118

Karlson Associates Inc....120
Kuhn Electronic Products....126

Lafayette Radio 128-129
Lansing (James B.) Sound Inc... 77
Lektron Inc....94, 120

MacFarlane Industries 121
Madison Fielding 110
Mallory (P.R.) & Co. Inc.... 78
Merit Coil & Transformer Corp...118
Moerke (Ed)....119
Moss Electronic Distributing Co. Inc. 80-81

National Radio Institute.... 3
National Schools 5
North American Philips Co. Inc.113
Northrop Aeronautical Institute..116

Opportunity Adlets 114
Oxford Components, Inc....116

Philco Techrep Division....130
Picture Tube Outlet....126
Pilot Radio Corp.... 98
Prentice-Hall, Inc....123
Progressive Edu-Kits, Inc....106
Pyramid Electric Co.... 16

Quality Electronics 126

RCA Electron Tube Division ....Back Cover
RCA Institutes....108-109
RCA (Test Equipment) 14
Radiart Corp. 102, 103
Raytheon Manufacturing Co.... 12
Rek-O-Kut Co. Inc.... 82
Rinehart & Co. Inc....121

Sams (Howard W.) & Co. Inc. 9, 118
Service Instruments Corp. 94, 113, 117, 119, 120, 123
Sleep-Learning Research Ass'n....119
Sprague Products Co....107
Sprayberry Academy of Radio Television 23
Stan-Burn Radio & Electronics..126

Tab 122
Trio Manufacturing Co.... 82
Triplett Electrical Instrument Co. ....Inside Front Cover
Tung-Sol Electric Co.... 8

Ultron Co....104
University Loudspeakers Inc.... 85

Vaco Products Co....122

Walsco Electronics Manufacturing Co. 10
Winegard Co.... 24

Xcelite Inc. 94

Zenith Radio Corp....18-19

SCHOOL DIRECTORY PAGE 125

Baltimore Technical Institute
Canadian Institute of Science & Technology
Candler System Co.
Central Technical Institute
Indiana Technical College
Milwaukee School of Engineering
Pacific International University
Tri-State College
Valparaiso Technical Institute

BRANCH ADVERTISING OFFICES: Chicago: 600 Waukegan Road, Glenview, Ill., GLenview 4-6900. **Los Angeles:** Ralph W. Harker and Associates, 600 South New Hampshire. Tel. DUnkirk 7-2328. **San Francisco:** Ralph W. Harker and Associates, 444 Market St. Tel. GArfield 1-2481.
FOREIGN AGENTS: Great Britain: Atlas Publishing and Distributing Co., Ltd., 18 Bride Lane, London E.C. 4. **Australia:** McGill's Agency, Melbourne. **France:** Brentano's, Paris 2e. **Belgium:** Agence et Messageries de la Presse, Brussels. **Holland:** Trilectron, Heemstede. **Greece:** International Book & News Agency, Athens. **So. Africa:** Central News Agency, Ltd., Johannesburg, Capetown, Durban, Natal; Universal Book Agency, Johannesburg. **India:** Broadway News Centre, Dadar, Bombay #14. **Pakistan:** Paradise Book Stall, Karachi 3.

HQ for the 5 TOP NAMES in TV & RECEIVING TYPE

TUBES
AT SENSIBLE PRICES!

Individually boxed. First quality only. Brand New

OA2	.75	5BQ7	1.40	6BH8	1.25	6V6M	1.50	12SG7	1.00		
OA3/		5CG8	1.15	6BJ6	.90	6W4GT	.85	12SH7	1.00		
VR75	.80	5J6	1.00	6BJ7	1.00	6W6GT	1.00	12SJ7	.95		
OB2	.75	5R4GY	1.50	6BK4	2.50	6X4	.60	12SK7GT			
OB3/		5T8	1.20	6BK5	1.10	6X5GT	.70		.95		
VR-90	.80	5U4G	.80	6BK7A	1.15	6X8	1.10	12SL7GT	.95		
OC3/VR-		5U4GB	.80	6BL7GT		6Y6G	1.00	12SN7GTA			
105	.80	5U8	1.15		1.35	7A4	.75		.90		
OD3/VR-		5V4G	1.15	6BN4	.85	7A5	.90	12SQ7GT	.85		
150	.75	5V6GT	.85	6BN6	1.00	7A6	.80	12SR7	.90		
OZ4	.60	5W4GT	.90	6BQ6GT		7A7	.90	12V6GT	.75		
OZ4G	.70	5X4G	.80		1.30	7A8	1.25	12W6GT			
1A3GT	.90	5Y3G	1.15	6BQ7A	1.35	7AD7	1.65		1.00		
1A7GT	1.00	5Y3GT	.60	6BR8	1.15	7AF7	1.00	12X4	.60		
1AD4	1.00	5Y4G	.80	6BS8	1.45	7AG7	1.00	14A4	1.25		
1AE4	1.35	5Z3	1.00	6BU8	1.00	7AH7	1.00	14A5	1.60		
1AG4	1.80	5Z4	1.60	6BX7GT		7AU7	.90	14A7	1.00		
1AX2	1.00	6A7	1.25		1.35	7B4	.75	14A7	1.05		
1B3GT	1.00	6A8M	1.35	6BY5G	1.25	7B5	1.00	14B6	.90		
1B5GT	.85	6AG7	1.35	6BY8	.80	7B6	1.00	14C7	.90		
1L4	.75	6AB4	.75	6BY8	.90	7B7	1.00	14E6	1.15		
1L6	1.05	6AB5	1.25	6BZ6	.80	7B8	1.00	14E7	1.20		
1LA4	1.00	6AB7	1.60	6BZ7	1.40	7C5	1.00	14F7	1.00		
1LA5	1.00	6AC5GT		6BZ8/		7C6	.95	14F8	1.20		
1LB4	1.25		1.35	X155	1.60	7C7	.90	14H7	1.20		
1LC5	1.10	6AC7	1.35	6C4	.60	7E7	1.20	14J7	1.00		
1LC6	1.10	6AD7G	1.85	6C5	.80	7F7	1.00	14Q7	1.20		
1LD5	1.10	6AF4	1.45	6C8	2.75	7F8	1.30	14R7	1.30		
1LE3	1.10	6AF6G	1.20	6CB6	.80	7G7	1.15	14S7	1.25		
1LG5	1.10	6AG5	.80	6CD6G	2.25	7H7	1.10	14W7	1.20		
1LH4	1.10	6AG7	1.50	6CF8	.90	7J7	1.00	19AU4	1.20		
1LN5	1.10	6AH4GT		6CG7	.85	7K7	1.20	19BG6G	2.25		
1N5GT	1.05		1.05	6CG8	1.10	7L7	1.30	19J6	1.10		
1Q5GT	1.10	6AH6	1.40	6CH8	1.25	7N7	.95	19T8	1.15		
1R4	1.00	6AK4	1.50	6CL6	1.30	7Q7	1.20	19X8	1.30		
1S5	.85	6AL5	1.85	6CM6	.90	7R7	1.40	25A5GT			
1S4	.80	6AK5	.90	6CM7	.95	7V7	1.30		1.25		
1S5	.80	6AK8	.95	6CM8	.85	7W7	1.30	25AX4GT			
1T4	.80	6AL5	.65	6CR6	.85	7X7	1.40		1.05		
1T5GT	.90	6AL7GT		6CS6	.95	7Y4	.80	25BK5	1.25		
1U4	.80		1.80	6CS7	.95	7Z4	.80	25BQ6GT			
1U5	.75	6AM4	1.90	6CU5	.90	8AW8A	1.40		1.60		
1V	1.00	6AM5	1.15	6CU6	1.50	8CG7	.90	25CD6GA			
1Y2	.65	6AN4	1.65	6D6	1.20	8CM7	.90		2.00		
1X2B	1.10	6AN5	3.70	6DC6	.95	12A6	.90	25CU6	1.60		
2A3	2.00	6AN8	1.20	6DA5	.85	12AB5	.80	25L6GT	.80		
2AF4A	1.35	6AQ5	.75	6DT6	.85	12AH7	1.25	25W4GT	.95		
2BN4	.90	6AQ6	.75	6DQ6	1.55	12AL5	.85	25Z5	.90		
2D21	1.10	6AQ7GT		6E5	1.00	12AQ5	.75	25Z6GT	1.00		
2X2	.55		1.15	6F5	1.10	12AT6	.70	25A5	1.00		
3A3	1.10	6AR5	.75	6F6M	1.35	12AT7	1.05	35B5	.90		
3A4	.75	6AR6	2.35	6F6G	1.00	12AU6	.75	35C5	.75		
3A5	.75	6AS5	.85	6H6	.75	12AU7	.85	35L6GT	.85		
3AL5	.65	6AS6	1.00	6J4	2.00	12AV6	.60	35W4	.80		
3AU6	.75	6AS7G	3.00	6J5	.85	12AV7	1.10	35Y4	.80		
3AV6	.60	6AS8	1.15	6J6	.75	12AW6	1.05	35Z3	.80		
3BE6	.85	6AT6	.70	6J7	1.20	12AX4GT		35Z4	.65		
3BC5	.85	6AT8	1.15	6K6GS	.80		.95	35Z5	.65		
3BN6	1.00	6AU4GT		6K7	1.00	12AX7	.85	41	.90		
3BU8	.95		1.15	6K8	1.40	12AY7	1.70	42	.90		
3BY5	.85	6AU5GT		6L6G	1.50	12AZ7	.95	43	1.00		
3BZ6	.85		1.50	6L6GA	1.50	12BA4	.90	50A5	1.00		
3C9H	.85	6AU6	.75	6L6M	2.00	12BA6	.70	50B5	.90		
3CF6	.90	6AU7	1.00	6L7	1.40	12BA7	1.25	50C5	.75		
3CS6	.85	6AU8	1.20	6N7	1.25	12BD6	.70	50C6	.75		
3DT6	.80	6AV6GT		6Q7	1.00	12BE6	.65	50L6GT	.85		
3LF4	1.25		1.25	6S4	.75	12BF6	.75	50X6GT	.90		
3Q4	.75	6AV6	.60	6S8GT	1.00	12BH7A	1.05	50Y6GT	.75		
3Q5GT	1.15	6AW8	1.25	6SA7GT	1.05	12BR5	1.20	50Y7GT	.75		
3S4	.85	6AX4GT		6SC7	1.05	12BN6	1.10	70L7GT	2.70		
3V4	.85		.90	6SF5	.85	12BQ6GTB					
4BC8	1.40	6AX5GT		6SF7	1.20		1.55	80	.85		
4BQ7A	1.40		1.05	6SG7	1.10	12BR7	.85	81	1.75		
4BS8	1.35	6AZ8	1.45	6SH7	.85	12BY7	1.00	83	1.35		
4BU8	1.20	6B4G	1.85	6SJ7M	.85	12BY7A	1.05	83V	1.25		
4BZ7	1.40	6BA6	.70	6SK7GT	1.40	12CR6	1.05	117L7GT			
5A6	2.10	6BA7	1.25	6SL7GT	1.10	12C5	.80		2.70		
5AM8	1.15	6BC4	1.80	6SN7GT	.90	12CA5	.85	117N7GT			
5AN8	1.25	6BC5	.80	6SQ7GT	.85	12CU6	1.55		2.00		
5AQ5	.75	6BC7	1.15	6SR7	.90	12DQ6	1.55	117P7GT			
5AS8	1.20	6BC8	1.40	6SS7	1.05	12FG6T	.85		2.00		
5AT8	1.15	6BD5	1.25	6ST7	1.10	12K7GT	1.00				
5AU4	1.30	6BD6	.70	6T4	1.30	12K8	1.30	117Z3	.85		
5AV8	1.35	6BE6	.75	6T8	1.15	12L6GT	.85	117Z4GT			
5AW4	1.25	6BF5	.80	6U5	1.00	12Q7GT	1.00		1.20		
5AZ4	.85	6BF6	.65	6V3	1.15	12SA7GT		117Z6GT			
5BK7	1.20	6BG6G	2.25	6V3A	1.45		1.05		1.40		
5BR8	1.20	6BH6	.95	6V6GT	.75	12SC7	1.00	5642	1.05		

2-COLOR TUBE CARTONS

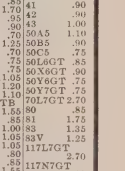

Keeps your tube stock neat. New safety partition prevents tube breakage. Distinctively lithographed in glossy red and black. The most distinctive tube carton available today. Minimum quantity: 100 of any one size. Write for case lot prices. Packed 1000 to case. F.O.B. N.Y.C.

Size	For Tube	Per 100
Miniature	6AU6, etc....	$1.00
GT	6SN7, etc....	1.25
Large GT	1B3, etc....	1.50
Large G	5U4G, etc....	2.00

WHITE GLOSSY BOXES

Completely blank. No printing or color. Otherwise same as above. Same high quality, same low prices. Specify "WHITE" when ordering. When color is not stated, 2 color cartons will be shipped.

Write for latest "Green Sheet," listing hundreds of equipment and component specials.

Write for complete tube list. All shipments F.O.B. Our Warehouse. Rated firms (Dun & Brad. current F.3 or better) Net 10 Days. 10 day guar. price of mdse. only. All merchandise guaranteed.

HOW TO ORDER: Send full remittance and save C.O.D. collection fee;—Include sufficient money for postage.—We refund unused amount.—If you desire shipment C.O.D., include 25% deposit.—Send cash by registered mail. Subject to price variation and stock depletion. No C.O.D.'s on tube cartons.

OPEN MONDAY TO SATURDAY
We are near Prince St./BMT Station
Spring St./IRT Station

BARRY ELECTRONICS CORP.
512 Broadway, Dept. RE-4, N.Y. 12, N.Y.
Phone: WAlker 5-7000

FREE LAFAYETTE CATALOG

A Must For Every Hi-Fi Enthusiast

New! Years Ahead!

NEW 180 PAGE ELECTRONIC CATALOG FEATURING THE BEST BUYS IN THE BUSINESS

The newest and largest assortment of Electronic, Radio and TV parts, Hi-Fi and Public Address Components and systems, Test Equipment, tubes, Transistor Kits and miniaturized components for transistor circuitry, Ham Equipment, Builders Kits, Tools, Books, Microscopes, Binoculars, Telescopes, Cameras, and Drafting Equipment.—*ALL AT LOWEST PRICES*—Catering to the economy minded dealer, serviceman, engineer, technician, experimenter and hobbyist. *CRAMMED FULL OF MONEY SAVING BUYS. SEND FOR YOUR FREE COPY TODAY.*

LAFAYETTE STEREO TUNER KIT

THE MOST FLEXIBLE TUNER EVER DESIGNED

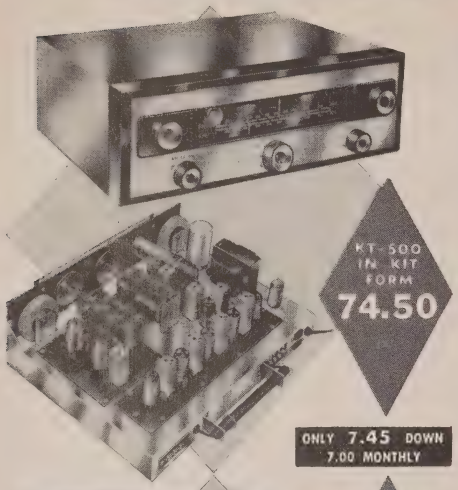

● Multiflex Output for New Stereo FM ● 11 Tubes (including 4 dual-purpose) + Tuning Eye-+ Selenium rectifier Provide 17 Tube Performance ● 10KC Whistle Filter ● Pre-aligned IF's ● Tuned Cascode FM ● Separately Tuned FM and AM Sections ● Armstrong Circuit with FM/AFC and AFC Defeat ● 12 Tuned Circuits ● Dual Cathode Follower Output ● Dual Double-Tuned Transformer Coupled Limiters.

More than a year of research, planning and engineering went into the making of the Lafayette Stereo Tuner. Its unique flexibility permits the reception of binaural broadcasting (simultaneous transmission on both FM and AM), the independent operation of both the FM and AM sections at the same time, and the ordinary reception of either FM or AM. The AM and FM sections are separately tuned, each with a separate 3-gang tuning condenser, separate flywheel tuning and separate volume control for proper balancing when used for binaural programs. Simplified accurate knife-edge tuning is provided by magic eye which operates independently on FM and AM. Automatic frequency control "locks in" FM signal permanently. Aside from its unique flexibility, this is, above all else, a quality high-fidelity tuner incorporating features found exclusively in the highest priced tuners.

FM specifications include grounded-grid triode low noise front end with triode mixer, double-tuned dual limiters with Foster-Seeley discriminator, less than 1% harmonic distortion, frequency response 20-20,000 cps ± ½ db, full 200 kc bandwidth and sensitivity of 2 microvolts for 30 db quieting with full limiting at one microvolt. AM specifications include 3 stages of AVC, 10 kc whistle filter, built-in ferrite loop antenna, less than 1% harmonic distortion, sensitivity of 5 microvolts, 8 kc bandwidth and frequency response 20-5000 cps ± 3 db.

The 5 controls of the KT-500 are FM Volume, AM Volume, FM Tuning, AM Tuning and 5-position Function Selector Switch. Tastefully styled with gold-brass escutcheon having dark maroon background plus matching maroon knobs with gold inserts. The Lafayette Stereo Tuner was designed with the builder in mind. Two separate printed circuit boards make construction and wiring simple, even for such a complex unit. Complete kit includes all parts and metal cover, a step-by-step instruction manual, schematic and pictorial diagrams. Size is 13¾" W x 10⅝" D x 4½" H. Shpg. wt., 18 lbs.

The new Lafayette Model KT-500 Stereo FM-AM Tuner is a companion piece to the Models KT-300 Audio Control Center Kit and KT-400 70-watt Basic Amplifier Kit and the "Triumvirate" of these 3 units form the heart of a top quality stereo hi-fi system.

KT-500.....Net **74.50**

LAFAYETTE MASTER AUDIO CONTROL CENTER with BINAURAL CHANNEL AND DUAL VOLUME CONTROL.

● Self-Powered ● DC On All Filaments ● 24 Positions of Equalization ● Tape Head Input, High Impedance ● Dual Cathode Follower Output Stages

This is not only the finest hi-fi preamp characterized by unmatched features, but it has been functionally designed to keep pace with the conversion of your present hi-fi system to binaural (Stereophonic) sound. Incorporates an extra channel and dual volume control for binaural reproduction. Features include DC on all tube filaments, negative feedback in every stage, dual cathode follower output stages and latest printed circuit construction. Less than 0.09% IM distortion and less than 0.07 harmonic distortion at 1V. Hum and noise level better than 80 db below 3V. Uniformly flat frequency response over entire audible spectrum. 7 inputs for every type of phono, tuner or tape. Tasteful styling, brilliantly executed. Size 12¾ x 9⅛ x 3¾". Shpg. wt., 10½ lbs.

KT-300—Lafayette Master Audio Control Kit Complete with cage and detailed assembly instructions. ..... Net **39.50**

LT-30—Same as above completely wired and tested with cage and instruction manual. Net **59.50**

DELUXE 70 WATT BASIC AMPLIFIER

● Conservatively Rated At 70 Watts ● Inverse Feedback ● Variable Damping ● Metered Balance And Bias Adjust Controls ● Available In Kit and Wired Form

Here's ultra-stability in a 70 watt basic power amplifier employing highest quality components conservatively rated to insure performance and long life. Features matched pair KT 88's and wire range linear Chicago output transformer, variable damping control, meter for bias and balance and gold finish chassis. Frequency response 10-100,000 cps ± 1db. Hum and noise 90 db below full output. IM distortion less than 1½% at 70 watts, less than 0.3% below 30 watts. Harmonic distortion less than 2% at 70 watts from 20 to 20,000 cps ± 1 db. Output impedance 4, 8 and 16 ohms. Handsome decorative cage perforated for proper ventilation. Size 14½ x 10 x 7⅜" including cage and knobs. Shpg. wt., 40 lbs.

KT-400—Lafayette 70 watt Deluxe Basic Amplifier Kit complete with cage and detailed assembly instructions. .....Net **69.50**

LA-70—Same as above completely wired and tested with cage and instruction manual. Net **94.50**

NEW! LAFAYETTE SCOOP!

DUAL WIDE-ANGLE TWEETER

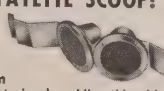

Only **5.95**

Modernize Your Hi-Fi System

Modernize your high fidelity listening by adding this wide-angle dual-tweeter to extend treble range in a 2-way or 3-way speaker system. Mounts directly on any 12" speaker and converts it to a coaxial type. Response 2500 to 16,000 cps. Recommended crossover 2500 to 4000 cps. Heavy magnets for high efficiency. Dispersion angle approx. 125° horizontally. Impedance 16 ohms (2-8 ohm units in series). Will handle up to 20 watts program in 2 or 3-way systems. Incorporates specially designed chrome-plated steel bracket of rigid construction to prevent resonances. Measures 12" L x 2" D x 2⅞" H overall. Shpg. wt. 2 lbs.

SK-100 Dual Tweeter ..... Net **5.95**

Lafayette Radio DEPT JF **P. O. BOX 511 JAMAICA 31, N. Y.**

☐ Send FREE LAFAYETTE Catalog 305

Name ..... CUT OUT AND MAIL TODAY

Address .....

City..... *Zone*.... *State*.....

LAFAYETTE PROFESSIONAL TURNTABLE
with AUTHENTIC HYSTERESIS SYNCHRONOUS MOTOR

Value ~~129.50~~ Only 64.50
SAVE OVER 50%

PROFESSIONAL TURNTABLE WITH HYSTERESIS-SYNCHRONOUS MOTOR

The **Lafayette Model PK-225** is a *true* hysteresis-synchronous motor and is free from speed variations due to fluctuations in line voltage, load and temperature. It is the smoothest type known, completely free from "cogging" (the minute variations of speed which show up as wow and flutter)!

ONLY LAFAYETTE'S HYSTERESIS—SYNCHRONOUS MOTOR, in its price class, is made to extremely fine tolerances (on the order of .00001 inches)! Only Lafayette's motor has 16 cores; a high permeability rotor magnet, ball thrust bearings, oilite sleeve bearings plus felt oil reservoir, cooling fins as an integral part of the rotor and a hollow rotor core for maximum efficiency and minimum heat. Only Lafayette's motor can be oiled from above, without disassembly, through a unique oil feed system. Only Lafayette's motor has a self-aligning armature.

Here's THE turntable—the last word in professional high-fidelity performance! A fine precision instrument in every sense. Just look at some of these ***OUTSTANDING FEATURES:*** **- WOW AND FLUTTER:** Less than 0.2% • **TURNTABLE:** Heavy, diecast aluminum. Lathe-turned for perfect balance and concentricity. 12" diameter—weighs approx. 4 lbs. and provides amazingly constant speed; the extra-heavy rim acts just like a flywheel to prevent speed variations • **TRUE-HYSTERESIS-SYNCHRONOUS MOTOR:** For smooth, low-noise, wow- and flutter-free operation • **RUMBLE AND NOISE:** 50db below average recorded level • **INTEGRATED SPEED CONTROL:** For all 3 speeds—78, 45 and 33⅓ rpm • **2 OVERSIZE, HEAVY DUTY IDLERS:** Precision-ground; provide positive constant-speed rim drive • **SINGLE BALL THRUST BEARING:** Turntable rides smoothly over ball bearing floating on thin film of oil • **FREE FLOATING, SHOCK-MOUNTED MOTOR** • **RUBBER CUSHION SHOCKMOUNTS** • **AUTOMATIC IDLER DISENGAGEMENT** • **CORK AND RUBBER MAT** • **STAINLESS STEEL PRECISION SPINDLE** • **POWER REQUIREMENTS:** For 105-130 volts, 60 cps AC; draws 16 V.A. • **ACCESSORIES SUPPLIED:** 45 RPM adapter. Strope disc • **SIZE:** 2⅛" above and 4" below motor board; 14¾" deep x 12¼" wide • **SHIPPING WEIGHT:** 16 lbs.

LAFAYETTE MODEL PK-225 ..... Net **64.50**
Deluxe Woodbase for PK-225 and 12" Tone Arm (Specify Finish). Shpg. wt., 13 lbs. ..... Net **14.95**
Deluxe Woodbase for PK-225 and 16" Tone Arm (Specify Finish). Shpg. wt., 15 lbs. ..... Net **15.95**

LAFAYETTE MODEL PK-225

VISCOUS DAMPED TRANSCRIPTION TONE ARMS

PK-90— **11.95** VISCOUS DAMPED ARM

LICENSED UNDER CBS U. S. PATENT NO. 2676806

PK-170— **17.95** VISCOUS DAMPED ARM

SPECIAL MONEY-SAVER COMBINATION

PK-225 Turntable, PK-90 12" Tone Arm, New GE VRII Series Triple-Play Cartridge Model 4G-052 with Genuine GE Diamond and Sapphire Styli. ***SPECIAL!*** ..... Net **81.50**

TINY 6 TRANSISTOR RADIO

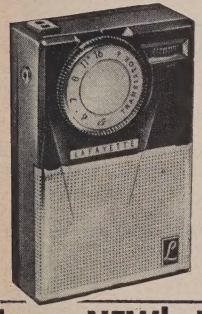

• LIGHT • SMALL • SENSITIVE
LOW PRICE HIGH PERFORMANCE

- PUSH-PULL AUDIO OUTPUT FOR FAITHFUL TONE QUALITY
- FULL TONE DYNAMIC SPEAKER
- BUILT-IN FERRITE BAR ANTENNA
- TROUBLE-FREE PRINTED CIRCUIT
- 6 ULTRA-MODERN TRANSISTORS PLUS GERMANIUM DIODE
- SUPERHETERODYNE CIRCUIT
- HIGHLY STYLED PLASTIC CASE
- EARPHONE JACK—BUILT IN—FOR PRIVATE LISTENING
- ECONOMICAL—USES ONLY ONE BATTERY

REGULARLY ~~48.50~~
29.95
Including Earphone, Battery and Carrying Case

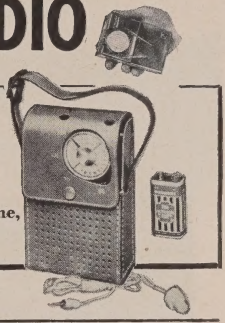

SIZE: 1⅜" x 2¾" x 4⅝" WEIGHT: 12 OUNCES

FS-110 — LAFAYETTE "TINY" TRANSISTOR RADIO COMPLETE with Battery, Carrying Case and Earphone ..... Net **29.95**

NEW! POWER MEGAPHONE... Portable Sound Broadcaster

• Uses 8 Flashlight Cells • Completely Self-Contained • Weighs only 6½ lbs. with Batteries • High Efficiency Horn Projects Sound 1000 Ft. • Shoulder Strap for Portability and Ease of Use • Microphone Detachable On 10-Foot Cord • For Construction, Auctions, Carnivals, Fire & Police Use • Also Ideal for Marine, Railroad, Civil Defense, Sporting Events

A power megaphone with many unusual features and many applications. Basically a highly efficient sound projector horn with a built-in microphone, capable of amplifying and projecting the voice with a range of 1000 feet. The microphone is a telephone-type element, easily replaceable, and may be detached and extended up to 10 feet from the horn. The reflex-type horn is extremely light-weight, rubber-rimmed, of strong, sturdy spun aluminum construction with 2¾" air column and is supplied with a strap for carrying or placing on the shoulder. A press-to-talk switch on the microphone provides for economy of power use—power is used only when actually talking. No warm-up time required—amplification is instantaneous. A patented non-linear current limiting device restricts current flow to safe levels for longest battery life. Uses 8 size "D" flashlight cells in series with an approximate life of about 10 hrs. of use. Battery housing serves as base for entire assembly. Battery compartment opens easily by means of 2 thumbscrews for battery replacement. Size 17" long overall; horn mouth is 12" diam. Shpg. wt., 8 lbs. less batteries.

PA-13— Power Megaphone, Less batteries ..... Net **29.50**

BATTERIES FOR ABOVE— Burgess No. 2 or RCA VS036—8 Required ..... Net each **.13**

Reg. Value ~~69.50~~
ONLY **29.50**

SHOULDER STRAP & DETACHABLE MIKE JUST AIM & TALK

Self-Contained— Only 6½ lbs. THROWS VOICE 1000 FT.

Lafayette Radio 165-08 Liberty Ave., JAMAICA 33; N. Y.
INCLUDE POSTAGE WITH ORDER

NEW YORK, N.Y.	BOSTON, Mass.	BRONX, N.Y.	NEWARK, N.J.	PLAINFIELD, N.J.
100 6th Ave.	110 Federal St.	542 E. Fordham Rd.	24 Central Ave.	139 W. 2nd St.
REctor 2-8600	HUbbard 2-7850	FOrdham 7-8813	MArket 2-1661	PLainfield 6-4718

LEARN SEMICONDUCTOR ELECTRONICS AT HOME

...prepare now for advancement in this growing, new technology!

GAIN VALUABLE KNOWLEDGE FOR A PROFITABLE CAREER IN ELECTRONICS WITH THIS SPECIALIZED CORRESPONDENCE COURSE ON TRANSISTORS THAT HAS BEEN SPECIALLY DEVELOPED BY THE PHILCO TECHNOLOGICAL CENTER

Learn by doing with complete training kit

Get practical experience, learn faster and easier. Conduct 18 experiments with training kit included. Build Amplifiers, Oscillators, Multivibrators, Pulse Circuits, AM Receivers, as well as Computer Circuits such as "AND," "OR" and "CARRY."

Learn theory, construction and all important applications of all major types of transistors—Junction, Point Contact, Surface Barrier and many other related types—with this advanced Correspondence Course specially developed for engineers and experienced technicians now engaged in Design, Installation, Maintenance or Manufacture of electronics equipment or systems.

ELECTRONICS SPECIALISTS ARE URGENTLY NEEDED. Even during hard times and periods of high unemployment such as we are going through now, the newspapers are full of help-wanted ads for electronics technicians and engineers. And the pay is good, too! Of course, the more you know the better your chances for better jobs and bigger pay.

GET INTO THE SEMICONDUCTOR FIELD NOW. This field is growing fast. Industry can't find enough experienced technicians and engineers. Career opportunities are unlimited. Now's the time to get in on the ground floor.

THE PHILCO TECHNOLOGICAL CENTER IS A DEPARTMENT OF PHILCO TECHREP DIVISION, THE WORLD'S LEADING ELECTRONICS FIELD ENGINEERING ORGANIZATION. You benefit from Philco's 17 years of experience in providing electronics training and technical assistance to the Armed Forces and industry all over the world ... and from advanced training methods developed through these many years. You learn from proven courses that have been developed by experienced electronics training specialists to give you a complete and practical knowledge of semiconductors.

Prepare for a Career in Field Engineering with these Philco Correspondence Courses

BASIC RADAR—an introductory course.

ADVANCED RADAR—Comprehensive course on radar equipment and systems.

BASIC ANALOG COMPUTERS — an introductory course.

ADVANCED ANALOG COMPUTERS—Comprehensive coverage of systems and equipment.

Mail Coupon Today for Detailed Information of Course Level and Materials!

(NO OBLIGATION)

PHILCO TECHNOLOGICAL CENTER

22nd and Lehigh Ave. Philadelphia 32, Pa.

PHILCO TECHNOLOGICAL CENTER
22nd and Lehigh Ave., Philadelphia 32, Pa. TC-14

Please send free booklet and course information on subjects checked below:

- ☐ SEMICONDUCTORS Transistor Principles and Practices
- ☐ BASIC RADAR
- ☐ ADVANCED RADAR
- ☐ BASIC ANALOG COMPUTERS
- ☐ ADVANCED ANALOG COMPUTERS

NAME_____

ADDRESS_____

CITY_____ STATE_____

Electro-Voice® **DYNAMIC MICROPHONES**

OUT-PERFORM ALL OTHERS for P.A. and RECORDING!

new acoustic principle — VARIABLE D acclaimed the most significant microphone development in 20 years!

Because of their durability and uniformity of response, dynamic microphones are almost universally used by recording studios. Electro-Voice dynamic microphones are a triumph of electro-acoustics in the recording, P.A. and general purpose fields. One of the many reasons for this is the Variable D principle which employs three distinct sound entrances, with acoustical filters; achieves flat response and excellent back cancellation while eliminating boominess caused by close talking—and susceptibility to shock. That's why those who want true fidelity, life-like recorded tape choose Electro-Voice dynamic microphones.

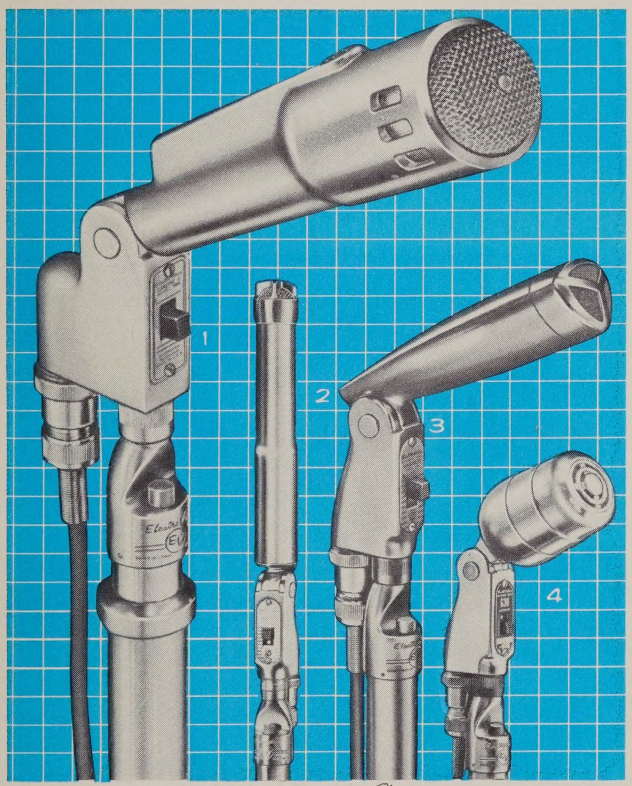

❶ E-V MODEL 664

Utilizing the revolutionary Variable D, this high-fidelity cardioid dynamic brings broadcast quality to tape recording and the P.A. and general purpose field. Proper placement of microphone stops unwanted sounds, gives accurate, natural pick-up of voice and music. Unprecedented ruggedness largely eliminates possibility of accidental damage.

Indestructible Acoustalloy diaphragm and precision manufacture assure long-life and dependable performance. Frequency response: 40 to 15,000 cps. Pressure cast case. Chrome finish. 18′ cable. Size: 7-3/16″ long, 1⅞″ diameter. Net weight: 1 lb. 10 oz. List price: $85.00 (less stand).

❷ E-V MODEL 636

This model brings style and quality to the recording and public address fields. Slim and trim—only 1⅛″ in diameter x 10¼″ long – it greatly reduces recording staging problems. Frequency response: 60 to 15,000 cps, essentially flat. Adjustable impedance. Gold or satin chrome finish. On-off switch standard equipment. Net weight: 15 oz. List price Chrome Finish: $72.50 (less stand).

❸ E-V MODEL 623

Excellent for both speech and music, its small, slim size makes it inconspicuous and easy to handle. Swivel mounting permits tilting microphone through a 57° arc toward the sound source. Acoustalloy diaphragm. Frequency response: 60 to 12,000 cps. Satin chrome finish. Net weight: 1 lb. List price: $57.00 (less stand).

❹ E-V MODEL 630

This is similar to Model 623 in performance characteristics but is traditionally styled. Frequency response: 60 to 11,000 cps. Satin chrome finish. Net weight: 1 lb. List price: $52.50.

Your tapes will have a new depth of realism when you record with Electro-Voice High-Fidelity Dynamic Microphones!

See your E-V hi-fi dealer **today**. Write for "The ABC's of Microphones," Booklet W-86

Electro-Voice®

ELECTRO-VOICE, INC.
BUCHANAN, MICHIGAN

anatomy of the tube... LESSON #1

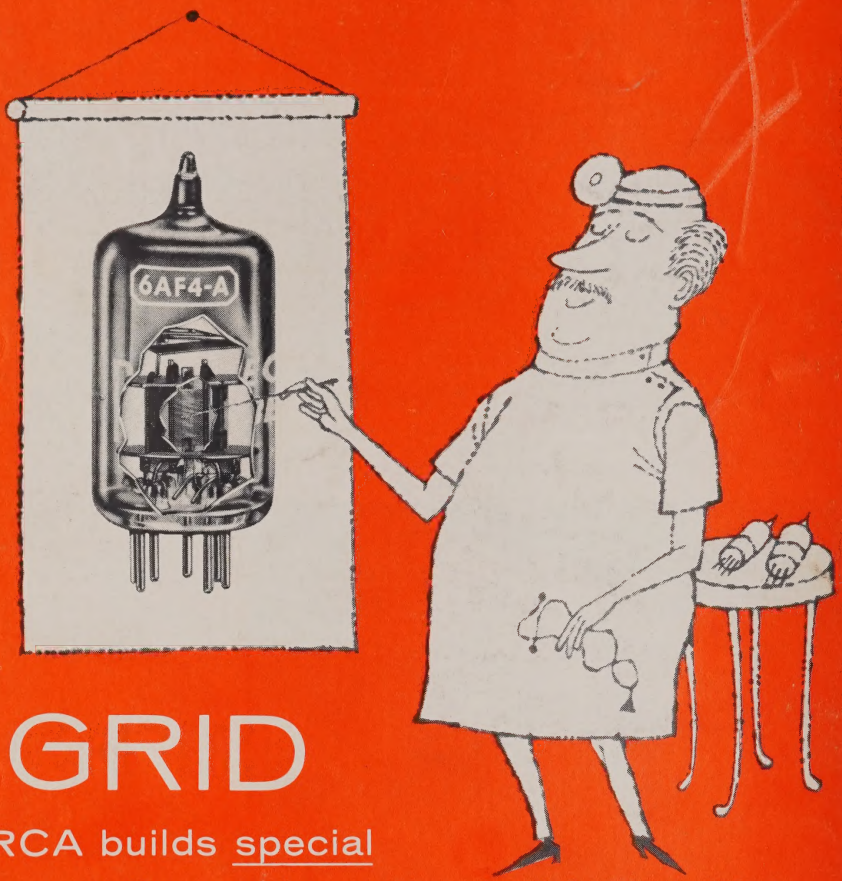

GRID

How RCA builds special prescription grids...extends 6AF4-A life!

RCA's redesign of the 6AF4-A has resulted in minimized slump, product uniformity, and projected average life *of 4,000 hours or more!*

Here are some of the materials RCA "prescribes" in manufacturing the new 6AF4-A. The grid is plated with Palladium, a rare metal capable of withstanding high temperatures. The use of this grid structure minimizes interelectrode leakage, prevents grid loading, and as a result, provides stable tube performance. The cathode, a nickel alloy, is specially selected to reduce interface resistance and thus minimizes slump. The use of pins which are silver-plated reduces skin effect at ultra high frequencies and improves tuner performance.

All these features, in addition to dynamic life tests, help to assure long and dependable performance. No wonder RCA's 6AF4-A is tops!

So, here's the #1 lesson in radio, phonograph, and TV service—when ordering tubes for replacement, specify *"RCA Tubes only."*

RCA® **RADIO CORPORATION OF AMERICA**

Electron Tube Division **Harrison, N. J.**